

MCR-85-641

NAS8-35922

PHASE TWO

(NASA-CR-179136) EXPERT SYSTEMS APPLIED TO
FAULT ISOLATION AND ENERGY STORAGE
MANAGEMENT, PHASE 2 Final Report (Martin
Marietta Aerospace) 386 p Avail: NTIS HC
A17/MF A01

N87-26530

Unclass
CSCI 09B 63/61 0085375

EXPERT SYSTEMS APPLIED TO FAULT ISOLATION
AND ENERGY STORAGE MANAGEMENT

FINAL REPORT

Prepared for: National Aeronautics and Space Administration
George C. Marshall Space Flight Center
Marshall Space Flight Center, AL 35812

TABLE OF CONTENTS

	<u>Page</u>
Chapter 1 Introduction	1
Chapter 2 Tutorial: A Simple Example	5
Chapter 3 System Versions	10
Chapter 4 LISP Interface Options	19
Chapter 5 Installation Guide	23
Chapter 6 Operating Constraints	26
Chapter 7 Battery Maintenance and Recharging	34
Chapter 8 Test Configuration Utility	41

APPENDICES

- A. Operation Flowcharts and Screens
- B. Test and Demonstration Plan
- C. Software Design
- D. Expert System Rules with Translation
- E. Hardware Description and Drawings

CHAPTER 1

INTRODUCTION

INTRODUCTION

This manual serves as a user guide for the FIES II system. This includes a brief discussion of the background and scope of the project, a discussion of basic and advanced operating installation and problem determination procedures for the FIES II system and information on hardware and software design and implementation. The final part of the document consists of a number of appendices including a detailed specification for the microprocessor software, a detailed description of the expert system rule base and a description and listings of the LISP interface software.

Martin Marietta has expended considerable effort researching and developing AI technologies appropriate for the automated management of spacecraft power systems.

The first FIES (Fault Isolation Expert System) program, conducted under IR&D funding, demonstrated the applicability of expert systems to fault isolation and detection in space-based power systems.

The EMES (Energy Management Expert System) program, conducted under CR&D funding from NSFC, demonstrated that an expert planning system is capable of load management in spacecraft power distribution systems under both normal and degrading conditions.

While these projects provided proof of the concept that expert systems technology may play an important role in power system automation, neither of the above systems addressed the critical issues of performance of the expert systems themselves or the continuous operation that are key requirements for expert systems that play a role in an actual energy management system that integrates both traditional hardware and software based control strategies as well as expert systems based control strategies.

The FIES II program, conducted under CR&D funding from NSFC, has begun to address these requirements.

For FIES II, a breadboard which models the essential power components in a space based power system was constructed. The breadboard allowed MMC to drive a FIES system in a real time, hardware based simulation environment.

The following describes the hardware and software used for FIES II.

FIES hardware is divided into three major subsystems. The first is the Breadboard which contains solar array simulators (power supply modules), batteries, network configuration relays, load simulation modules, measurement networks, and control logic. These components may be configured into a power subsystem (also referred to as a power network) manually at the Bread Board Fault Insertion Panel, via keyboard entry at the Microprocessor Terminal, or through the Graphics/Mouse Interface on the SYMBOLICS Terminal. Four fault types are supported and may be inserted via the Bread Board Front Panel Fault Insertion switches. The fault types include:

- 'opened relay' - which interrupts current through some point in the power subsystem,
- 'closed relay' - which allows fault current to flow to some point in the power subsystem,
- 'resistive shunt' - which causes excessive current drain (1-2 amperes) at some point in the power subsystem, and
- 'direct shunt' - which causes an infinite current sink at some point in the power subsystem that is limited only by the current sourcing capability of the power modules.

The second major hardware subsystem is the Microprocessor. The Sensor Data Acquisition Schedule (SDAS) which is located on the microprocessor provides an operating system for managing and monitoring the Bread Board Subsystem. A bit oriented memory map allows individual control over the network configuration relays. Writing a '1' to the corresponding memory bit forces a relay contact closure and writing a '0' forces the relay contacts open. In this way, various power networks can be dynamically configured for evaluation and demonstration of the fault isolating capabilities of FIES.

The Microprocessor provides hardware for monitoring the voltage and current levels at 24 sensor node locations in the power subsystem. It is also equipped with added I/O capabilities for interfacing to the Bread Board Front Panel, the Monitor Terminal, and the SYMBOLICS machine.

The third hardware subsystem is the SYMBOLICS LISP machine. The SYMBOLICS provides the processing environment for the Expert System software, which is an extension of the Automated Reasoning Tool (ART). Graphic capabilities supported by the SYMBOLICS terminal provides a user environment that is easy to master.

The FIKE II software is divided into three main subsystems (or layers). The layer closest to the Bread Board is the Sensor Data Acquisition Scheduler (SDAS) whose task is to coordinate the activities of the microprocessor. These activities include controlling the Bread Board hardware, monitoring the sensor measurement nodes for steady or fault states, and handling communications with the SYMBOLICS.

The middle layer, the Expert System Communications Interface, resides on the SYMBOLICS. Its activities include communicating with the microprocessor, supervising the sensor load network configuration, managing the sensor load measurement data, interacting with human operators, and interfacing to the Expert System.

The outermost layer is the Expert System itself. Its activities include interacting with the Expert System Interface and hypothesizing the source of faults manually introduced via the Fault Insertion Panel on the Bread Board.

CHAPTER 2

TUTORIAL: A SIMPLE EXAMPLE

TUTORIAL: A SIMPLE EXAMPLE

2.0 Overview

This section provides a programmed instruction approach to operating the FIES II system. A new user should be able to successfully execute all the instructions in the sequence prior to attempting to use the more sophisticated options provided by the system. Upon completion of the instructions, the user should have a basic understanding of how to operate the FIES II system. This tutorial is presented in 3 phases, hardware initialization, software initialization, and runtime. For each of the phases there is a flow chart in Appendix A keyed to the following text. Where appropriate, nodes in the flow chart reference graphic displays that are copies of what an operation should produce at each step in the sequence.

2.1 Hardware Initialization

Steps 2.1.1 thru 2.1.4 are concerned with correct initialization of the hardware.

2.1.1 Power up the breadboard. This is accomplished by throwing the main circuit breaker on the breadboard front panel to the "ON" position.

2.1.2 Ensure that all faults have been removed from the network. This implies that none of the 48 relay switches are toggled up or down. Ensure that the operating constraints detailed in chapter 6 are in effect.

2.1.3 Verify that the microprocessor operating system has completed self test. Operating system load and self test will occur automatically when the breadboard is powered on. Successful completion is verified by the presence of a '-' prompt on the microprocessor terminal.

2.1.4 Boot the Symbolics processor. This is accomplished by entering: `logout` `<return>` then: `halt machine` `<return>`. At this time the system will prompt for input. Enter `boot art.boot` `<RETURN>`. Booting the system will take about 3 minutes. Verify that the boot sequence has completed by observing the "please login message" on the terminal.

2.2 Software Initialization

Steps 2.2.1 thru 2.2.9 are concerned with correct initialization of system and application software.

2.2.1 Enter "SDAS.EXE" at the microprocessor terminal. The system should not respond in any way.

2.2.2 Turn the switch on the front panel of the breadboard to self test. This should result in a sequence of relay led configurations displayed on the breadboard.

2.2.3 After observing the "self test completed" message on the breadboard status display, return the front panel switch to reset.

2.2.4 After observing the "system has been reset" message on the breadboard status display, turn the front panel switch to slave mode. Verify that the status display reads "SYMBOLICS MODE".

2.2.5 At the Symbolics terminal enter (login 'files-... production). This will cause the interface software to be loaded. If the "MORE" message appears at the bottom of the terminal, simply depress the space bar.

2.2.6 Enter ART by depressing the SELECT key, waiting 2-3 seconds and then entering A. Verify that you are in the ART command window, more recent versions of ART go to the next step (clear) automatically.

2.2.7 In response to the `= >` prompt in the ART command window, enter "clear". Verify that the system clears. If no prompt is visible after a clear, depress `<RETURN>`.

2.2.8 In response to the = > prompt in the ART command window, enter "load". The system will respond by prompting for a file name. Enter c: > files-art-production> load-files.lisp. Observe that the entire system is loaded by watching that rules compile as they are loaded. This will take about 5 minutes. Upon completion the system should display the = > prompt.

2.2.9 In response to the = > prompt enter reset. The system will initialize the ART schemata and database. This will take about 3 minutes.

2.3.0 Initiate Runtime

Sections 2.3.1 thru 2.3.10 describe the steps taken to run a fault isolation case.

2.3.1 In response to the = > prompt in the ART command window enter "run". The system should transfer control to the LISP interface schematic display.

2.3.2 Position the mouse to the middle of the display and click once on the middle button. This should result in a pop up menu.

2.3.3 Position the crosshair cursor to the RETRIEVE CONFIGURATION option in the menu. Observe that a box appears around the option. Now click on the left mouse button.

2.3.4 A window should now appear at the top of the screen. In response to the "enter file name" prompt type in msfc-demo-1.cnf and hit return.

2.3.5 Observe that the configuration stored in the above file has been loaded into the LISP interface schematic display.

2.3.6 Click on the middle mouse button, resulting in the pop up menu. Now select the download configuration option and click left on the mouse.

2.3.7 Watch the Fies interface status display. When the message in the display reads "I/O wait: fault data" you may insert a fault in the breadboard.

2.3.8 Ensure that the second shunt type switch is toggled down to direct. Then toggle the relay numbered 23 down. This introduces a direct short on the path leading from power module 2 to the low power bus.

2.3.9 The microprocessor will then transfer the faulted state to the LISP machine. Following this data transfer, control will be passed to ART. ART will run the FIES application. Typical times for this will be between 1.5 and 4 minutes.

2.4 Repeated Runs

It is not necessary to complete the entire sequence described above for every fault isolation run. Once the ART application has been loaded (step 2.2.8) there is no need to reload it. The procedure for a repeated run is to begin with step 2.2.9, continuing through section 2.3.9 until completion.

CHAPTER 3

SYSTEM VERSIONS

SYSTEM VERSIONS

3.0 Overview

MMC has provided two FIES II systems. The first of these systems is called the production version. This system operates in near-real time mode. For this reason, the production version offers no explanation facility beyond that of the screen that displays fault types and locations. The second of these systems is called the interactive system. Here the user can examine the behavior of the LISP interface and the sort runtime environment through a variety of switches available through both LISP and ART.

3.1 Production Version

The operating instructions for the production version appear below. These steps are represented graphically by the flowchart for the production version which appears in Appendix A.

3.1.1 Hardware Initialization

Steps 3.1.1 thru 3.1.4 are concerned with correct initialization of the hardware.

3.1.1.1 Power up the breadboard. This is accomplished by throwing the main circuit breaker on the breadboard front panel to the "ON" position.

3.1.1.2 Ensure that all faults have been removed from the network. This implies that none of the 48 relay switches are toggled up or down. Ensure that the operating constraints detailed in chapter 6 are in effect.

3.1.1.3 Verify that the microprocessor operating system has completed self test. Operating system load and self test will occur automatically when the breadboard is powered on. Successful completion is verified by the presence of a '-' prompt on the microprocessor terminal.

3.1.1.4 Boot the Symbolics processor. This is accomplished by entering: logout <return> then: machine halt <return>. At this time the system will prompt for input. Enter boot art.boot <RETURN>. Booting the system will take about 3 minutes. Verify that the boot sequence has completed by observing the "please login message" on the terminal.

3.1.2 Software Initialization

Steps 3.1.2.1 thru 3.1.2.9 are concerned with correct initialization of system and application software.

3.1.2.1 Enter "SDAS.EXE" at the microprocessor terminal. The system should not respond in any way.

3.1.2.2 Turn the switch on the front panel of the breadboard to self test. This should result in a sequence of relay leds configurations displayed on the breadboard.

3.1.2.3 After observing the "self test completed" message on the breadboard status display, return the front panel switch to reset.

3.1.2.4 After observing the "system has been reset" message on the breadboard status display, turn the front panel switch to slave mode. Verify that the status display reads "SYMBOLICS MODE".

3.1.2.5 At the symbolics terminal enter (login 'fies... production). This will cause the interface software to be loaded. If the *MORE* message appears at the bottom of the terminal, simply depress the space bar.

3.1.2.6 Enter ART by depressing the SELECT key, waiting 2-3 seconds and then entering A. Verify that you are in the ART command window more recent versions of ART go to the next step (clear) automatically.

3.1.2.7 In response to the = > prompt in the ART command window, enter "clear". Verify that the system clears. If no prompt is visible after a clear, depress <RETURN>.

3.1.2.8 In response to the = > prompt in the ART command window, enter "load". The system will respond by prompting for a file name. Enter the string C: > files-art-production> load-files.lisp. Observe that the entire system is loaded by watching that rules compile as they are loaded. This will take about 5 minutes. Upon completion the system should display the = > prompt.

3.1.2.9 In response to the = > prompt enter reset. The system will initialize the ART schemata and database. This will take about 3 minutes.

3.1.3 Initiate Runtime

Sections 3.1.3.1 thru 3.1.3.9 describe the steps taken to run a fault isolation case.

3.1.3.1 In response to the = > prompt in the ART command window enter "run". The system should transfer control to the LISP interface schematic display.

3.1.3.2 Position the mouse to the middle of the display and click once on the middle button. This should result in a pop up menu.

3.1.3.3 Position the crosshair cursor to the RETRIEVE CONFIGURATION option in the menu. Observe that a box appears around the option. Now click on the left mouse button. Alternatively the user may enter a configuration by mousing on the desired relays. If this is done the user may skip step 3.1.3.4.

3.1.3.4 A window should now appear at the top of the screen. In response to the "enter file name" prompt type in the name of the desired configuration file.

3.1.3.5 Observe that the configuration stored in the above file has been loaded into the LISP interface schematic display.

3.1.3.6 Click on the middle mouse button, resulting in the pop up menu. Now select the download configuration option and click left on the mouse.

3.1.3.7 Watch the Fies interface status display. When the message in the display reads "I/O wait: fault data" you may insert a fault in the breadboard

3.1.3.8 Insert the required fault in breadboard.

3.1.3.9 The microprocessor will then transfer the faulted state to the LISP machine. Following this data transfer, control will be passed to ART. ART will run the FIES application. Typical times for this will be between 1.5 and 4 minutes.

3.1.4 Repeated Runs

It is not necessary to complete the entire sequence a described above for every fault isolation run. Once the ART application has been loaded (Step 3.1.2.8) there is no need to reload it. The procedure for a repeated run is to begin with step 3.1.2.9, continuing through section 3.1.3.9 until completion.

3.2 Interactive Version

Operation for the interactive model is described in the following section. This version allows the operator to step through the runtime system, examining steady state and faulted data, as they are received by the LISP interface, setting up ART runtime options and finally controlling the execution of the ART application.

In general, the operation is very similar to the operations described in the tutorial. The major differences are the directory from which the applications is loaded and the availability of ART options during runtimes.

The operating instruction for the interactive version appear below. These steps are represented graphically by the flowchart for the interactive version in Appendix A.

3.2.1 Hardware Initialization

Steps 3.2.1.1 thru 3.2.1.4 are concerned with correct initialization of the hardware.

3.2.1.1 Power up the breadboard. This is accomplished by throwing the main circuit breaker on the breadboard front panel to the "ON" position.

3.2.1.2 Ensure that all faults have been removed from the network. This implies that none of the 48 relay switches are toggled up or down. Ensure that the operating constraints detailed in chapter 6 are in effect.

3.2.1.3 Verify that the microprocessor operating system has completed self test. Operating system load and self test will occur automatically when the breadboard is powered on. Successful completion is verified by the presence of a "-" prompt on the microprocessor terminal.

3.2.1.4 Boot the symbolics processor. This is accomplished by entering: logout <return> then: halt machine. At this time the system will prompt for input. Enter boot art.boot <RETURN>. Booting the system will take about 3 minutes. Verify that the boot sequence has completed by observing the "please login message" on the terminal.

3.2.2 Software Initialization

Steps 3.2.2.1 thru 3.2.2.9 are concerned with correct initialization of system and application software.

3.2.2.1 Enter "SDAS.EXE" at the microprocessor terminal. The system should not respond in any way.

3.2.2.2 Turn the switch on the front panel of the breadboard to self test. This should result in a sequence of relay leds configurations displayed on the breadboard.

3.2.2.3 After observing the "self test completed" message on the breadboard status display, return the front panel switch to reset.

3.2.2.4 After observing the "system has been reset" message on the breadboard status display, turn the front panel switch to slave mode. Verify that the status display reads "SYMBOLICS MODE".

3.2.2.5 At the symbolics terminal enter (login 'fies-- interactive). This will cause the interface software to be loaded. If the *MORE* message appears at the bottom of the terminal, simply depress the space bar.

3.2.2.6 Enter ART by depressing the SELECT key, waiting 2-3 seconds and then entering A. Verify that you are in the ART command window (more recent versions of ART go to the next step (clear) automatically).

3.2.2.7 In response to the = > prompt in the ART command window, enter "clear". Verify that the system clears. If no prompt is visible after a clear, depress <RETURN>.

3.2.2.8 In response to the = > prompt in the ART command window, enter "load". The system will respond by prompting for a file name. Enter the string C: > files-art-interactive> load-files.liup. Observe that the entire system is loaded by watching that rules compile as they are loaded. This will take about 5 minutes. Upon completion the system should display the = > prompt.

3.2.2.9 In response to the = > prompt enter reset. The system will initialize the ART schemata and database. This will take about 3 minutes.

3.2.3 Initiate Runtime

Sections 3.2.3.1 thru 3.2.3.10 describe the steps taken to run a fault isolation case.

3.2.3.1 In response to the = > prompt in the ART command window enter "run". The system should transfer control to the LISP interface schematic display.

3.2.3.2 Position the mouse to the middle of the display and click once on the middle button. This should result in a pop up menu.

3.2.3.3 Position the crosshair cursor to the RETRIEVE CONFIGURATION option in the menu. Observe that a box appears around the option. Now click on the left mouse button. Alternatively the user may enter a configuration by mousing on the desired relays. If this is done the user may skip step 3.3.4.

3.2.3.4 A window should now appear at the top of the screen. In response to the "enter file name" prompt type in the name of the file and hit return.

- 3.2.3.5 Observe that the configuration stored in the above file has been loaded into the LISP interface schematic display.
- 3.2.3.6 Click on the middle mouse button, resulting in the pop up menu. Now select the download configuration option and click left on the mouse. After the configuration has been loaded and the steady state table returned to the LISP interface, the user may examine the steady state data using the EXAMINE STEADY STATE menu option.
- 3.2.3.7 Watch the Fies interface status display. When the message in the display reads "I/O wait: fault data" you may insert a fault in the breadboard
- 3.2.3.8 Insert the required fault into the breadboard.
- 3.2.3.9 The microprocessor will then transfer the faulted state to the LISP machine. The user may then examine the faulted state, using the EXAMINE Breadboard data menu option.
- 3.2.3.10 The user may now set up the ART runtime environment. This is accomplished by clicking on "WATCH" in the ART ROOT MENU and selecting 1 or more of the rules, facts, goals, agenda, activations, statistics and dribble options. Then click twice on the middle mouse button to return to the ROOT menu. Now click on "RUN" to start the application.

3.2.4 Repeated Runs

It is not necessary to complete the entire sequence as described above for every fault isolation run. Once the ART application has been loaded (Step 3.2.2.8) there is no need to reload it. The procedure for a repeated run is the begin with step 3.2.2.9, continuing through section 3.2.3.10 until completion. If any of the WATCH options have been turned on, the user should turn them off prior to the reset command. Failure to do so will cause errors in the interface between LISP and ART.

CHAPTER 4
LISP INTERFACE OPTIONS

LISP INTERFACE OPTIONS

4.0 Overview

This section provides a description of the options available in the LISP interface. It is anticipated that these options will be primarily used in conjunction with the interactive version of the FIES system.

4.1 Structure

Options are provided through a menu system. The menu system is only one level deep, that is, the only option available to a user after selecting and executing an option from the main menu is to return to the main menu.

4.2 Options

The following options are available through the menu system. Each of the options is described below.

4.2.1 Download Configuration

This option is used to download a configuration to the microprocessor prior to a run. The configuration is specified either by using the RETRIEVE CONFIGURATION menu option to load a previously saved configuration into the display or by clicking the required relays off or on using the mouse.

4.2.2 Retrieve Configuration

This option is used to load a previously saved configuration into the display from the files-library-directory. Upon clicking left on this menu item the user should observe a window at the top of the screen. The window may be exited by using the ABORT key.

Once the window is visible, type in the name of the file corresponding to the desired configuration. After the name is entered, hit <RETURN>. The window should

disappear and the user should observe that the configuration has been loaded into the display. If the file does not exist the message "file does not exist" will appear in the FIES Interface Status window. At this point the user will be reprompted for the file name. Use the ABORT key to exit the window or reenter the file name. In order to view all saved configurations, the user should use the LISP machine file system. This is accomplished by the following steps:

- 1) SELECT F
- 2) Click left on TREE EDIT ANY Option
- 3) Enter c:files > files-library > *.*.*

The user should maintain this directory using commands native to the LISP environment. These commands are discussed in the ZMACS edit manual.

4.2.3 Archive Configuration

This option is used to store a configuration that is currently loaded in the display into a file in the files-library directory.

After selecting this option, the user should observe a window at the top of the display. Enter the name of the file in which the configuration is to be stored and hit <RETURN>. If the file already exists the message "File exists" will appear in the FIES Interface status window. In this case, the user will be reprompted for a new file name. Enter the new file name or use the ABORT key to exit the window.

While any naming conventions may be used, it is suggested that a common extension such as ".cnf" be employed. This is the extension use for MHC provided configuration files. A directory name need not be entered, as the default will be to store the files in c: > files > files-library.

4.2.4 Examine Steady State Data

This option allows the user to examine the state of the breadboard following a download and the subsequent transmission of the steady-state table to the LISP machine. To return from the steady state window display, the user should click the middle mouse button and select the option "RETURN TO PREVIOUS SCREEN".

4.2.5 Examine Breadboard Data

This option may only be used in the interactive version of the system. The option allows the user to examine the state of the breadboard following fault insertion and the subsequent transmission of the fault table to the LISP machine. To return from the breadboard window display, the user should click the middle mouse button and select the option "RETURN TO PREVIOUS SCREEN".

4.2.6 Art Command Window

This option is only useful in the interactive version of the system. Typically, it is used following a configuration download steady state transmission, fault insertion and fault state transmission. It allows the user to transfer control to ART after reviewing the data (i.e. using examine steady state or examine breadboard data command options).

If the option is used in any other sequence, result of the ART run will be meaningless since ART is expecting a fault state data input.

4.2.7 QUIT

This option allows the user to exist the interface and return to the LISP LISTENER.

CHAPTER 5
INSTALLATION GUIDE

INSTALLATION

5.0 Overview

This section details the steps necessary to install the FIES software. Installation includes microprocessor, LISP machine interface and expert system software.

5.1 Microprocessor Installation

- 5.1.1 Ensure that the IRMX operating system has been correctly installed. This may be accomplished by booting the microprocessor and observing that the microprocessor self confidence test runs to completion.
- 5.1.2 Use the backup utility to load the FIES microprocessor software from the 8" floppy disk to the winchester.
- 5.1.3 Enter "SDAS.EXE" from the microprocessor console. If there is no response, the system is functioning normally.
- 5.1.4 Further microprocessor software verification test procedures may be found in the test and demonstration plan document.

5.2 Lisp Machine Interface Software Installation

- 5.2.1 Mount the cartridge tape containing the FIES system in the tape drive.
- 5.2.2 Create the following directories:
 - 1) c: > fies
 - 2) c: > fies > fies-library
 - 4) c: > fies > fies-art-production
 - 5) c: > fies > fies-art-interactive
- 5.2.3 From the Symbolics terminal, enter the file system editor by entering SELECT F.

5.2.4 Click the mouse left on Local File Maintenance option in the File System editor command window.

5.2.5 Click the mouse left on the Reload/Retrieve option in the command window.

5.2.6 Enter the following pathnames into the options window:

- 1) c: > fies > *.*.*
- 2) c: > fies > fies-library *.*.*
- 3) c: > fies > fies-test-library *.*.*
- 4) c: > fies > fies-art-production *.*.*
- 5) c: > fies > fies-art-interactive *.*.*

5.2.7 Click left on the Reload all option in the options window.

5.2.8 Click left on DO IT in the options window.

5.2.9 Observe that the files have been loaded into the appropriate directories

5.2.10 From the Lisp Listener, enter (logout).

5.2.11 From the Lisp Listener, enter (login 'fies). Observe that the FIES Interface software is loaded into the system.

5.2.12 Further LISP interface software verification procedures may be found in the test and demonstration plan document.

5.3 Expert System Installation

5.3.1 Installation of the expert system application is accomplished at the same time the LISP machine interface software is installed.

CHAPTER 6
OPERATING CONSTRAINTS

OPERATING CONSTRAINTS

6.0 This chapter details operational constraints for the breadboard. These conditions must be in effect at runtime for the conclusion of a successful demonstration. Section 6.4 presents a Breadboard Readiness checkout procedure.

6.1 Constraints

Sink - Source relationships

The sum of the amperages drawn by sinks (loads) in the system must be less than or equal to the sum of amperages supplied by sources (solar arrays and batteries in the system). Each solar array is capable of providing approximately 1.8 amps. A battery is considered to be capable of safely providing .5 amps to the system. Hence the configuration in example 6-1, which draws 3.74 amps is permissible, while the configuration in example 6-2, which draws 4.84 amps is not.

6.2 Single Battery Configuration


As stated in 6.1, no battery should drive loads requiring more than .5 amps

6.3 Battery Maintenance

Batteries should be fully charged prior to any demonstration of the system. Failure to do so will result in spurious faults in most configurations, resulting in incorrect diagnosis by the expert system.

Since there is no way to determine whether or not a battery is fully charged, all batteries should be trickle charged for 8 hours in advance of any demonstration. Using the test-configuration utility to download the battery charge configuration (Example 6-3) to the breadboard and allowing the breadboard to remain stable for at least 8 hours.

A detailed discussion of battery maintenance and recharging may be found in chapter 7.0.

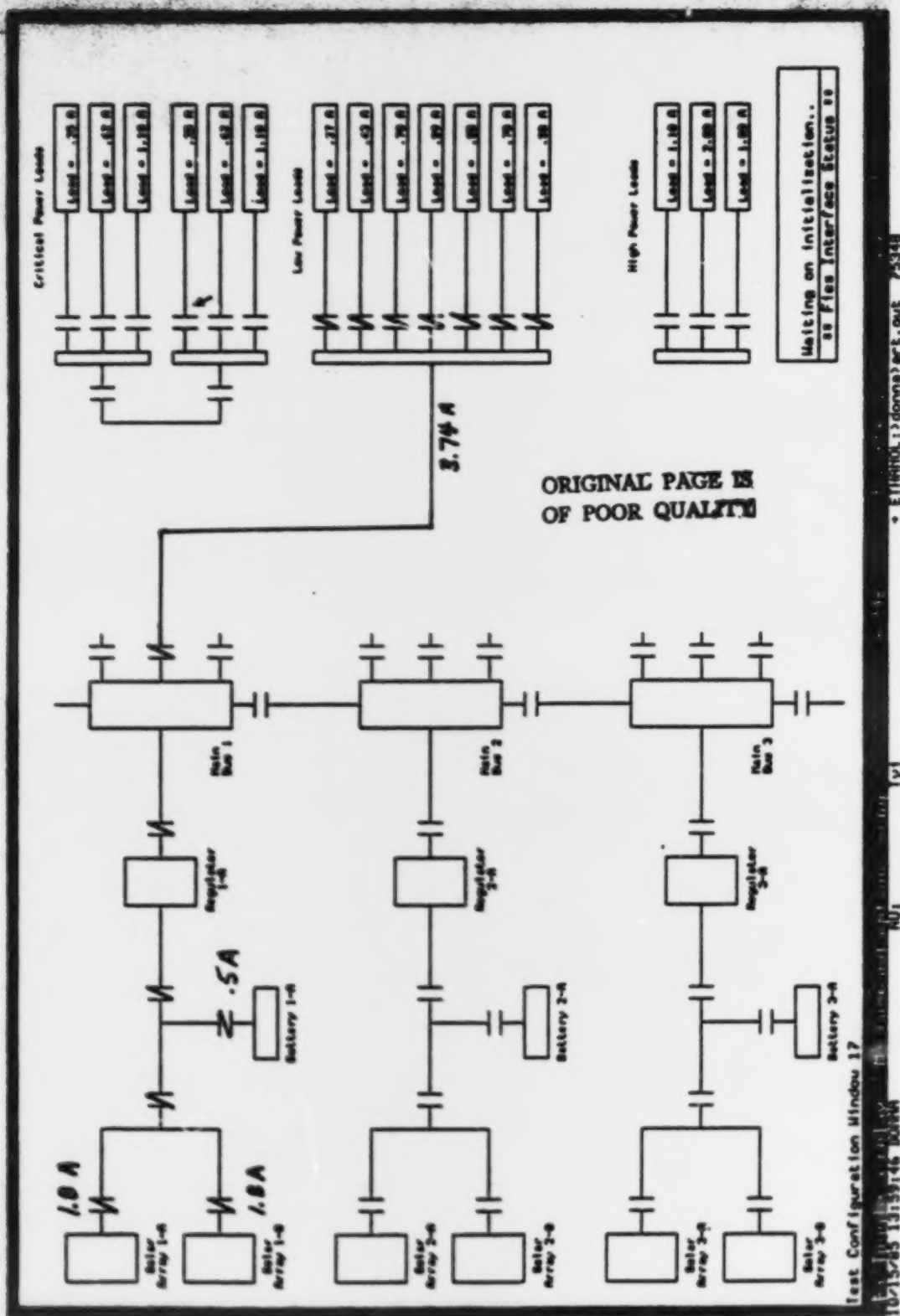

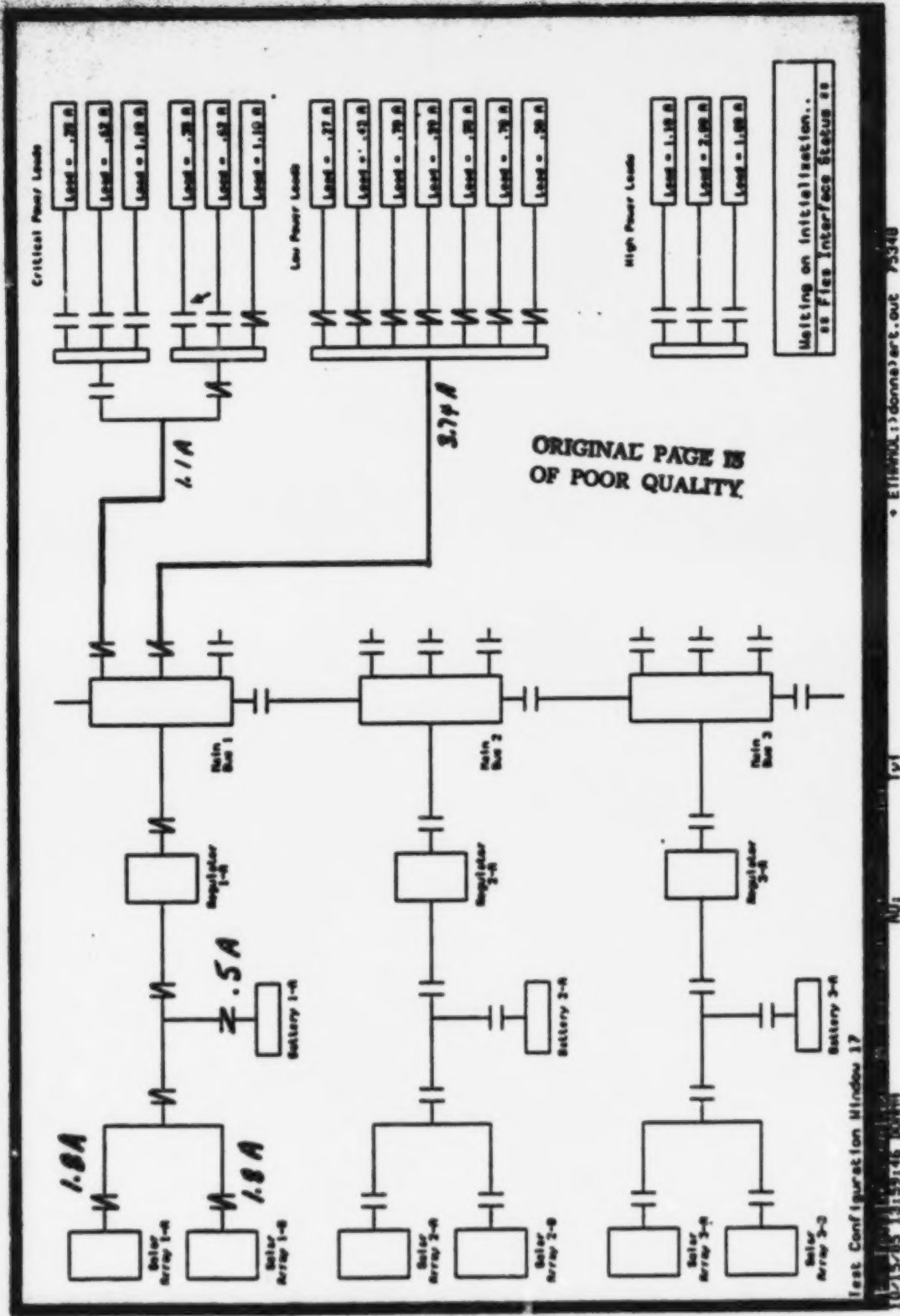


Figure 6-2

6.4 Breadboard Readiness Checkout Procedure

6.4.1 Because the microcomputer system "learns" what the correct voltage and current conditions are for a given configuration during the download phase, it is important to be sure that the what is "learned" is proper for the configuration.

Some examples of improper downloading are:

- a) A fault exists in the network from a previous run. If the fault was not removed prior to downloading a new configuration, this fault is learned as being part of the new configuration.
- b) Power Supply voltages not set properly. If one of the desired power supplies has been turned off or has had its voltage re-adjusted for battery charging, the over/under voltage condition will be treated as proper.
- c) Batteries not fully charged. If one of the batteries has had significant current used, power will be diverted from the intended path to charge the battery. This can result in insufficient power being available to drive the network, or cause the battery voltage to drift during a run.
- d) Downloading of configurations which cause the breadboard protection circuitry to activate.

6.4.2 To insure that the downloaded configuration will be meaningful, two important steps must be followed.

6.4.2.1 Insure that the desired configuration is both meaningful and allowable from an electrical sense.

The network is fairly versatile and will allow improper configurations to be placed upon it. Those conditions which are likely to damage the network will be removed, but the configuration imposed on the network will undoubtedly be meaningless.

Some examples of configurations to avoid are:

- a) Those which connect the output of more than 1 voltage regulator together.

- b) Those which require more power to be supplied than is available.
- c) Those which charge a battery from a module other than the one in which the battery resides.
- d) Those which charge a deeply depleted battery.

A tool has been made available to assist in "trying out" selected configurations prior to linking the configuration with expert system. This tool is interactive and allows the user to verify that the configuration is meaningful. This tool is described in Chapter 8, titled Test Configuration Utility.

ACTION	VERIFICATION OF COMPLETENESS
Place rotary switch in 'Reset' position.	Message "System has been reset" will be visible in the alphanumeric display.
Place all toggle switches on will the fault insertion panel to the center or 'normal' position.	No LED's will be on, and no current be drawn from any of the H.P. supplies.
If current is still being drawn from the H.P. supplies, turn supply off, the on. This resets the SCR's which provide the direct short faults.	No current is being drawn from the H.P. supplies.
Reset the circuit breakers on the battery modules by pressing the center pole of the breaker in.	The breaker center pole is flush with the breaker "plate".
Verify that the batteries have a normal voltage. Place the rotary switch in the 'status' position. Key in 22 on the thumbwheel switch. depress the 'Repeat Function' button. Repeat for 23, 24.	The alphanumeric display contains the normal unloaded voltage for a fully charged battery, 33.75V.
Place the rotary switch in the 'slave' position.	Message 'SYMBOLICS SRC MODE' will be visible in the alphanumeric display

6.4.2.2 Secondly, the breadboard must be ready to accept the meaningful configuration. Following the steps below will place the breadboard in a condition for receiving configurations.

6.4.3 The breadboard is now ready to accept a new configuration from the Symbolics machine. After the configuration has been downloaded, and the message 'STEADY STATE ACHIEVED' is visible, the breadboard is ready to be faulted.

As an additional verification that the downloaded configuration is proper check that the front panel lamps (corresponding to the activated load areas) are glowing with full intensity. This indicates that the network has received full power to the loads.

CHAPTER 7

BATTERY MAINTENANCE AND RECHARGING

BATTERY MAINTENANCE AND RECHARGING

7.0 OVERVIEW

The Power Subsystem Automation Study Breadboard incorporates three Nickel-Cadmium batteries. These batteries are composed of 25 cells, mounted in a stainless steel case. The cells have a capacity of approximately 14 amp-hours. The batteries were manufactured in Colorado Springs, Colorado by Eagle-Picher Industries. Connection to the batteries is made through connector type MS3124T-10-6P. Pins A, B, C, are the positive terminal of the battery, while pins D, E, F are the negative terminal.

The batteries are able to be trickle charged by the breadboard. This is primarily intended to be a "station keeping" function rather than a complete charge ramp up. The relay connecting the battery to the power network does not need to be closed, nor does the circuit breaker need to be reset. Extra power available from the Hewlett-Packard power supplies is diverted to replenishing the consumed power. This allows configurations to be tested on the breadboard which don't actually use the battery as a power source.

7.1 * * * CAUTION * * *

If a configuration was placed on the breadboard which required the battery to supply a large portion of its capacity, the resulting trickle charge occurring on subsequent runs may cause false error reporting to the Expert System. The errors can result from the following situation:

- 1) Some configuration was run in which a large amount of current was drawn from a battery. The run completed normally, leaving the battery in a state which will require more than 10% of the H.P. supplies capacity to re-charge.
- 2) A new configuration is downloaded to the breadboard for testing. This configuration does not use the battery, but does connect the power supplies of the same power module to the network. Trickle charging of the battery begins.
- 3) The microprocessor "learns" the new configuration voltages and currents and ships them to the expert system. The microprocessor issues the message "Steady State Achieved" and awaits a fault.

- 4) During this time the battery is re-charging. Its voltage is increasing, and the trickle charge current is diminishing. The microcomputer will determine that this is a fault, and erroneously uplink fault data.

This situation can be avoided if a charge situation is placed on the battery sufficient to reduce the trickle current to 200 mA or less prior to the subsequent runs.

7.2 Periodic Maintenance

The batteries will also require periodic maintenance to assure continued stable characteristics. This involves performing a deep cycle discharge and recharging. The procedure outlined in the Battery Maintenance Manual (supplied by Eagle-Picher) should be used. This procedure may be followed by removing the batteries to a remote location where a constant current source is available. Alternatively, the procedure may be closely approximated by leaving the batteries in the system and following the steps outlined below:

7.2.1 Simultaneous discharge of batteries

The batteries may be discharged simultaneously while in the breadboard at a one hour rate. This is useful in observing the characteristics of the batteries. Loads equivalent to 1.1 amperes can be obtained on each of the load busses in the network. A battery in each power module can be connected to these equivalent 1.1 ampere loads.

Figure 7.1 shows the discharge characteristic for the battery in module 3. Notice that the battery drops quickly from its unloaded voltage of approximately 35 volts to the normal loaded voltage of 31.6 volts. From here the voltage remains relatively stable until the dropoff voltage of 29.3 volts. Here the battery output avalanches to 20 volts within a period of several minutes.

As the voltage regulation scheme chosen for the breadboard is linear, and requires approximately 2.0 volts of margin between the unregulated source and its output, the battery actually has a useful lifespan of 13 AMP-HOURS.

7.2.2 Discharge of a single battery

A single battery may be rapidly discharged at up to a 5 A-H rate by connecting loads on each of the high power, low power, and critical busses.

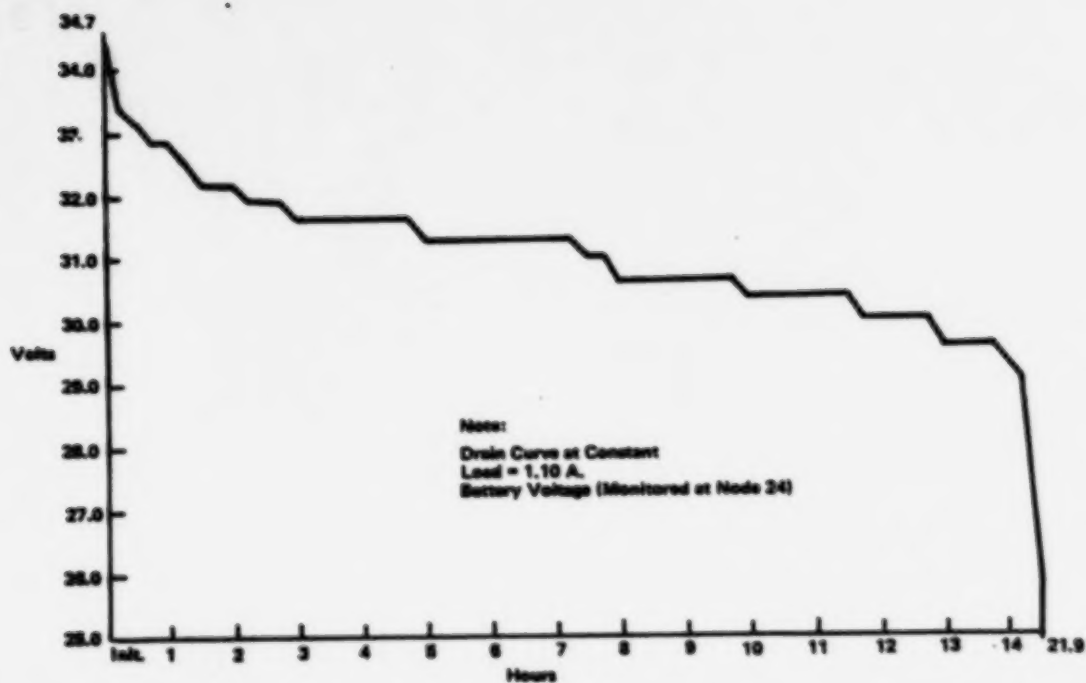


Figure 1 | PSAS Battery No. 3 Discharge Characteristics

7.2.3 Charging of Batteries

The breadboard is able to charge the batteries in a "constant potential" mode only. However, a constant current charge can be approximated. This approach requires operator intervention at intervals of 1 hour, but has the advantage of completing the charge cycle in less than 1 day. Also, all three batteries may be charged in the system at the same time. Follow the steps below to charge the battery from a discharged condition:

- 1) Initialize the breadboard and the microcomputer system. Place the network in a configuration where the relays are all open.
- 2) Using a voltmeter connected to the sense jacks on the H.P. supply faceplate, set the voltage on both power channels from 38.5 volts to 40.5 volts. Assure that the current limit on the supply is wide open.
- 3) Close the relays along the path from the supplies to the battery, leaving all other relays open. Verify that current is being drawn evenly from both power supplies by observing the meters on the H.P. supplies. Adjust the voltage until a balance of current is drawn from both power channels in the 6255A supply.
- 4) Using the front panel display; examine the battery voltage. This is available at nodes 22, 23, 24 for the batteries in power modules 1, 2, and 3 respectively. Note that the current sensors at the battery are disabled and forced to zero. The initial battery voltage should be approximately 33 volts.
- 5) Monitor the current flowing into the batteries in modules 1, 2, 3 at the nodes 3, 9, 15. The initial reading of battery current at this point should be approximately - 3.0 Amperes. However, this reading will rapidly diminish to the - 2.5 A range. The minus sign at this node indicates that current is flowing into the battery.

- 6) Continue monitoring the current flowing into the battery. Usually, once an hour will be sufficient to re-adjust the current. As the current drops below 2.0 Amperes, adjust the voltage upwards on both power channels of the H.P. supply. As a guideline, increasing the voltage on each power channel by .5V will return the battery current to the 2.5A range.
- 7) Figure 7.2 is an example of this type of charging practice used on the battery in power module 3. The charging cycle may be terminated when the accumulated charge (the area under the current plot) reaches 14 AMP-HOURS. Alternatively, the charge may be terminated when the battery voltage displays the "head and shoulders" characteristic shown in the figure.

The battery protection hardware will prevent the battery from overcharging (by shunting away excess current and limiting the raise in battery voltage to 39.0V), but charging should be terminated when either of the above two conditions is reached.

* * * CAUTION * * *

Finally, return the H.P. supply voltages to 38.5 volts. Failure to do this will overdrive the voltage regulator when power is applied to the regulator circuit from the supplies.

The battery connections to the battery protection circuitry have been sealed in plastic cement. Do not attempt to defeat this protection. Never remove the batteries from the battery module unless they have been drained of power first.

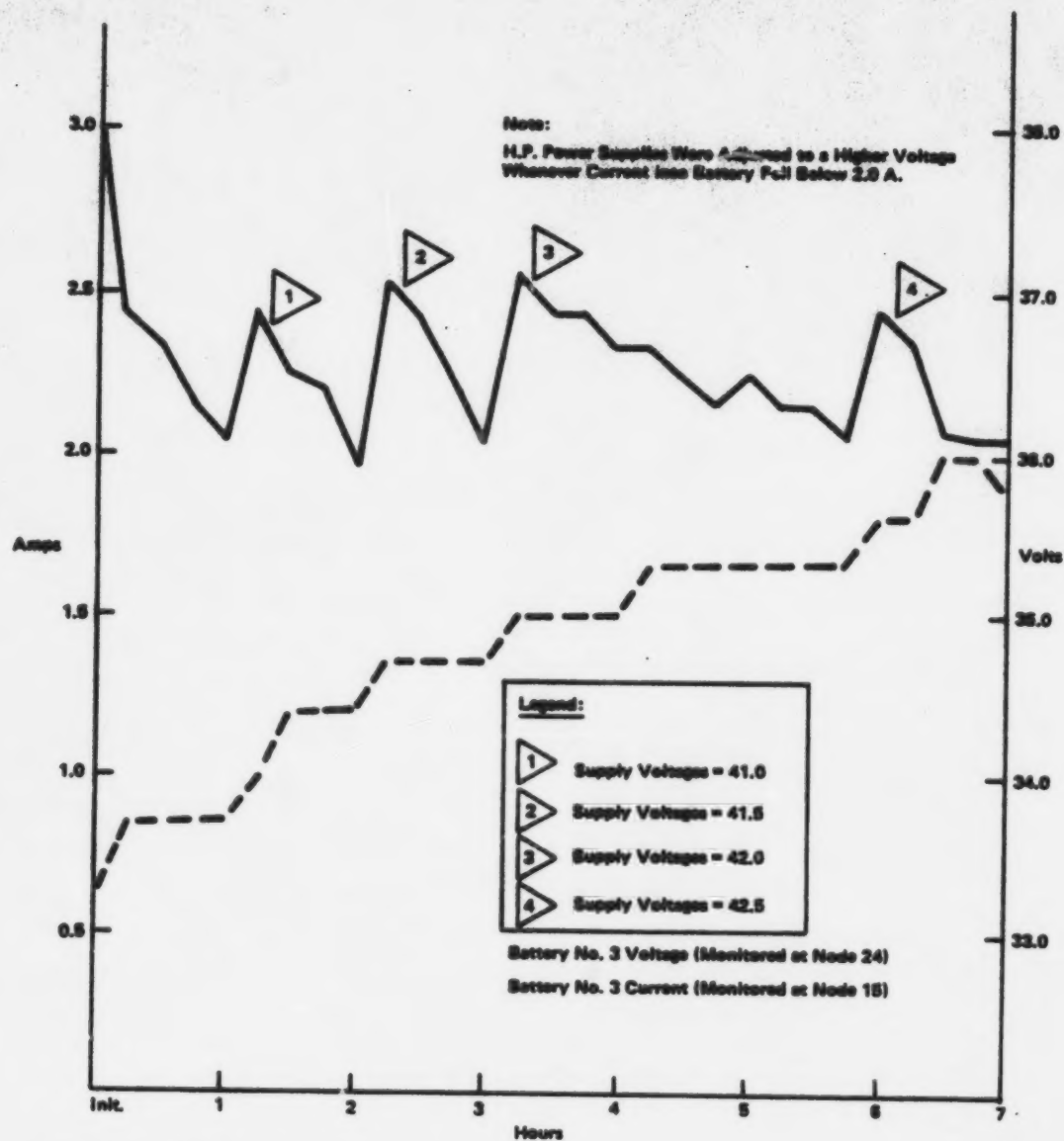


Figure 2 PSAS Battery No. 3 Charge Characteristics

CHAPTER 8

TEST CONFIGURATION UTILITY

TEST CONFIGURATION UTILITY

8.0 Overview

This section provides a description of the test configuration utility. The purpose of this program is to allow the user to exercise the interface between the microprocessor and the LISP machine without the overhead involved in a full ART run. This program will be used for system verification prior to a run or for problem determination.

8.1 Program Startup

The program is invoked from a LISP LISTENER by entering (test-configuration).

8.2 Test Configuration Options

The following options are available through the menu system. The main menu is handled exactly as described in chapter 4, the only difference being an expanded set of command options.

8.2.1 Download Configuration

This option is used to download a configuration to the microprocessor prior to a run. The configuration is specified either by using the RETRIEVE CONFIGURATION menu option to load a previously saved configuration into the display or by clicking the required relays off or on using the mouse.

8.2.2 Refresh

This option causes the microprocessor to transmit the current state of the breadboard to the LISP machine. The data can then be viewed through the EXAMINE BREADBOARD DATA option.

8.2.3 Retrieve Configuration

This option is used to load a previously saved configuration into the display from the files-library-directory. Upon clicking left on this menu item the user should observe a window at the top of the screen. The window may be exited by using the ABORT key.

Once the window is visible, type in the name of the file corresponding to the desired configuration. After the name is entered, hit <RETURN>. The window should disappear and the user should observe that the configuration has been loaded into the display. If the file does not exist the message "file does not exist" will appear in the FIES Interface Status window.

8.2.4 Archive Configuration

This option is used to store a configuration that is currently loaded in the display into a file in the files-library directory.

After selecting this option, the user should observe a window at the top of the display. Enter the name of the file in which the configuration is to be stored and hit <RETURN>. If the file already exists the message "File exists" will appear in the FIES Interface status window. In this case, the user will be reprompted for a new file name. Enter the new file name or use the ABORT key to exit the window.

While any naming conventions may be used, it is suggested that a common extension such as ".cnf" be employed. This is the extension use for MMC provided configuration files. A directory name need not be entered, as the default will be to store the files in c: > files > files-library.

8.2.5 Examine Steady State Data

This option allows the user to examine the state of the breadboard following a download and the subsequent transmission of the steady-state table to the LISP machine. To return from the steady state window display, the user should click the middle mouse button and select the option "RETURN TO PREVIOUS SCREEN".

8.2.6 Examine Breadboard Data

This option may only be used in the interactive version of the system. The option allows the user to examine the state of the breadboard following fault insertion and the subsequent transmission of the fault table to the LISP machine. To return from the breadboard window display, the user should click the middle mouse button and select the option "RETURN TO PREVIOUS SCREEN".

8.2.7 Retrieve Scenario

This option allows the user to retrieve a data set that has archived a breadboard configuration, the corresponding steady state and a faulted configuration. This data may be used to verify current breadboard values or to drive an ART run.

8.2.8 Archive Scenario

This option allows a user to save a configuration, the corresponding steady state table and a faulted data set. This is used to save data sets for breadboard verification or for testing independent of the breadboard.

8.2.9 Art Command Window

This option passes control to ART. Typically, this option will be used following a Retrieve Scenario command, where the intent is to exercise the ART application independently of the breadboard.

8.2.10 QUIT

This option causes a return to the LISP LISTENER.

APPENDICES

APPENDIX A

Operation Flowcharts and Screens

TUTORIAL


Overview

TEXT

Section 2.1

Section 2.2


Section 2.3

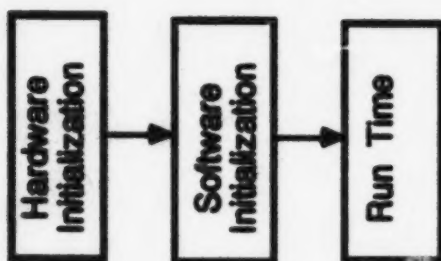

TUTORIAL

TEXT

SCREENS

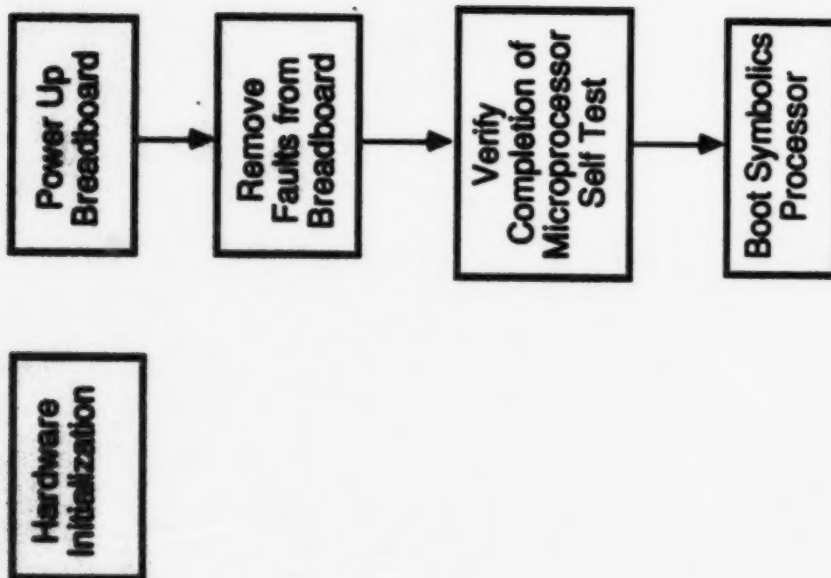

2.1

2.2

2.3

2.4

2.1.4

Symbolics 3670[™] System

This machine is Martin Marietta Danvers Aerospace - Machine Intelligence Lab Einbecker

Symbolics[™] System, Release 6.1
Loaded from FEP0:Amli-r6-1-color.load.1
1536K words Physical memory, 37500K words Swapping space.

Release	6.1
CPU	135.00
OS	48.7
SWAP	35.21
FB	127

You are typing to *Lisp Listener 1*. Control characters are interpreted as commands to edit input. Type Control-~~ESC~~ for a list of input editor commands.

Use the "i:help" command to display a list of all the Command Processor commands.

Type ~~ESC~~ 0 to select the Document Examiner to read online documentation.

Type ~~ESC~~ ~~ESC~~ for a list of programs.

Type ~~ESC~~ ~~ESC~~ ~~ESC~~ for a list of asynchronous and window operations.

Click the rightmost mouse button to select the System Menu of programs and window operations.

Type Symbol-~~ESC~~ for a list of special function keys and special character keys.

Please login.

Lisp Listener 1

SCREEN 2.1.4

(c) Copyright 1985, 1984, 1983, 1982, 1981, 1980, Symbolics, Inc.
All Rights Reserved.

Use the command "Show Legal Notice" to see important legal notices.

Symbolics, Symbolics 3600 and Symbolics 3670 are trademarks of Symbolics, Inc.

TUTORIAL

TEXT

SCREENS

Software
Initialization

Run SDAS.EXE
on
Microprocessor

Microprocessor
Self Test

Microprocessor
Reset

Microprocessor
Communication
Enable

2.2.1


2.2.2

2.2.3

2.2.4

TUTORIAL

TEXT SCREENS

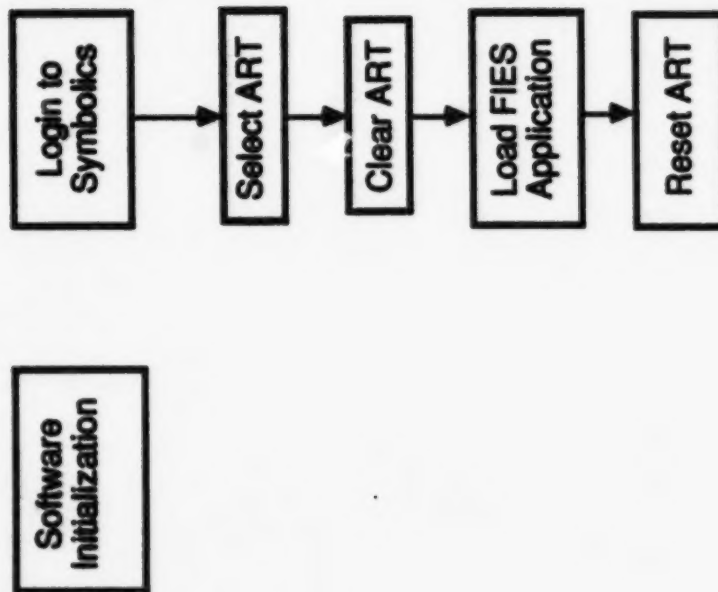

2.2.5

2.2.5

2.2.6

2.2.7

2.2.7

2.2.8.1, 2.2.8.2

2.2.8

2.2.9

2.2.9

ORIGINAL PAGE IS
OF POOR QUALITY

Loading DIOMINI>files-art-production>files-unit-relay-configuration.bin
Loading DIOMINI>files-art-production>files-set-art-sensors.bin
Loading DIOMINI>files-art-production>files-power-distribution-lines-funcs.bin
Loading DIOMINI>files-art-production>files-under-powar-distribution-lines.bin
Loading DIOMINI>files-art-production>files-red-ar-powar-distribution-lines.bin
Loading DIOMINI>files-art-production>files-recat-powar-distribution-lines.bin
Loading DIOMINI>files-art-production>files-archive-configuration.bin
Loading DIOMINI>files-art-production>files-retrieve-configuration.bin
Loading DIOMINI>files-art-production>files-archive-scenario.bin
Loading DIOMINI>files-art-production>files-retrieve-scenario.bin
Loading DIOMINI>files-art-production>files-unit-request.bin
Loading DIOMINI>files-art-production>files-parse-raw-data-for-scenario.bin
Loading DIOMINI>files-art-production>files-start-art-scenario.bin
Loading DIOMINI>files-art-production>files-send-lisp.bin
Loading DIOMINI>files-art-production>files-initialize-nouse.bin
Loading DIOMINI>files-art-production>files-initial-configuration.bin
Loading DIOMINI>files-art-production>files-serial-interface.bin
Loading DIOMINI>files-art-production>files-test-configuration.bin
Loading DIOMINI>files-art-production>files-serial-interface-test.bin
Loading DIOMINI>files-art-production>files-refresh-data-display.bin
Loading DIOMINI>files-art-production>files-serial-interface-level-2.bin
Loading DIOMINI>files-art-production>files-steady-state-data-display.bin
Loading DIOMINI>files-art-production>files-fault-data-display.bin
Loading DIOMINI>files-art-production>files-display-faults-from-art.bin

You are typing to *Lisp Listener*: 1. Control characters are
interpreted as commands to edit input. Type Control-~~END~~
for a list of input editor commands.

Use the "Help" command to display a list of all the Command Processor commands.

Type ~~END~~ D to select the Document Examiner to read online documentation.

Type ~~END~~ ~~END~~ for a list of programs.

Type ~~END~~ ~~END~~ for a list of asynchronous and window operations.

Click the rightmost mouse button to select the System Menu of programs and window operations.

Type Symbol-~~END~~ for a list of special function keys and special character keys.

(login "files-art-production")
Loading DIOMINI>files-art-production>lisp-init.lisp into package USER
Loading DIOMINI>files-art-production>make-files-interface.lisp into package RAT-USER
Loading DIOMINI>files-art-production>files-interface-defs.bin
Loading DIOMINI>files-art-production>files-get-edges.bin
Loading DIOMINI>files-art-production>files-clear-status-window-display.bin
Loading DIOMINI>files-art-production>files-display-status-message.bin
Loading DIOMINI>files-art-production>files-set-configuration-file-name.bin
Loading DIOMINI>files-art-production>files-make-configuration-file-name.bin
Loading DIOMINI>files-art-production>files-get-scenario-file-name.bin
Loading DIOMINI>files-art-production>files-make-scenario-file-name.bin
Loading DIOMINI>files-art-production>files-unidraw-selected-configuration.bin
Loading DIOMINI>files-art-production>files-draw-selected-configuration.bin
Loading DIOMINI>files-art-production>files-set-art-relays.bin

Lisp Listener 1

SCREEN 2.2.5

COMMAND WINDOW

```
>> clear  
Clearing RT...  
>>  
>> █
```

ROOT

```
clear  
load  
reset  
watch  
run  
step  
browse  
miscellaneous  
icon editor  
examples
```

COMMAND WINDOW

```
>> clear
Clearing ART...
>>
>> load
File name: 0
```

ROOT

```
clear
load
reset
watch
run
stop
browse
miscellaneous
icon editor
examples
```

COMMAND WINDOW
 Compiling rule SENSOR-INCONSISTENCY-CHECK-SX... =P=P-J=P-J=P-J=P-J=P-J
 =P-J=P-J=P-J=P-J
 Loading DIXIE/art-test/p-summary.art.1 in package ART-USER and base
 10.
 Compiling rule PRINTOUT-ALL-FAULTS... =P-J
 Compiling rule SUMMARIZE-ALL-FAULTS... =P=P-J
 Compiling rule PRINTOUT-REMAINING-FAULTS-FLAG... =P-J
 Compiling rule PRINTOUT-REMAINING-FAULTS... =P=P-J=P-J=P-J
 =P-J=P-J=P-J=P-J=P-J
 Compiling rule SENSOR-INCONSISTENCY-CHECK-SOURCE... =P=P-J=P-J=P-J=P-J=P-J
 =P-J=P-J=P-J=P-J=P-J


ROOT
 clear
 load
 reset
 watch
 run
 stop
 browse
 nlsellencus
 icon editor
 examples

ORIGINAL PAGE IS
 OF POOR QUALITY

SCREEN 2.2.8.2

TUTORIAL

Runtime

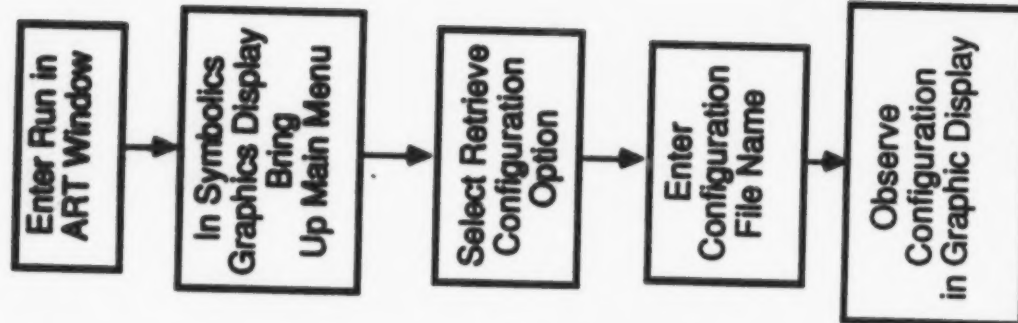

TEXT SCREENS

2.3.1

2.3.1

2.3.2

2.3.2



2.3.3

2.3.3.1, 2.3.3.2

2.3.4

2.3.4

2.3.5

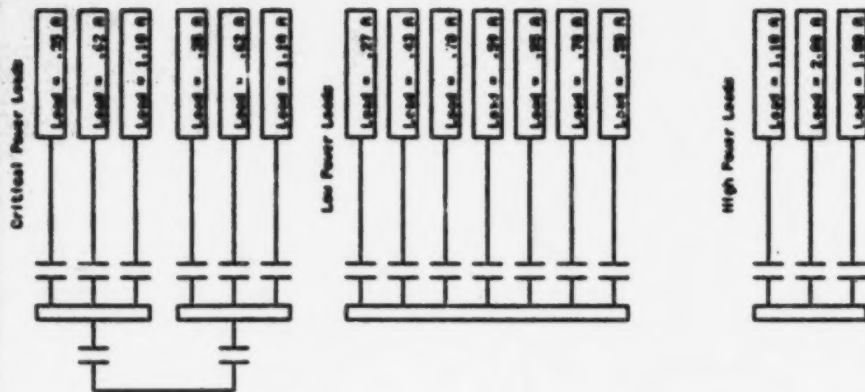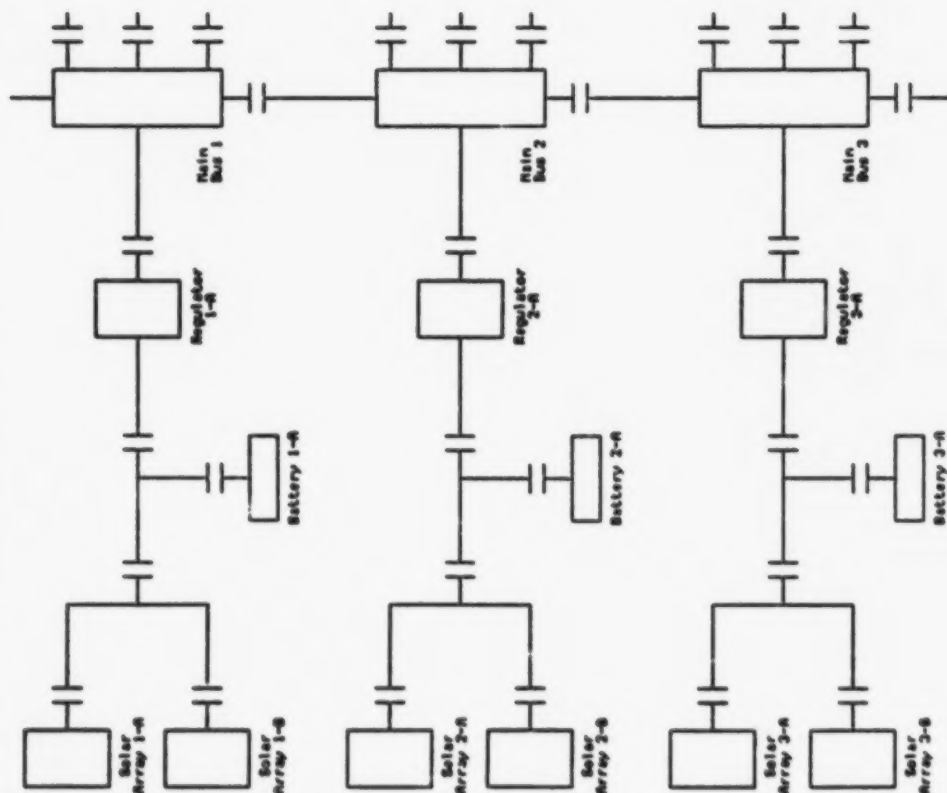


ORIGINAL PAGE IS
OF POOR QUALITY


Waiting on initialization...
see Files Interface Status at

Test Configuration Window 3

SCREEN 2.3.1

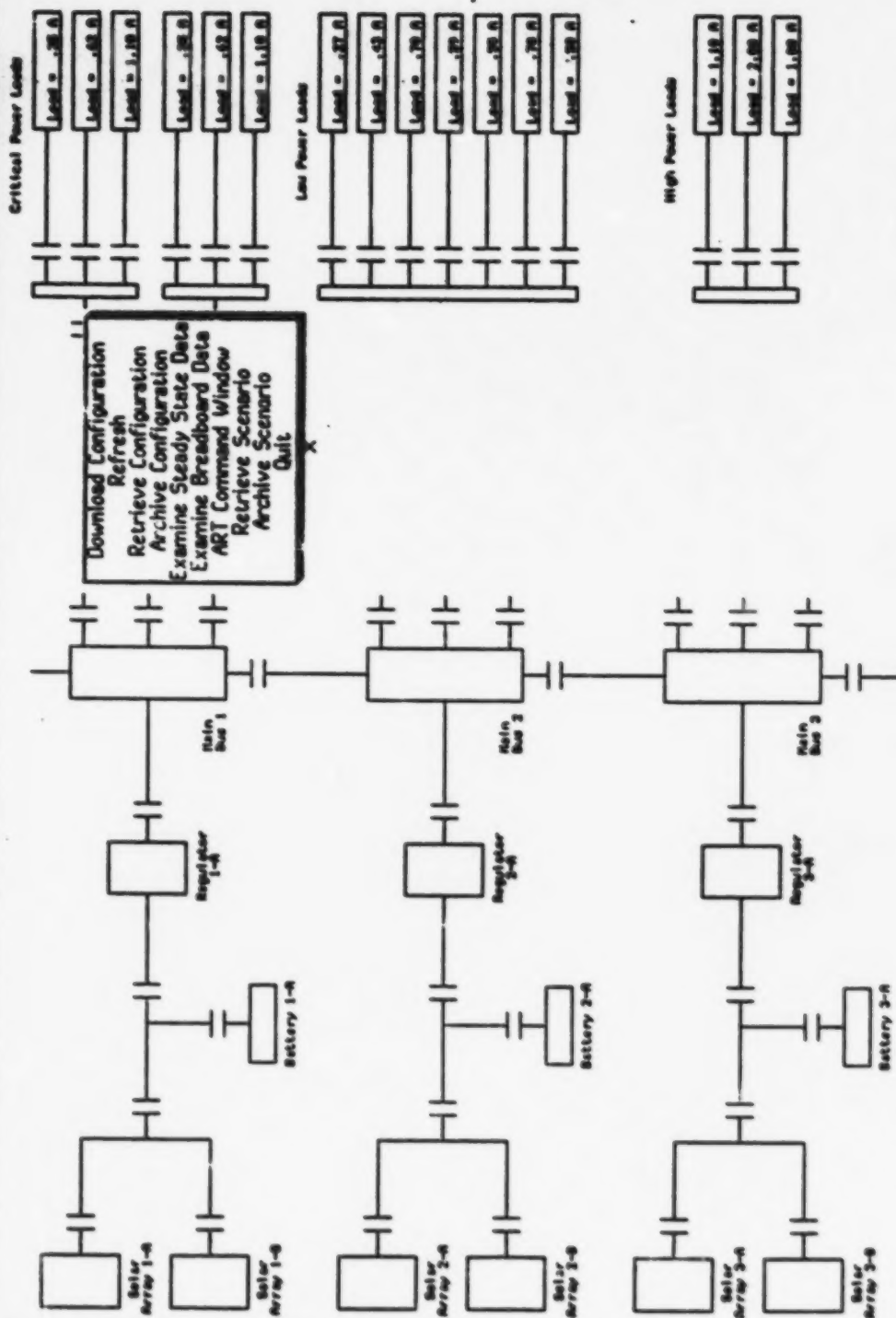


SCREEN 2.3.2

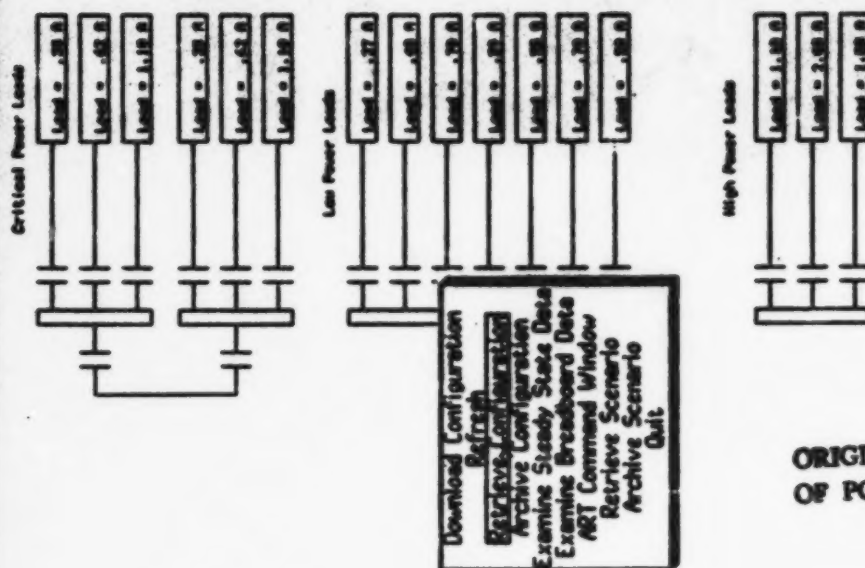

Waiting on initialization...
as File Interface Status is


ORIGINAL PAGE IS
OF POOR QUALITY

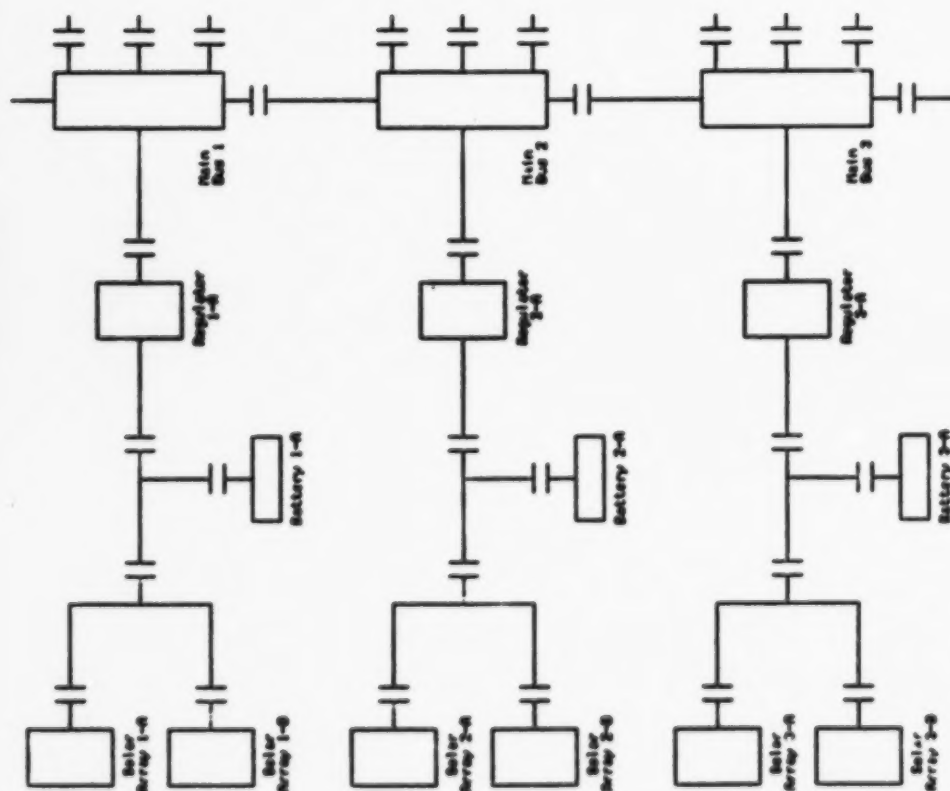

File Configuration Window 1


SCREEN 2.3.3.1

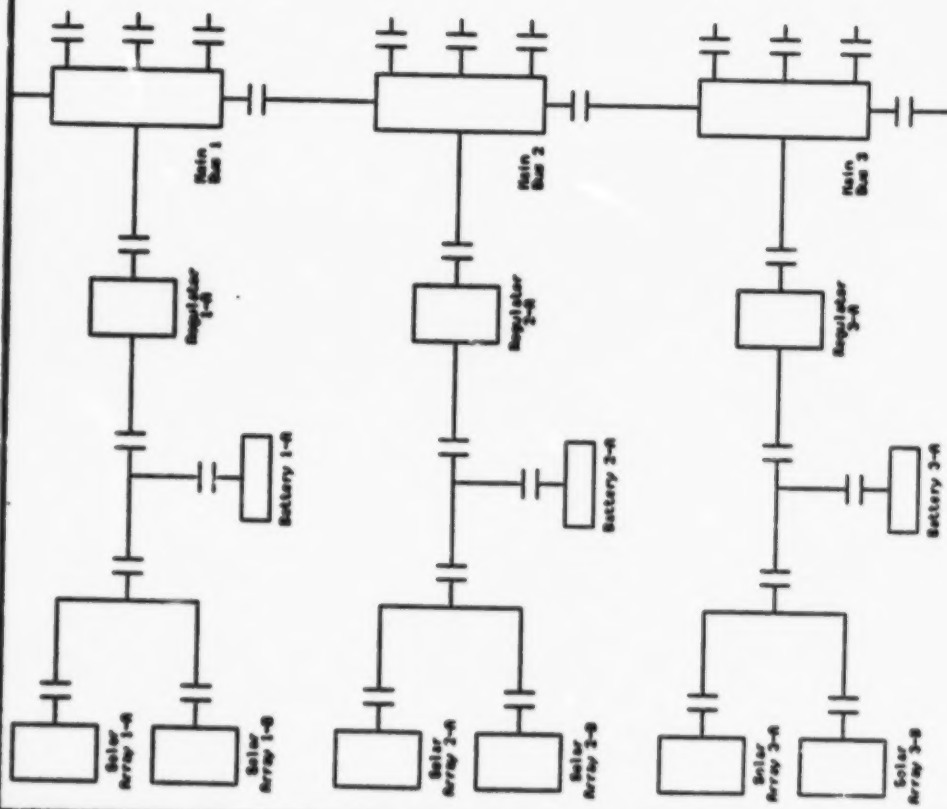Please enter the path and filename. Default is d:\files\lib-library



ORIGINAL PAGE IS
OF POOR QUALITY

Low Power Loads

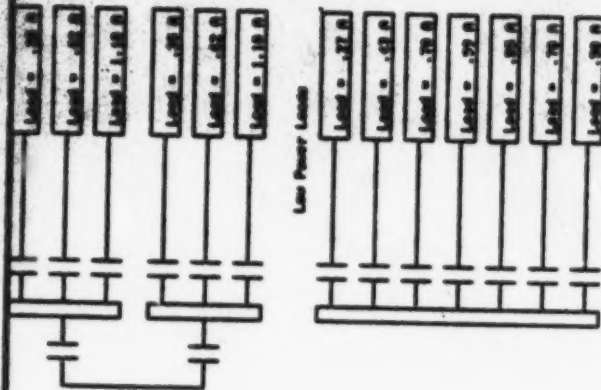


High Power Loads



Library select.....
as File Interface Status is:

Test Configuration Window 3

SCREEN 2.3.3.2

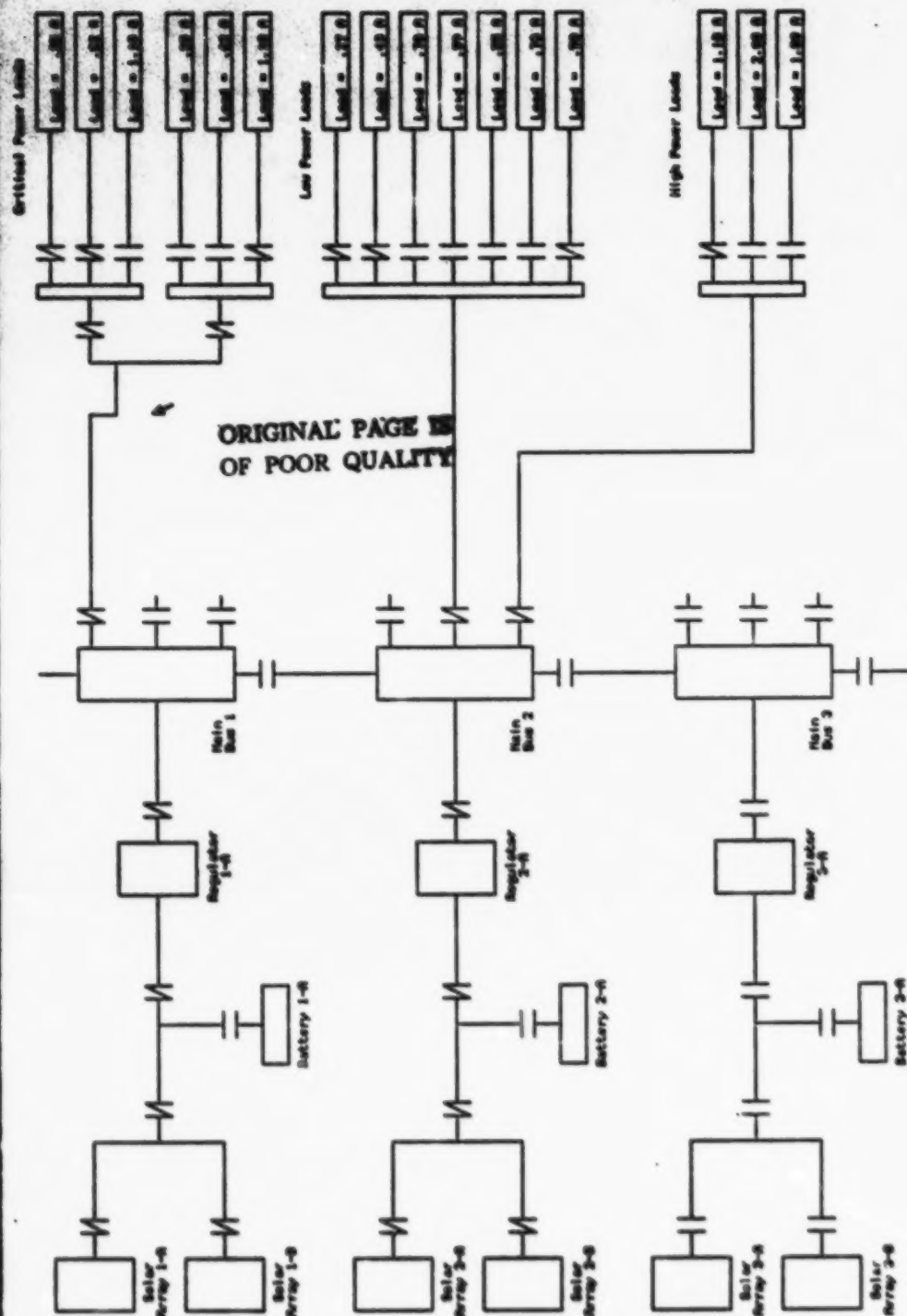


Waiting on initialization...
as File Interface Status is


Test Configuration Window 3

SCREEN 2.3.4

TUTORIAL

TEXT SCREENS

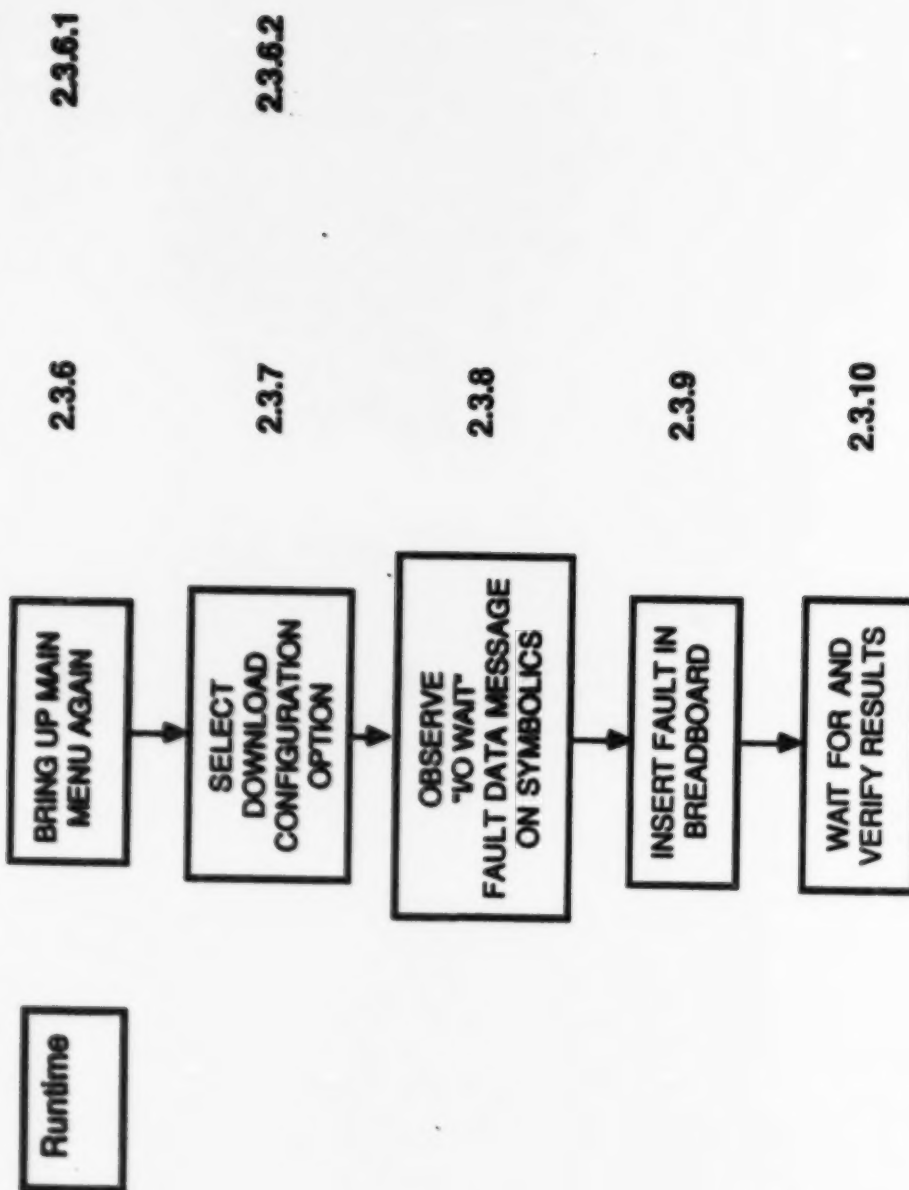

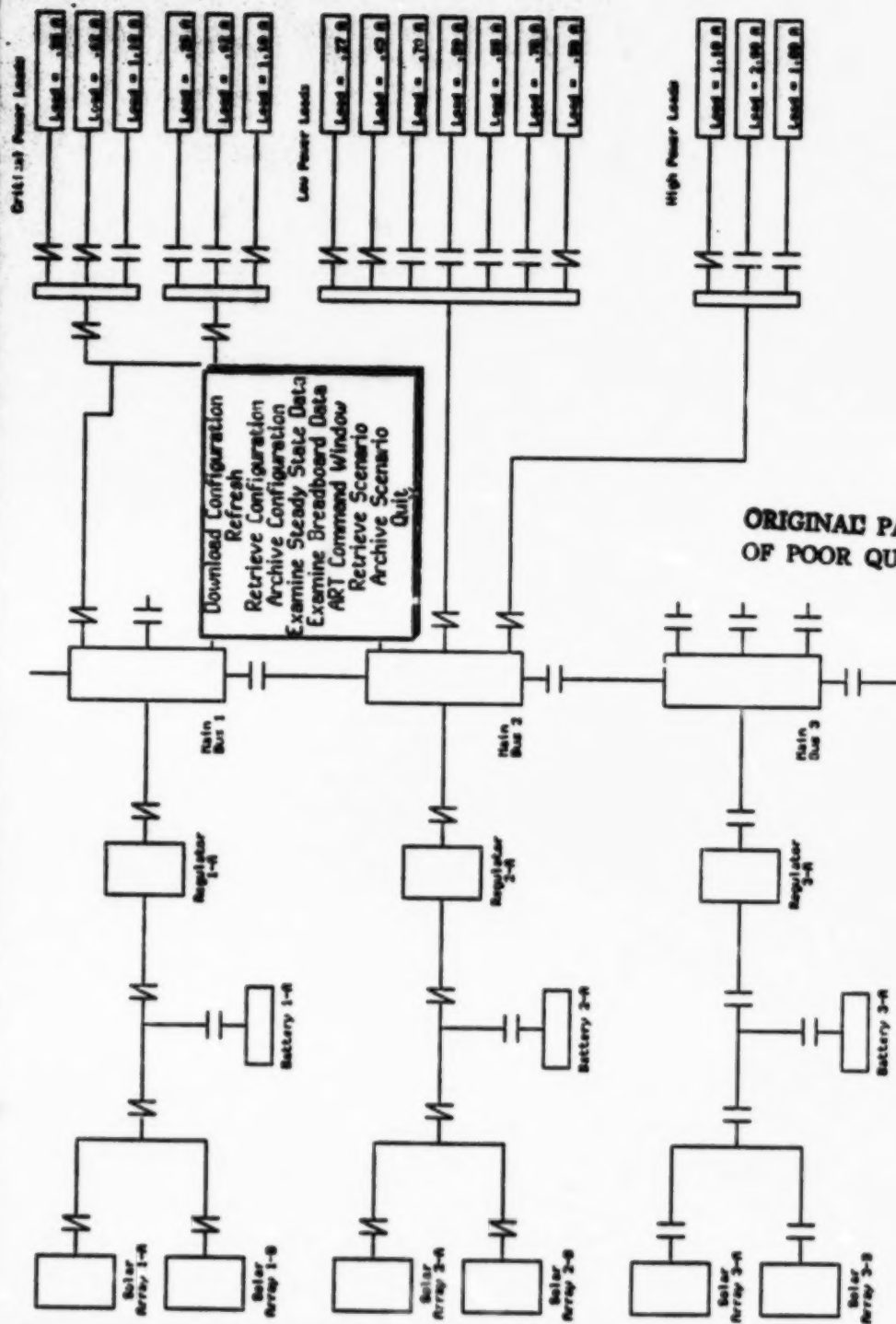


ORIGINAL PAGE IS
OF POOR QUALITY

Waiting on initialization...
to File Interface Status as

Test Configuration Window 3

SCREEN 2.3.6.1

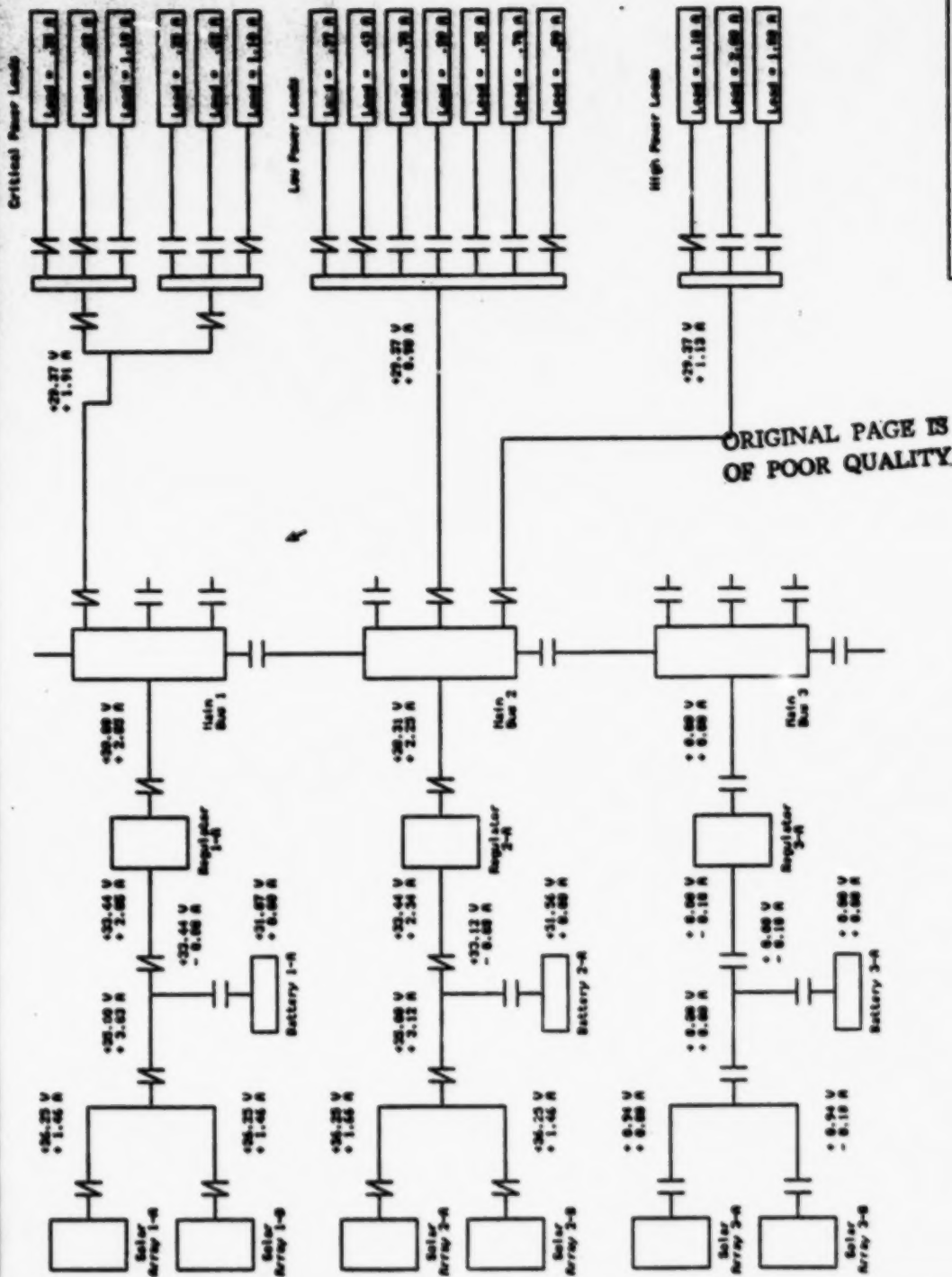


Displaying steady state..
as Figs interface status is

Figs Steady State Data Display Window 1

SCREEN 2.3.6.2

PRODUCTION

TEXT

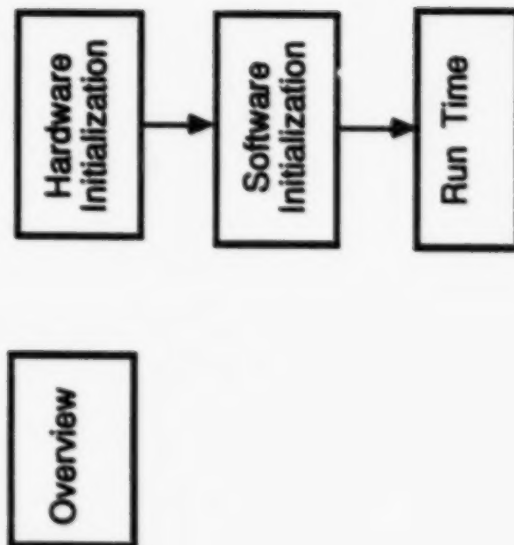

3.1.1


3.1.2

3.1.3

PRODUCTION

TEXT

SCREENS

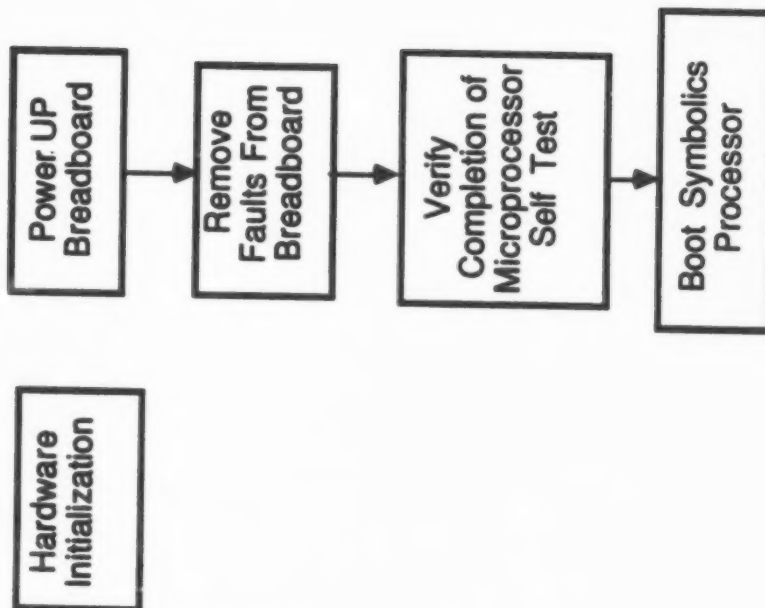

3.1.1.1

3.1.1.2

3.1.1.3

3.1.1.4

3.1.1.4

Symbolics 3870™ System

This machine is Martin Marietta Denver Aerospace - Machine Intelligence Lab Einbecker

Symbolics™ System, Release 6.1
Loaded from FEP0:Mill-r6-1-color.load.1
1538K words Physical memory, 37500K words Swapping space.

Release	6.1
COLOR	135.36
COLOR-8070	66.7
INDEXES	54.21
FEP	127

You are typing to *Lisp Listener 1*. Control characters are interpreted as commands to edit input. Type Control-~~xxx~~ for a list of input editor commands.

Use the "Help" command to display a list of all the Command Processor commands. Type ~~xxxx~~ D to select the Document Examiner to read online documentation. Type ~~xxxx~~ ~~xxxx~~ for a list of programs. Type ~~xxxx~~ ~~xxxx~~ ~~xxxx~~ for a list of asynchronous and window operations. Click the rightmost mouse button to select the System Menu of programs and window operations. Type Symbol-~~xxx~~ for a list of special function keys and special character keys.

Please login.


Lisp Listener 1

(c) Copyright 1985, 1984, 1983, 1982, 1981, 1980, Symbolics, Inc.
All Rights Reserved.
Use the command "Show Legal Notice" to see important legal notices.
Symbolics, Symbolics 3600 and Symbolics 3870 are trademarks of Symbolics, Inc.

SCREEN 3.1.1.4


PRODUCTION

TEXT

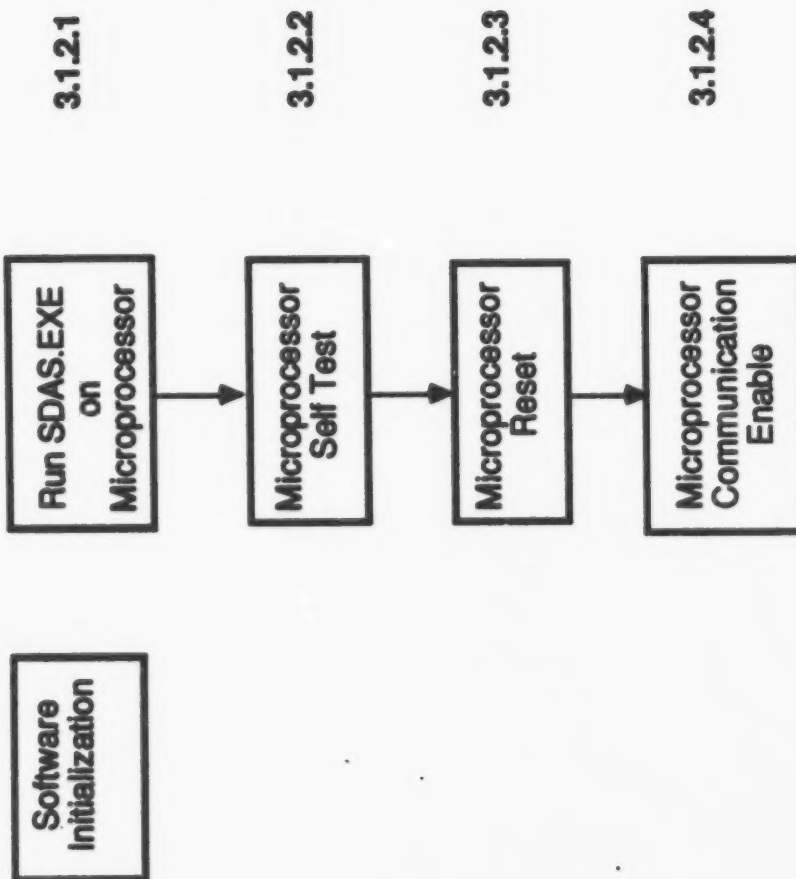

PRODUCTION

TEXT SCREENS

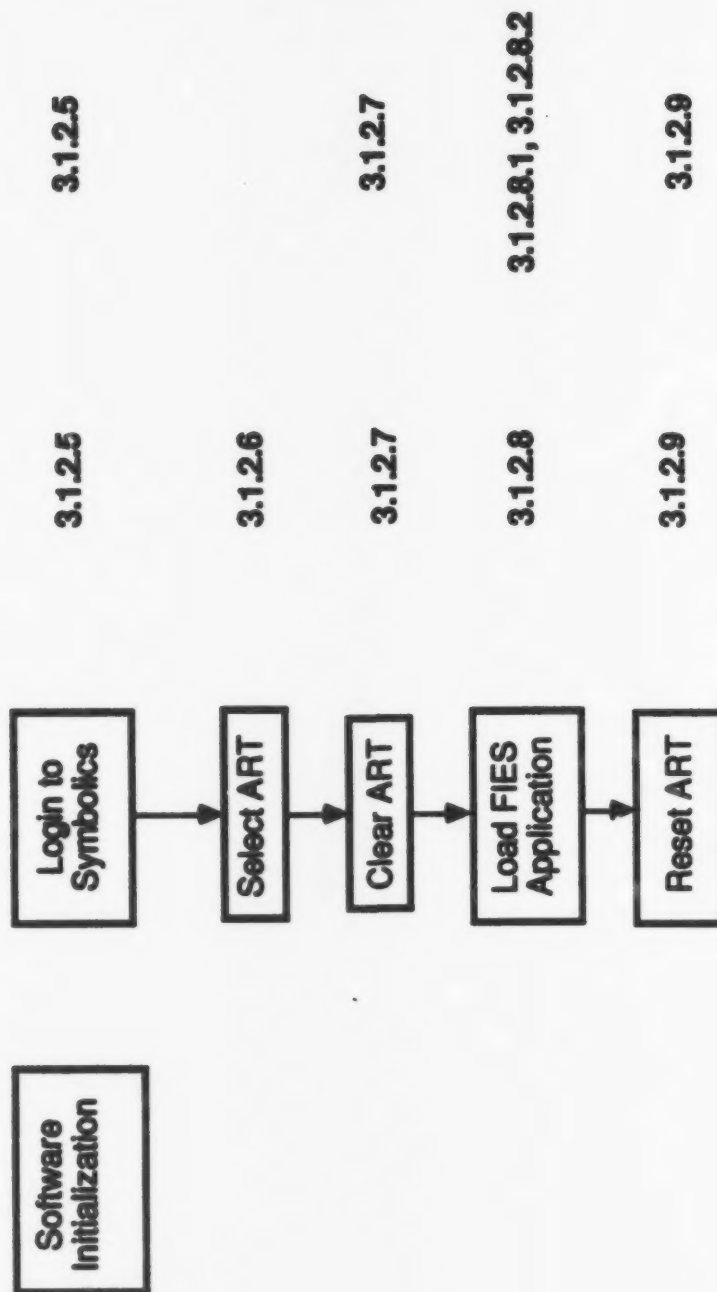

ORIGINAL PAGE IS
OF POOR QUALITY

```

Loading B10XIN: >files-art-production>files-wit-relay-configuration.bin
Loading B10XIN: >files-art-production>files-set-art-sensors.bin
Loading B10XIN: >files-art-production>files-set-art-fault-sensors.bin
Loading B10XIN: >files-art-production>files-pour-distribution-lines-funcs.bin
Loading B10XIN: >files-art-production>files-und-au-pour-distribution-lines.bin
Loading B10XIN: >files-art-production>files-red-au-pour-distribution-lines.bin
Loading B10XIN: >files-art-production>files-reset-pour-distribution-lines.bin
Loading B10XIN: >files-art-production>files-archiver-configuration.bin
Loading B10XIN: >files-art-production>files-retrieve-configuration.bin
Loading B10XIN: >files-art-production>files-archive-scenario.bin
Loading B10XIN: >files-art-production>files-retrieve-scenario.bin
Loading B10XIN: >files-art-production>files-init-request.bin
Loading B10XIN: >files-art-production>files-start-art-scenario.bin
Loading B10XIN: >files-art-production>files-send-lisp.bin
Loading B10XIN: >files-art-production>files-initialize-mouse.bin
Loading B10XIN: >files-art-production>files-initial-configuration.bin
Loading B10XIN: >files-art-production>files-serial-interface.bin
Loading B10XIN: >files-art-production>files-test-configuration.bin
Loading B10XIN: >files-art-production>files-serial-interface-test.bin
Loading B10XIN: >files-art-production>files-refresh-data-display.bin
Loading B10XIN: >files-art-production>files-serial-interface-level-2.bin
Loading B10XIN: >files-art-production>files-fault-data-display.bin
Loading B10XIN: >files-art-production>files-display-faults-from-art.bin

```

You are typing to *Lisp Listener 1*. Control characters are interpreted as commands to edit input. Type Control-**Q** for a list of input editor commands.

Use the "Help" command to display a list of all the Command Processor commands. Type **Q** to select the Document Examiner to read online documentation. Type **Q** for a list of programs. Click the rightmost mouse button to select the System Menu of programs and window operations. Type Symbol-**Q** for a list of special function keys and special character keys.

```

(Login "files-art-production)
Loading B10XIN: >files-art-production>lisp-init.lisp into package USER
Loading B10XIN: >files-art-production>make-files-interface.lisp into package USER
Loading B10XIN: >files-art-production>files-interface-defs.bin
Loading B10XIN: >files-art-production>files-get-edges.bin
Loading B10XIN: >files-art-production>files-clear-status-window-display.bin
Loading B10XIN: >files-art-production>files-display-status-message.bin
Loading B10XIN: >files-art-production>files-get-configuration-file-name.bin
Loading B10XIN: >files-art-production>files-make-configuration-file-name.bin
Loading B10XIN: >files-art-production>files-get-scenario-file-name.bin
Loading B10XIN: >files-art-production>files-make-scenario-file-name.bin
Loading B10XIN: >files-art-production>files-und-au-selected-configuration.bin
Loading B10XIN: >files-art-production>files-set-art-relays.bin

```

Lisp Listener 1

SCREEN 3.1.2.5

ROOT
clear
load
reset
watch
run
step
break
miscellaneous
load editor
examples

ORIGINAL PAGE IS
OF POOR QUALITY

COMMAND WINDOW

>> clear
Clearing MT...
>>
>> ■

SCREEN 3.1.2.7

COMMAND WINDOW

```
>> clear
Clearing ANT...
>>
>> load
File names: 2
```

ROOT

```
clear
load
reset
watch
run
stop
browse
miscellaneous
icon editor
examples
```

SCREEN 3.1.2.8.1

COMMAND WINDOW
 Compiling rule SENSOR-INCONSISTENCY-CHECK-SK... =P=P=J=P=J=P=J=P=J
 =P=J=P=J=P=J=P=J
 Loading BIGNIN:art-test:p-summary.art.1 in package ART-USER and base
 18.
 Compiling rule PRINTOUT-ALL-FAULTS... =P=J
 Compiling rule SUMMARIZE-ALL-FAULTS... =P=P=J
 Compiling rule PRINTOUT-REMAINING-FAULTS-FLAG... =P=J
 Compiling rule PRINTOUT-REMAINING-FAULTS... =P=P=J=P=J=P=J
 ==
 =P=J=P=J=P=J=P=J
 Compiling rule SENSOR-INCONSISTENCY-CHECK-SOURCE... =P=P=J=P=J=P=J=P=J
 =P=J=P=J=P=J=P=J

ROOT
 clear
 load
 reset
 watch
 run
 stop
 browse
 miscellaneous
 icon editor
 examples

ORIGINAL PAGE IS
 OF POOR QUALITY

SCREEN 3.1.2.8.2

COMMAND WINDOW
 Compiling rule SENSOR-INCONSISTENCY-CHECK-6K... #P#J#P#J#P#J#P#J#P#J
 #J#P#J#P#J#P#J
 Loading DIXON:bert-testp-summary.art.1 in package ART-USER and base
 18.
 Compiling rule PRINTOUT-ALL-FAULTS... #P#J
 Compiling rule SUMMARIZE-ALL-FAULTS... #P#J
 Compiling rule PRINTOUT-REMAINING-FAULTS-FLAG... #P#J
 Compiling rule PRINTOUT-REMAINING-FAULTS... #P#J#P#J#P#J
 #J reset
 Resetting ART...
 #P#J#P#J#P#J#P#J#P#J

ROOT
 clear
 load
 reset
 watch
 run
 step
 browse
 miscellaneous
 icon editor
 examples


ORIGINAL PAGE IS
 OF POOR QUALITY



SCREEN 3.1.2.9

PRODUCTION

TEXT

SCREENS

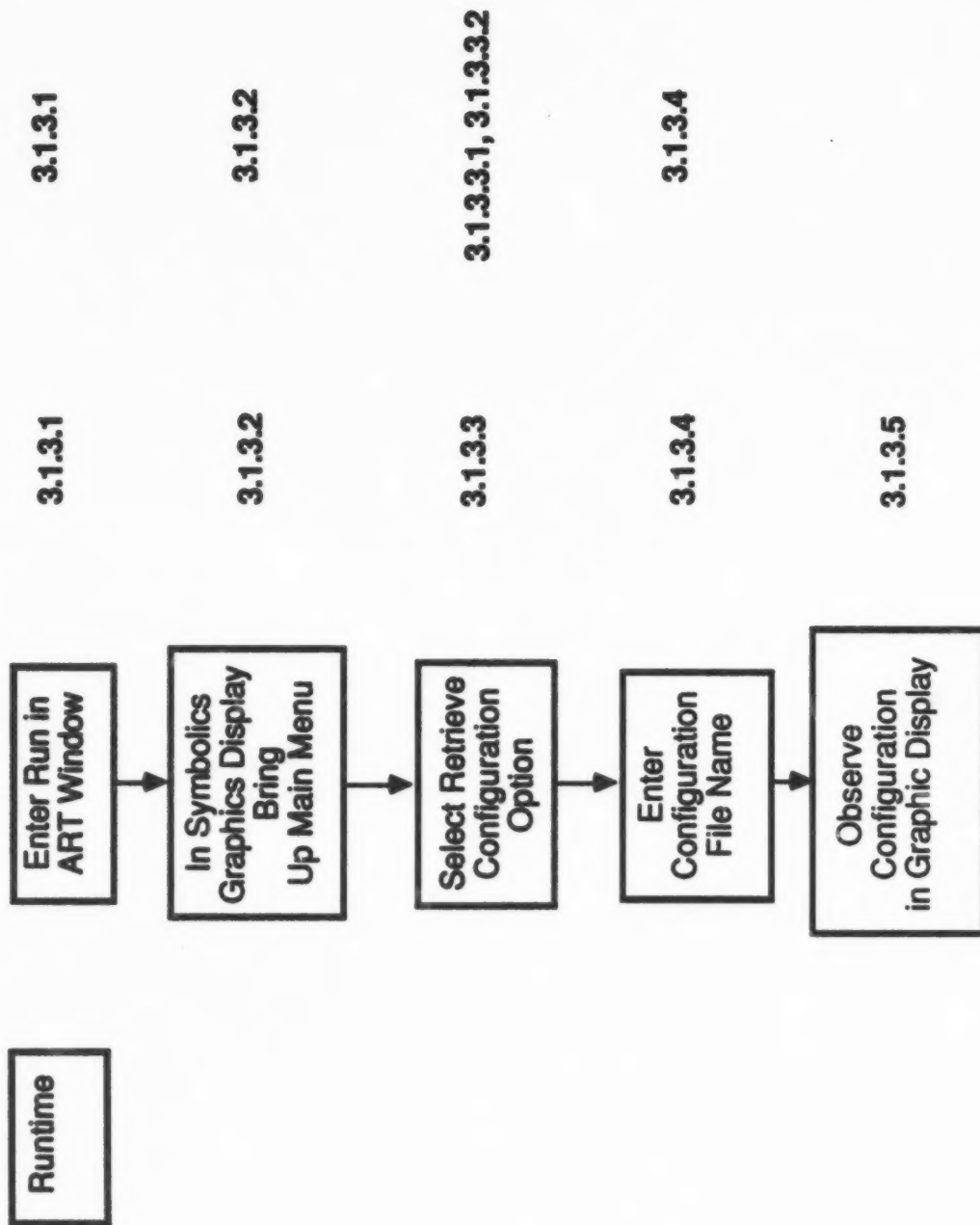

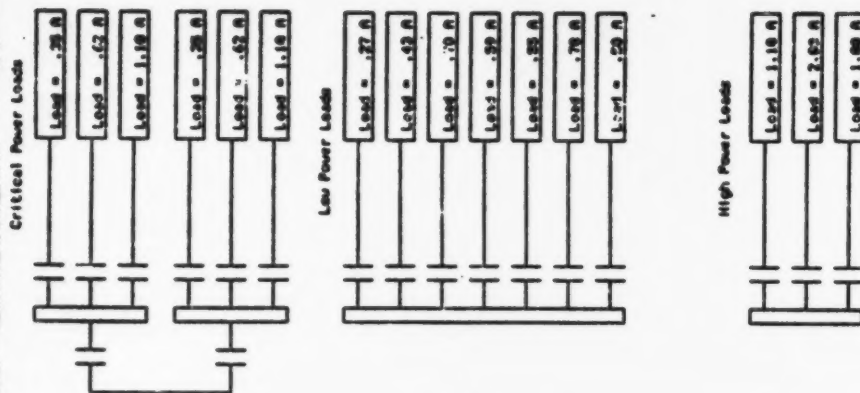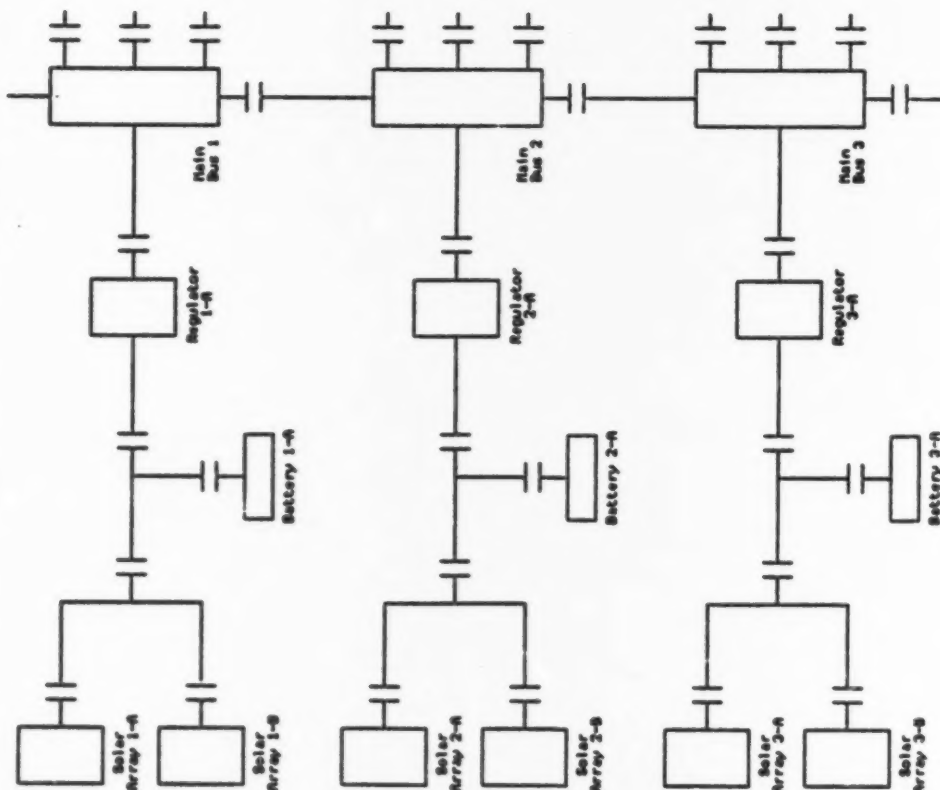


ORIGINAL PAGE IS
OF POOR QUALITY

Waiting on initialization..
as File Interface Status as

Test Configuration Window 3

SCREEN 3.1.3.1

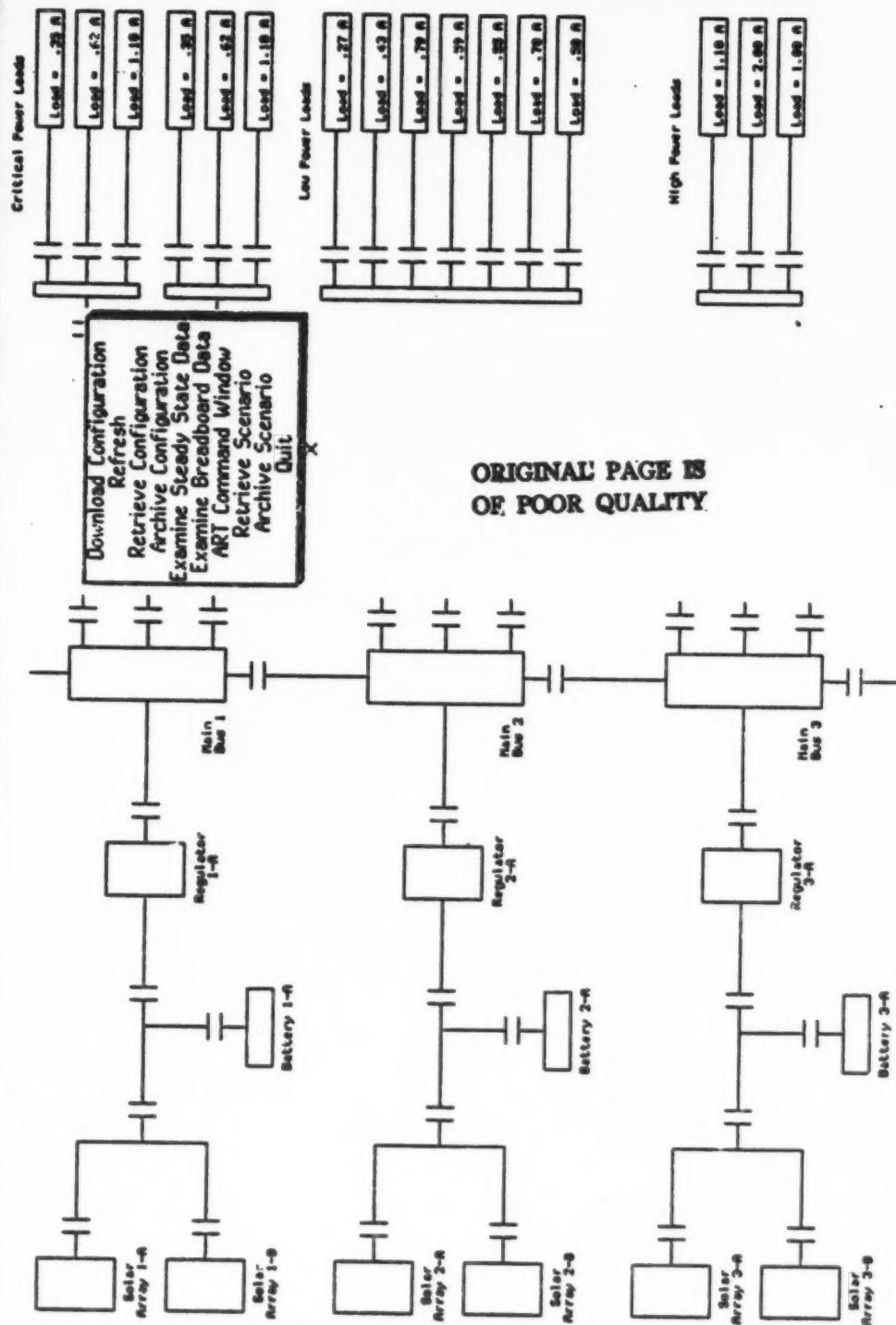


ORIGINAL PAGE IS
OF POOR QUALITY

Test Configuration Window 3


Waiting on initialization..
see Files Interface Status as

SCREEN 3.1.3.2

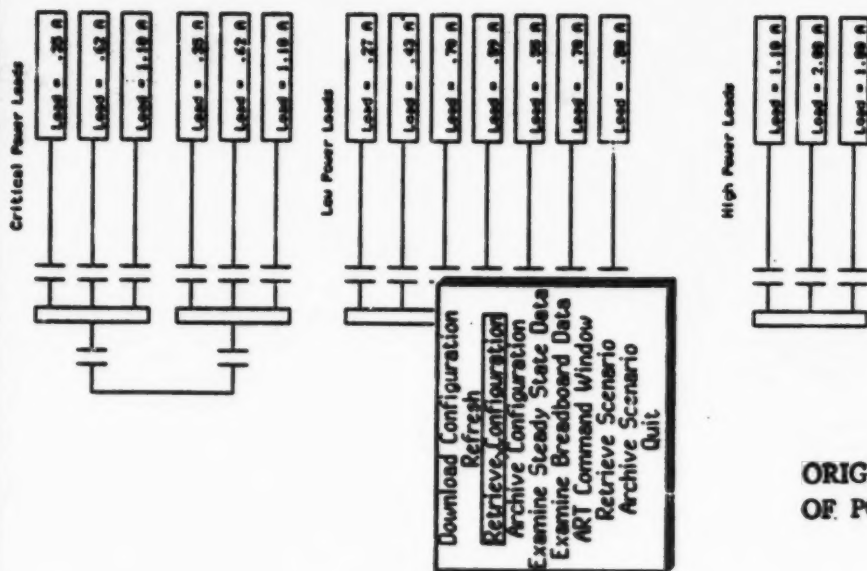

Waiting on initialization..
 as Fies Interface Status ..


ORIGINAL PAGE IS
 OF POOR QUALITY

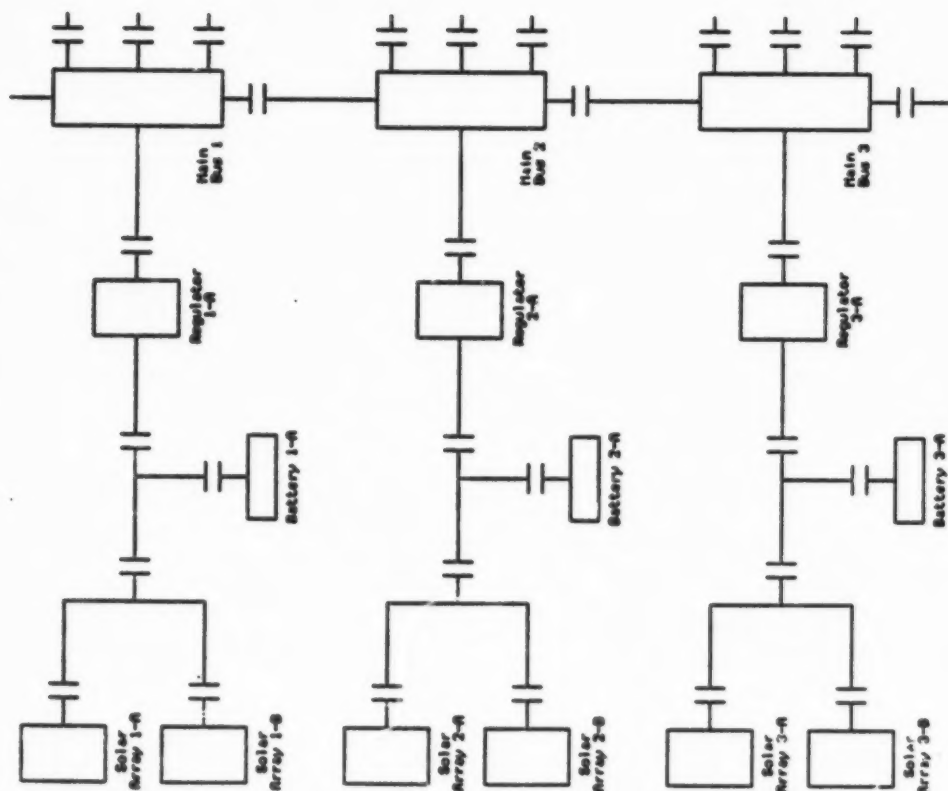

Test Configuration Window 1

SCREEN 3.1.3.3.1

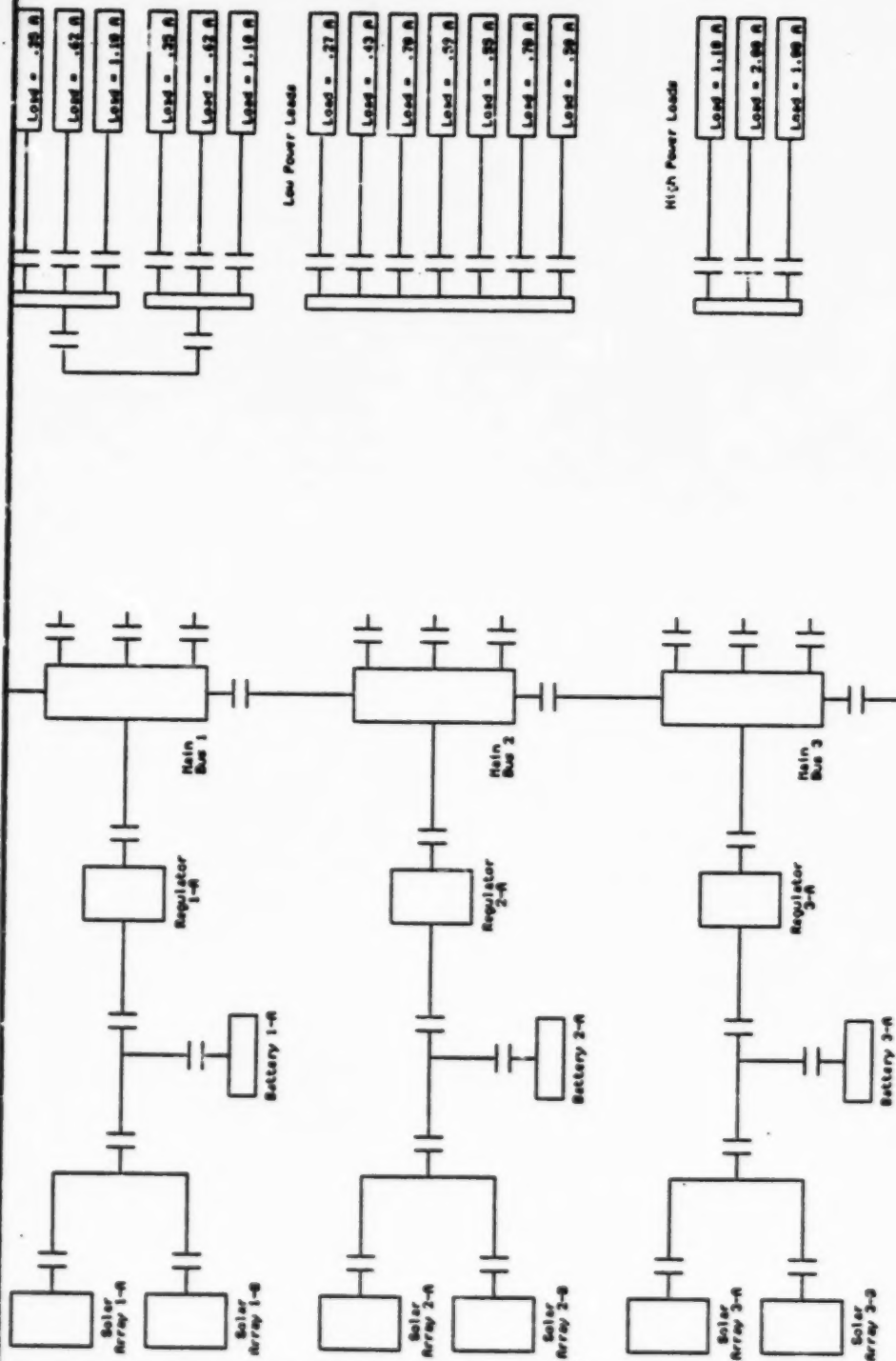
Please enter the path and filename. Default is d:\files\files-library



Library select....
 ** Files Interface Status **

Test Configuration Window 3

SCREEN 3.1.3.3.2

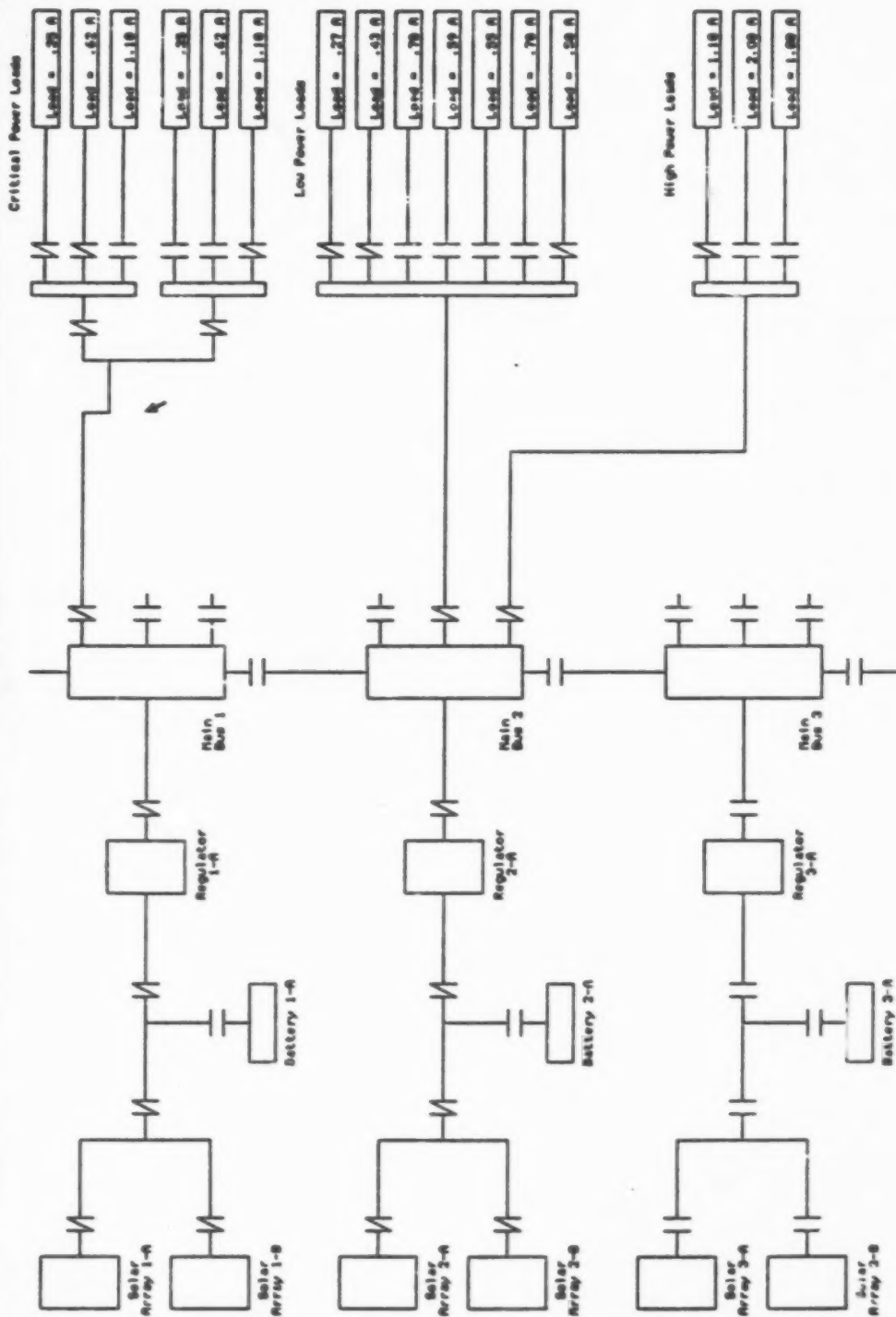

Waiting on initialization...
as File Interface Status as


Test Configuration Window 3


SCREEN 3.1.3.4

PRODUCTION

TEXT

SCREENS

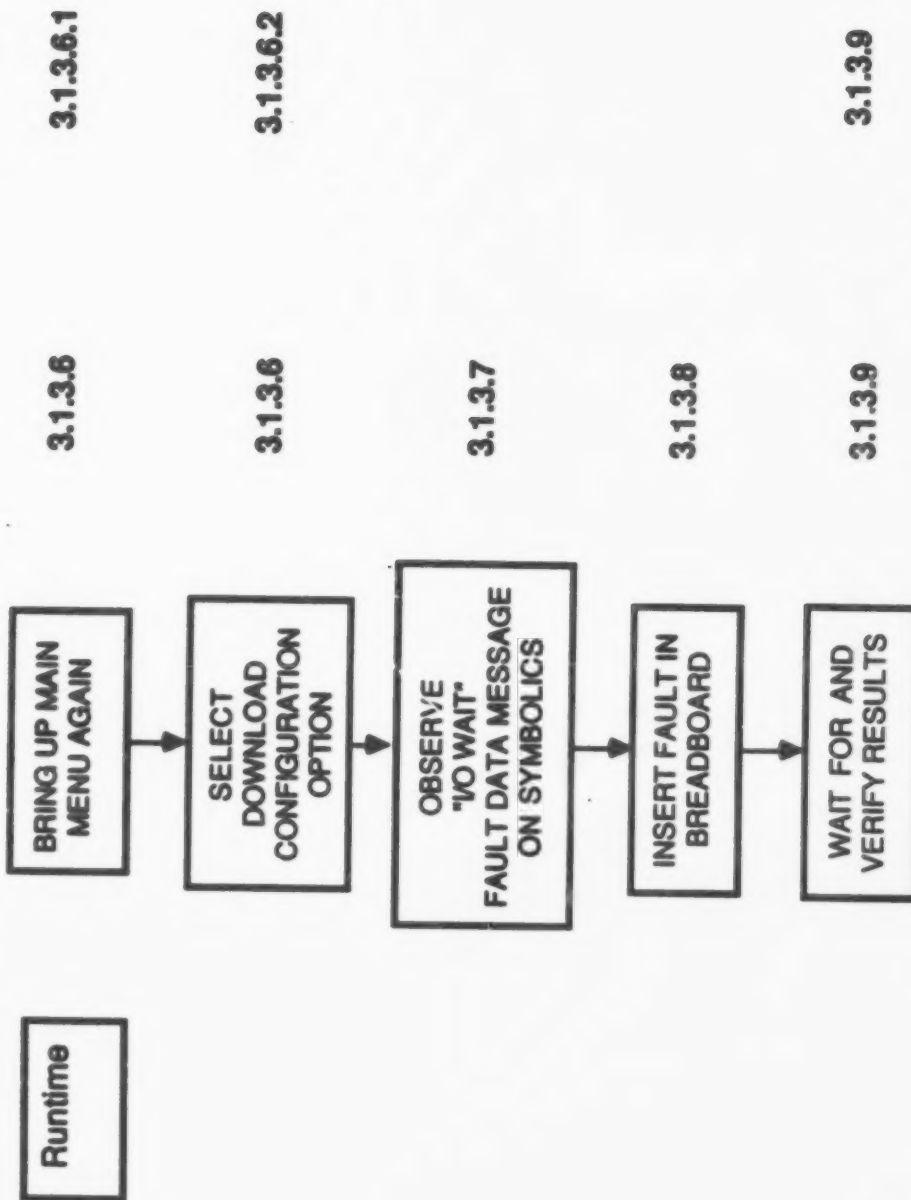


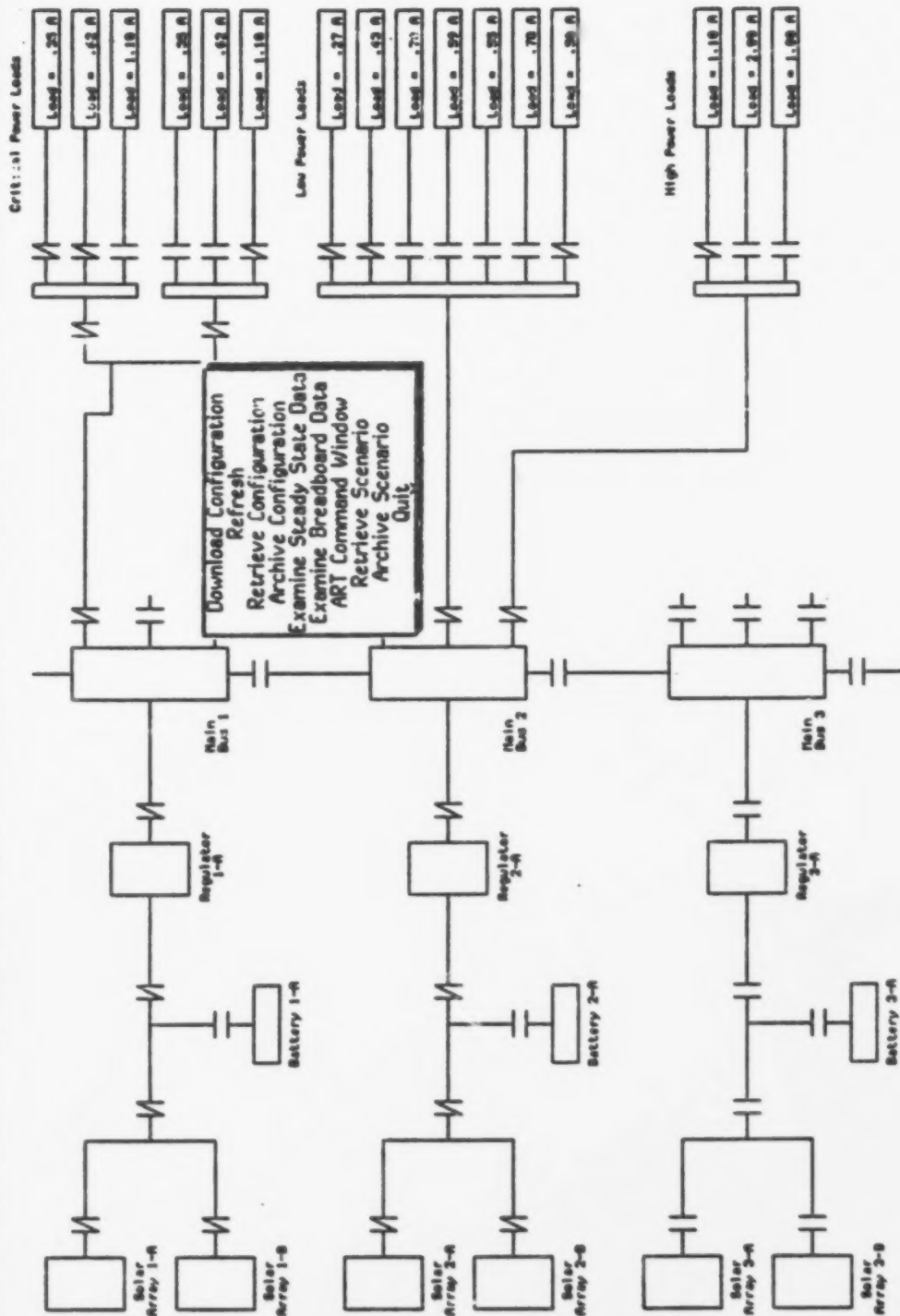

Waiting on initialization...
see File Interface Status

Test Configuration Window 3

SCREEN 3.1.3.6.1

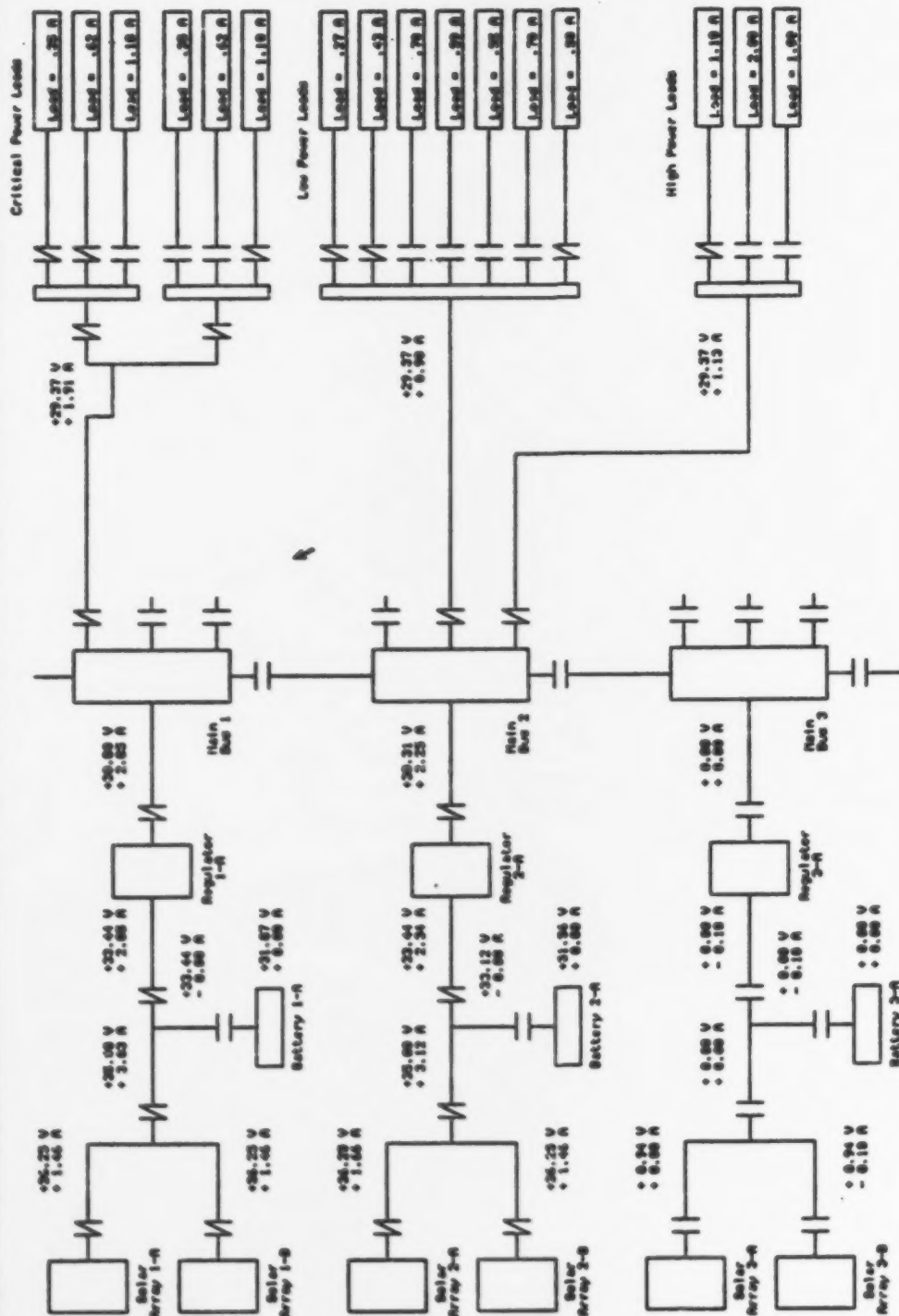

Displaying steady state.
as File Interface Status is

File Steady State Data Display Window 1

SCREEN 3.1.3.6.2

COMMAND WINDOW

FIRE 418 PRINTOUT-REMAINING-FAULTS r-3188 in (STATE-2)
 (= Activation PRINTOUT-REMAINING-FAULTS r-3188 in (STATE-2)
 OPEN-CIRCUIT BUS-2A

FIRE 419 MULT-FIES-END in (STATE-1)
 (= Activation MULT-FIES-END in (STATE-1)
 Program halted.
 =)

OPEN-CIRCUIT RELAY-2C.

ROOT


clear
 load
 reset
 watch
 stop
 browse
 miscellaneous
 icon editor
 examples

ORIGINAL PAGE 1
 OF POOR QUALITY

SCREEN 3.1.3.9

INTERACTIVE

Overview

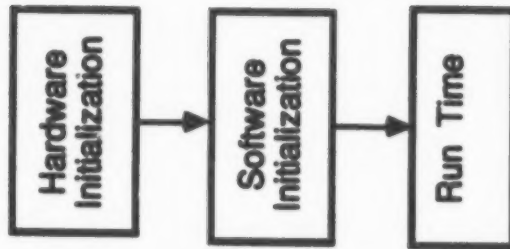

TEXT

3.2.1


3.2.2

3.2.3

INTERACTIVE

TEXT

SCREENS

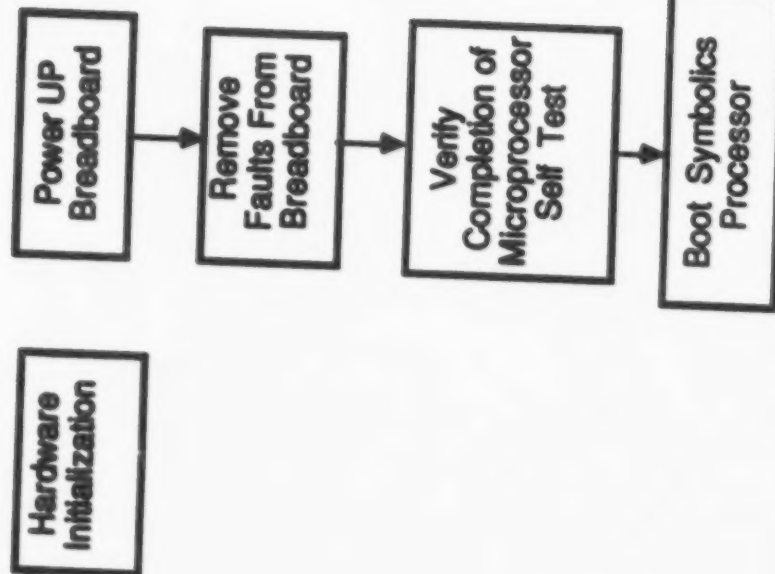

3.2.1.1

3.2.1.2

3.2.1.3

3.2.1.4

3.2.1.4

Symbolics 3670[®] System

This machine is Martin Marietta Denver Aerospace - Machine Intelligence Lab Einbecker

Symbolics[™] System, Release 6.1
Loaded from FEP0:mli-r6-1-color.load.1
1536K words Physical memory, 37500K words Swapping space.

Release	6.1
COLOR	156,88
COLOR-8880	64.7
171028	84.21
FEP	127

You are typing to *Lisp Listener 1*. Control characters are interpreted as commands to edit input. Type Control-~~ESC~~ for a list of input editor commands.

Use the "help" command to display a list of all the Command Processor commands.

Type ~~ESC~~ D to select the Document Examiner to read online documentation.

Type ~~ESC~~ ~~ESC~~ ~~ESC~~ for a list of programs.

Type ~~ESC~~ ~~ESC~~ ~~ESC~~ for a list of asynchronous and window operations.

Click the rightmost mouse button to select the System Menu of programs and window operations.

Type Symbol-~~ESC~~ for a list of special function keys and special character keys.

Please login.

Lisp Listener 1

(c) Copyright 1985, 1984, 1983, 1982, 1981, 1980, Symbolics, Inc.
All Rights Reserved.


Use the command "Show Legal Notice" to see important legal notices.

Symbolics, Symbolics 3600 and Symbolics 3670 are trademarks of Symbolics, Inc.

SCREEN 3.2.1.4


INTERACTIVE

TEXT

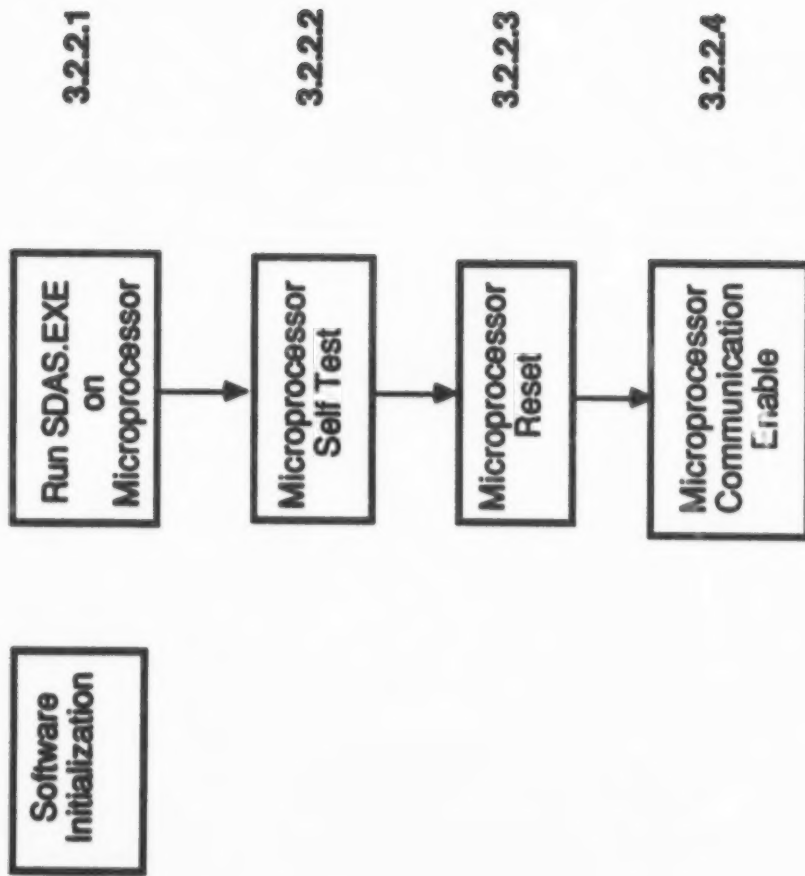

INTERACTIVE

TEXT SCREENS

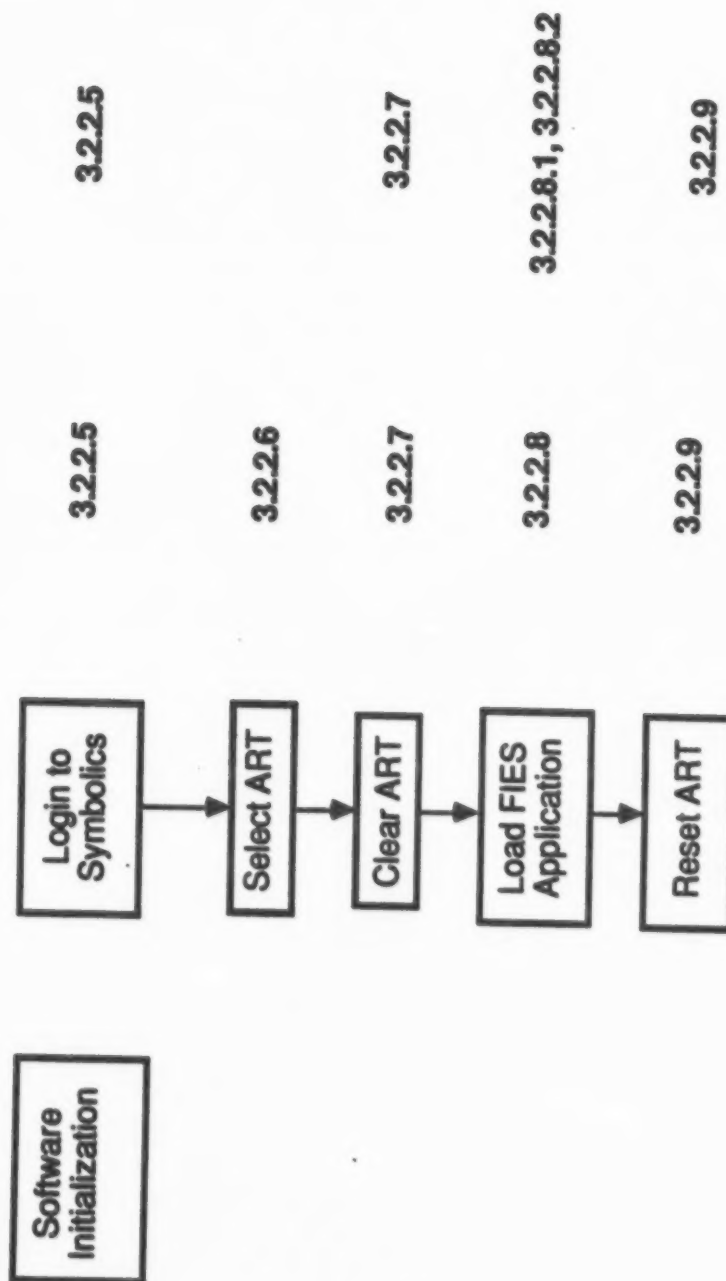

ORIGINAL PAGE IS
POOR QUALITY

```
(log in fies-art-interactive) lisp-init.lisp into package ART-USER
Loading BIXMIN: >FIES-ART-INTERACTIVE> lisp-init.lisp into package ART-USER
Loading BIXMIN: >FIES-ART-INTERACTIVE> make-fies-interface-defs.bin
Loading BIXMIN: >FIES-ART-INTERACTIVE> fies-clear-status-window-display.bin
Loading BIXMIN: >FIES-ART-INTERACTIVE> fies-clear-status-message.bin
Loading BIXMIN: >FIES-ART-INTERACTIVE> fies-get-configuration-file-name.bin
Loading BIXMIN: >FIES-ART-INTERACTIVE> fies-make-configuration-file-name.bin
Loading BIXMIN: >FIES-ART-INTERACTIVE> fies-get-scenario-file-name.bin
Loading BIXMIN: >FIES-ART-INTERACTIVE> fies-make-scenario-file-name.bin
Loading BIXMIN: >FIES-ART-INTERACTIVE> fies-under-a-selected-configuration.bin
Loading BIXMIN: >FIES-ART-INTERACTIVE> fies-draw-selected-configuration.bin
Loading BIXMIN: >FIES-ART-INTERACTIVE> fies-set-art-relays.bin
Loading BIXMIN: >FIES-ART-INTERACTIVE> fies-kill-relay-configuration.bin
Loading BIXMIN: >FIES-ART-INTERACTIVE> fies-set-art-sensors.bin
Loading BIXMIN: >FIES-ART-INTERACTIVE> fies-act-art-fault-distribution-lines-funcs.bin
Loading BIXMIN: >FIES-ART-INTERACTIVE> fies-power-distribution-lines.bin
Loading BIXMIN: >FIES-ART-INTERACTIVE> fies-under-a-power-distribution-lines.bin
Loading BIXMIN: >FIES-ART-INTERACTIVE> fies-redraw-power-distribution-lines.bin
Loading BIXMIN: >FIES-ART-INTERACTIVE> fies-reset-power-distribution-lines.bin
Loading BIXMIN: >FIES-ART-INTERACTIVE> fies-archive-configuration.bin
Loading BIXMIN: >FIES-ART-INTERACTIVE> fies-retrieve-scenario.bin
Loading BIXMIN: >FIES-ART-INTERACTIVE> fies-retrieve-scenario.bin
Loading BIXMIN: >FIES-ART-INTERACTIVE> fies-kill-request.bin
Loading BIXMIN: >FIES-ART-INTERACTIVE> fies-perseus-data-for-scenario.bin
Loading BIXMIN: >FIES-ART-INTERACTIVE> fies-start-art-scenario.bin
Loading BIXMIN: >FIES-ART-INTERACTIVE> fies-send-lisp.bin
Loading BIXMIN: >FIES-ART-INTERACTIVE> fies-initialize-nouse.bin
Loading BIXMIN: >FIES-ART-INTERACTIVE> fies-initialize-configuration.bin
Loading BIXMIN: >FIES-ART-INTERACTIVE> fies-serial-interface.bin
Loading BIXMIN: >FIES-ART-INTERACTIVE> fies-test-configuration-test.bin
Loading BIXMIN: >FIES-ART-INTERACTIVE> fies-serial-interface-test.bin
Loading BIXMIN: >FIES-ART-INTERACTIVE> fies-refresh-data-display-2.bin
Loading BIXMIN: >FIES-ART-INTERACTIVE> fies-serial-interface-level-2.bin
Loading BIXMIN: >FIES-ART-INTERACTIVE> fies-steady-state-data-display.bin
Loading BIXMIN: >FIES-ART-INTERACTIVE> fies-fault-data-display.bin
Loading BIXMIN: >FIES-ART-INTERACTIVE> fies-display-faults-from-art.bin
Loading BIXMIN: >FIES-ART-INTERACTIVE>
```

Lisp Listener 1

SCREEN 3.2.2.5

ROOT
clear
load
reast
watch
run
step
break
miscellaneous
icon editor
examples

ORIGINAL PAGE IS
OF POOR QUALITY

COMMAND WINDOW

=> clear
Clearing ARI...
=>
=>

SCREEN 3.2.2.7

COMMAND WINDOW

>> clear
Clearing ART...
>>
>> load
File name:

ROOT

clear
load
reset
watch
run
step
browse
miscellaneous
icon editor
examples

SCREEN 3.2.2.8.1

ROOT

clear
load
reset
watch
run
step
browse
miscellaneous
icon editor
examples

COMMAND WINDOW

Compiling rule SENSOR-INCONSISTENCY-CHECK-SK... =P=P=J=P=J=P=J=P=J=P=J
=P=J=P=J=P=J=P=J
Loading DIONIS:art-testp-summary.art.1 in package ART-USER and base
Loading DIONIS:art-testp-summary.art.1 in package ART-USER and base
18. Compiling rule PRINTOUT-ALL-FAULTS... =P=P=J
Compiling rule MINIMIZE-ALL-FRAG-FAULTS... =P=P=J
Compiling rule PRINTOUT-REMAINING-FAULTS... =P=P=J=P=J=P=J
Compiling rule PRINTOUT-REMAINING-FAULTS... =P=P=J=P=J=P=J
Compiling rule PRINTOUT-REMAINING-FAULTS... =P=P=J=P=J=P=J
=> [P=P=J=P=J=P=J=P=J
Compiling rule SENSOR-INCONSISTENCY-CHECK-SOURCE... =P=P=J=P=J=P=J=P=J
=P=J=P=J=P=J=P=J


COMMAND WINDOW
 Compiling rule SENSOR-INCONSISTENCY-CHECK-SE... #P#J#P#J#P#J#P#J
 Loading D:\XIN\bert-test\p-summary-art.1 in package ART-USER and base
 18.
 Compiling rule PRINTOUT-ALL-FAULTS... #P#J
 Compiling rule SUMMARIZE-ALL-FAULTS... #P#J
 Compiling rule PRINTOUT-REMAINING-FAULTS-FLD... #P#J
 Compiling rule PRINTOUT-REMAINING-FAULTS... #P#J#P#J#P#J
 #J print
 Rescanning ART...
 #P#J#P#J#P#J#P#J

ROOT
 clear
 load
 reset
 watch
 run
 stop
 browse
 miscellaneous
 icon editor
 examples

SCREEN 3.2.2.9

INTERACTIVE

TEXT SCREENS

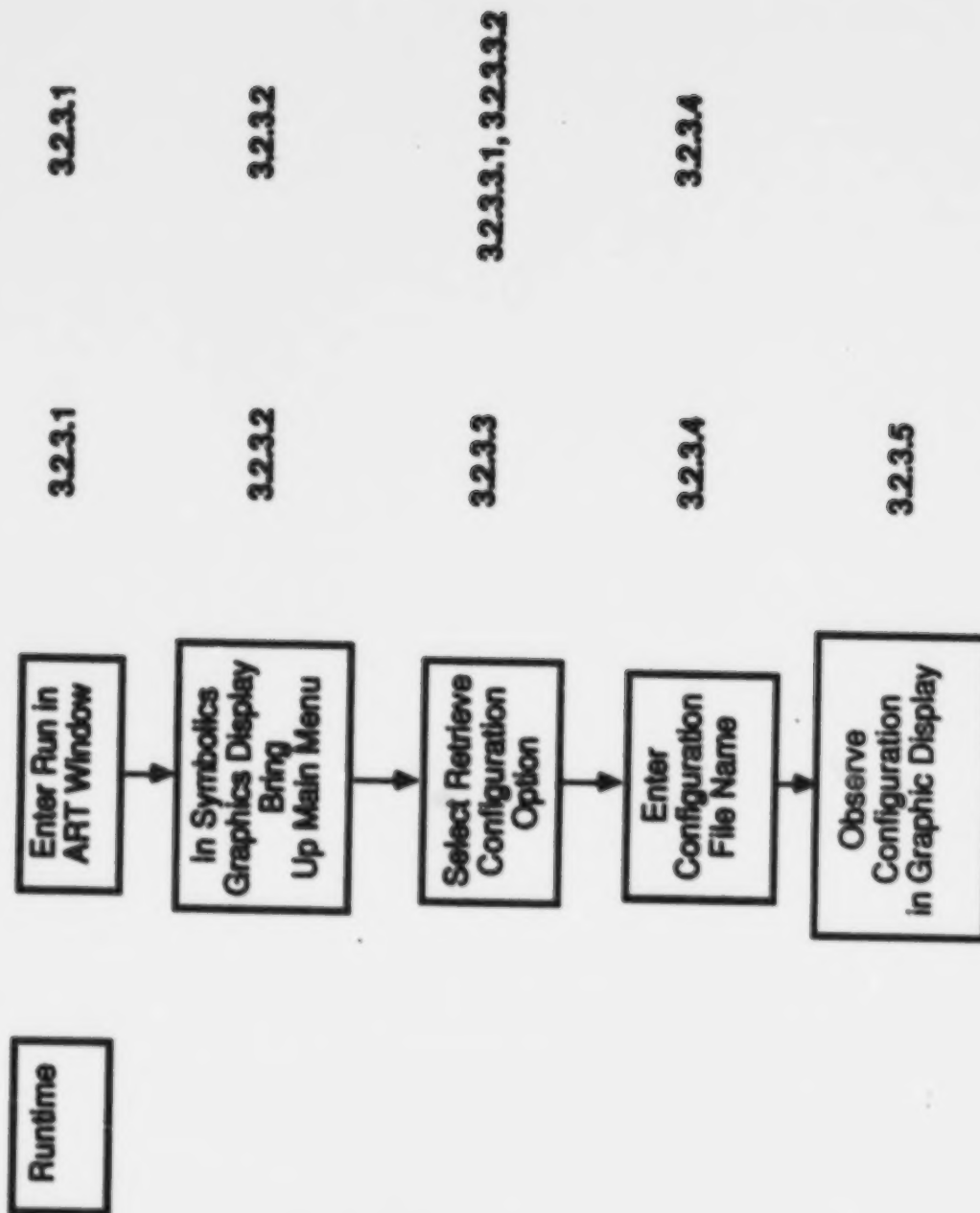

3.2.3.1

3.2.3.1

3.2.3.2

3.2.3.2

3.2.3.3.1, 3.2.3.3.2


3.2.3.3

3.2.3.4


3.2.3.4

3.2.3.5

Critical Power Loads

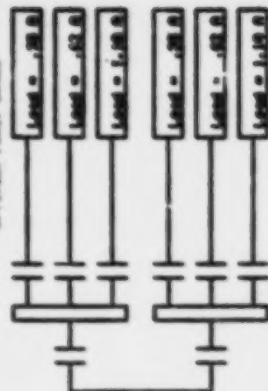

Low Power Loads

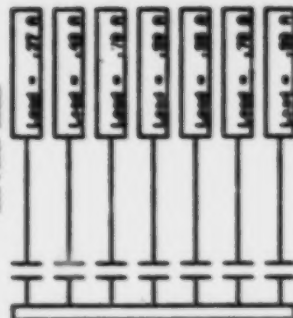


High Power Loads




Waiting on initialization...
as File Interface Status is

ORIGINAL PAGE IS
OF POOR QUALITY

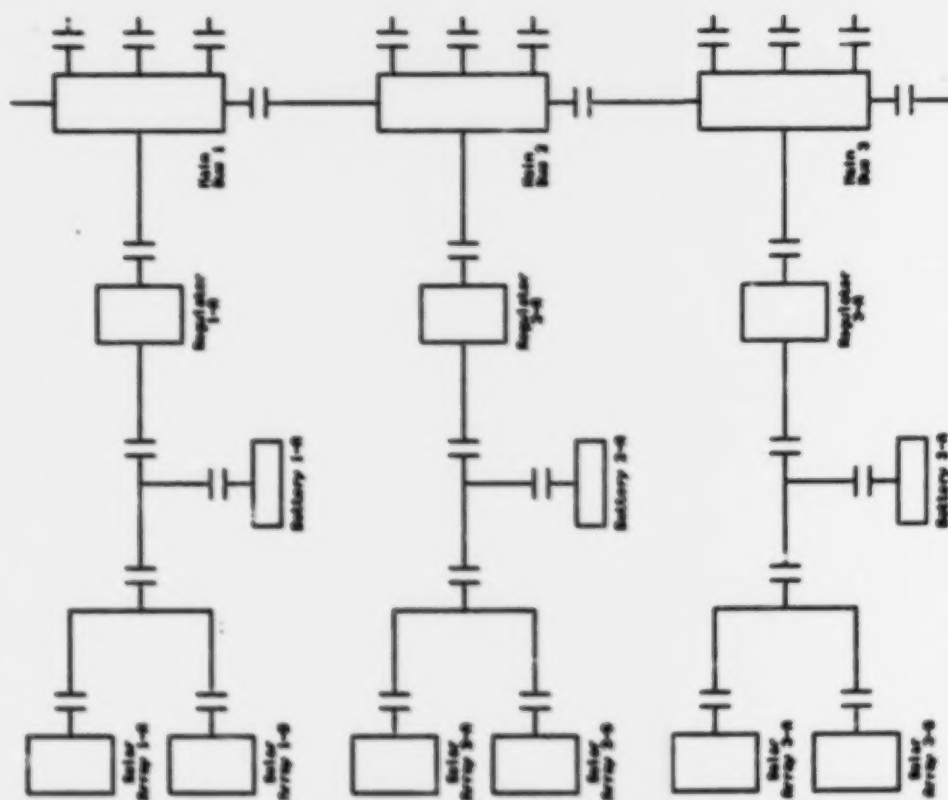


Test Configuration Window 3

SCREEN 3.2.3.1

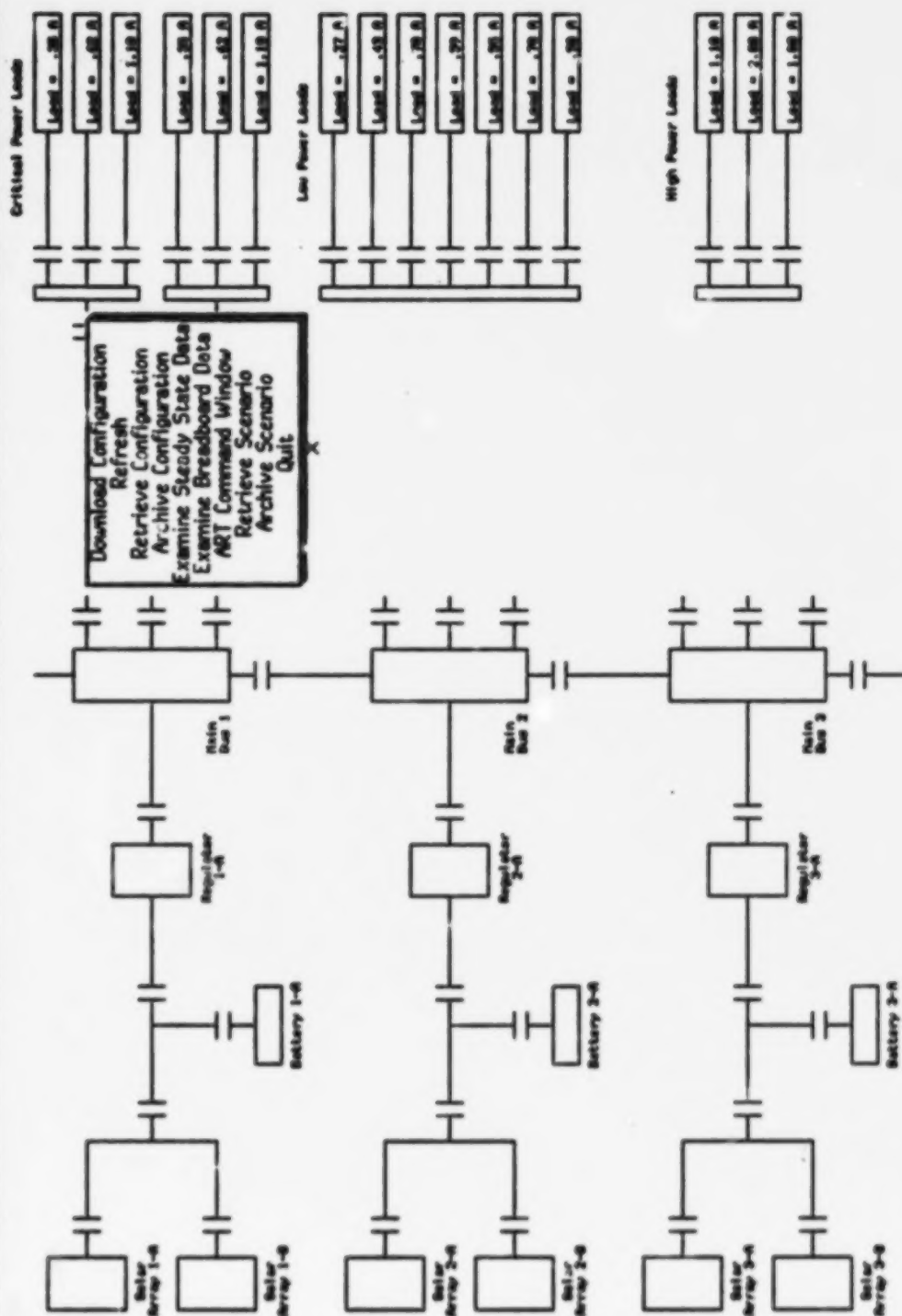

Waiting on initialization...
as File Interface Status as


SCREEN 3.2.3.2

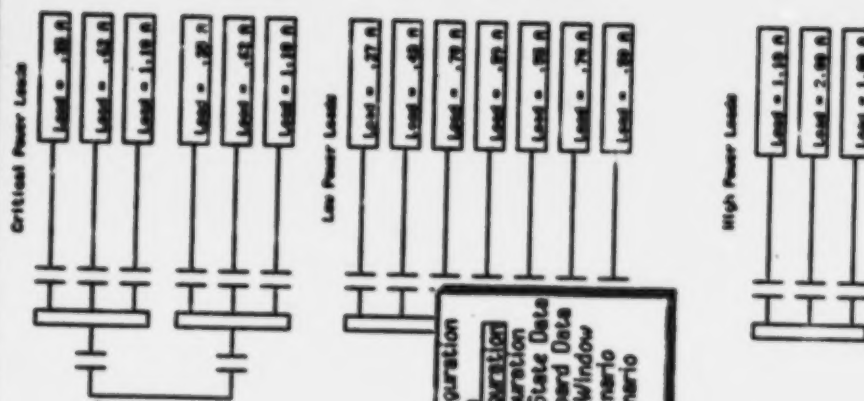

Download Configuration
 Refresh
 Retrieve Configuration
 Archive Configuration
 Examine Steady State Data
 Examine Breadboard Data
 APT Command Window
 Retrieve Scenario
 Archive Scenario
 Quit

ORIGINAL PAGE IS
 OF POOR QUALITY

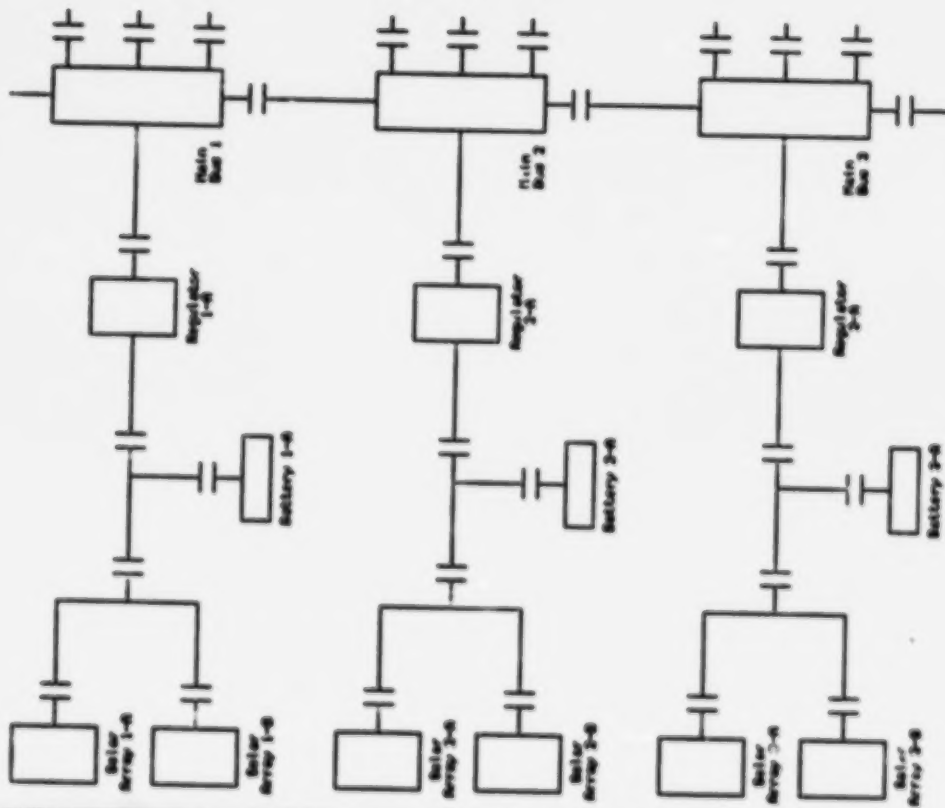
Waiting on initialization..
 as File Interface Status as



Test Configuration Window 1

SCREEN 3.2.3.3.1

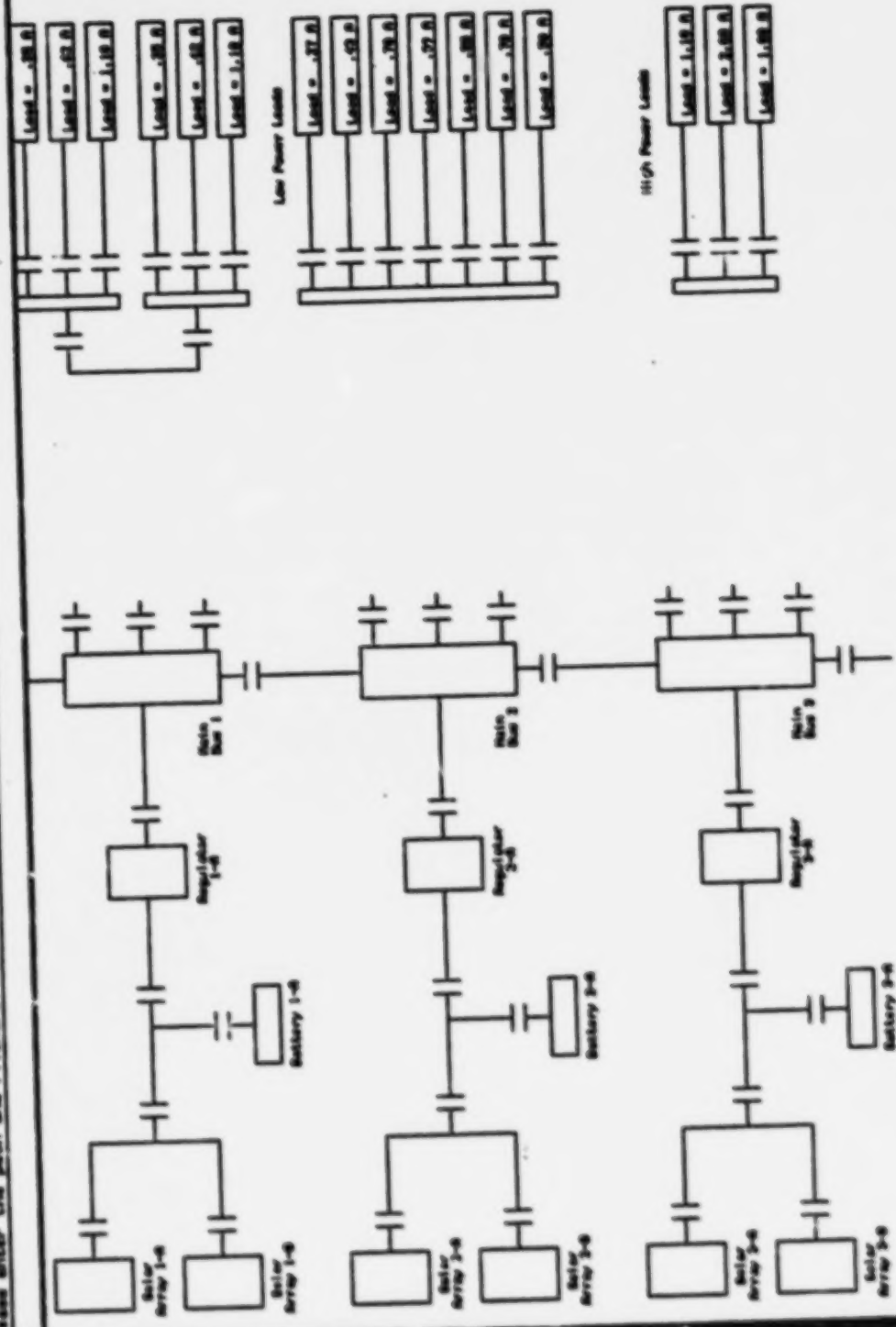
Please enter the path and filename. Default is diffies/libary



Library select.....
as Pigs Interface Status is

Test Configuration Window 3

SCREEN 3.2.3.3.2

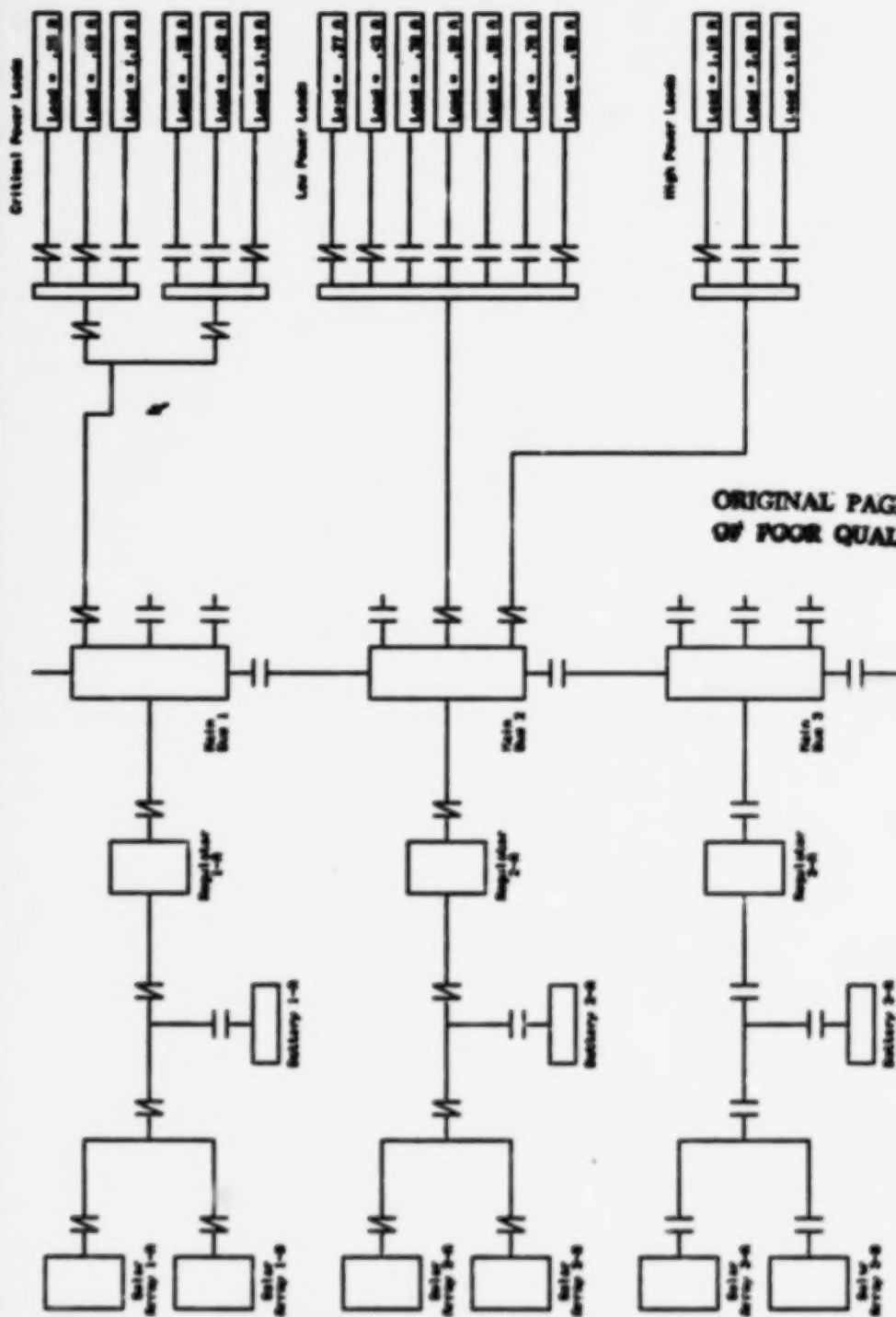

ORIGINAL PAGE 12
OF POOR QUALITY

Waiting on initialization...
as Fire Interface Status is


Last Configuration Window 3


SCREEN 3.2.3.4

INTERACTIVE

SCREENS

TEXT

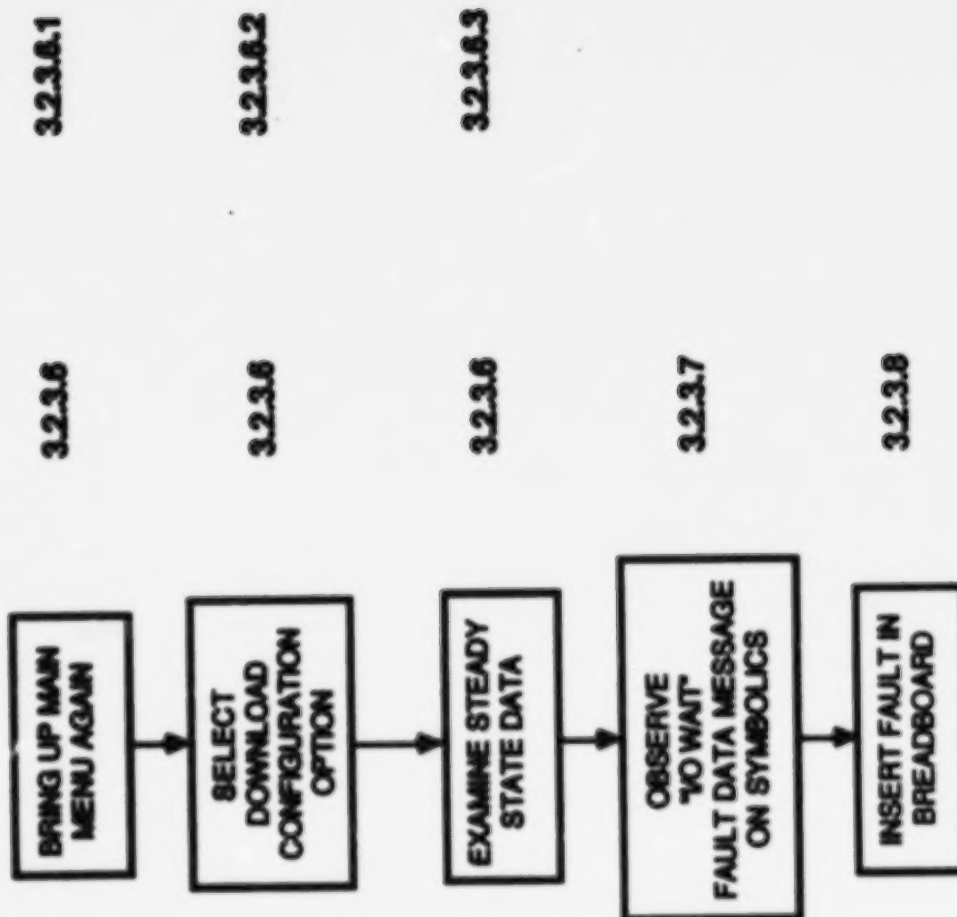


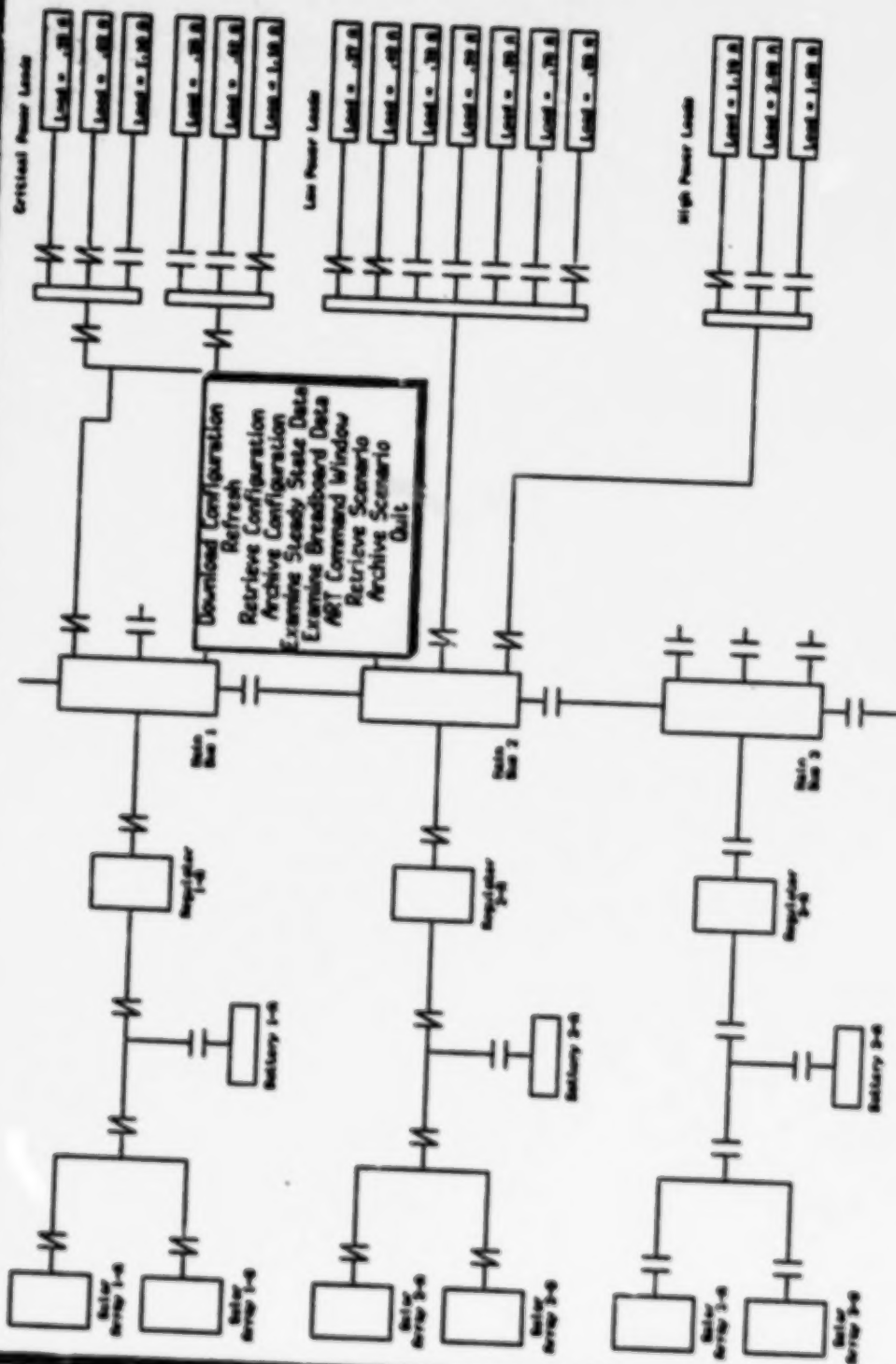


Waiting on initialization...
in File Interface Status as

Test Configuration Window 3

SCREEN 3.2.3.6.1

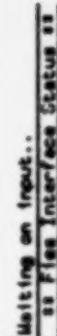

SCREEN 3.2.3.6.2

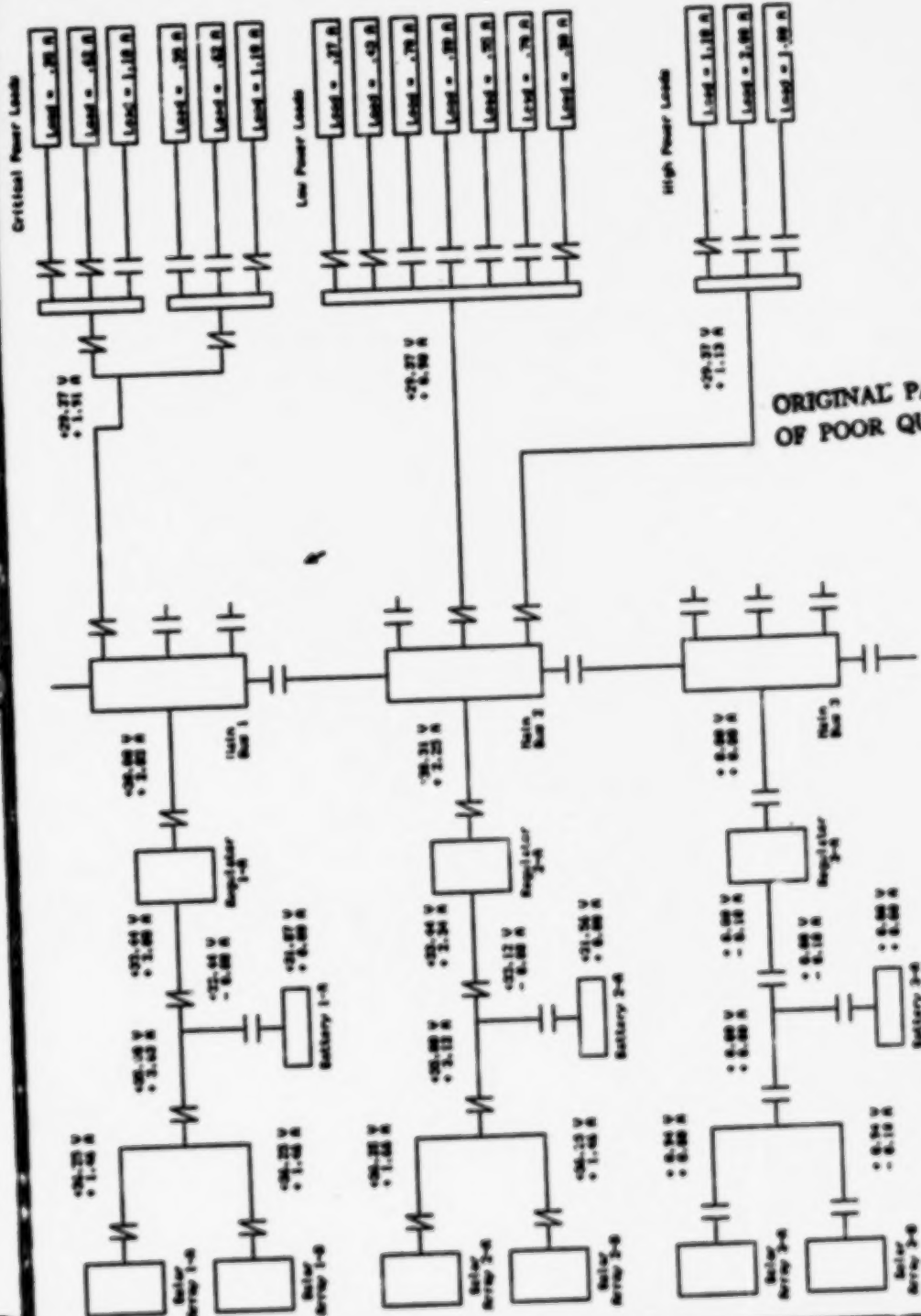


Displaying steady state..

INTERACTIVE

TEXT

SCREENS

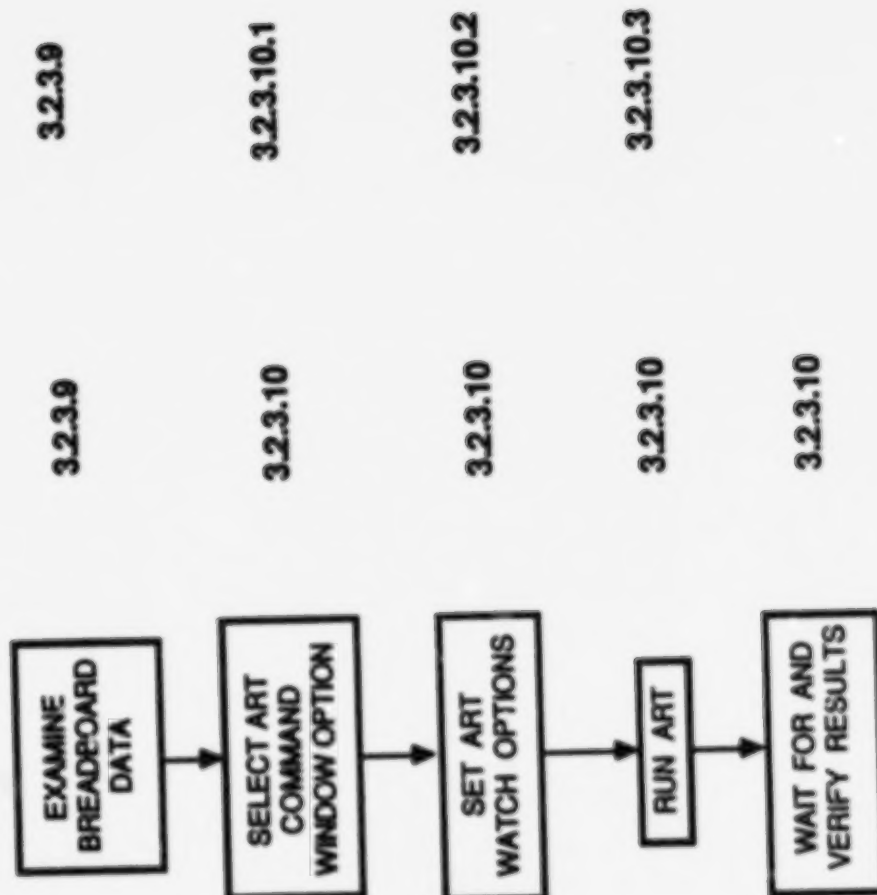

3.2.3.9

3.2.3.9

3.2.3.10.1

3.2.3.10


3.2.3.10.2

3.2.3.10

3.2.3.10.3

3.2.3.10


3.2.3.10

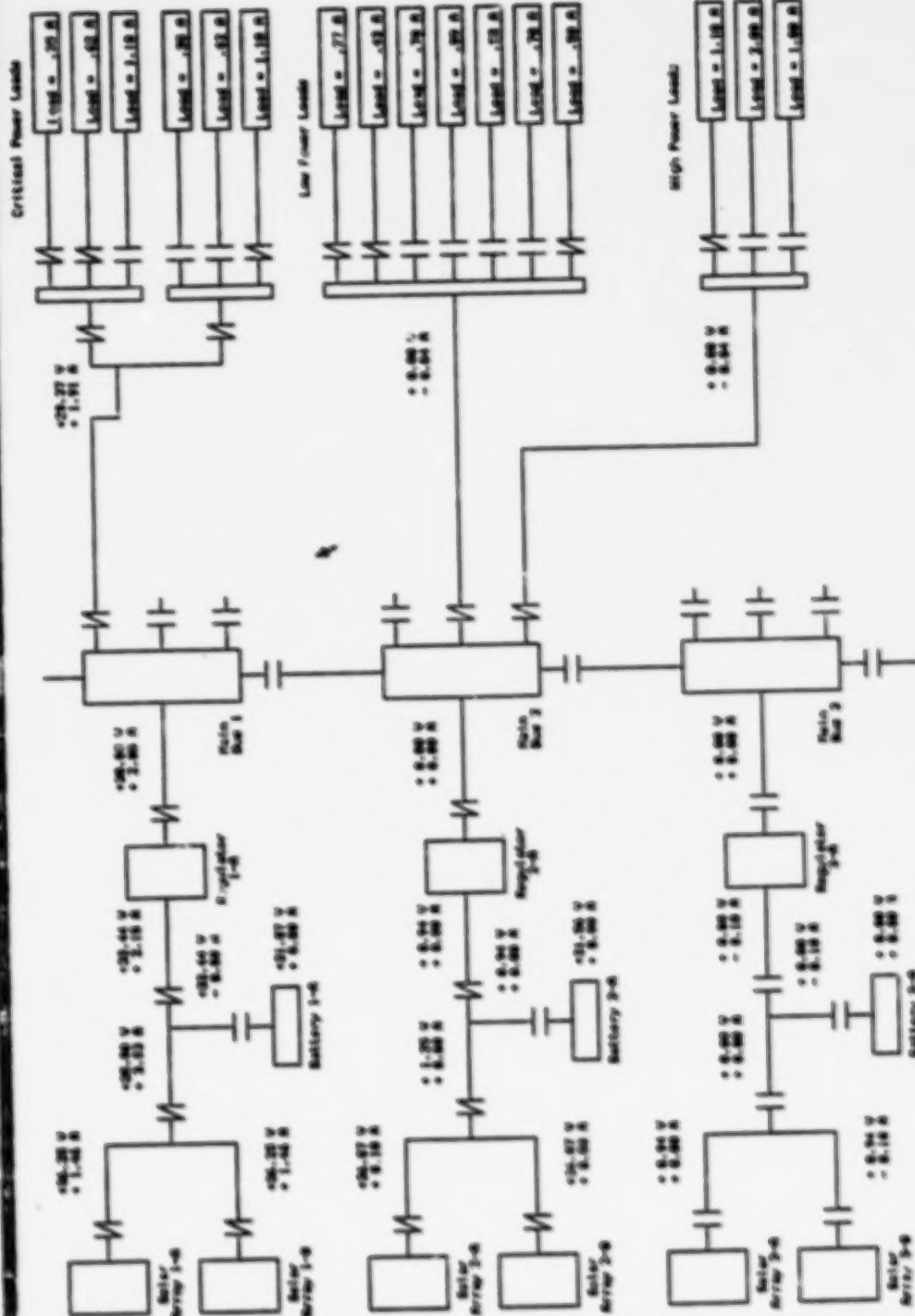

Displaying faulted state...
 as Figs interface status as

View Fault State Display Window 1

SCREEN 3.2.3.9

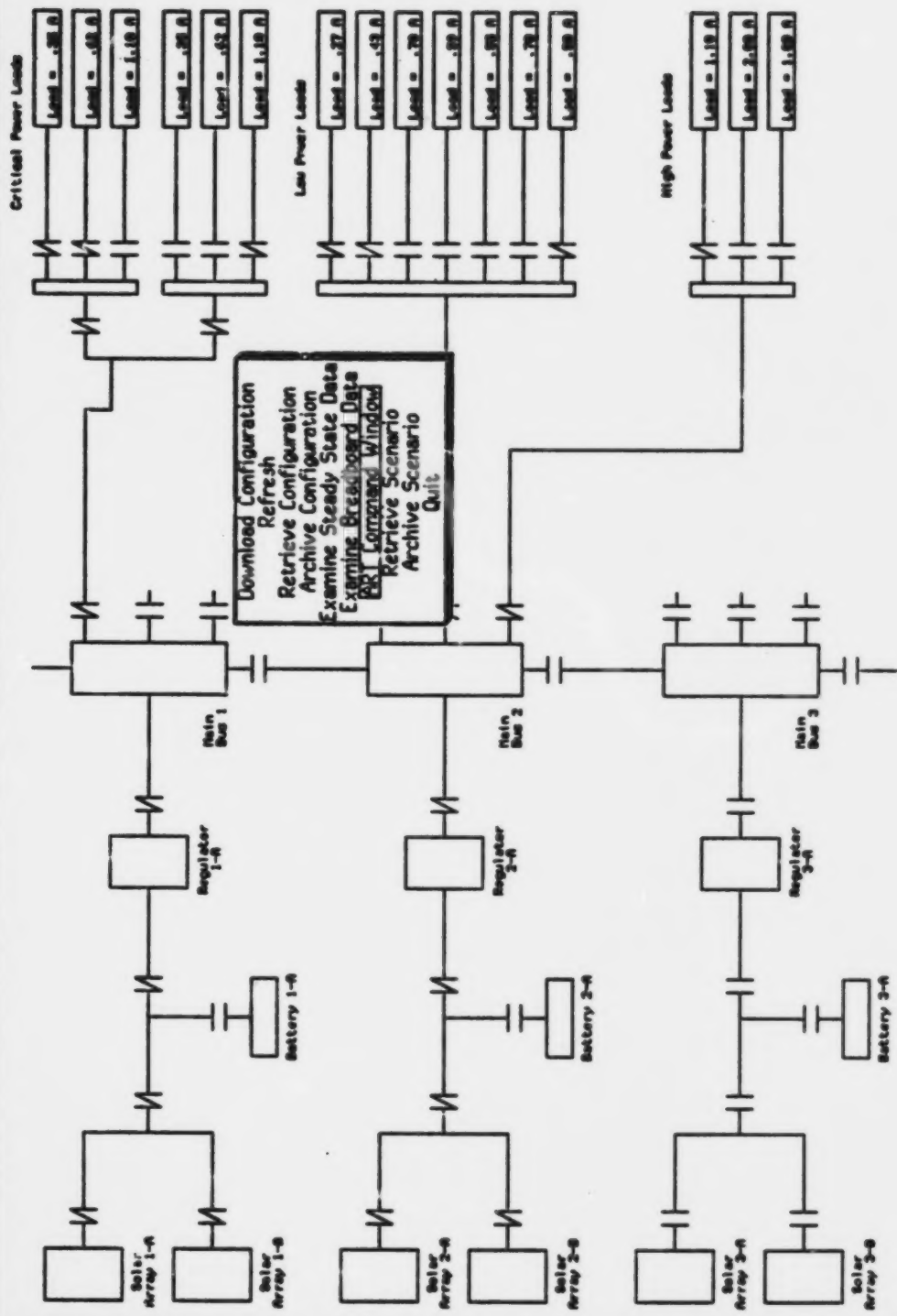

Waiting on input...
 as File Interface Status is

Test Configuration Window 3

SCREEN 3.2.3.10.1

COMMAND WINDOW

```

=>
=P=J=P=J=P=J=P=J
Loading SIGNIN:art-test>p-summary.art.1 in package ART-USER and base
18.
Compiling rule PRINTOUT-ALL-FAULTS... =P=J
Compiling rule SUMMARIZE-ALL-FAULTS... =P=J
Compiling rule PRINTOUT-REMAINING-FAULTS-FLAG... =P=J
Compiling rule PRINTOUT-REMAINING-FAULTS... =P=J=P=J=P=J
=> reset
Resetting ART...
=> run
Program halted.
    
```

ROOT

```

clear
load
reset
run
stop
browse
miscellaneous
icon editor
examples
    
```

ORIGINAL PAGE IS
OF POOR QUALITY

SCREEN 3.2.3.10.2

COMMAND WINDOW

FINE 418 PRINTOUT-REMAINING-FAULTS F-5100 in (STATE-2)
 == Activation PRINTOUT-REMAINING-FAULTS F-5100 in (STATE-2)
 OPEN-CIRCUIT BUS-2A

FINE 419 MALT-FIES-END in (STATE-1)
 == Activation MALT-FIES-END in (STATE-1)
 Program halted.

== OPEN-CIRCUIT RELAY-2C

ROOT

clear
 load
 reset
 watch
 stop
 browse
 miscellaneous
 tape editor
 examples

ORIGINAL PAGE IS
 OF POOR QUALITY

SCREEN 3.2.3.10.3

APPENDIX B

Fault Isolation Expert System Test and Demonstration Plan

APPENDIX - B

Fault Isolation Expert System (FIES) Test and Demonstration Plan

0.0 PURPOSE

The purpose of the FIES Test and Demonstration Plan, as the name suggests, is twofold. First it discusses the considerations, scope, and procedures for verifying the operational status and system capabilities of FIES. And secondly, it presents a scenario for the final acceptance demonstration at the Marshall Space Flight Center.

1.0 FIES DESCRIPTION

FIES consists of a number of integrated hardware and software subsystems. The overall "health" of FIES is determined by the combined operational status of these subsystems. The strategy behind testing FIES operational status is based on testing "first things first". A brief description of the subsystems is presented below.

1.1 FIES Hardware

FIES hardware is divided into three major subsystems. The first is the Breadboard which contains solar array simulators (power supply modules), batteries, network configuration relays, load simulation modules, measurement networks, and control logic. These components may be configured into a power subsystem (also referred to as a power network) manually at the Bread Board Fault Insertion Panel, via keyboard entry at the Micro Processor Terminal (Monitor), or through the Graphics/Mouse Interface on the SYMBOLICS Terminal. Four fault types are supported and may be inserted via the Bread Board Front Panel Fault Insertion switches. The fault types include:

- 'opened relay' - which interrupts current through some point in the power subsystem,
- 'closed relay' - which allows fault current to flow to some point in the power subsystem,
- 'resistive shunt' - which causes excessive current drain (1-2 amperes) at some point in the power subsystem, and
- 'direct shunt' - which causes an infinite current sink at some point in the power subsystem that is limited only by the current sourcing capability of the power modules.

The second major hardware subsystem is the Micro Processor. The Microprocessor provides an operating system for managing and monitoring the Bread Board Subsystem. A bit oriented memory map allows individual control over the network configuration relays. Writing a '1' to the corresponding memory bit forces a relay contact closure and writing a '0' forces the relay contacts open. In this way, various power networks can be dynamically configured for evaluation and demonstration of the fault isolating capabilities of FIES.

The Microprocessor provides hardware for monitoring the voltage and current levels at 24 sensor node locations in the power subsystem. It is also equipped with added I/O capabilities for interfacing to the Bread Board Front Panel, the Monitor Terminal, and the SYMBOLICS machine.

The third hardware subsystem is the SYMBOLICS machine. The SYMBOLICS provides the processing environment for the Expert System software, which is an extension of the Automated Reasoning Tool (ART). Graphic capabilities supported by the SYMBOLICS terminal provides a user environment that is easy to master.

1.2 FIES Software

The software is divided into three main subsystems (or Layers). The layer closest to the Bread Board is the Sensor Data Acquisition Scheduler (SDAS) whose task is to coordinate the activities of the Micro Processor. These activities include controlling the Bread Board hardware, monitoring the sensor measurement nodes for steady or fault states, and handling communications with the SYMBOLICS.

The middle layer, the Expert System Communications Interface, resides on the SYMBOLICS. Its activities include communicating with SDAS (on the Micro Processor), supervising the sensor load network configuration, managing the sensor load measurement data, interacting with Human Operators, and interfacing to the Expert System.

The outermost layer is the Expert System itself. Its activities include interacting with the Expert System Interface and hypothesizing the source of faults manually introduced via the Fault Insertion Panel on the Bread Board.

2.0 FIES Testing Strategy

FIES testing is clearly divided into two areas of effort. The first area involves verify that the hardware and software system are working normally. In this context, 'normally' means that the hardware is operating within its normal limits and that the software is basically 'same'. This portion of the testing effort will hereafter be referred as "FIES Operational Status Testing".

The second area of testing involves exercising the fault isolating capabilities of the Expert System software. This testing effort assumes that the operational status of FIES has been verified and that all faults detected correspond to faults manually inserted at the Bread Board Fault Insertion Panel.

2.1 FIES Operational Status Testing

Testing of FIES operational status is approached from a "layered" point of view and will be done in the following four phases:

- 1) The Bread Board Hardware Integrity Test (Procedure A) verifies that the fault insertion and sensor load hardware are operational.
- 2) The Microprocessor Software Integrity Test (Procedure B) verifies that the Sensor Data Acquisition Scheduler (SDAS) is running normally, that sensor node voltage/current levels can be measured accurately, and that steady and fault states can be achieved.
- 3) The Microprocessor - SYMBOLICS Communication Subsystem Test (Procedure C) verifies that control handshaking and sensor node data transferral between the SYMBOLICS and Micro Processor are operational.

- 4) The SYMBOLICS - FIES Operational Test (Procedure D) verifies that the FIES Software is operational and capable of hypothesizing a single fault correctly. (This test is a simple sanity test; its intention is not to exhaustively prove the fault isolating capabilities of FIES.)

2.2 FIES Capability Testing

While the previous tests verify the basic operational status and integrity of FIES, they do not attempt to fully exercise the reasoning and fault isolation capabilities of the underlying Automated Reasoning Tool (ART) software upon which FIES is built. For that matter, no test will be able to verify all possible permutations of the FIES sensor load network. The best that can be done is to cover as many configuration/fault combinations as is reasonable and yet still practical.

Some important considerations come to mind when choosing a benchmark set of configuration/fault combinations. FIES should be able to isolate faults in small, minimally loaded configurations as well as more complicated, heavily loaded configurations. It should be able to deal with single bus configurations as well as multi bus arrangements. All four supported fault types, 'open relay', 'closed relay', 'resistive shunt', and 'direct shunt', should be applied in various test cases but for at least one complete multiply-loaded bus configuration, all fault types should be applied at each and every point in the sensor load network.

Test Procedure E presents a test procedure for generically testing the fault isolating capabilities for any configuration/fault combination.

3.0 Demonstration Strategy

This section outlines the procedure and context for the demonstration performed at NSFC.

3.1 Content

The demonstration consists of a selected number of test uses. This set is a subset of the cases used for the formal acceptance test. These cases represent a range of network configurations, ranging from single sink, single source configurations to multiple sink multiple source configurations. These cases were chosen using 3 criteria:

- 1) A case must be representation of a possible power system configuration.
- 2) A case must not cause a power overload in the system.
- 3) A case must not violate any of the conditions described in chapter 6.

3.2 Procedure

3.2.1 Initialization

The computer system was initialized by MMC personnel. This included all phases of integrity testing described in procedures A-E.

3.2.2 Demonstration

The rationale for each case (based on the criteria of section 3.1) was presented. Following this presentation on each case MSFC personnel executed the FIES system for the case. Discussion as required followed.

**Bread Board Hardware Integrity Test
(Procedure A)**

- 1.0 o With power cord unplugged, use an ohmmeter to verify that no short exists between the hot and neutral AC lines. If none exists, plug the AC power cord into a 115VAC, 10AMP circuit.
- 2.0 o With the circuit breaker in the 'off' position, verify that +115AC is present between the "neutral" and the "line" terminals of the CONNELL-DUBILIER line filter.
- 3.0 o Apply power to the breadboard by throwing the circuit breaker to the 'ON' position. Verify that the "digital subsystem" and the "power subsystem" lamps are glowing.
- 4.0 o Measure the voltage between the + and - sense terminals on the H.P. 6264B power supply. This voltage should be +5VDC, $\pm 5\%$. Verify that the current display is reading approximately 10 amperes of current load.
- 5.0 o Measure the voltage between the + and - sense terminals of the 6 power modules contained in the 3H.P. 6255A power supplies. This voltage should be + 38.5 VDC, $\pm 2\%$. With the meter switch set to the 1.8A scale, verify that the current load is presently reading 0 amperes.
- 6.0 o Verify that the "boot" procedure has completed by observing the "-" prompt on the system console. Enter "SDAS.EXE" and a carriage return on the system console.
- 7.0 o Place the rotary switch in the "status" position. Place the node I.D. thumbwheel switch to '22'. Depress the "Repeat Function" momentary switch on the main panel. Observe that the node 22 voltage reads +33.75VDC, $\pm 5\%$ in the alphanumeric display. This indicates that the power module 1 battery is in place, and appears to have a sufficient charge to drive the breadboard.
- 8.0 o Set the Node I.D. to 23. Again depress the "Repeat Function" switch and observe that the module 2 battery voltage is +33.75VDC, $\pm 5\%$.
- 9.0 o Set the Node I.D. to 24. Depress the "Repeat Function" switch and observe that the module 3 battery voltage is +33.75VDC, $\pm 5\%$.
- 10.0 o Set the two paddle switches on the Fault Insertion panel to "closed" and "resistive", respectively.

- 11.0 o Raise toggle switches 1, 4, 5, 6, 22, 27, and 30. Verify that all other toggle switches are in the center position. Verify that the "Low Power", "High Power", and "Critical Power" lamps are glowing. This verifies that power module #1-A is supplying power to the system.
- 12.0 o Set toggle switch #1 to the center position and verify that the "Low Power", "High Power", and "Critical Power" lamps are extinguished. Raise toggle switch #2 and verify that the three lamps are again illuminated. This verifies that power module #1-B is supplying power to the system.
- 13.0 o Lower toggle switch #2 to the center position and verify all three of the power load branch lamps go out. Raise toggle switch #3. Verify that the three lamps are again illuminated. This assures that the battery in module 1 is supplying power to the system. Return all toggle switches to the center position.
- 14.0 o Raise toggle switches 7, 10, 11, 12, 23, 25, and 28. Again all three load branch lamps should be illuminated. Returning toggle switch #7 to the center position should cause all three lights to go out.
- 15.0 o Raise toggle switch #8, verifying that the three load branch lamps are re-powered. Returning #8 to center position extinguishes the lamps. If all three lamps are again lit when switch #9 is raised, then the battery in module #2 has sufficient power to drive the network. Return all relays to center position.
- 16.0 o Raise toggle switches 13, 16, 17, 18, 24, 26, 29. As before the three load branch lamps should be lit. Returning #13 to center position and then raising #14 should cause the lamps to momentarily go out. Lowering #14 and then raising #15 should have the same effect. Return all toggle switches to center position.
- 17.0 o The breadboard is now ready for microprocessor software testing.

Micro Processor Software Integrity Test (Procedure B)

- 1.0 o Perform and verify Micro Pro hardware test
- 2.0 o Boot micropro and verify startup diagnostics: (Refer to INTEL's Software Diagnostic Test Manual if error)
- 3.0 o Load and start SDAS.EXE
- 4.0 o Put the bread board rotary switch in 'TEST MODE'. Bread board will respond with "MONITOR SRC MODE" on ASCII Display Device. This action will cause the MONITOR keyboard to be substituted for the SYMBOLICS (at the communication interface level only).
- o Care must be taken when entering command strings in this mode because the format is fixed and the Micro Pro software is not very forgiving (a misformed command string can hang the Micro Pro thus requiring a reboot). (A <BACKSPACE> character can be entered to discard previously mistyped characters.)
- o Note that command strings entered from the MONITOR use decimal for relay and sensor node ID numbers (the SYMBOLICS would normally use hex encoding).
- 5.0 o Verify that all Fault Insertion switches are in the 'NORMAL' position.
- 6.0 o Enter a configuration ('config') string, for example:
 c010102010401050106012201310133013501
- o Observe the ASCII Display Device output message "LOADING CONFIGURATION."
- o Verify that the proper relay LEDs are lighted (for this example, relays 1, 2, 4, 5, 6, 22, 31, 33, and 35 should be lighted and other relay LEDs should be extinguished).
- o At MONITOR, verify the resulting 'config' status message, the string for this example would be as follows:

 c010102010300040105010601070008000900100011001200130014001500
 1600170018001900200021002201230024002500260027002800290030003
 1013200330134003501360037003800390040004100420043004400450046
 0047004800
- o Verify that Power Supplies 1 and 2 of Power Module 1 are supplying current and that the remaining supplies are not.

- 7.0 o At this point SDAS.EXE will wait for the bread board to achieve a steady state condition that will be indicated by an ASCII Display Device message "STEADY STATE ACHIEVED".
- o Verify that some rendition of the following 'steady state' sensor node data string is output at the MONITOR: (Slightly varying conditions will cause some deviation in voltage and current values output in the 'steady state' string.)
- ```

#017507027407036E0204710E056D10065F10070300080300090000100000
1100001200001303001403001500FF1600001700FF180000195F232000FF2
100FF226C00236D00246200

```

- 8.0      o    SDAS.EXE will then enter a "looking for fault" mode that periodically compares new measurement data to the steady state data. (A difference filter of +3 and -3 counts is applied to minimize the effects of spontaneous noise.)
- o    Insert a fault into the configuration. (For this example, set the RELAY FAULT TYPE switch to OPEN and the fault insertion switch for Relay 1 to RELAY. This fault will cause the current supplied by Power Supply 1 to be interrupted completely thus requiring Power Supply 2 to take on the additional current load.)

- 9.0      o    Upon detection of the fault, "FAULT DETECTED" will be output on the ASCII Display Device.
- o    Verify that some rendition of the following 'fault state' sensor node data string is output at the MONITOR: (Slightly varying conditions will cause some deviation in voltage and current values output in the 'fault state' string.)
- ```

#01730002740E036D0104710E056D10066010070300080300090000100000
1100001200001303001403001500FF1600001700FF180000195F242000FF2
100FF226C00236D00246200

```

- 10.0 o Change the rotary switch setting to FAULT NODES
- o Observe the ASCII Display Device which should be displaying data for sensor node 1 (N01) in the following form: (Values may not be exactly the same but they should be reasonable.)

```
N01 00.000a  <=  00.780a
```

The first value represents the fault state node current while the second value represents the steady state node current. As expected, the current for Power Supply should be zero (or slightly positive or negative) after the fault is inserted.

- o Depress the REPEAT FUNCTION switch to advance the fault display to the next mismatching voltage/current measurement which in this case should be:

N02 01.463a <= 00.780a

Note that the fault current for Power Supply 2 should be close to twice the steady state value.

- o Depressing the REPEAT FUNCTION switch again should result in an ASCII Display Device message that reads "FAULT DISPLAY FINISHED". If not, reactivate the switch to scroll through any other voltage/current mismatches that have been detected until the above message is displayed.

- 11.0 o Return the switch for relay 1 to NORMAL (vs. RELAY), select a NODE I.D. of 01, and set the rotary switch to STATUS.
- o The ASCII Display Device will display the present voltage/current measurement data for Sensor Node 1 as follows: (Values may vary.)

N01 36.563v 00.780a

The first value represents the node voltage (in volts) and the second value represents the node current (in amperes). As expected the current level supplied by Power Supply 1 has returned to a nominal value.

- o Change NODE ID to 02 and depress the REPEAT FUNCTION switch.
- o This action will display the voltage/current measurement data for Sensor Node 2 which should be close to:

N02 36.563v 00.780a

And again as expected the current supplied by Power Supply 2 has returned to its nominal value.

- 12.0 o Repeat steps 5.0 through 11.0 for the other configurations and verify that the Bread Board responds properly, that inserted faults can be detected and the voltage/current data is reasonable.

Micro Processor - SYMBOLICS Communication Subsystem Test
(Procedure C)

- 1.0 o Power on Monitor and SYMBOLICS CRT terminals.
- 2.0 o Apply power to SYMBOLICS
- o To bootstrap SYMBOLICS, enter: logout <return> then: halt machine <return>, watch for the Fep > prompt at the top of the terminal display, and enter b <return>.
- o Login to SYMBOLICS by entering:
 (login'fies)
- o Load and start the SYMBOLICS Interface Software Subsystem:
 (load "c: >fies> make-fies-interface.bin")
 (make-system'fies-interface':noconfirm)
- 3.0 o Apply power to the Bread Board (this action will auto-boot the Micro Processor).
- o Verify Micro Processor boot and self-test diagnostic results (If problem, refer to INTEL's Software Diagnostic Test Documentation).
- 4.0 o Rotate Front Panel selector switch to RESET.
- o At Monitor CRT terminal, enter:
 SDAS.EXE
- o After a small delay, the Bread Board should respond with "SYSTEM HAS BEEN RESET" on the ASCII Display Device.
- 5.0 o At SYMBOLICS terminal, start the test configuration software as follows:
 (test-configuration)
- o Verify that an unconfigured graphic representation of the FIES network is displayed on the SYMBOLICS terminal.
- 6.0 o Set all Fault Insertion switches to NORMAL.
- o Rotate Fron Panel selector switch to SLAVE MODE.
- o Verify ASCII Display Device message reads "SYMBOLICS SRC MODE".

- o If ASCII Display Device message is not as expected, depress the REPEAT FUNCTION and recheck.
- 7.0
- o At SYMBOLICS terminal, establish a configuration via the mouse input device.
 - o Visually reverify the configuration is as desired.
 - o Download the configuration via the mouse/menu selection window.
 - o Verify that the status message in lower corner of SYMBOLICS terminal reads "EMIT configuration to micro".
- 8.0
- o Verify that ASCII Display Device message reads "LOADING CONFIGURATION".
 - o Verify that the LEDS are lighted for relays that were turned on and extinguished for those relays that were turned off in the configuration download.
 - o Verify that the Power Module current meters register a reasonable level of current flow for the selected configuration.
 - o Verify that the status message in lower corner of SYMBOLICS terminal reads "IO Wait: Steady State..".
- 9.0
- o After waiting a few moments, verify that the Bread Board has stabilized by observing the ASCII Display Device message, "STEADY STATE ACHIEVED".
 - o Verify that the steady state data stream has been received at the SYMBOLICS by observing "IO Complete: Steady State" in the status display window in the lower right hand corner of the SYMBOLICS terminal.
 - o Verify that this status message changes to "IO Wait: Fault Data" which means that the SYMBOLICS is ready for a fault to be inserted.
 - o Using the mouse/menu, display the steady state graphic display window and verify that the voltage/current values are reasonable.
 - o Return to the previous configuration window and verify that the status is still "IO Wait: Fault Data. (If it is not then spurious noise has caused a false fault report and the test procedure should be restarted from step 6.0.)

- 10.0
 - o Insert a fault by depressing one of the Front Panel Fault Insertion switches.
 - o Verify that the associated LED is extinguished or illuminated if the fault type was an open or closed type fault, respectively.
 - o Verify that the inserted fault is detected by observing the ASCII Display Device message, "FAULT DETECTED".
 - o Verify that the fault data string is received at the SYMBOLICS by observing the message in the status window of the SYMBOLICS terminal which should read "IO Complete: Fault Data".
 - o Using mouse/menu window, display the fault state graphic display window and verify that the voltage/current values are reasonable for the type and location of the fault inserted.
- 11.0
 - o Remove the inserted fault by returning the Fault Insertion switch to its NORMAL position.
 - o If a direct shunt fault was applied, power cycle the associated Power Module to restore the Power Supplies to a "non-folded over" state.
- 12.0
 - o Repeat steps 6.0 through 11.0 for all applicable configurations.

**SYMBOLICS - FIES Operational Test
(Procedure D)**

- 1.0 o Power on Monitor and Symbolics CRT terminals.
- 2.0 o Apply power to SYMBOLICS.
 - o To bootstrap SYMBOLICS, enter: logout <return> then: halt machine <return>, then watch for the Fep > prompt at the top of the terminal display, and enter b <return>.
 - o Login to SYMBOLICS by entering:
 (login'fies:host "d")
- 3.0 o Apply power to the Bread Board (this action will auto-boot the Micro Pro).
 - o Verify Micro Pro boot and self-test diagnostic results (If problem, refer to INTEL's Software Diagnostic Test Documentation).
- 4.0 o Rotate Front Panel selector switch to RESET.
 - o At Monitor CRT terminal, enter:
 SDAS.EXE
 - o After a small delay, the Bread Board should respond with "SYSTEM HAS BEEN RESET" on the ASCII Display Device.
- 5.0 o Load and start the ART application software (i.e., the Expert System):
 - o To enter the ART world enter <select> A at the SYMBOLICS Terminal.
 - o Using mouse/menu window, clear ART
 - o Using mouse/menu window, load ART using the following file name:
 d: >art-test> load-fies.lisp

- o Using mouse/menu window, reset ART
 - o Using mouse/menu window, run ART
 - o Verify that an unconfigured graphic representation of the FIES network is displayed on the SYMBOLICS terminal.
- 6.0
- o Set all Fault Insertion switches to NORMAL.
 - o Rotate Front Panel selector switch to SLAVE MODE.
 - o Verify ASCII Display Device message reads "SYMBOLICS SRC MODE".
 - o If ASCII Display Device message is not as expected, depress the REPEAT FUNCTION and recheck.
- 7.0
- o At SYMBOLICS terminal, establish a configuration via the mouse input device or file archiving facility.
 - o Visually reverify the configuration is as desired.
 - o Download the configuration via the mouse/menu selection window.
 - o Verify that the status message in lower corner of SYMBOLICS terminal reads "XMIT configuration to micro".
- 8.0
- o Verify that ASCII Display Device message reads "LOADING CONFIGURATION".
 - o Verify that the LEDS are lighted for relays that were turned on and extinguished for those relays that were turned off in the configuration download.
 - o Verify that the Power Module current meters register a reasonable level of current flow for the selected configuration.
 - o Verify that the status message in lower corner of SYMBOLICS terminal reads "IO Wait: Steady State..".
- 9.0
- o After waiting a few moments, verify that the Bread Board has stabilized by observing the ASCII Display Device message, "STEADY STATE ACHIEVED".
 - o Verify that the steady state data stream has been received at the SYMBOLICS by observing "IO Complete: Steady State" in the status display window in the lower right hand corner of the SYMBOLICS terminal.
 - o Verify that this status message changes to "IO Wait: Fault Data" which means that the SYMBOLICS is ready for a fault to be inserted.

- o Using the mouse/mem, display the steady state graphic display window and verify that the voltage/current values are reasonable.
- o Return to the previous configuration window and verify that the status is still "IO Wait: Fault Data. (if it is not then spurious noise or battery charging has caused a false fault report and the test procedure should be restarted from the 'reset' in step 5.0.)"
- 10.0 o Insert a fault by depressing one of the Front Panel Fault Insertion switches.
- o Verify that the associated LED is extinguished.
- o Verify that the inserted fault is detected by observing the ASCII Display Device message, "FAULT DETECTED IN SYSTEM".
- o Verify that the fault data string is received at the SYMBOLICS by observing the message in the status window of the SYMBOLICS terminal which should read "IO Complete: Fault Data".
- 11.0 o At SYMBOLICS, wait for completion of the Expert System run.
- 12.0 o Verify the integrity of the fault hypothesis generated by the Expert System.
- 13.0 o Remove the inserted fault by returning the Fault Insertion switch to its NORMAL position.
- o If a direct shunt fault was applied, power cycle the associated Power Module to restore the Power Supplies to a "non-folded over" state.
- 14.0 o Repeat step 5.0 (from 'reset') through 13.0 for all applicable configurations.

Formal Acceptance Test Procedure (Procedure E)

1.0 Overview

This describes the procedure to be used in testing fault isolation capability for any selected case. The procedure is an implementation of the end to end testing specified in the FIES software development plan.

2.0 Case selection

The number of cases have been identified for formal acceptance test. These cases represent the full range of reasonable configurations possible in the power network. A reasonable configuration is selected based on the following criteria:

- 1) A case must be representative of a possible power system configuration.
- 2) A case must not cause a power overload in the system, or violate any of the conditions described in chapter 6 of the user's manual.

3.0 Procedure

- 3.1 Complete initialization and integrity testing as described in test procedures A-D.
- 3.2 For each test configuration in para. 3.3, perform the following steps
 - 3.2.1 Reset bread board
 - 3.2.2 Reset ART application
 - 3.2.3 Run ART application
 - 3.2.4 Select a configuration from configuration library
 - 3.2.5 Download configuration to the breadboard
 - 3.2.6 When the I/OWait: Fault Data message appears in the FIES Interface window, insert the desired fault into the breadboard
 - 3.2.7 Verify results against expected results. Expected results appear in 3.3 below with the test configuration case descriptions.

3.3 Description

3.3.1 Single Source to single-sink, low load requirements

3.3.1.1 Resistive Short Circuits (Example F-1)

3.3.1.2 Direct Short Circuit (Example F-2)

3.3.1.3 Open Circuits (Example F-3)

3.3.2 Two Sources to multiple sinks, low load requirements

3.3.2.1 Resistive Short Circuits (Example F-4)

3.3.2.2 Direct Short Circuits (Example F-5)


3.3.2.3 Open Circuits (Example F-6)

3.3.3 Four Sources to multiple sinks, high load requirements

3.3.3.1 Resistive Short Circuits (Example F-7)

3.3.3.2 Direct Short Circuits (Example F-8)

3.3.3.3 Open Circuits (Example F-9)

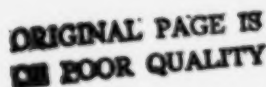

• **Enfield, Donna**, art, out, 75310

res 45 dat

Test Configuration Window 17

6-12-89 11:51 AM


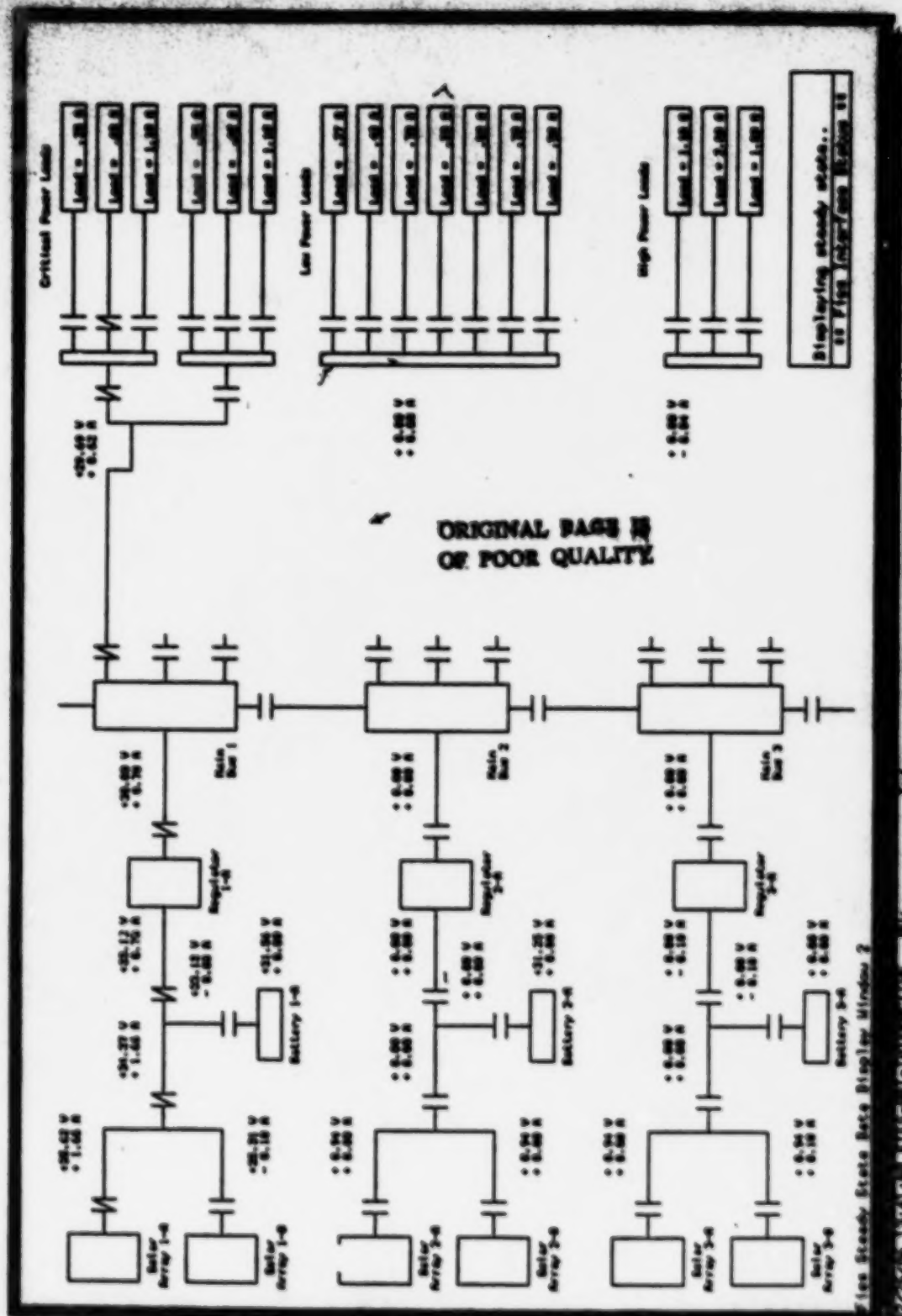


Fig. R-1

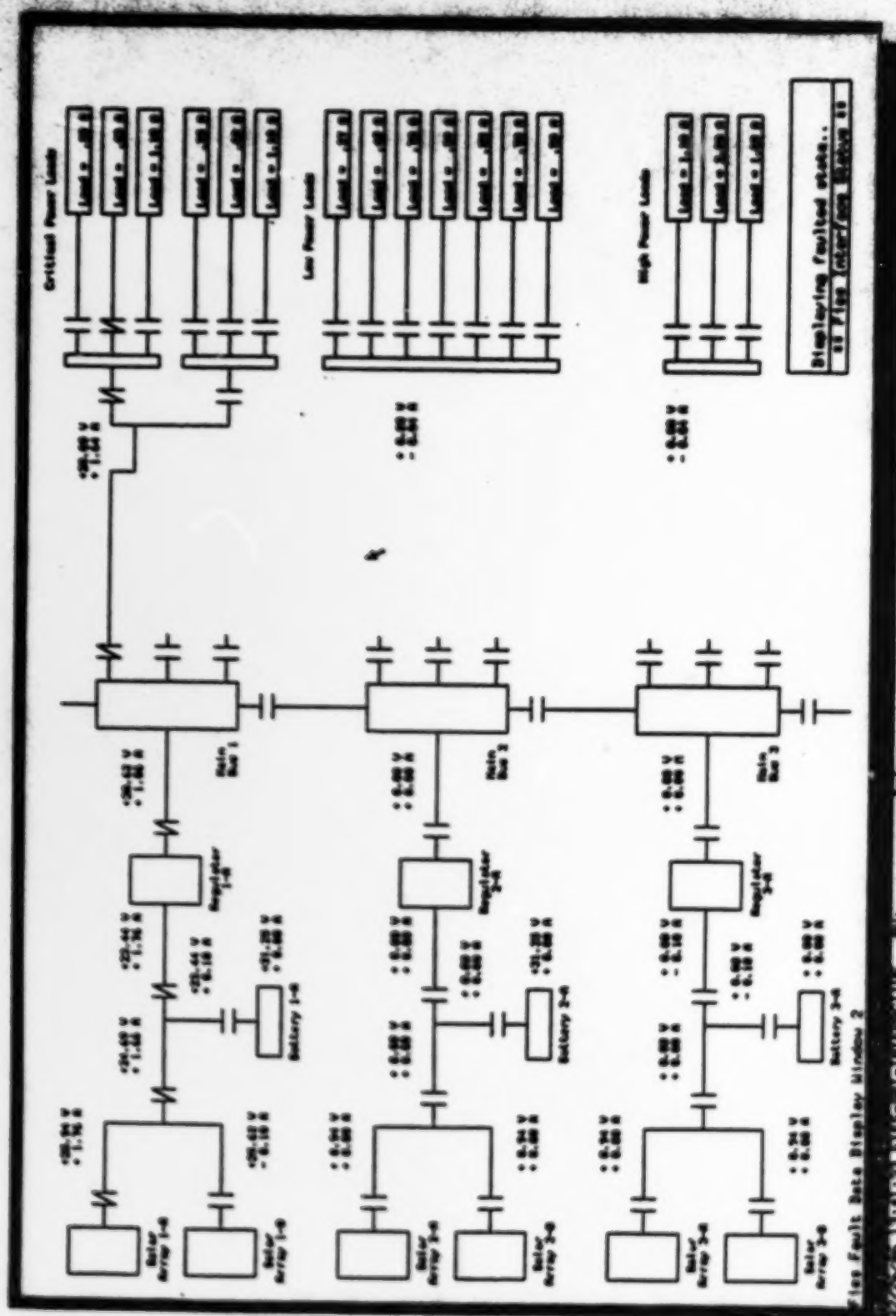

F-1

ORIGINAL PAGE IS
OF POOR QUALITY



www.izumi.co.jp

STRENGTHENING DELAWARE TITLE

RES 45-DAT

ORIGINAL PAGE IS
OF POOR QUALITY

File: F-1

4

=> pop

=> run

Beginning run at 2/26/88 13:42:43: type ^C to halt.
Initializing Circuit Description

Create Errorbands

Assigning Qualitative Values to Sensors

Hypothesizing Faults:

Fault-Hypothesis: Closed-Relay RELAY-1N

Fault-Hypothesis: Closed-Relay RELAY-1P

Fault-Hypothesis: Resistive-Short-Circuit BUS-1D

Fault-Hypothesis: Resistive-Short-Circuit BUS-1E

Fault-Hypothesis: Resistive-Short-Circuit LOAD-10

Fault-Hypothesis: Short-Circuit BUS-1D

Fault-Hypothesis: Short-Circuit BUS-1E

Fault-Hypothesis: Short-Circuit LOAD-10

Reject Fault Hypothesis Short-Circuit at LOAD-10
Reason: Predicted Voltage Effect Is Inconsistent at Sensor SENSOR-1G

Reject Fault Hypothesis Short-Circuit at BUS-1E
Reason: Predicted Voltage Effect Is Inconsistent at Sensor SENSOR-1G

Reject Fault Hypothesis Short-Circuit at BUS-1D
Reason: Predicted Voltage Effect Is Inconsistent at Sensor SENSOR-1G

Reject Fault Hypothesis Closed-Relay at RELAY-1P
Reason: Predicted Voltage Effect Is Inconsistent at Sensor SENSOR-1G

Reject Fault Hypothesis Closed-Relay at RELAY-1N
Reason: Predicted Voltage Effect Is Inconsistent at Sensor SENSOR-1G

Fault-hyp: Resistive-Short-Circuit BUS-1E
Source Propagation from BUS-1E to RELAY-1K

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-1E
Source Propagation from RELAY-1K to BUS-1D

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-1E
Source Propagation from BUS-1D to SENSOR-1G

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-1E
Predicted Current Effect: HIGH Consistent at Sensor SENSOR-1G
Source Propagation from SENSOR-1G to RELAY-1G

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-1E
Source Propagation from RELAY-1G to BUS-1C

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-1E
Source Propagation from BUS-1C to SENSOR-1F

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-1E
Predicted Current Effect: HIGH Consistent at Sensor SENSOR-1F
Source Propagation from SENSOR-1F to RELAY-1F

F-1

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-1E
Source Propagation from RELAY-1F to REGULATOR-1A

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-1E
Source Propagation from REGULATOR-1A to SENSOR-1E

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-1E
Predicted Current Effect: HIGH Constant at Sensor SENSOR-1E
Source Propagation from SENSOR-1E to RELAY-1E

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-1E
Source Propagation from RELAY-1E to BUS-1B

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-1E
Source Propagation from BUS-1B to SENSOR-1C

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-1E
Predicted Current Effect: HIGH Constant at Sensor SENSOR-1C
Source Propagation from SENSOR-1C to RELAY-1C

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-1E
Source Propagation from RELAY-1C to BUS-1A

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-1E
Source Propagation from BUS-1A to SENSOR-1A

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-1E
Predicted Current Effect: HIGH Constant at Sensor SENSOR-1A
Source Propagation from SENSOR-1A to RELAY-1A

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-1E
Source Propagation from RELAY-1A to SOLAR-ARRAY-1A

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-1E
End-Source Propagation from SOLAR-ARRAY-1A

Fault-hyp: Resistive-Short-Circuit BUS-1E
Sink Propagation from BUS-1E to RELAY-1D

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-1E
Sink Propagation from RELAY-1D to LOAD-1D

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-1E
End-Sink Propagation from LOAD-1D

Fault-hyp: Resistive-Short-Circuit BUS-1D
Source Propagation from BUS-1D to SENSOR-1G

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-1D
Predicted Current Effect: HIGH Constant at Sensor SENSOR-1G
Source Propagation from SENSOR-1G to RELAY-1G

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-1D
Source Propagation from RELAY-1G to BUS-1C

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-1D
Source Propagation from BUS-1C to SENSOR-1F

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-1D
Predicted Current Effect: HIGH Constant at Sensor SENSOR-1F
Source Propagation from SENSOR-1F to RELAY-1F

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-1D
Source Propagation from RELAY-1F to REGULATOR-1A

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-1D
Source Propagation from REGULATOR-1A to SENSOR-1E

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-1D
Predicted Current Effect: HIGH Constant at Sensor : JNSCR-1E
Source Propagation from SENSOR-1E to RELAY-1E

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-1D
Propagation from RELAY-1E to BUS-1B

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-1D
Source Propagation from BUS-1B to SENSOR-1C

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-1D
Predicted Current Effect: HIGH Consistent at Sensor SENSOR-1C
Source Propagation from SENSOR-1C to RELAY-1C

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-1D
Source Propagation from RELAY-1C to BUS-1A

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-1D
Source Propagation from BUS-1A to SENSOR-1A

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-1D
Predicted Current Effect: HIGH Consistent at Sensor SENSOR-1A
Source Propagation from SENSOR-1A to RELAY-1A

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-1D
Source Propagation from RELAY-1A to SOLAR-ARRAY-1A

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-1D
End-Source Propagation from SOLAR-ARRAY-1A

Fault-hyp: Resistive-Short-Circuit BUS-1D
Sink Propagation from BUS-1D to RELAY-1K

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-1D
Sink Propagation from RELAY-1K to BUS-1E

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-1D
Sink Propagation from BUS-1E to RELAY-10

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-1D
Sink Propagation from RELAY-10 to LOAD-10

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-1D
End-Sink Propagation from LOAD-10

Fault-hyp: Resistive-Short-Circuit LOAD-10
Source Propagation from LOAD-10 to RELAY-10

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-10
Source Propagation from RELAY-10 to BUS-1E

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-10
Source Propagation from BUS-1E to RELAY-1K

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-10
Source Propagation from RELAY-1K to BUS-1D

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-10
Source Propagation from BUS-1D to SENSOR-1G

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-10
Predicted Current Effect: HIGH Consistent at Sensor SENSOR-1G
Source Propagation from SENSOR-1G to RELAY-1G

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-10
Source Propagation from RELAY-1G to BUS-1C

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-10
Source Propagation from BUS-1C to SENSOR-1F

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-10
Predicted Current Effect: HIGH Consistent at Sensor SENSOR-1F
Source Propagation from SENSOR-1F to RELAY-1F

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-10
Source Propagation from RELAY-1F to REGULATOR-1A

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-10
Source Propagation from REGULATOR-1A to SENSOR-1E

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-10
Predicted Current Effect: HIGH Consistent at Sensor SENSOR-1E
Source Propagation from SENSOR-1E to RELAY-1E

6. F-1

7

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-10
Source Propagation from RELAY-1E to BUS-1B

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-10
Source Propagation from BUS-1B to SENSOR-1C

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-10
Predicted Current Effect: HIGH Consistent at Sensor SENSOR-1C
Source Propagation from SENSOR-1C to RELAY-1C

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-10
Source Propagation from RELAY-1C to BUS-1A

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-10
Source Propagation from BUS-1A to SENSOR-1A

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-10
Predicted Current Effect: HIGH Consistent at Sensor SENSOR-1A
Source Propagation from SENSOR-1A to RELAY-1A

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-10
Source Propagation from RELAY-1A to SOLAR-ARRAY-1A

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-10
End-Source Propagation from SOLAR-ARRAY-1A

Reporting All Initial Fault Hypotheses:

SHORT-CIRCUIT LOAD-10

SHORT-CIRCUIT BUS-1E

SHORT-CIRCUIT BUS-1D

RESISTIVE-SHORT-CIRCUIT LOAD-10

RESISTIVE-SHORT-CIRCUIT BUS-1E

RESISTIVE-SHORT-CIRCUIT BUS-1D

CLOSED-RELAY RELAY-1P

CLOSED-RELAY RELAY-1N

Reporting Final Fault Hypotheses:

RESISTIVE-SHORT-CIRCUIT LOAD-10

RESISTIVE-SHORT-CIRCUIT BUS-1E

RESISTIVE-SHORT-CIRCUIT BUS-1D

Readings at SENSOR-3Z

Normal Voltage: 0.0
Faulted Voltage: 0.0
Qual Voltage: NORMAL

Normal Current: 0.0
Faulted Current: 0.0
Qual Current: NORMAL

Readings at SENSOR-2Z

Normal Voltage: 31.24892
Faulted Voltage: 31.24992
Qual Voltage: NORMAL

Normal Current: 0.0
Faulted Current: 0.0

END: F-1

Qual Current: NORMAL

Readings at SENSOR-1Z

Normal Voltage: 31.662418
Faulted Voltage: 31.24992
Qual Voltage: NORMAL

Normal Current: 0.0
Faulted Current: 0.0
Qual Current: NORMAL

Readings at SENSOR-3G

Normal Voltage: 0.0
Faulted Voltage: 0.0
Qual Voltage: NORMAL

Normal Current: -0.0390624
Faulted Current: -0.0390624
Qual Current: NORMAL

Readings at SENSOR-2G

Normal Voltage: 0.0
Faulted Voltage: 0.0
Qual Voltage: NORMAL

Normal Current: 0.0
Faulted Current: -0.0390624
Qual Current: NORMAL

Readings at SENSOR-1G

Normal Voltage: 29.687424
Faulted Voltage: 19.999949
Qual Voltage: LOW

Normal Current: 0.6249984
Faulted Current: 1.6406208
Qual Current: HIGH

Readings at SENSOR-3F

Normal Voltage: 0.0
Faulted Voltage: 0.0
Qual Voltage: NORMAL

Normal Current: 0.0
Faulted Current: 0.0
Qual Current: NORMAL

Readings at SENSOR-3E

Normal Voltage: 0.0
Faulted Voltage: 0.0
Qual Voltage: NORMAL

Normal Current: -0.097656
Faulted Current: -0.097656
Qual Current: NORMAL

Readings at SENSOR-2C
 Normal Voltage: 0.0
 Faulted Voltage: 0.0
 Qual Voltage: NORMAL
 Normal Current: 0.0
 Faulted Current: 0.0
 Qual Current: NORMAL

Readings at SENSOR-2D
 Normal Voltage: 0.0
 Faulted Voltage: 0.0
 Qual Voltage: NORMAL
 Normal Current: -0.007000
 Faulted Current: -0.007000
 Qual Current: NORMAL

Readings at SENSOR-2E
 Normal Voltage: 0.9374876
 Faulted Voltage: 0.9374876
 Qual Voltage: NORMAL
 Normal Current: 0.007000
 Faulted Current: 0.0
 Qual Current: NORMAL

Readings at SENSOR-2F
 Normal Voltage: 0.9374876
 Faulted Voltage: 0.9374876
 Qual Voltage: NORMAL
 Normal Current: 0.0
 Faulted Current: 0.0
 Qual Current: NORMAL

Readings at SENSOR-2G
 Normal Voltage: 0.0
 Faulted Voltage: 0.0
 Qual Voltage: NORMAL
 Normal Current: 0.0
 Faulted Current: 0.0
 Qual Current: NORMAL

Readings at SENSOR-2H
 Normal Voltage: 0.0
 Faulted Voltage: 0.0
 Qual Voltage: NORMAL
 Normal Current: 0.0
 Faulted Current: 0.0
 Qual Current: NORMAL

Readings at SENSOR-2C
 Normal Voltage: 0.0
 Faulted Voltage: 0.0

Qual Voltage: NORMAL
Normal Current: 0.0
Faulted Current: 0.0
Qual Current: NORMAL

Readings at SENSOR-2D
Normal Voltage: 0.0
Faulted Voltage: 0.0
Qual Voltage: NORMAL
Normal Current: 0.0
Faulted Current: 0.0
Qual Current: NORMAL

Readings at SENSOR-2B
Normal Voltage: 0.9374878
Faulted Voltage: 0.9374878
Qual Voltage: NORMAL
Normal Current: 0.0
Faulted Current: 0.0
Qual Current: NORMAL

Readings at SENSOR-2A
Normal Voltage: 0.9374878
Faulted Voltage: 0.9374878
Qual Voltage: NORMAL
Normal Current: 0.0
Faulted Current: 0.0
Qual Current: NORMAL

Readings at SENSOR-1F
Normal Voltage: 29.988824
Faulted Voltage: 29.824847
Qual Voltage: LOW
Normal Current: 0.781248
Faulted Current: 1.885484
Qual Current: HIGH

Readings at SENSOR-1E
Normal Voltage: 33.124816
Faulted Voltage: 23.437438
Qual Voltage: LOW
Normal Current: 0.781248
Faulted Current: 1.757888
Qual Current: HIGH

Readings at SENSOR-1C
Normal Voltage: 34.374812
Faulted Voltage: 24.667437
Qual Voltage: LOW

al Current: 1.880152
led Current: 1.880152

F-1

11

Qual Current: NORMAL

Readings at SENSOR-10

Normal Voltage: 33.124816
Faulted Voltage: 23.437438
Qual Voltage: LOW

Normal Current: -0.878894
Faulted Current: 0.887888
Qual Current: NORMAL

Readings at SENSOR-18

Normal Voltage: 35.31241
Faulted Voltage: 25.824833
Qual Voltage: LOW

Normal Current: -0.887888
Faulted Current: -0.887888
Qual Current: NORMAL

Readings at SENSOR-1A

Normal Voltage: 35.82481
Faulted Voltage: 25.837433
Qual Voltage: LOW

Normal Current: 1.888152
Faulted Current: 1.757888
Qual Current: NORMAL


Program halted.

Ending run at 2/26/86 13:43:48.

=> watch

=> dribble

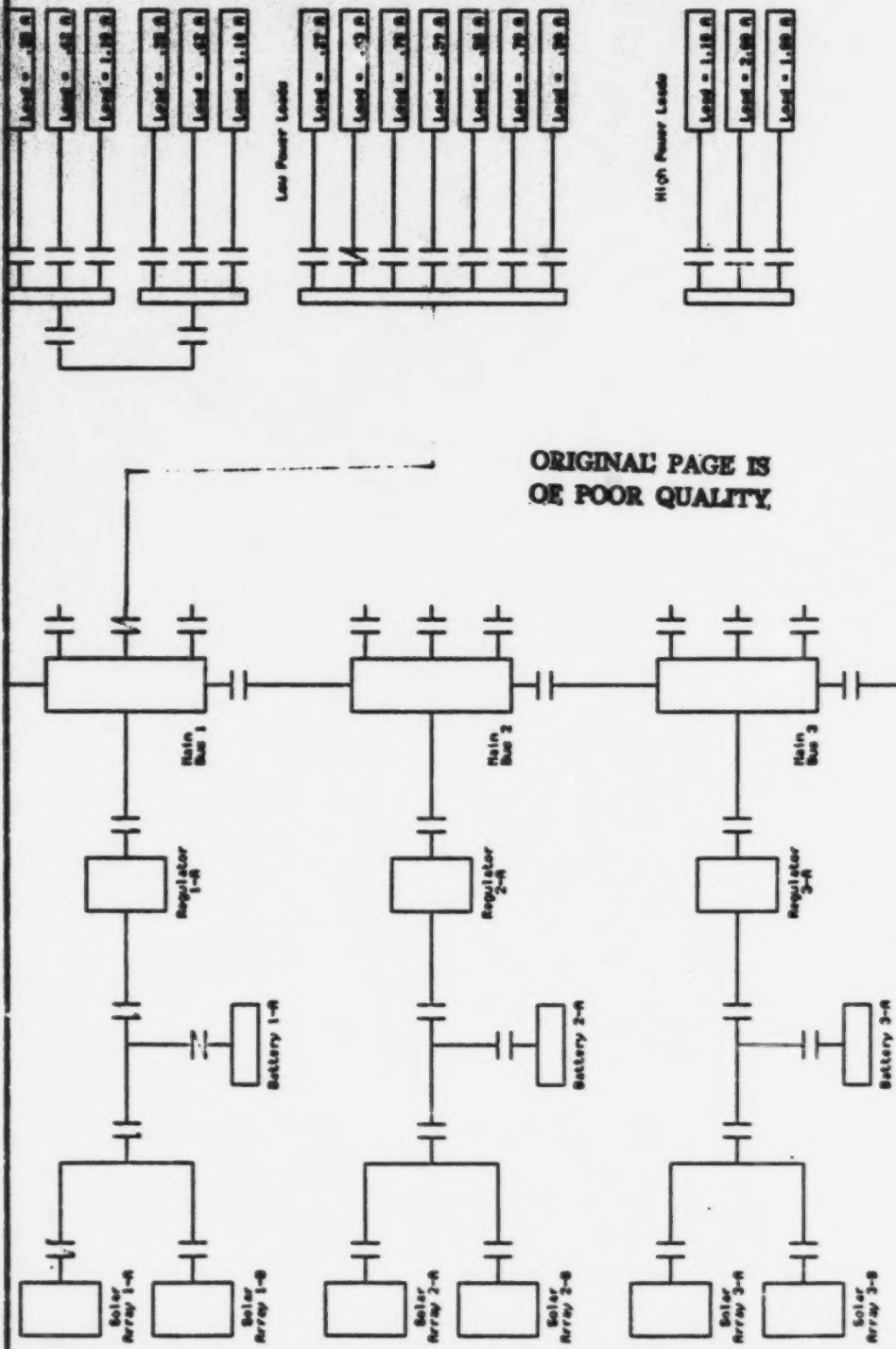Please enter the path and filename. Default is d:\files\files-library\




ORIGINAL PAGE IS
OF POOR QUALITY.

Library select....
 ** Flash Interface Status **

Test Configuration Window 3

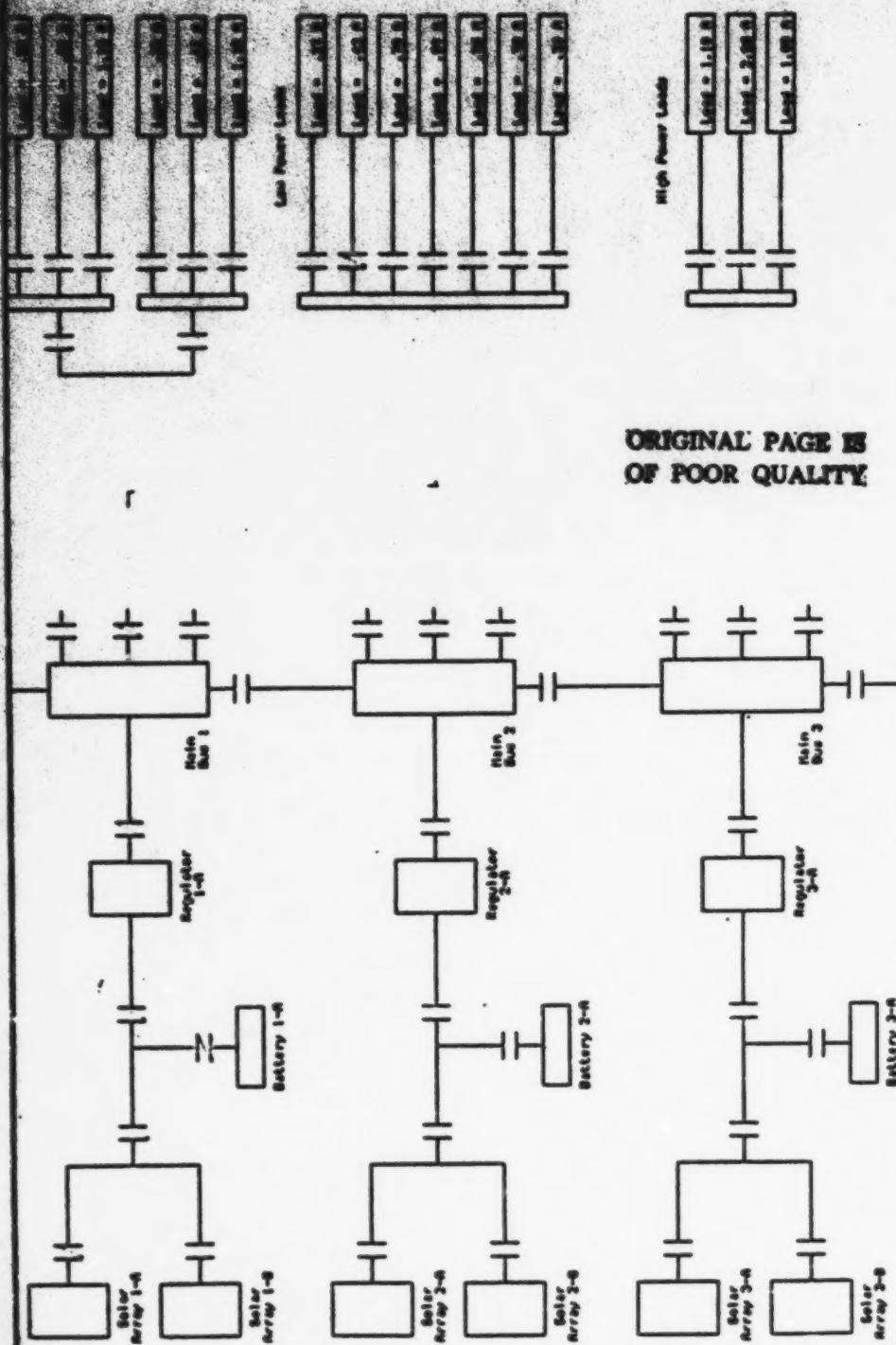Please enter the path and filename. Default is d:\test\tes-lib\ery




ORIGINAL PAGE IS
OF POOR QUALITY

Library select.....
as File Interface Status is

Test Configuration Window 3

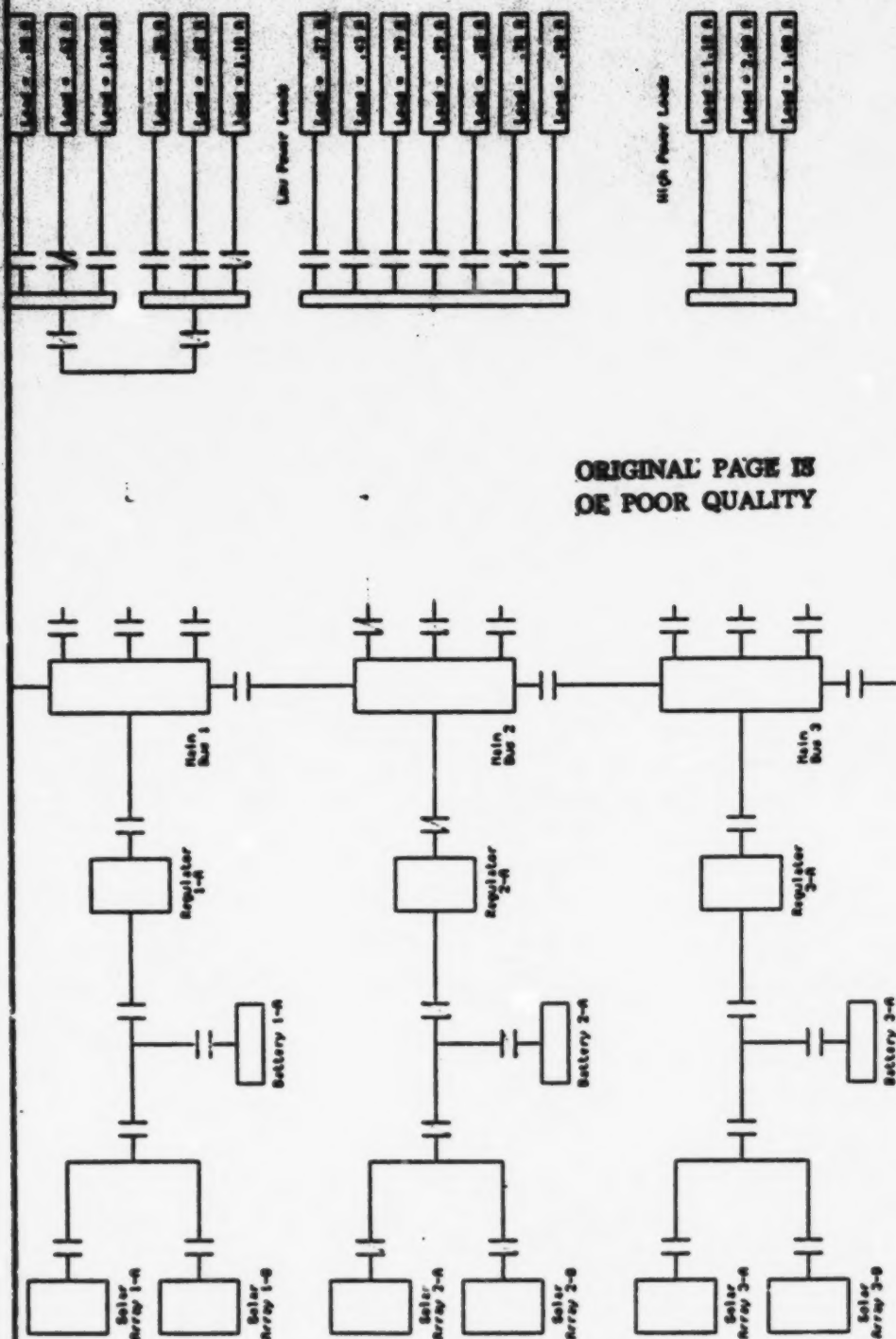
Please enter the path and filename. Default is d:\files\files-library



ORIGINAL PAGE IS
OF POOR QUALITY

Library select.....
in File Interface Status at

Test Configuration Window 3

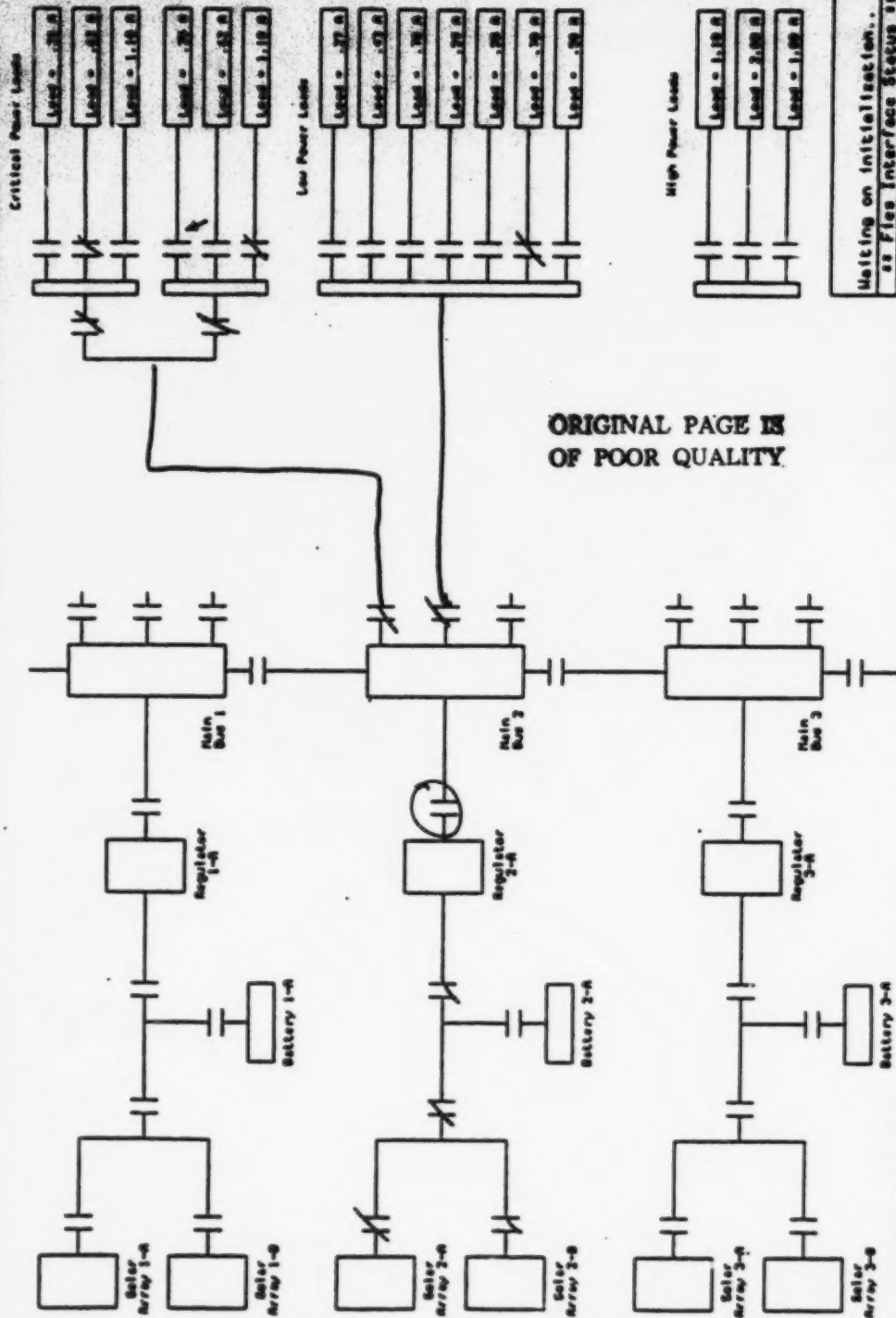

Test Configuration Window 17

16-15-05 13:39:46 100%

10-15-05 13:39:46 100%

• E:\HWID\1\done\art.out 75348

short D.

Cx: F-5

Cellular Power Supply

1000	1000	1000	1000	1000	1000
1000	1000	1000	1000	1000	1000
1000	1000	1000	1000	1000	1000
1000	1000	1000	1000	1000	1000
1000	1000	1000	1000	1000	1000
1000	1000	1000	1000	1000	1000

Cellular Power Supply


1000	1000	1000	1000	1000	1000
1000	1000	1000	1000	1000	1000
1000	1000	1000	1000	1000	1000
1000	1000	1000	1000	1000	1000
1000	1000	1000	1000	1000	1000
1000	1000	1000	1000	1000	1000

Cellular Power Supply

1000	1000	1000	1000	1000	1000
1000	1000	1000	1000	1000	1000
1000	1000	1000	1000	1000	1000
1000	1000	1000	1000	1000	1000
1000	1000	1000	1000	1000	1000
1000	1000	1000	1000	1000	1000

Cellular Power Supply


ORIGINAL PAGE IS
OF POOR QUALITY

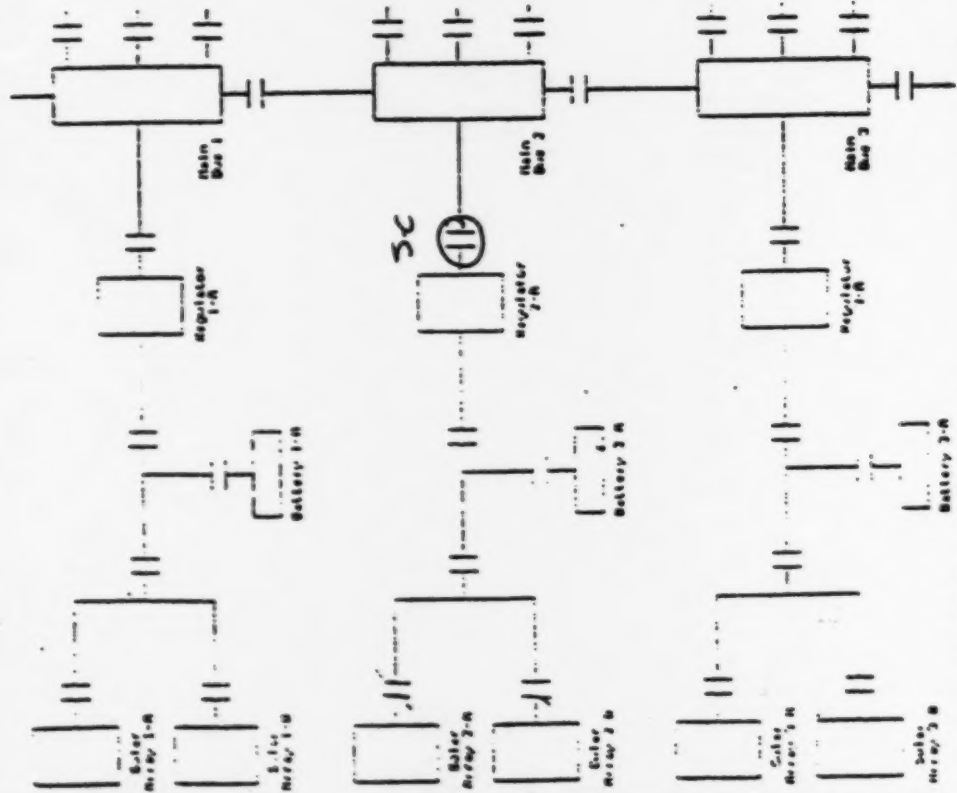

First Used Type at this Mission 17


SHORTED. DAT

Ex F-5

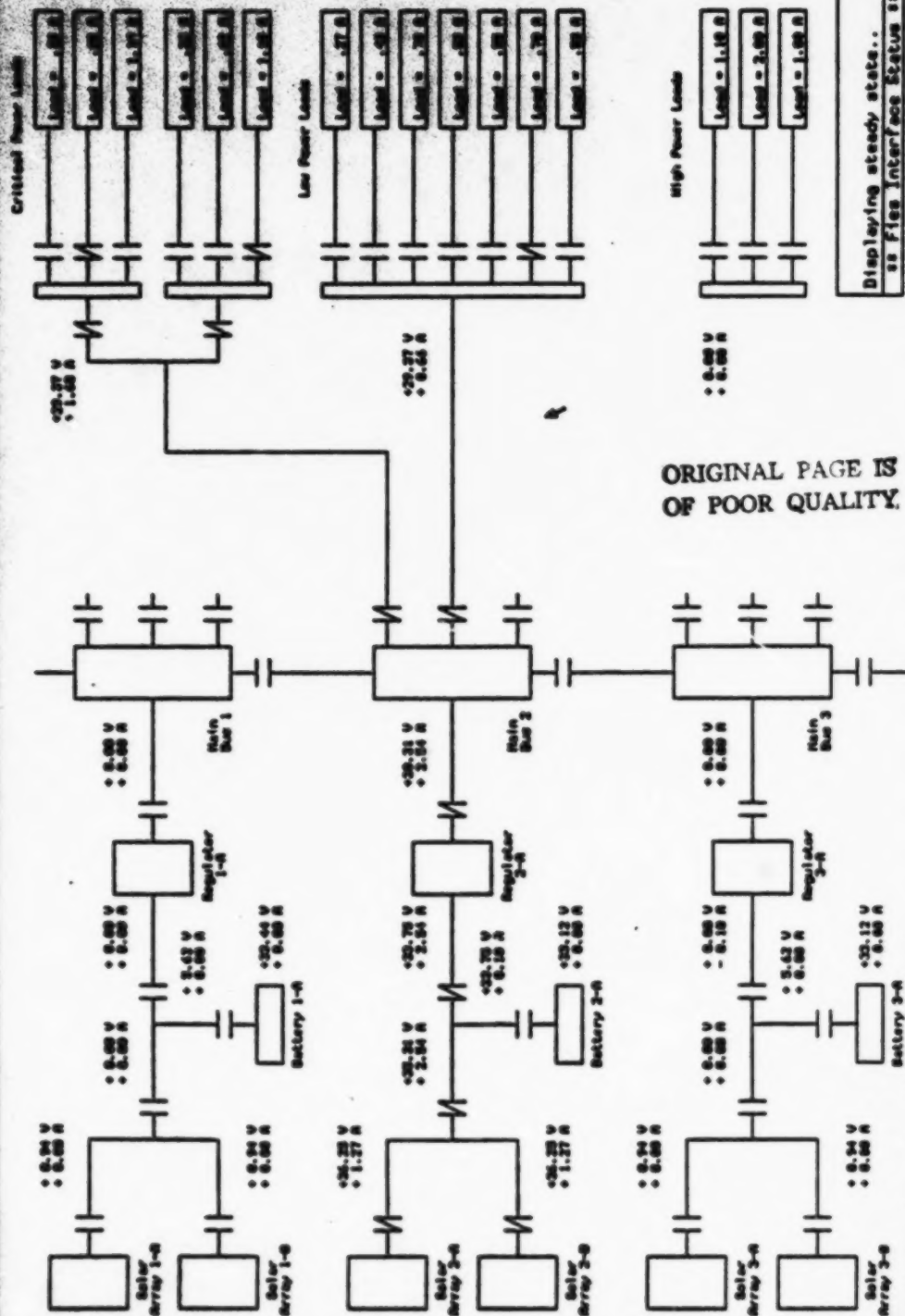

File Steady State Data Display Window 3

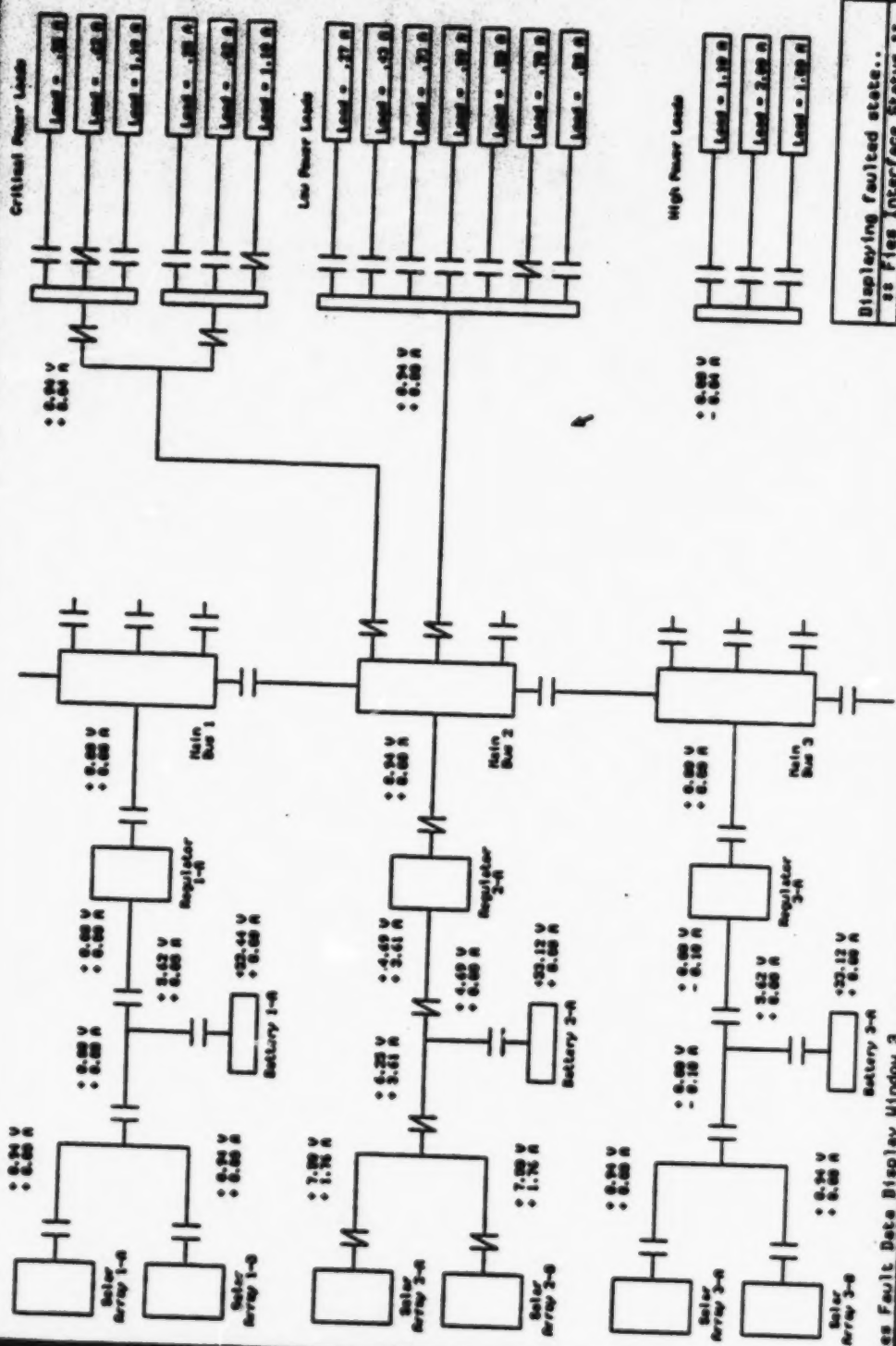02728786 12125129 FIES-WRT-INTERACTIVE AU: 1



Displaying faulted state..
as File Interface Status as

File Fault Data Display Window 3

12/26/86 12:25:54 FIES-INT-INTERACTIVE NJ:

=> pop

=> run

Beginning run at 2/28/86 12:27:05: type ^C to halt.
Initializing Circuit Description

Create Errorbands

Assigning Qualitative Values to Sensors

Hypothesizing Faults:

Fault-Hypothesis: Short-Circuit REGULATOR-2A

Fault-hyp: Short-Circuit REGULATOR-2A
Source Propagation from REGULATOR-2A to SENSOR-2E

Fault-hyp: SHORT-CIRCUIT REGULATOR-2A
Predicted Current Effect: HIGH Consistent at Sensor SENSOR-2E
Source Propagation from SENSOR-2E to RELAY-2E

Fault-hyp: SHORT-CIRCUIT REGULATOR-2A
Source Propagation from RELAY-2E to BUS-2B

Fault-hyp: SHORT-CIRCUIT REGULATOR-2A
Source Propagation from BUS-2B to SENSOR-2C

Fault-hyp: SHORT-CIRCUIT REGULATOR-2A
Predicted Current Effect: HIGH Consistent at Sensor SENSOR-2C
Source Propagation from SENSOR-2C to RELAY-2C

Fault-hyp: SHORT-CIRCUIT REGULATOR-2A
Source Propagation from RELAY-2C to BUS-2A

Fault-hyp: SHORT-CIRCUIT REGULATOR-2A
Source Propagation from BUS-2A to SENSOR-2B

Fault-hyp: SHORT-CIRCUIT REGULATOR-2A
Predicted Current Effect: HIGH Consistent at Sensor SENSOR-2B
Source Propagation from SENSOR-2B to RELAY-2B

Fault-hyp: SHORT-CIRCUIT REGULATOR-2A
Source Propagation from RELAY-2B to SOLAR-ARRAY-2B

Fault-hyp: SHORT-CIRCUIT REGULATOR-2A
End-Source Propagation from SOLAR-ARRAY-2B

Fault-hyp: SHORT-CIRCUIT REGULATOR-2A
Source Propagation from BUS-2A to SENSOR-2A

Fault-hyp: SHORT-CIRCUIT REGULATOR-2A
Predicted Current Effect: HIGH Consistent at Sensor SENSOR-2A
Source Propagation from SENSOR-2A to RELAY-2A

Fault-hyp: SHORT-CIRCUIT REGULATOR-2A
Source Propagation from RELAY-2A to SOLAR-ARRAY-2A

Fault-hyp: SHORT-CIRCUIT REGULATOR-2A
End-Source Propagation from SOLAR-ARRAY-2A

Fault-hyp: Short-Circuit REGULATOR-2A
Sink Propagation from REGULATOR-2A to RELAY-2F

Fault-hyp: SHORT-CIRCUIT REGULATOR-2A
Sink Propagation from RELAY-2F to SENSOR-2F

Fault-hyp: SHORT-CIRCUIT REGULATOR-2A
Predicted Current Effect: ZERO Consistent at Sensor SENSOR-2F
Source Propagation from SENSOR-2F to BUS-2C

yp: SHORT-CIRCUIT REGULATOR-2A

6-5
5

Sink Propagation from BUS-2C to RELAY-2G

Fault-hyp: SHORT-CIRCUIT REGULATOR-2A

Sink Propagation from RELAY-2G to SENSOR-1G

Fault-hyp: SHORT-CIRCUIT REGULATOR-2A

Predicted Current Effect: ZERO Consistent at Sensor SENSOR-1G

Sink Propagation from SENSOR-1G to BUS-1D

Fault-hyp: SHORT-CIRCUIT REGULATOR-2A

Sink Propagation from BUS-1D to RELAY-1K

Fault-hyp: SHORT-CIRCUIT REGULATOR-2A

Sink Propagation from RELAY-1K to BUS-1E

Fault-hyp: SHORT-CIRCUIT REGULATOR-2A

Sink Propagation from BUS-1E to RELAY-1O

Fault-hyp: SHORT-CIRCUIT REGULATOR-2A

Sink Propagation from RELAY-1O to LOAD-1O

Fault-hyp: SHORT-CIRCUIT REGULATOR-2A

End-Sink Propagation from LOAD-1O

Fault-hyp: SHORT-CIRCUIT REGULATOR-2A

Sink Propagation from BUS-1D to RELAY-1M

Fault-hyp: SHORT-CIRCUIT REGULATOR-2A

Sink Propagation from RELAY-1M to BUS-1F

Fault-hyp: SHORT-CIRCUIT REGULATOR-2A

Sink Propagation from BUS-1F to RELAY-1S

Fault-hyp: SHORT-CIRCUIT REGULATOR-2A

Sink Propagation from RELAY-1S to LOAD-1S

Fault-hyp: SHORT-CIRCUIT REGULATOR-2A

End-Sink Propagation from LOAD-1S

Fault-hyp: SHORT-CIRCUIT REGULATOR-2A

Sink Propagation from BUS-2C to RELAY-2H

Fault-hyp: SHORT-CIRCUIT REGULATOR-2A

Sink Propagation from RELAY-2H to SENSOR-2G

Fault-hyp: SHORT-CIRCUIT REGULATOR-2A

Predicted Current Effect: ZERO Consistent at Sensor SENSOR-2G

Sink Propagation from SENSOR-2G to BUS-2D

Fault-hyp: SHORT-CIRCUIT REGULATOR-2A

Sink Propagation from BUS-2D to RELAY-2Q

Fault-hyp: SHORT-CIRCUIT REGULATOR-2A

Sink Propagation from RELAY-2Q to LOAD-2Q

Fault-hyp: SHORT-CIRCUIT REGULATOR-2A

End-Sink Propagation from LOAD-2Q

Reporting All Initial Fault Hypotheses:

SHORT-CIRCUIT REGULATOR-2A

Reporting Final Fault Hypotheses:

SHORT-CIRCUIT REGULATOR-2A

Readings at SENSOR-3Z

Voltage: 33.124916

ed Voltage: 33.124916

Voltage: NORMAL

6: F-5

6

Normal Current: 0.0
 Faulted Current: 0.0
 Qual Current: NORMAL

Readings at SENSOR-2Z
 Normal Voltage: 33.124816
 Faulted Voltage: 33.124816
 Qual Voltage: NORMAL

Normal Current: 0.0
 Faulted Current: 0.0
 Qual Current: NORMAL

Readings at SENSOR-1Z
 Normal Voltage: 33.437412
 Faulted Voltage: 33.437412
 Qual Voltage: NORMAL

Normal Current: 0.0
 Faulted Current: 0.0
 Qual Current: NORMAL

Readings at SENSOR-3G
 Normal Voltage: 0.0
 Faulted Voltage: 0.0
 Qual Voltage: NORMAL

Normal Current: 0.0
 Faulted Current: -0.0390624
 Qual Current: NORMAL

Readings at SENSOR-2G
 Normal Voltage: 29.374924
 Faulted Voltage: 0.9374976
 Qual Voltage: ZERO

Normal Current: 0.6640806
 Faulted Current: 0.0
 Qual Current: ZERO

Readings at SENSOR-1G
 Normal Voltage: 29.374924
 Faulted Voltage: 0.9374976
 Qual Voltage: ZERO

Normal Current: 1.6798832
 Faulted Current: 0.0390624
 Qual Current: ZERO

Readings at SENSOR-3F
 Normal Voltage: 0.0
 Faulted Voltage: 0.0
 Qual Voltage: NORMAL

Normal Current: 0.0
 Faulted Current: 0.0
 Qual Current: NORMAL

F-5
 7

Readings at SENSOR-3E

Normal Voltage: 0.0
 Faulted Voltage: 0.0
 Qual Voltage: NORMAL

Normal Current: -0.097856
 Faulted Current: -0.097856
 Qual Current: NORMAL

Readings at SENSOR-3C

Normal Voltage: 0.0
 Faulted Voltage: 0.0
 Qual Voltage: NORMAL

Normal Current: 0.0
 Faulted Current: -0.097856
 Qual Current: NORMAL

Readings at SENSOR-3D

Normal Voltage: 5.6249857
 Faulted Voltage: 5.6249857
 Qual Voltage: NORMAL

Normal Current: 0.0
 Faulted Current: 0.0
 Qual Current: NORMAL

Readings at SENSOR-3B

Normal Voltage: 0.9374976
 Faulted Voltage: 0.9374976
 Qual Voltage: NORMAL

Normal Current: 0.0
 Faulted Current: 0.0
 Qual Current: NORMAL

Readings at SENSOR-3A

Normal Voltage: 0.9374976
 Faulted Voltage: 0.9374976
 Qual Voltage: NORMAL

Normal Current: 0.0
 Faulted Current: 0.0
 Qual Current: NORMAL

Readings at SENSOR-2F

Normal Voltage: 30.312422
 Faulted Voltage: 0.9374976
 Qual Voltage: ZERO

Normal Current: 2.5390558
 Faulted Current: 0.0
 Qual Current: ZERO

En. F-5
 8

Readings at SENSOR-2E

Normal Voltage: 33.748812
Faulted Voltage: 4.887488
Qual Voltage: LOW

Normal Current: 2.5380558
Faulted Current: 3.813272
Qual Current: HIGH

Readings at SENSOR-2C

Normal Voltage: 35.31241
Faulted Voltage: 6.248884
Qual Voltage: LOW

Normal Current: 2.5380558
Faulted Current: 3.813272
Qual Current: HIGH

Readings at SENSOR-2D

Normal Voltage: 33.748812
Faulted Voltage: 4.887488
Qual Voltage: LOW

Normal Current: 0.097656
Faulted Current: 0.0
Qual Current: ZERO

Readings at SENSOR-2B

Normal Voltage: 38.24891
Faulted Voltage: 7.488881
Qual Voltage: LOW

Normal Current: 1.2885279
Faulted Current: 1.757808
Qual Current: HIGH

Readings at SENSOR-2A

Normal Voltage: 38.24891
Faulted Voltage: 7.488881
Qual Voltage: LOW

Normal Current: 1.2885279
Faulted Current: 1.757808
Qual Current: HIGH

Readings at SENSOR-1F

Normal Voltage: 0.0
Faulted Voltage: 0.0
Qual Voltage: NORMAL

Normal Current: 0.0
Faulted Current: 0.0
Qual Current: NORMAL

Readings at SENSOR-1E

Normal Voltage: 0.0
Faulted Voltage: 0.0
Qual Voltage: NORMAL

Normal Current: 0.0
 Faulted Current: 0.0
 Qual Current: NORMAL

Readings at SENSOR-1C

Normal Voltage: 0.0
 Faulted Voltage: 0.0
 Qual Voltage: NORMAL

Normal Current: 0.0
 Faulted Current: 0.0
 Qual Current: NORMAL

Readings at SENSOR-1D

Normal Voltage: 5.6248857
 Faulted Voltage: 5.6248857
 Qual Voltage: NORMAL

Normal Current: 0.0
 Faulted Current: 0.0
 Qual Current: NORMAL

Readings at SENSOR-1B

Normal Voltage: 0.9374976
 Faulted Voltage: 0.9374976
 Qual Voltage: NORMAL

Normal Current: 0.0
 Faulted Current: 0.0
 Qual Current: NORMAL

Readings at SENSOR-1A

Normal Voltage: 0.9374976
 Faulted Voltage: 0.9374976
 Qual Voltage: NORMAL

Normal Current: 0.0
 Faulted Current: 0.0
 Qual Current: NORMAL

Program halted.

Ending run at 2/28/86 12:28:07.

=> watch
 => dribble

En: FS

Example F-6

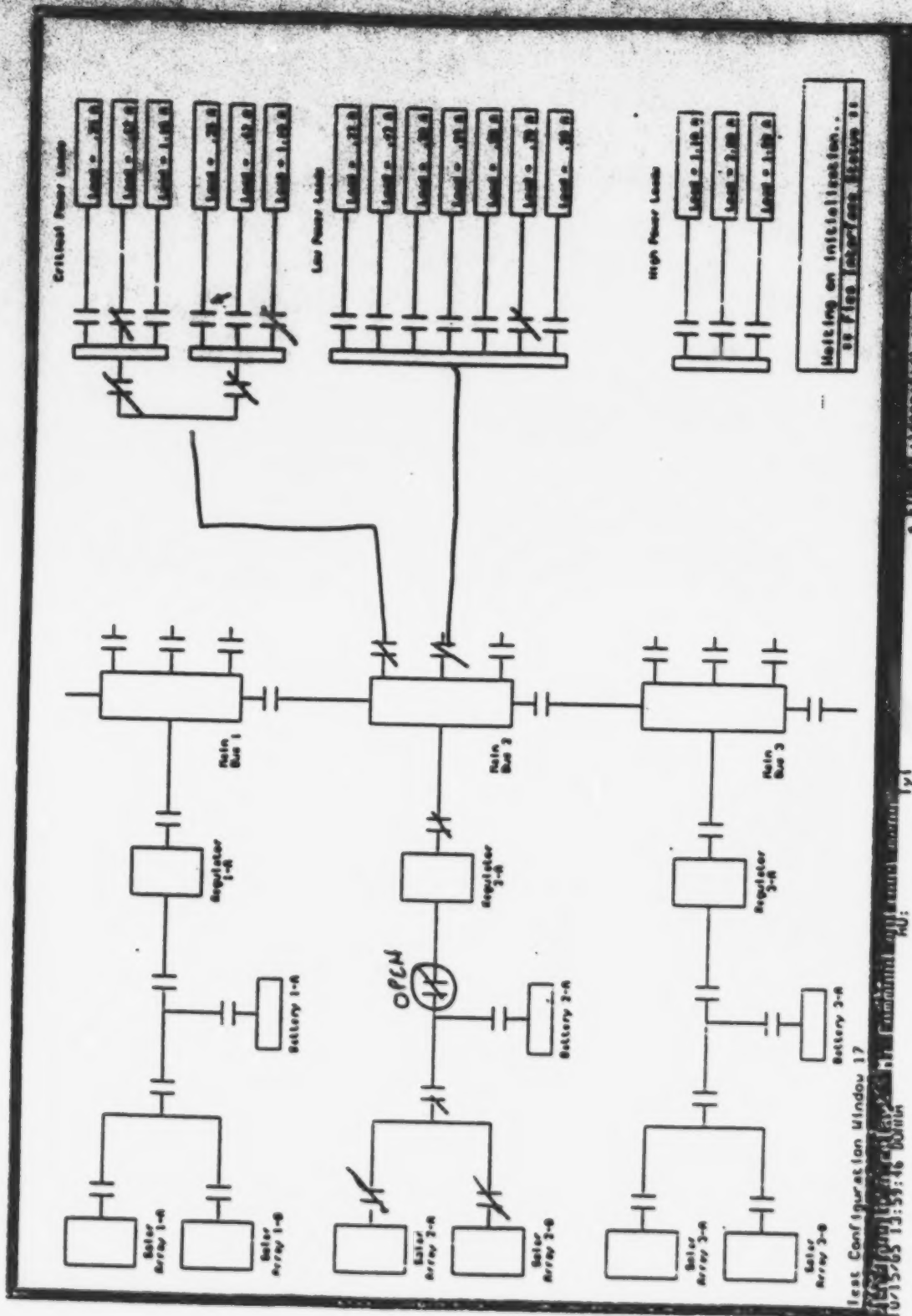


Fig. F-6

ORIGINAL PAGE IS
OF POOR QUALITY

1000-1 1210 7A Dec 56 11:20 PD Mod Aded



100 AUTOMOBILES 1941-1945

14

100% (100%)

open 1

Displaying steady state..

11/11/11

En: P-6
2

Fault-hyp: OPEN-CIRCUIT RELAY-2E
Predicted Current Effect: ZERO Consistent at Sensor SENSOR-2B
Source Propagation from SENSOR-2B to RELAY-2B

Fault-hyp: OPEN-CIRCUIT RELAY-2E
Source Propagation from RELAY-2B to SOLAR-ARRAY-2B

Fault-hyp: OPEN-CIRCUIT RELAY-2E
End-Source Propagation from SOLAR-ARRAY-2B

Fault-hyp: OPEN-CIRCUIT RELAY-2E
Source Propagation from BUS-2A to SENSOR-2A

Fault-hyp: OPEN-CIRCUIT RELAY-2E
Predicted Current Effect: ZERO Consistent at Sensor SENSOR-2A
Source Propagation from SENSOR-2A to RELAY-2A

Fault-hyp: OPEN-CIRCUIT RELAY-2E
Source Propagation from RELAY-2A to SOLAR-ARRAY-2A

Fault-hyp: OPEN-CIRCUIT RELAY-2E
End-Source Propagation from SOLAR-ARRAY-2A

Fault-hyp: Open-Circuit RELAY-2E
Sink Propagation from RELAY-2E to SENSOR-2E

Fault-hyp: OPEN-CIRCUIT RELAY-2E
Predicted Current Effect: ZERO Consistent at Sensor SENSOR-2E
Sink Propagation from SENSOR-2E to REGULATOR-2A

Fault-hyp: OPEN-CIRCUIT RELAY-2E
Sink Propagation from REGULATOR-2A to RELAY-2F

Fault-hyp: OPEN-CIRCUIT RELAY-2E
Sink Propagation from RELAY-2F to SENSOR-2F

Fault-hyp: OPEN-CIRCUIT RELAY-2E
Predicted Current Effect: ZERO Consistent at Sensor SENSOR-2F
Sink Propagation from SENSOR-2F to BUS-2C

Fault-hyp: OPEN-CIRCUIT RELAY-2E
Sink Propagation from BUS-2C to RELAY-2G

Fault-hyp: OPEN-CIRCUIT RELAY-2E
Sink Propagation from RELAY-2G to SENSOR-1G

Fault-hyp: OPEN-CIRCUIT RELAY-2E
Predicted Current Effect: ZERO Consistent at Sensor SENSOR-1G
Sink Propagation from SENSOR-1G to BUS-1D

Fault-hyp: OPEN-CIRCUIT RELAY-2E
Sink Propagation from BUS-1D to RELAY-1K

Fault-hyp: OPEN-CIRCUIT RELAY-2E
Sink Propagation from RELAY-1K to BUS-1E

Fault-hyp: OPEN-CIRCUIT RELAY-2E
Sink Propagation from BUS-1E to RELAY-10

Fault-hyp: OPEN-CIRCUIT RELAY-2E
Sink Propagation from RELAY-10 to LOAD-10

Fault-hyp: OPEN-CIRCUIT RELAY-2E
End-Sink Propagation from LOAD-10

Fault-hyp: OPEN-CIRCUIT RELAY-2E
Sink Propagation from BUS-1D to RELAY-1H

Fault-hyp: OPEN-CIRCUIT RELAY-2E
Sink Propagation from RELAY-1H to BUS-1F

Fault-hyp: OPEN-CIRCUIT RELAY-2E
Sink Propagation from BUS-1F to RELAY-1S

5: F-6
3

Fault-hyp: OPEN-CIRCUIT RELAY-2E
Sink Propagation from RELAY-1B to LOAD-1B

Fault-hyp: OPEN-CIRCUIT RELAY-2E
End-Sink Propagation from LOAD-1B

Fault-hyp: OPEN-CIRCUIT RELAY-2E
Sink Propagation from BUS-2C to RELAY-2H

Fault-hyp: OPEN-CIRCUIT RELAY-2E
Sink Propagation from RELAY-2H to SENSOR-2B

Fault-hyp: OPEN-CIRCUIT RELAY-2E
Predicted Current Effect: ZERO Consistent at Sensor SENSOR-2B
Sink Propagation from SENSOR-2B to BUS-2D

Fault-hyp: OPEN-CIRCUIT RELAY-2E
Sink Propagation from BUS-2D to RELAY-2Q

Fault-hyp: OPEN-CIRCUIT RELAY-2E
Sink Propagation from RELAY-2Q to LOAD-2Q

Fault-hyp: OPEN-CIRCUIT RELAY-2E
End-Sink Propagation from LOAD-2Q

Fault-hyp: Open-Circuit BUS-2B
Source Propagation from BUS-2B to SENSOR-2C

Fault-hyp: OPEN-CIRCUIT BUS-2B
Predicted Current Effect: ZERO Consistent at Sensor SENSOR-2C
Source Propagation from SENSOR-2C to RELAY-2C

Fault-hyp: OPEN-CIRCUIT BUS-2B
Source Propagation from RELAY-2C to BUS-2A

Fault-hyp: OPEN-CIRCUIT BUS-2B
Source Propagation from BUS-2A to SENSOR-2B

Fault-hyp: OPEN-CIRCUIT BUS-2B
Predicted Current Effect: ZERO Consistent at Sensor SENSOR-2B
Source Propagation from SENSOR-2B to RELAY-2B

Fault-hyp: OPEN-CIRCUIT BUS-2B
Source Propagation from RELAY-2B to SOLAR-ARRAY-2B

Fault-hyp: OPEN-CIRCUIT BUS-2B
End-Source Propagation from SOLAR-ARRAY-2B

Fault-hyp: OPEN-CIRCUIT BUS-2B
Source Propagation from BUS-2A to SENSOR-2A

Fault-hyp: OPEN-CIRCUIT BUS-2B
Predicted Current Effect: ZERO Consistent at Sensor SENSOR-2A
Source Propagation from SENSOR-2A to RELAY-2A

Fault-hyp: OPEN-CIRCUIT BUS-2B
Source Propagation from RELAY-2A to SOLAR-ARRAY-2A

Fault-hyp: OPEN-CIRCUIT BUS-2B
End-Source Propagation from SOLAR-ARRAY-2A

Fault-hyp: Open-Circuit BUS-2B
Sink Propagation from BUS-2B to RELAY-2E

Fault-hyp: OPEN-CIRCUIT BUS-2B
Sink Propagation from RELAY-2E to SENSOR-2E

Fault-hyp: OPEN-CIRCUIT BUS-2B
Predicted Current Effect: ZERO Consistent at Sensor SENSOR-2E
Sink Propagation from SENSOR-2E to REGULATOR-2A

hyp: OPEN-CIRCUIT BUS-2B
Propagation from REGULATOR-2A to RELAY-2F

F-6

4

Fault-hyp: OPEN-CIRCUIT BUS-2B
Sink Propagation from RELAY-2F to SENSOR-2F

Fault-hyp: OPEN-CIRCUIT BUS-2B
Predicted Current Effect: ZERO Consistent at Sensor SENSOR-2F
Sink Propagation from SENSOR-2F to BUS-2C

Fault-hyp: OPEN-CIRCUIT BUS-2B
Sink Propagation from BUS-2C to RELAY-2E

Fault-hyp: OPEN-CIRCUIT BUS-2B
Sink Propagation from RELAY-2E to SENSOR-1G

Fault-hyp: OPEN-CIRCUIT BUS-2B
Predicted Current Effect: ZERO Consistent at Sensor SENSOR-1G
Sink Propagation from SENSOR-1G to BUS-1D

Fault-hyp: OPEN-CIRCUIT BUS-2B
Sink Propagation from BUS-1D to RELAY-1K

Fault-hyp: OPEN-CIRCUIT BUS-2B
Sink Propagation from RELAY-1K to BUS-1E

Fault-hyp: OPEN-CIRCUIT BUS-2B
Sink Propagation from BUS-1E to RELAY-1O

Fault-hyp: OPEN-CIRCUIT BUS-2B
Sink Propagation from RELAY-1O to LOAD-1O

Fault-hyp: OPEN-CIRCUIT BUS-2B
End-Sink Propagation from LOAD-1O

Fault-hyp: OPEN-CIRCUIT BUS-2B
Sink Propagation from BUS-1D to RELAY-1H

Fault-hyp: OPEN-CIRCUIT BUS-2B
Sink Propagation from RELAY-1H to BUS-1F

Fault-hyp: OPEN-CIRCUIT BUS-2B
Sink Propagation from BUS-1F to RELAY-1S

Fault-hyp: OPEN-CIRCUIT BUS-2B
Sink Propagation from RELAY-1S to LOAD-1S

Fault-hyp: OPEN-CIRCUIT BUS-2B
End-Sink Propagation from LOAD-1S

Fault-hyp: OPEN-CIRCUIT BUS-2B
Sink Propagation from BUS-2C to RELAY-2H

Fault-hyp: OPEN-CIRCUIT BUS-2B
Sink Propagation from RELAY-2H to SENSOR-2G

Fault-hyp: OPEN-CIRCUIT BUS-2B
Predicted Current Effect: ZERO Consistent at Sensor SENSOR-2G
Sink Propagation from SENSOR-2G to BUS-2D

Fault-hyp: OPEN-CIRCUIT BUS-2B
Sink Propagation from BUS-2D to RELAY-2Q

Fault-hyp: OPEN-CIRCUIT BUS-2B
Sink Propagation from RELAY-2Q to LOAD-2Q

Fault-hyp: OPEN-CIRCUIT BUS-2B
End-Sink Propagation from LOAD-2Q

Fault-hyp: Resistive-Short-Circuit SOLAR-ARRAY-2A
Sink Propagation from SOLAR-ARRAY-2A to RELAY-2A

Fault-hyp: RESISTIVE-SHORT-CIRCUIT SOLAR-ARRAY-2A
Propagation from RELAY-2A to SENSOR-2A

C.: F-6

5

Fault-hyp: RESISTIVE-SHORT-CIRCUIT SOLAR-ARRAY-2A
Predicted Current Effect: ZERO Consistent at Sensor SENSOR-2A
Sink Propagation from SENSOR-2A to BUS-2A

Fault-hyp: RESISTIVE-SHORT-CIRCUIT SOLAR-ARRAY-2A
Sink Propagation from BUS-2A to RELAY-2C
Source Propagation from BUS-2A to SENSOR-2B

Reject Fault Hypothesis RESISTIVE-SHORT-CIRCUIT at SOLAR-ARRAY-2A
Reason: Predicted Effect Is Inconsistent at Sensor SENSOR-2B
Predicted Value: HIGH
Sensor Value: LOW

Fault-hyp: Resistive-Short-Circuit SOLAR-ARRAY-2B
Sink Propagation from SOLAR-ARRAY-2B to RELAY-2B

Fault-hyp: RESISTIVE-SHORT-CIRCUIT SOLAR-ARRAY-2B
Sink Propagation from RELAY-2B to SENSOR-2B

Fault-hyp: RESISTIVE-SHORT-CIRCUIT SOLAR-ARRAY-2B
Predicted Current Effect: ZERO Consistent at Sensor SENSOR-2B
Sink Propagation from SENSOR-2B to BUS-2A

Fault-hyp: RESISTIVE-SHORT-CIRCUIT SOLAR-ARRAY-2B
Sink Propagation from BUS-2A to RELAY-2C
Source Propagation from BUS-2A to SENSOR-2A

Reject Fault Hypothesis RESISTIVE-SHORT-CIRCUIT at SOLAR-ARRAY-2B
Reason: Predicted Effect Is Inconsistent at Sensor SENSOR-2A
Predicted Value: HIGH
Sensor Value: LOW

Reporting All Initial Fault Hypotheses:

RESISTIVE-SHORT-CIRCUIT SOLAR-ARRAY-2A

RESISTIVE-SHORT-CIRCUIT SOLAR-ARRAY-2B

OPEN-CIRCUIT RELAY-2E

OPEN-CIRCUIT BUS-2B

Reporting Final Fault Hypotheses:

OPEN-CIRCUIT RELAY-2E

OPEN-CIRCUIT BUS-2B

Readings at SENSOR-3Z

Normal Voltage: 33.124916

Faulted Voltage: 0.0

Qual Voltage: NORMAL

Normal Current: 0.0

Faulted Current: 0.0

Qual Current: NORMAL

Readings at SENSOR-2Z

Normal Voltage: 33.124916

Faulted Voltage: 0.0

Qual Voltage: NORMAL

Normal Current: 0.0

Faulted Current: 0.0

Qual Current: NORMAL

6: F-6

Readings at SENSOR-1Z
 Normal Voltage: 33.437412
 Faulted Voltage: 0.0
 Qual Voltage: NORMAL

Normal Current: 0.0
 Faulted Current: 0.0
 Qual Current: NORMAL

Readings at SENSOR-3G
 Normal Voltage: 0.0
 Faulted Voltage: -0.0390624
 Qual Voltage: NORMAL

Normal Current: 0.0
 Faulted Current: -0.0390624
 Qual Current: NORMAL

Readings at SENSOR-2G
 Normal Voltage: 29.687424
 Faulted Voltage: 0.0
 Qual Voltage: ZERO

Normal Current: 0.6640608
 Faulted Current: 0.0
 Qual Current: ZERO

Readings at SENSOR-1G
 Normal Voltage: 29.687424
 Faulted Voltage: 0.0
 Qual Voltage: ZERO

Normal Current: 1.1328096
 Faulted Current: 0.0
 Qual Current: ZERO

Readings at SENSOR-3F
 Normal Voltage: 0.0
 Faulted Voltage: 0.0
 Qual Voltage: NORMAL

Normal Current: 0.0
 Faulted Current: 0.0
 Qual Current: NORMAL

Readings at SENSOR-3E
 Normal Voltage: 0.0
 Faulted Voltage: -0.097656
 Qual Voltage: NORMAL

Normal Current: -0.097656
 Faulted Current: -0.097656
 Qual Current: NORMAL

Readings at SENSOR-3C
 Normal Voltage: 0.0

En: F26
 7

Faulted Voltage: 0.0
Qual Voltage: NORMAL

Normal Current: 0.0
Faulted Current: 0.0
Qual Current: NORMAL

Readings at SENSOR-3D

Normal Voltage: 5.6248857
Faulted Voltage: 0.0
Qual Voltage: NORMAL

Normal Current: 0.0
Faulted Current: 0.0
Qual Current: NORMAL

Readings at SENSOR-3B

Normal Voltage: 0.9374976
Faulted Voltage: 0.0
Qual Voltage: NORMAL

Normal Current: 0.0
Faulted Current: 0.0
Qual Current: NORMAL

Readings at SENSOR-3A

Normal Voltage: 0.9374976
Faulted Voltage: 0.0
Qual Voltage: NORMAL

Normal Current: 0.0
Faulted Current: 0.0
Qual Current: NORMAL

Readings at SENSOR-2F

Normal Voltage: 30.312422
Faulted Voltage: 0.0
Qual Voltage: ZERO

Normal Current: 2.050776
Faulted Current: 0.0
Qual Current: ZERO

Readings at SENSOR-2E

Normal Voltage: 34.062412
Faulted Voltage: 0.0
Qual Voltage: ZERO

Normal Current: 2.050776
Faulted Current: 0.0
Qual Current: ZERO

Readings at SENSOR-2C

Normal Voltage: 35.31241
Faulted Voltage: 0.585936
Qual Voltage: NORMAL

Normal Current: 2.148432

Volts 6.6
8

Faulted Current: 0.585836
Qual Current: LOW

Readings at SENSOR-2D

Normal Voltage: 34.062412
Faulted Voltage: -0.585836
Qual Voltage: NORMAL

Normal Current: 0.0
Faulted Current: -0.585836
Qual Current: NORMAL

Readings at SENSOR-2B

Normal Voltage: 36.562405
Faulted Voltage: 0.292968
Qual Voltage: NORMAL

Normal Current: 1.074216
Faulted Current: 0.292968
Qual Current: LOW

Readings at SENSOR-2A

Normal Voltage: 36.24991
Faulted Voltage: 0.390624
Qual Voltage: NORMAL

Normal Current: 1.074216
Faulted Current: 0.390624
Qual Current: LOW

Readings at SENSOR-1F

Normal Voltage: 0.0
Faulted Voltage: 0.0
Qual Voltage: NORMAL

Normal Current: 0.0
Faulted Current: 0.0
Qual Current: NORMAL

Readings at SENSOR-1E

Normal Voltage: 0.0
Faulted Voltage: 0.0
Qual Voltage: NORMAL

Normal Current: 0.0
Faulted Current: 0.0
Qual Current: NORMAL

Readings at SENSOR-1C

Normal Voltage: 0.0
Faulted Voltage: 0.0
Qual Voltage: NORMAL

Normal Current: 0.0
Faulted Current: 0.0
Qual Current: NORMAL

Readings at SENSOR-1D

Normal Voltage: 5.6249857
 Faulted Voltage: 0.0
 Qual Voltage: NORMAL

Normal Current: 0.0
 Faulted Current: 0.0
 Qual Current: NORMAL

Readings at SENSOR-1B

Normal Voltage: 0.9374976
 Faulted Voltage: 0.0
 Qual Voltage: NORMAL

Normal Current: 0.0
 Faulted Current: 0.0
 Qual Current: NORMAL

Readings at SENSOR-1A

Normal Voltage: 0.9374976
 Faulted Voltage: 0.0
 Qual Voltage: NORMAL

Normal Current: 0.0
 Faulted Current: 0.0
 Qual Current: NORMAL

Program halted.

Ending run at 2/08/86 13:39:49.

=> Resetting ART...

Knowledge base has been reset.

=> Beginning run at 2/08/86 13:43:21: type ^C to halt.

Program halted.

Ending run at 2/08/86 14:00:20.

=> => Beginning run at 2/08/86 14:00:34: type ^C to halt.

Initializing Circuit Description

Create Errorbands

Assigning Qualitative Values to Sensors

Hypothesizing Faults:

Fault-Hypothesis: Open-Circuit BUS-2B

Fault-Hypothesis: Open-Circuit RELAY-2E

Fault-Hypothesis: Resistive-Short-Circuit SOLAR-ARRAY-2B

Fault-Hypothesis: Resistive-Short-Circuit SOLAR-ARRAY-2A


Fault-hyp: Open-Circuit RELAY-2E

Source Propagation from RELAY-2E to BUS-2B

Fault-hyp: OPEN-CIRCUIT RELAY-2E

Propagation from BUS-2B to SENSOR-2C

-hyp: OPEN-CIRCUIT RELAY-2E

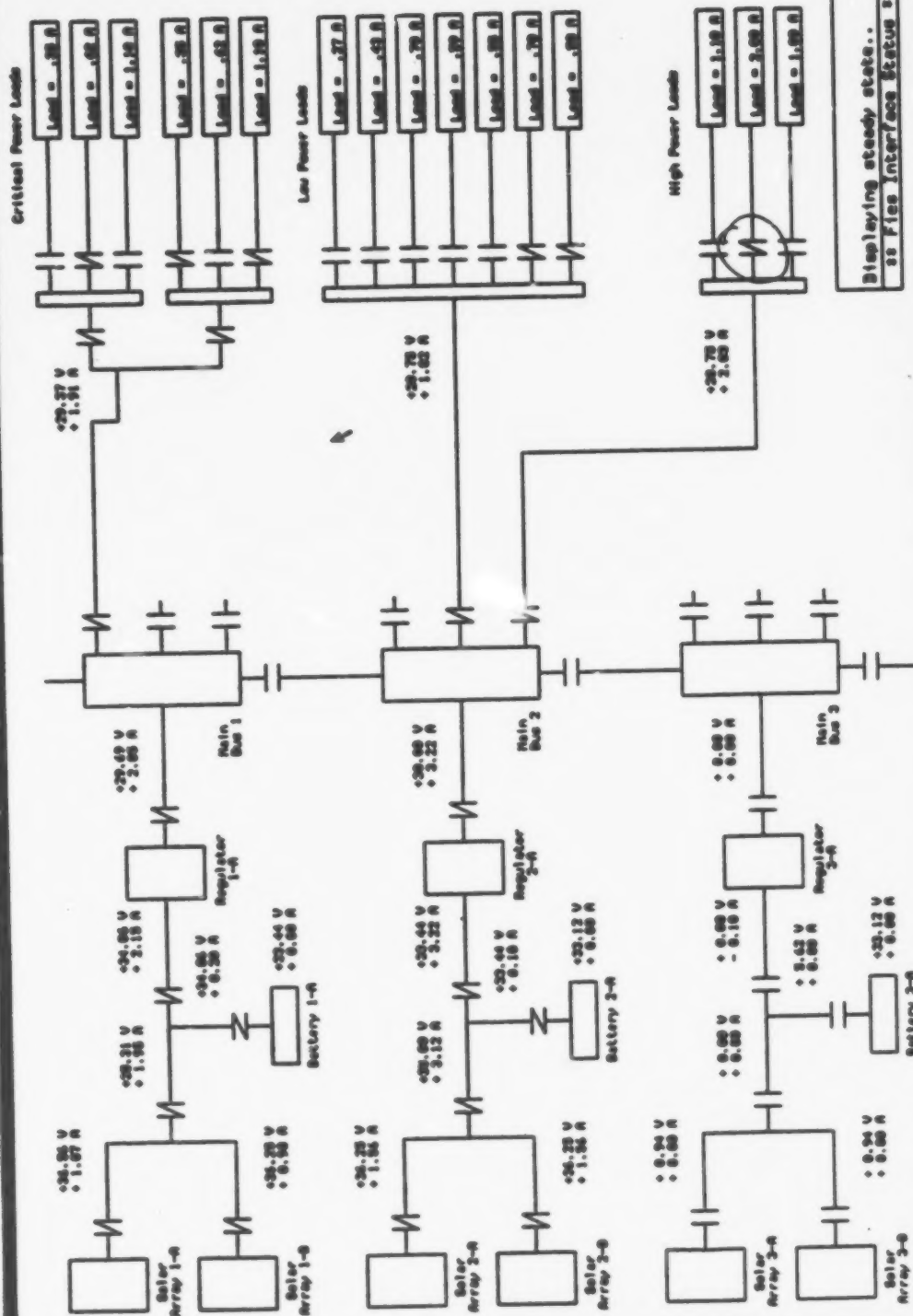

1527

ORIGINAL PAGE IS
OF POOR QUALITY

File Steady State Data Display Window 2

02/17/86 16:31:24 FIES-WFI-INTERACTIVE AU:


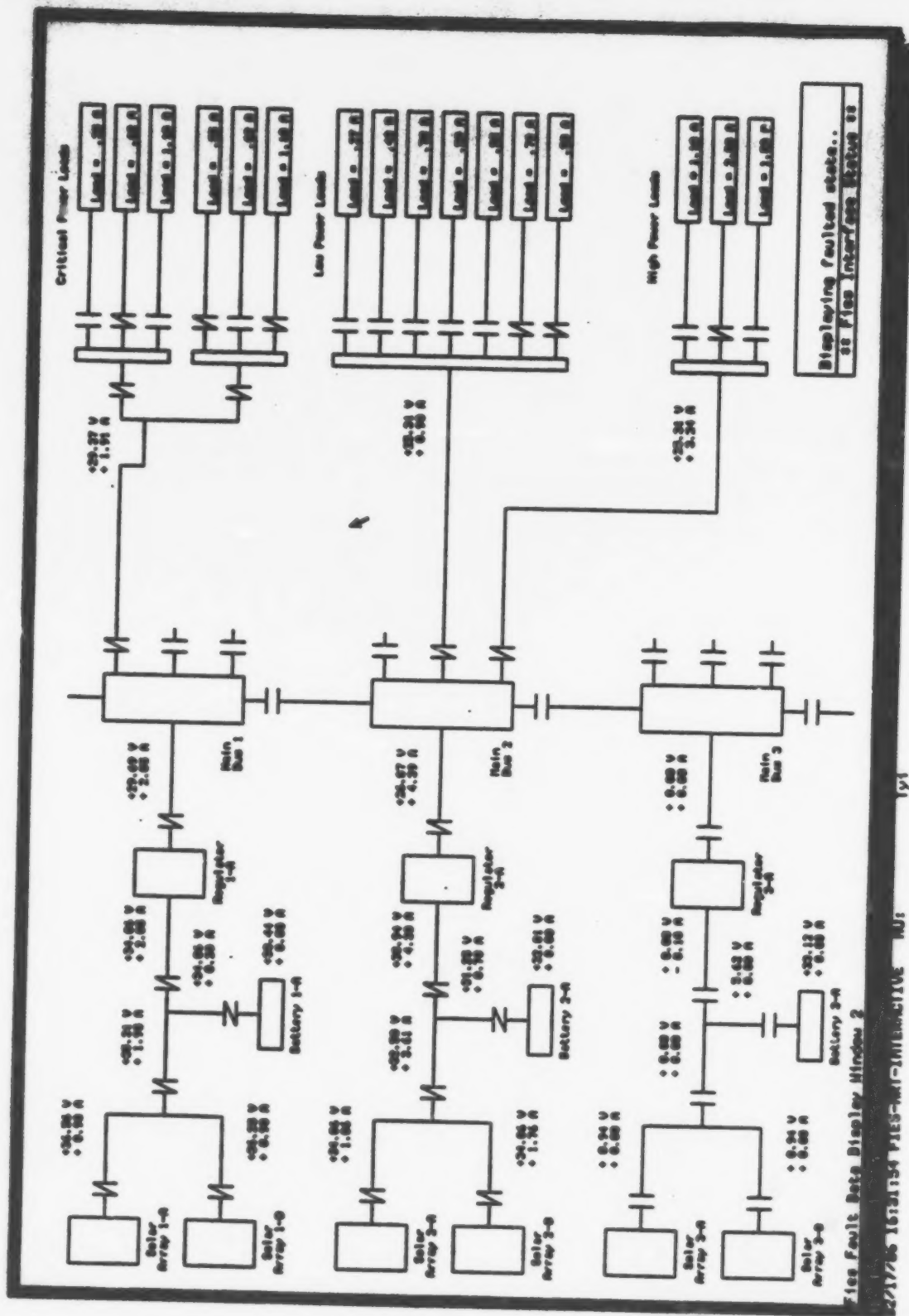


FIG. F-9
2

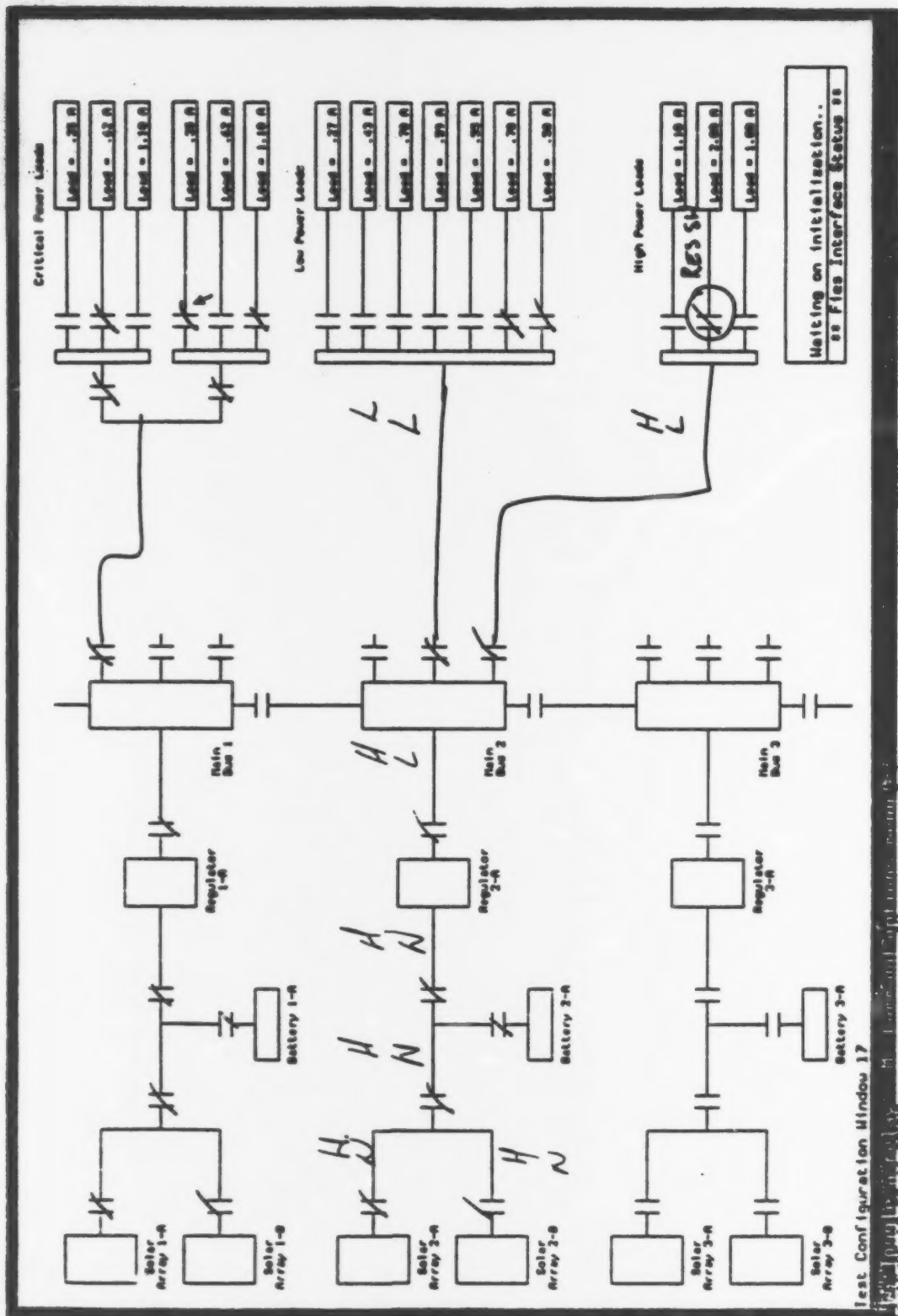

F-1

3

ORIGINAL PAGE 13
OF POOR QUALITY

• E1H1H1L1>donna>art.out 75318

RES 27. DAT

11/11

S-C LOAD 3M
BUS 3D

RES SH
SATA 1
SATA 2
SATA 3
BUS 2C
BUS 3D
LOAD 3M

=> pop
=> run
Beginning run at 2/17/86 16:32:49: type ^C to halt.
Initializing Circuit Description

Create Errorbands

Assigning Qualitative Values to Sensors

Hypothesizing Faults:

Fault-Hypothesis: Resistive-Short-Circuit BUS-2C

Fault-Hypothesis: Closed-Relay RELAY-3N

Fault-Hypothesis: Closed-Relay RELAY-3K

Fault-Hypothesis: Resistive-Short-Circuit BUS-3D

Fault-Hypothesis: Resistive-Short-Circuit LOAD-3M

Fault-Hypothesis: Short-Circuit BUS-3D

Fault-Hypothesis: Short-Circuit LOAD-3M

Reject Fault Hypothesis Short-Circuit at BUS-3D
Reason: Predicted Voltage Effect Is Inconsistent at Sensor SENSOR-3G

Reject Fault Hypothesis Short-Circuit at LOAD-3M
Reason: Predicted Voltage Effect Is Inconsistent at Sensor SENSOR-3G

Fault-hyp: Resistive-Short-Circuit BUS-2C
Source Propagation from BUS-2C to SENSOR-2F

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-2C
Predicted Current Effect: HIGH Consistent at Sensor SENSOR-2F
Source Propagation from SENSOR-2F to RELAY-2F

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-2C
Source Propagation from RELAY-2F to REGULATOR-2A

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-2C
Source Propagation from REGULATOR-2A to SENSOR-2E

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-2C
Predicted Current Effect: HIGH Consistent at Sensor SENSOR-2E
Source Propagation from SENSOR-2E to RELAY-2E

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-2C
Source Propagation from RELAY-2E to BUS-2B

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-2C
Source Propagation from BUS-2B to SENSOR-2D

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-2C
Predicted Current Effect: HIGH Consistent at Sensor SENSOR-2D
Source Propagation from SENSOR-2D to RELAY-2D

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-2C
Source Propagation from RELAY-2D to BATTERY-2A

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-2C
Source Propagation from BATTERY-2A

hyp: RESISTIVE-SHORT-CIRCUIT BUS-2C

F-7

4

Source Propagation from BUS-2B to SENSOR-2C

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-2C
Predicted Current Effect: HIGH Consistent at Sensor SENSOR-2C
Source Propagation from SENSOR-2C to RELAY-2C

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-2C
Source Propagation from RELAY-2C to BUS-2A

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-2C
Source Propagation from BUS-2A to SENSOR-2B

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-2C
Predicted Current Effect: HIGH Consistent at Sensor SENSOR-2B
Source Propagation from SENSOR-2B to RELAY-2B

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-2C
Source Propagation from RELAY-2B to SOLAR-ARRAY-2B

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-2C
End-Source Propagation from SOLAR-ARRAY-2B

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-2C
Source Propagation from BUS-2A to SENSOR-2A

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-2C
Predicted Current Effect: HIGH Consistent at Sensor SENSOR-2A
Source Propagation from SENSOR-2A to RELAY-2A

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-2C
Source Propagation from RELAY-2A to SOLAR-ARRAY-2A

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-2C
End-Source Propagation from SOLAR-ARRAY-2A

Fault-hyp: Resistive-Short-Circuit BUS-2C
Sink Propagation from BUS-2C to RELAY-2H

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-2C
Sink Propagation from RELAY-2H to SENSOR-2G

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-2C
Predicted Current Effect: LOW Consistent at Sensor SENSOR-2G
Sink Propagation from SENSOR-2G to BUS-2D

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-2C
Sink Propagation from BUS-2D to RELAY-2Q

FFFault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-2C
Sink Propagation from RELAY-2Q to LOAD-2Q

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-2C
End-Sink Propagation from LOAD-2Q

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-2C
Sink Propagation from BUS-2D to RELAY-2R

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-2C
Sink Propagation from RELAY-2R to LOAD-2R

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-2C
End-Sink Propagation from LOAD-2R

Fault-hyp: Resistive-Short-Circuit BUS-2C
Sink Propagation from BUS-2C to RELAY-2J

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-2C
Sink Propagation from RELAY-2J to SENSOR-3G

Reject Fault Hypothesis RESISTIVE-SHORT-CIRCUIT at BUS-2C
Reason: Predicted Effect Is Inconsistent at Sensor SENSOR-3G
Predicted Value: LOW
Lower Value: HIGH

/p: Resistive-Short-Circuit BUS-3D

6-7

5

Source Propagation from BUS-3D to SENSOR-3G

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D
Predicted Current Effect: HIGH Consistent at Sensor SENSOR-3G
Source Propagation from SENSOR-3G to RELAY-2J

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D
Source Propagation from RELAY-2J to BUS-2C

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D
Source-Propagation from BUS-2C to SENSOR-2F
Sink-Propagation from BUS-2C to RELAY-2H

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D
Predicted Current Effect: HIGH Consistent at Sensor SENSOR-2F
Source Propagation from SENSOR-2F to RELAY-2F

FFFault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D
Source Propagation from RELAY-2F to REGULATOR-2A

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D
Source Propagation from REGULATOR-2A to SENSOR-2E

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D
Predicted Current Effect: HIGH Consistent at Sensor SENSOR-2E
Source Propagation from SENSOR-2E to RELAY-2E

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D
Source Propagation from RELAY-2E to BUS-2B

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D
Source Propagation from BUS-2B to SENSOR-2D

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D
Predicted Current Effect: HIGH Consistent at Sensor SENSOR-2D
Source Propagation from SENSOR-2D to RELAY-2D

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D
Source Propagation from RELAY-2D to BATTERY-2A

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D
End-Source Propagation from BATTERY-2A

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D
Source Propagation from BUS-2B to SENSOR-2C

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D
Predicted Current Effect: HIGH Consistent at Sensor SENSOR-2C
Source Propagation from SENSOR-2C to RELAY-2C

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D
Source Propagation from RELAY-2C to BUS-2A

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D
Source Propagation from BUS-2A to SENSOR-2B

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D
Predicted Current Effect: HIGH Consistent at Sensor SENSOR-2B
Source Propagation from SENSOR-2B to RELAY-2B

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D
SSSource Propagation from RELAY-2B to SOLAR-ARRAY-2B

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D
End-Source Propagation from SOLAR-ARRAY-2B

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D
Source Propagation from BUS-2A to SENSOR-2A

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D
Predicted Current Effect: HIGH Consistent at Sensor SENSOR-2A
Source Propagation from SENSOR-2A to RELAY-2A

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D
Source Propagation from RELAY-2A to SOLAR-ARRAY-2A

F-7

6

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D
End-Source Propagation from SOLAR-ARRAY-2A

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D
Sink Propagation from RELAY-2H to SENSOR-2G

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D
Predicted Current Effect: LOW Consistent at Sensor SENSOR-2G
Sink Propagation from SENSOR-2G to BUS-2D

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D
Sink Propagation from BUS-2D to RELAY-2Q

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D
Sink Propagation from RELAY-2Q to LOAD-2Q

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D
End-Sink Propagation from LOAD-2Q

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D
Sink Propagation from BUS-2D to RELAY-2R

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D
Sink Propagation from RELAY-2R to LOAD-2R

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D
End-Sink Propagation from LOAD-2R

FFFault-hyp: Resistive-Short-Circuit BUS-3D
Sink Propagation from BUS-3D to RELAY-3M

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D
Sink Propagation from RELAY-3M to LOAD-3M

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D
End-Sink Propagation from LOAD-3M

Fault-hyp: Resistive-Short-Circuit LOAD-3M
Source Propagation from LOAD-3M to RELAY-3M

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3M
Source Propagation from RELAY-3M to BUS-3D

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3M
Source Propagation from BUS-3D to SENSOR-3G

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3M
Predicted Current Effect: HIGH Consistent at Sensor SENSOR-3G
Source Propagation from SENSOR-3G to RELAY-2J

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3M
Source Propagation from RELAY-2J to BUS-2C

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3M
Source-Propagation from BUS-2C to SENSOR-2F
Sink-Propagation from BUS-2C to RELAY-2H

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3M
Predicted Current Effect: HIGH Consistent at Sensor SENSOR-2F
Source Propagation from SENSOR-2F to RELAY-2F

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3M
Source Propagation from RELAY-2F to REGULATOR-2A

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3M
Source Propagation from REGULATOR-2A to SENSOR-2E

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3M
Predicted Current Effect: HIGH Consistent at Sensor SENSOR-2E
Source Propagation from SENSOR-2E to RELAY-2E

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3M
Source Propagation from RELAY-2E to BUS-2B

yp: RESISTIVE-SHORT-CIRCUIT LOAD-3M

F-7
7

Source Propagation from BUS-2B to SENSOR-2D

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3M
Predicted Current Effect: HIGH Consistent at Sensor SENSOR-2D
Source Propagation from SENSOR-2D to RELAY-2D

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3M
Source Propagation from RELAY-2D to BATTERY-2A

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3M
End-Source Propagation from BATTERY-2A

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3M
Source Propagation from BUS-2B to SENSOR-2C

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3M
Predicted Current Effect: HIGH Consistent at Sensor SENSOR-2C
Source Propagation from SENSOR-2C to RELAY-2C

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3M
Source Propagation from RELAY-2C to BUS-2A

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3M
Source Propagation from BUS-2A to SENSOR-2B

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3M
Predicted Current Effect: HIGH Consistent at Sensor SENSOR-2B
Source Propagation from SENSOR-2B to RELAY-2B

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3M
Source Propagation from RELAY-2B to SOLAR-ARRAY-2B

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3M
End-Source Propagation from SOLAR-ARRAY-2B

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3M
Source Propagation from BUS-2A to SENSOR-2A

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3M
Predicted Current Effect: HIGH Consistent at Sensor SENSOR-2A
Source Propagation from SENSOR-2A to RELAY-2A

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3M
Source Propagation from RELAY-2A to SOLAR-ARRAY-2A

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3M
End-Source Propagation from SOLAR-ARRAY-2A

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3M
Sink Propagation from RELAY-2H to SENSOR-2G

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3M
Predicted Current Effect: LOW Consistent at Sensor SENSOR-2G
Sink Propagation from SENSOR-2G to BUS-2D

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3M
Sink Propagation from BUS-2D to RELAY-2Q

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3M
Sink Propagation from RELAY-2Q to LOAD-2Q

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3M
End-Sink Propagation from LOAD-2Q

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3M
Sink Propagation from BUS-2D to RELAY-2R

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3M
Sink Propagation from RELAY-2R to LOAD-2R

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3M
End-Sink Propagation from LOAD-2R

ing All Initial Fault Hypotheses:


62: F-7
b

RESISTIVE-SHORT-CIRCUIT BUS-2C
CLOSED-RELAY RELAY-3M
CLOSED-RELAY RELAY-3K
RESISTIVE-SHORT-CIRCUIT BUS-3D
RESISTIVE-SHORT-CIRCUIT LOAD-3M
SHORT-CIRCUIT BUS-3D
SHORT-CIRCUIT LOAD-3M

Reporting Final Fault Hypotheses:

CLOSED-RELAY RELAY-3M
CLOSED-RELAY RELAY-3K
RESISTIVE-SHORT-CIRCUIT BUS-3D
RESISTIVE-SHORT-CIRCUIT LOAD-3M

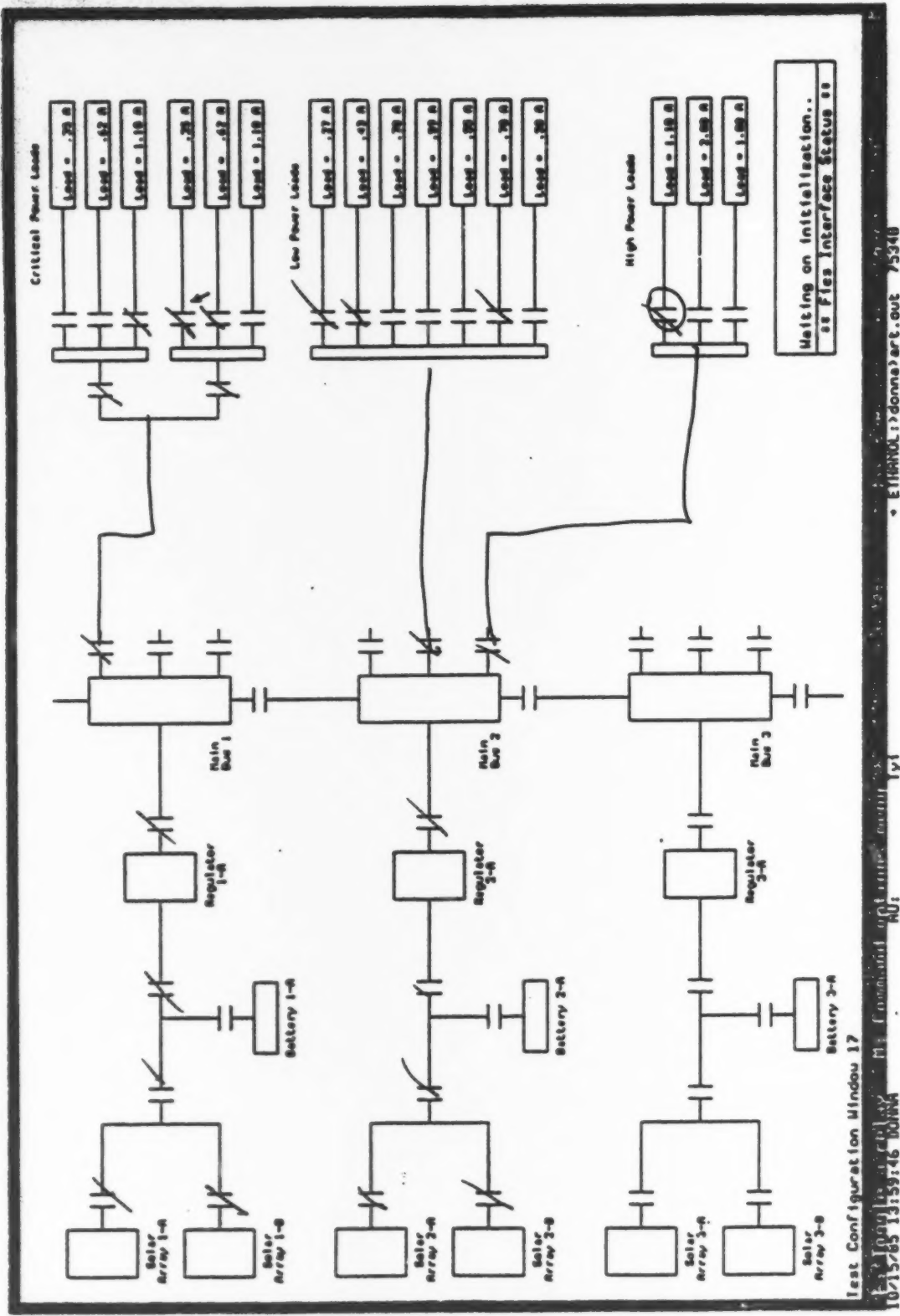
Program halted.
Ending run at 2/17/86 16:33:51.
=> watch
=> dribble



ORIGINAL PAGE 3
OF POOR QUALITY

short 9 dat

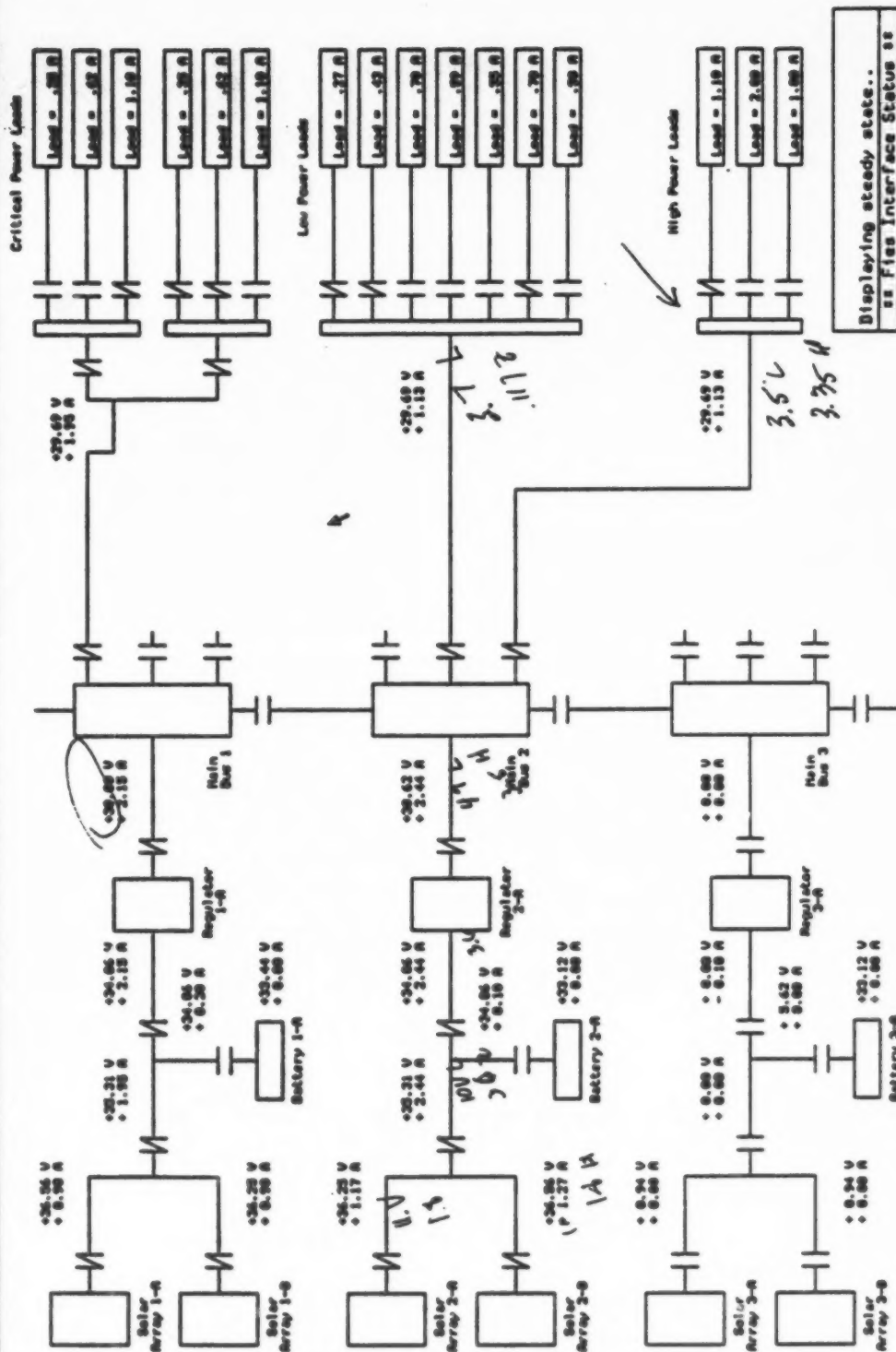10/15/85 13:59:46 DOWNS M: Command optime menu 171
• E:\HNDL\>donna\art.out 75348




File Steady State Data Display Window 3

02/13/86 15:46:18 FIES-MRI-INTERACTIVE NU:

191

• EINHOLD: donna'short6.out 16/56

Ex: F-8

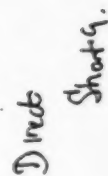

ORIGINAL PAGE IS
OF POOR QUALITY

Readings at SENSOR-1D

Normal Voltage: 34.062412
 Faulted Voltage: 34.062412
 Qual Voltage: NORMAL

Normal Current: 0.195312
 Faulted Current: 0.097656
 Qual Current: NORMAL

Readings at SENSOR-1B

Normal Voltage: 36.24991
 Faulted Voltage: 36.24991
 Qual Voltage: NORMAL

Normal Current: 0.878904
 Faulted Current: 0.97656
 Qual Current: NORMAL

Readings at SENSOR-1A

Normal Voltage: 36.562405
 Faulted Voltage: 36.562405
 Qual Voltage: NORMAL

Normal Current: 1.074216
 Faulted Current: 1.074216
 Qual Current: NORMAL

Program halted.

Ending run at 2/13/86 15:44:27.

=> reset

Resetting ART...

Knowledge base has been reset.

=> run

Beginning run at 2/13/86 15:45:17: type ^C to halt.

Program halted.

Ending run at 2/13/86 15:47:03.

=> Beginning run at 2/13/86 15:47:05: type ^C to halt.

Initializing Circuit Description

Create Errorbands

Assigning Qualitative Values to Sensors

Hypothesizing Faults:

Fault-Hypothesis: Closed-Relay RELAY-3N

Fault-Hypothesis: Closed-Relay RELAY-3M

Fault-Hypothesis: Resistive-Short-Circuit BUS-3D

Fault-Hypothesis: Resistive-Short-Circuit LOAD-3K

Fault-Hypothesis: Short-Circuit BUS-3D

Fault-Hypothesis: Short-Circuit LOAD-3K

Fault Hypothesis Resistive-Short-Circuit at BUS-3D

F-8

4

Reason: Predicted Voltage Effect Is Inconsistent at Sensor SENSOR-3G

Reject Fault Hypothesis Closed-Relay at RELAY-3M

Reason: Predicted Voltage Effect Is Inconsistent at Sensor SENSOR-3G

Reject Fault Hypothesis Closed-Relay at RELAY-3M

Reason: Predicted Voltage Effect Is Inconsistent at Sensor SENSOR-3G

Fault-hyp: Short-Circuit BUS-3D

Source Propagation from BUS-3D to SENSOR-3G

Fault-hyp: SHORT-CIRCUIT BUS-3D

Predicted Current Effect: HIGH Consistent at Sensor SENSOR-3G

Source Propagation from SENSOR-3G to RELAY-2J

Fault-hyp: SHORT-CIRCUIT BUS-3D

Source Propagation from RELAY-2J to BUS-2C

Fault-hyp: SHORT-CIRCUIT BUS-3D

Source-Propagation from BUS-2C to SENSOR-2F

Sink-Propagation from BUS-2C to RELAY-2H

Fault-hyp: SHORT-CIRCUIT BUS-3D

Predicted Current Effect: HIGH Consistent at Sensor SENSOR-2F

Source Propagation from SENSOR-2F to RELAY-2F

Fault-hyp: SHORT-CIRCUIT BUS-3D

Source Propagation from RELAY-2F to REGULATOR-2A

Fault-hyp: SHORT-CIRCUIT BUS-3D

Source Propagation from REGULATOR-2A to SENSOR-2E

Fault-hyp: SHORT-CIRCUIT BUS-3D

Predicted Current Effect: HIGH Consistent at Sensor SENSOR-2E

Source Propagation from SENSOR-2E to RELAY-2E

Fault-hyp: SHORT-CIRCUIT BUS-3D

Source Propagation from RELAY-2E to BUS-2B

Fault-hyp: SHORT-CIRCUIT BUS-3D

Source Propagation from BUS-2B to SENSOR-2C

Fault-hyp: SHORT-CIRCUIT BUS-3D

Predicted Current Effect: HIGH Consistent at Sensor SENSOR-2C

Source Propagation from SENSOR-2C to RELAY-2C

Fault-hyp: SHORT-CIRCUIT BUS-3D

Source Propagation from RELAY-2C to BUS-2A

Fault-hyp: SHORT-CIRCUIT BUS-3D

Source Propagation from BUS-2A to SENSOR-2B

Fault-hyp: SHORT-CIRCUIT BUS-3D

Predicted Current Effect: HIGH Consistent at Sensor SENSOR-2B

Source Propagation from SENSOR-2B to RELAY-2B

Fault-hyp: SHORT-CIRCUIT BUS-3D

Source Propagation from RELAY-2B to SOLAR-ARRAY-2B

Fault-hyp: SHORT-CIRCUIT BUS-3D

End-Source Propagation from SOLAR-ARRAY-2B

Fault-hyp: SHORT-CIRCUIT BUS-3D

Source Propagation from BUS-2A to SENSOR-2A

Fault-hyp: SHORT-CIRCUIT BUS-3D

Predicted Current Effect: HIGH Consistent at Sensor SENSOR-2A

Source Propagation from SENSOR-2A to RELAY-2A

Fault-hyp: SHORT-CIRCUIT BUS-3D

Source Propagation from RELAY-2A to SOLAR-ARRAY-2A

Fault-hyp: SHORT-CIRCUIT BUS-3D

Source Propagation from SOLAR-ARRAY-2A

yp: SHORT-CIRCUIT BUS-3D

F-8

5

Sink Propagation from RELAY-2H to SENSOR-2G

Fault-hyp: SHORT-CIRCUIT BUS-3D
Predicted Current Effect: LOW Consistent at Sensor SENSOR-2G
Sink Propagation from SENSOR-2G to BUS-2D

Fault-hyp: SHORT-CIRCUIT BUS-3D
Sink Propagation from BUS-2D to RELAY-2K

Fault-hyp: SHORT-CIRCUIT BUS-3D
Sink Propagation from RELAY-2K to LOAD-2K

Fault-hyp: SHORT-CIRCUIT BUS-3D
End-Sink Propagation from LOAD-2K

Fault-hyp: SHORT-CIRCUIT BUS-3D
Sink Propagation from BUS-2D to RELAY-2H

Fault-hyp: SHORT-CIRCUIT BUS-3D
Sink Propagation from RELAY-2H to LOAD-2H

Fault-hyp: SHORT-CIRCUIT BUS-3D
End-Sink Propagation from LOAD-2H

Fault-hyp: SHORT-CIRCUIT BUS-3D
Sink Propagation from BUS-2D to RELAY-2Q

Fault-hyp: SHORT-CIRCUIT BUS-3D
Sink Propagation from RELAY-2Q to LOAD-2Q

Fault-hyp: SHORT-CIRCUIT BUS-3D
End-Sink Propagation from LOAD-2Q

Fault-hyp: Short-Circuit BUS-3D
Sink Propagation from BUS-3D to RELAY-3K

Fault-hyp: SHORT-CIRCUIT BUS-3D
Sink Propagation from RELAY-3K to LOAD-3K

Fault-hyp: SHORT-CIRCUIT BUS-3D
End-Sink Propagation from LOAD-3K

Fault-hyp: Short-Circuit LOAD-3K
Source Propagation from LOAD-3K to RELAY-3K

Fault-hyp: SHORT-CIRCUIT LOAD-3K
Source Propagation from RELAY-3K to BUS-3D

Fault-hyp: SHORT-CIRCUIT LOAD-3K
Source Propagation from BUS-3D to SENSOR-3G

Fault-hyp: SHORT-CIRCUIT LOAD-3K
Predicted Current Effect: HIGH Consistent at Sensor SENSOR-3G
Source Propagation from SENSOR-3G to RELAY-2J

Fault-hyp: SHORT-CIRCUIT LOAD-3K
Source Propagation from RELAY-2J to BUS-2C

Fault-hyp: SHORT-CIRCUIT LOAD-3K
Source-Propagation from BUS-2C to SENSOR-2F
Sink-Propagation from BUS-2C to RELAY-2H

Fault-hyp: SHORT-CIRCUIT LOAD-3K
Predicted Current Effect: HIGH Consistent at Sensor SENSOR-2F
Source Propagation from SENSOR-2F to RELAY-2F

Fault-hyp: SHORT-CIRCUIT LOAD-3K
Source Propagation from RELAY-2F to REGULATOR-2A

Fault-hyp: SHORT-CIRCUIT LOAD-3K
Source Propagation from REGULATOR-2A to SENSOR-2E

Fault-hyp: SHORT-CIRCUIT LOAD-3K
Predicted Current Effect: HIGH Consistent at Sensor SENSOR-2E
Propagation from SENSOR-2E to RELAY-2E

16 a: F-9

6

Fault-hyp: SHORT-CIRCUIT LOAD-3K
Source Propagation from RELAY-2E to BUS-2B

Fault-hyp: SHORT-CIRCUIT LOAD-3K
Source Propagation from BUS-2B to SENSOR-2C

Fault-hyp: SHORT-CIRCUIT LOAD-3K
Predicted Current Effect: HIGH Consistent at Sensor SENSOR-2C
Source Propagation from SENSOR-2C to RELAY-2C

Fault-hyp: SHORT-CIRCUIT LOAD-3K
Source Propagation from RELAY-2C to BUS-2A

Fault-hyp: SHORT-CIRCUIT LOAD-3K
Source Propagation from BUS-2A to SENSOR-2B

Fault-hyp: SHORT-CIRCUIT LOAD-3K
Predicted Current Effect: HIGH Consistent at Sensor SENSOR-2B
Source Propagation from SENSOR-2B to RELAY-2B

Fault-hyp: SHORT-CIRCUIT LOAD-3K
Source Propagation from RELAY-2B to SOLAR-ARRAY-2B

Fault-hyp: SHORT-CIRCUIT LOAD-3K
End-Source Propagation from SOLAR-ARRAY-2B

Fault-hyp: SHORT-CIRCUIT LOAD-3K
Source Propagation from BUS-2A to SENSOR-2A

Fault-hyp: SHORT-CIRCUIT LOAD-3K
Predicted Current Effect: HIGH Consistent at Sensor SENSOR-2A
Source Propagation from SENSOR-2A to RELAY-2A

Fault-hyp: SHORT-CIRCUIT LOAD-3K
Source Propagation from RELAY-2A to SOLAR-ARRAY-2A

Fault-hyp: SHORT-CIRCUIT LOAD-3K
End-Source Propagation from SOLAR-ARRAY-2A

Fault-hyp: SHORT-CIRCUIT LOAD-3K
Sink Propagation from RELAY-2H to SENSOR-2G

Fault-hyp: SHORT-CIRCUIT LOAD-3K
Predicted Current Effect: LOW Consistent at Sensor SENSOR-2G
Sink Propagation from SENSOR-2G to BUS-2D

Fault-hyp: SHORT-CIRCUIT LOAD-3K
Sink Propagation from BUS-2D to RELAY-2K

Fault-hyp: SHORT-CIRCUIT LOAD-3K
Sink Propagation from RELAY-2K to LOAD-2K

Fault-hyp: SHORT-CIRCUIT LOAD-3K
End-Sink Propagation from LOAD-2K

Fault-hyp: SHORT-CIRCUIT LOAD-3K
Sink Propagation from BUS-2D to RELAY-2H

Fault-hyp: SHORT-CIRCUIT LOAD-3K
Sink Propagation from RELAY-2H to LOAD-2H

Fault-hyp: SHORT-CIRCUIT LOAD-3K
End-Sink Propagation from LOAD-2H

Fault-hyp: SHORT-CIRCUIT LOAD-3K
Sink Propagation from BUS-2D to RELAY-2G

Fault-hyp: SHORT-CIRCUIT LOAD-3K
Sink Propagation from RELAY-2G to LOAD-2G

Fault-hyp: SHORT-CIRCUIT LOAD-3K
Sink Propagation from LOAD-2G

yp: Resistive-Short-Circuit BUS-2D

6. F-1

7

Source Propagation from BUS-3D to SENSOR-3G

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D

Predicted Current Effect: HIGH Consistent at Sensor SENSOR-3G

Source Propagation from SENSOR-3G to RELAY-2J

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D

Source Propagation from RELAY-2J to BUS-2C

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D

Source-Propagation from BUS-2C to SENSOR-2F

Sink-Propagation from BUS-2C to RELAY-2H

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D

Predicted Current Effect: HIGH Consistent at Sensor SENSOR-2F

Source Propagation from SENSOR-2F to RELAY-2F

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D

Source Propagation from RELAY-2F to REGULATOR-2A

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D

Source Propagation from REGULATOR-2A to SENSOR-2E

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D

Predicted Current Effect: HIGH Consistent at Sensor SENSOR-2E

Source Propagation from SENSOR-2E to RELAY-2E

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D

Source Propagation from RELAY-2E to BUS-2B

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D

Source Propagation from BUS-2B to SENSOR-2C

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D

Predicted Current Effect: HIGH Consistent at Sensor SENSOR-2C

Source Propagation from SENSOR-2C to RELAY-2C

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D

Source Propagation from RELAY-2C to BUS-2A

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D

Source Propagation from BUS-2A to SENSOR-2B

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D

Predicted Current Effect: HIGH Consistent at Sensor SENSOR-2B

Source Propagation from SENSOR-2B to RELAY-2B

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D

Source Propagation from RELAY-2B to SOLAR-ARRAY-2B

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D

End-Source Propagation from SOLAR-ARRAY-2B

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D

Source Propagation from BUS-2A to SENSOR-2A

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D

Predicted Current Effect: HIGH Consistent at Sensor SENSOR-2A

Source Propagation from SENSOR-2A to RELAY-2A

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D

Source Propagation from RELAY-2A to SOLAR-ARRAY-2A

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D

End-Source Propagation from SOLAR-ARRAY-2A

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D

Sink Propagation from RELAY-2H to SENSOR-2G

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D

Predicted Current Effect: LOW Consistent at Sensor SENSOR-2G

Sink Propagation from SENSOR-2G to BUS-2D

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D

Propagation from BUS-2D to RELAY-2K

Ex: P-8

8

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D
Sink Propagation from RELAY-2K to LOAD-2K

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D
End-Sink Propagation from LOAD-2K

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D
Sink Propagation from BUS-2D to RELAY-2M

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D
Sink Propagation from RELAY-2M to LOAD-2M

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D
End-Sink Propagation from LOAD-2M

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D
Sink Propagation from BUS-2D to RELAY-2Q

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D
Sink Propagation from RELAY-2Q to LOAD-2Q

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D
End-Sink Propagation from LOAD-2Q

Fault-hyp: Resistive-Short-Circuit BUS-3D
Sink Propagation from BUS-3D to RELAY-3K

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D
Sink Propagation from RELAY-3K to LOAD-3K

Fault-hyp: RESISTIVE-SHORT-CIRCUIT BUS-3D
End-Sink Propagation from LOAD-3K

Fault-hyp: Resistive-Short-Circuit LOAD-3K
Source Propagation from LOAD-3K to RELAY-3K

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3K
Source Propagation from RELAY-3K to BUS-3D

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3K
Source Propagation from BUS-3D to SENSOR-3G

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3K
Predicted Current Effect: HIGH Consistent at Sensor SENSOR-3G
Source Propagation from SENSOR-3G to RELAY-2J

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3K
Source Propagation from RELAY-2J to BUS-2C

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3K
Source-Propagation from BUS-2C to SENSOR-2F
Sink-Propagation from BUS-2C to RELAY-2H

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3K
Predicted Current Effect: HIGH Consistent at Sensor SENSOR-2F
Source Propagation from SENSOR-2F to RELAY-2F

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3K
Source Propagation from RELAY-2F to REGULATOR-2A

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3K
Source Propagation from REGULATOR-2A to SENSOR-2E

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3K
Predicted Current Effect: HIGH Consistent at Sensor SENSOR-2E
Source Propagation from SENSOR-2E to RELAY-2E

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3K
Source Propagation from RELAY-2E to BUS-2B

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3K
Source Propagation from BUS-2B to SENSOR-2C

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3K
Predicted Current Effect: HIGH Consistent at Sensor SENSOR-2C

Source Propagation from SENSOR-2C to RELAY-2C

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3K

Source Propagation from RELAY-2C to BUS-2A

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3K

Source Propagation from BUS-2A to SENSOR-2B

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3K

Predicted Current Effect: HIGH Consistent at Sensor SENSOR-2B

Source Propagation from SENSOR-2B to RELAY-2B

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3K

Source Propagation from RELAY-2B to SOLAR-ARRAY-2B

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3K

End-Source Propagation from SOLAR-ARRAY-2B

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3K

Source Propagation from BUS-2A to SENSOR-2A

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3K

Predicted Current Effect: HIGH Consistent at Sensor SENSOR-2A

Source Propagation from SENSOR-2A to RELAY-2A

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3K

Source Propagation from RELAY-2A to SOLAR-ARRAY-2A

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3K

End-Source Propagation from SOLAR-ARRAY-2A

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3K

Sink Propagation from RELAY-2H to SENSOR-2G

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3K

Predicted Current Effect: LOW Consistent at Sensor SENSOR-2G

Sink Propagation from SENSOR-2G to BUS-2D

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3K

Sink Propagation from BUS-2D to RELAY-2K

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3K

Sink Propagation from RELAY-2K to LOAD-2K

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3K

End-Sink Propagation from LOAD-2K

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3K

Sink Propagation from BUS-2D to RELAY-2H

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3K

Sink Propagation from RELAY-2H to LOAD-2H

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3K

End-Sink Propagation from LOAD-2H

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3K

Sink Propagation from BUS-2D to RELAY-2Q

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3K

Sink Propagation from RELAY-2Q to LOAD-2Q

Fault-hyp: RESISTIVE-SHORT-CIRCUIT LOAD-3K

End-Sink Propagation from LOAD-2Q

Reporting All Initial Fault Hypotheses:

SHORT-CIRCUIT LOAD-3K

SHORT-CIRCUIT BUS-3D

RESISTIVE-SHORT-CIRCUIT LOAD-3K

RESISTIVE-SHORT-CIRCUIT BUS-3E

CLOSED-RELAY RELAY-3M

CLOSED-RELAY RELAY-3M

Reporting Final Fault Hypotheses:

SHORT-CIRCUIT LOAD-3K

SHORT-CIRCUIT BUS-3D

RESISTIVE-SHORT-CIRCUIT LOAD-3K

RESISTIVE-SHORT-CIRCUIT BUS-3D

Readings at SENSOR-3Z

Normal Voltage: 33.124916

Faulted Voltage: 33.124916

Qual Voltage: NORMAL

Normal Current: 0.0

Faulted Current: 0.0

Qual Current: NORMAL

Readings at SENSOR-2Z

Normal Voltage: 33.124916

Faulted Voltage: 33.124916

Qual Voltage: NORMAL

Normal Current: 0.0

Faulted Current: 0.0

Qual Current: NORMAL

Readings at SENSOR-1Z

Normal Voltage: 33.437412

Faulted Voltage: 33.437412

Qual Voltage: NORMAL

Normal Current: 0.0

Faulted Current: 0.0

Qual Current: NORMAL

Readings at SENSOR-3G

Normal Voltage: 29.687424

Faulted Voltage: 3.4374912

Qual Voltage: LOW

Normal Current: 1.1328096

Faulted Current: 3.3583684

Qual Current: HIGH

Readings at SENSOR-2G

Normal Voltage: 29.687424

Faulted Voltage: 3.7488885

Qual Voltage: LOW

Normal Current: 1.1328096

Faulted Current: 0.1171872

Qual Current: ZERO

C: F-8

11

Readings at SENSOR-1G

Normal Voltage: 29.687424
 Faulted Voltage: 29.374824
 Qual Voltage: NORMAL

Normal Current: 1.95312
 Faulted Current: 1.9140576
 Qual Current: NORMAL

Readings at SENSOR-3F

Normal Voltage: 0.0
 Faulted Voltage: 0.0
 Qual Voltage: NORMAL

Normal Current: 0.0
 Faulted Current: 0.0
 Qual Current: NORMAL

Readings at SENSOR-3E

Normal Voltage: 0.0
 Faulted Voltage: 0.0
 Qual Voltage: NORMAL

Normal Current: -0.097656
 Faulted Current: -0.097656
 Qual Current: NORMAL

Readings at SENSOR-3C

Normal Voltage: 0.0
 Faulted Voltage: 0.0
 Qual Voltage: NORMAL

Normal Current: 0.0
 Faulted Current: 0.0
 Qual Current: NORMAL

Readings at SENSOR-3D

Normal Voltage: 5.6249857
 Faulted Voltage: 5.6249857
 Qual Voltage: NORMAL

Normal Current: 0.0
 Faulted Current: 0.097656
 Qual Current: NORMAL

Readings at SENSOR-3B

Normal Voltage: 0.9374976
 Faulted Voltage: 0.9374976
 Qual Voltage: NORMAL

Normal Current: 0.0
 Faulted Current: 0.0
 Qual Current: NORMAL

En: F-1

12

Readings at SENSOR-3A

Normal Voltage: 0.9374976

Faulted Voltage: 0.9374978
Qual Voltage: NORMAL

Normal Current: 0.0
Faulted Current: 0.0
Qual Current: NORMAL

Readings at SENSOR-2F
Normal Voltage: 30.624922
Faulted Voltage: 4.999907
Qual Voltage: LOW

Normal Current: 2.4414
Faulted Current: 3.515616
Qual Current: HIGH

Readings at SENSOR-2E
Normal Voltage: 34.062412
Faulted Voltage: 8.437478
Qual Voltage: LOW

Normal Current: 2.4414
Faulted Current: 3.613272
Qual Current: HIGH

Readings at SENSOR-2C
Normal Voltage: 35.31241
Faulted Voltage: 10.312473
Qual Voltage: LOW

Normal Current: 2.4414
Faulted Current: 3.613272
Qual Current: HIGH

Readings at SENSOR-2D
Normal Voltage: 34.062412
Faulted Voltage: 8.749977
Qual Voltage: LOW

Normal Current: 0.097656
Faulted Current: 0.0
Qual Current: ZERO

Readings at SENSOR-2B
Normal Voltage: 36.562405
Faulted Voltage: 11.56247
Qual Voltage: LOW

Normal Current: 1.2695279
Faulted Current: 1.855484
Qual Current: HIGH

Readings at SENSOR-2A
Normal Voltage: 36.24991
Faulted Voltage: 11.56247
Qual Voltage: LOW

Current: 1.171872

F-8

Faulted Current: 1.757808
Qual Current: HIGH

Readings at SENSOR-1F

Normal Voltage: 29.999924
Faulted Voltage: 29.999924
Qual Voltage: NORMAL

Normal Current: 2.148432
Faulted Current: 2.148432
Qual Current: NORMAL

Readings at SENSOR-1E

Normal Voltage: 34.062412
Faulted Voltage: 34.062412
Qual Voltage: NORMAL

Normal Current: 2.148432
Faulted Current: 2.148432
Qual Current: NORMAL

Readings at SENSOR-1C

Normal Voltage: 35.31241
Faulted Voltage: 35.31241
Qual Voltage: NORMAL

Normal Current: 1.95312
Faulted Current: 1.95312
Qual Current: NORMAL

Readings at SENSOR-1D

Normal Voltage: 34.062412
Faulted Voltage: 34.062412
Qual Voltage: NORMAL

Normal Current: 0.195312
Faulted Current: 0.195312
Qual Current: NORMAL

Readings at SENSOR-1B

Normal Voltage: 36.24891
Faulted Voltage: 36.24891
Qual Voltage: NORMAL

Normal Current: 0.97858
Faulted Current: 0.97858
Qual Current: NORMAL

Readings at SENSOR-1A

Normal Voltage: 36.562405
Faulted Voltage: 36.562405
Qual Voltage: NORMAL

Normal Current: 0.97858
Faulted Current: 0.97858
Qual Current: NORMAL


6-8
14

ETHANOL:>DONNA>short0.out.1

2/13/86 15:50:02 Page 23

Program halted.
Ending run at 2/13/86 15:49:12.
=> watch
=> dribble

V. F-8

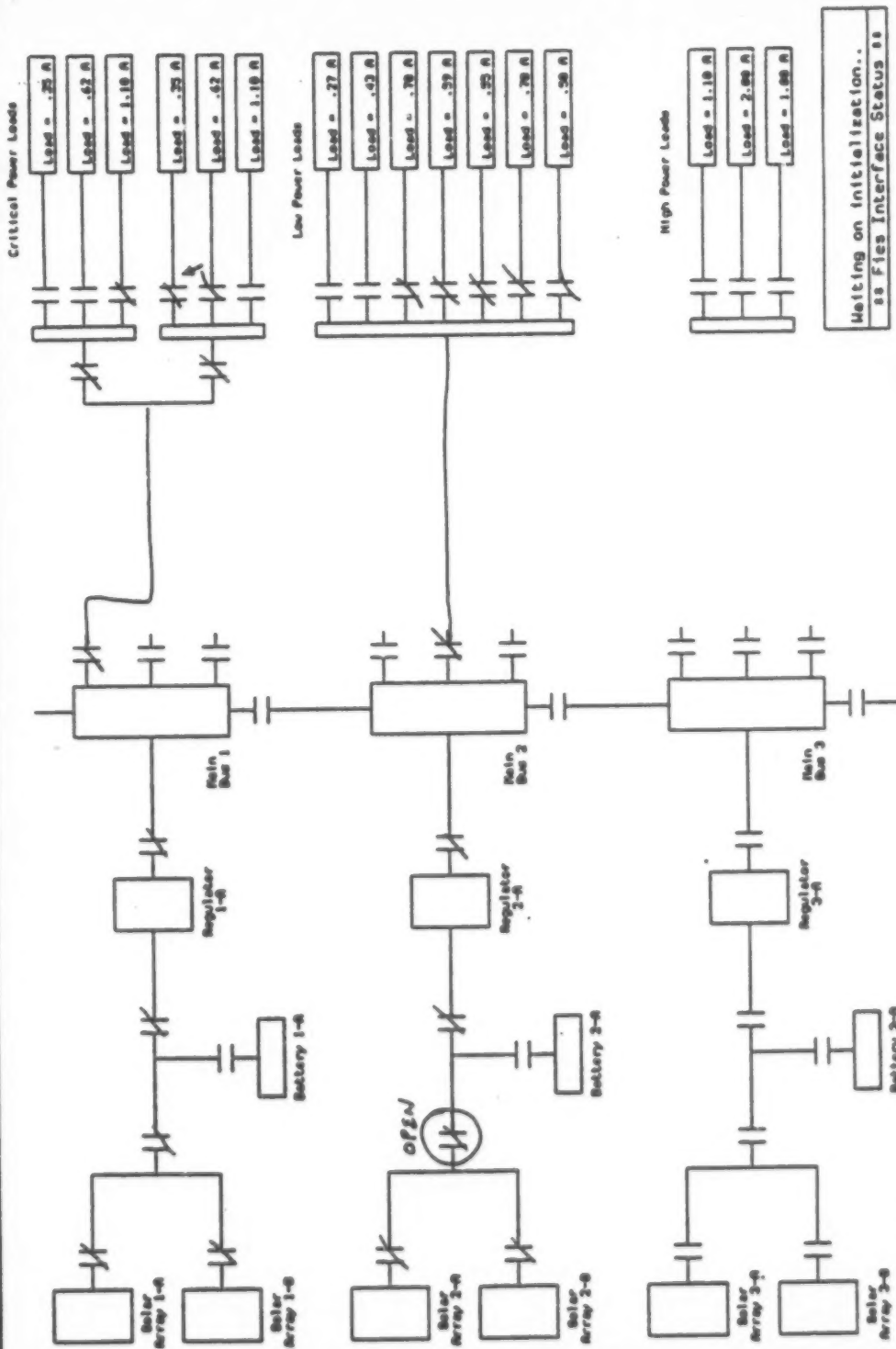

Test Configuration Window 17

18/15/85 13:59:46 10111


191

• ETHANOL:donner>art.out 75348


open5.dat

E: F-9

Critical Power Leads

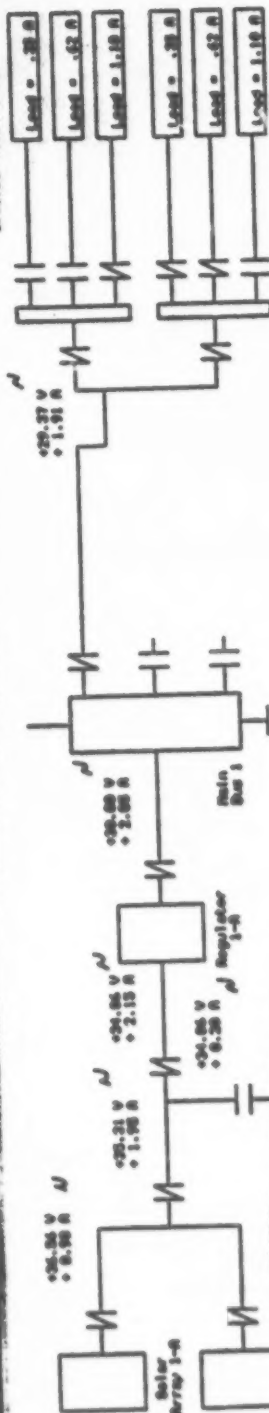

Low Power Leads

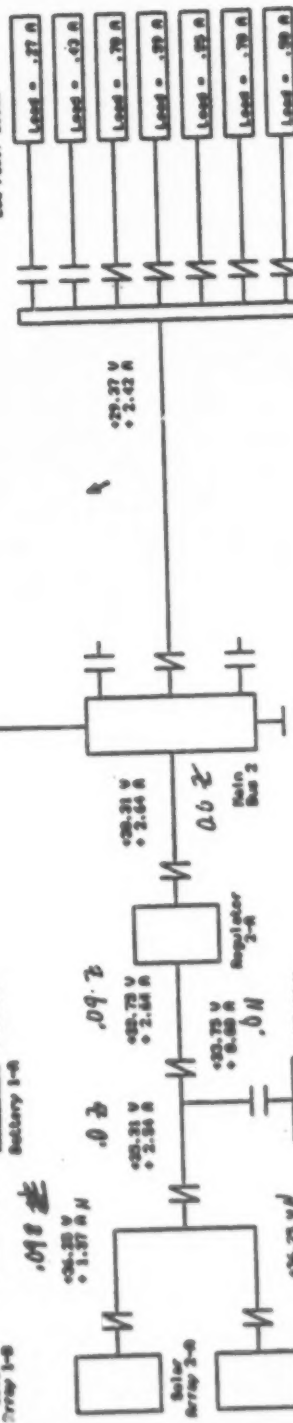

High Power Leads




Displaying steady state...
as Fies Interface Status is

Fies Steady State Data Display Window 8

11- (comm and apt) out: 16186158 FIES-INT-INTERACTIVE AU:

open 5. dat

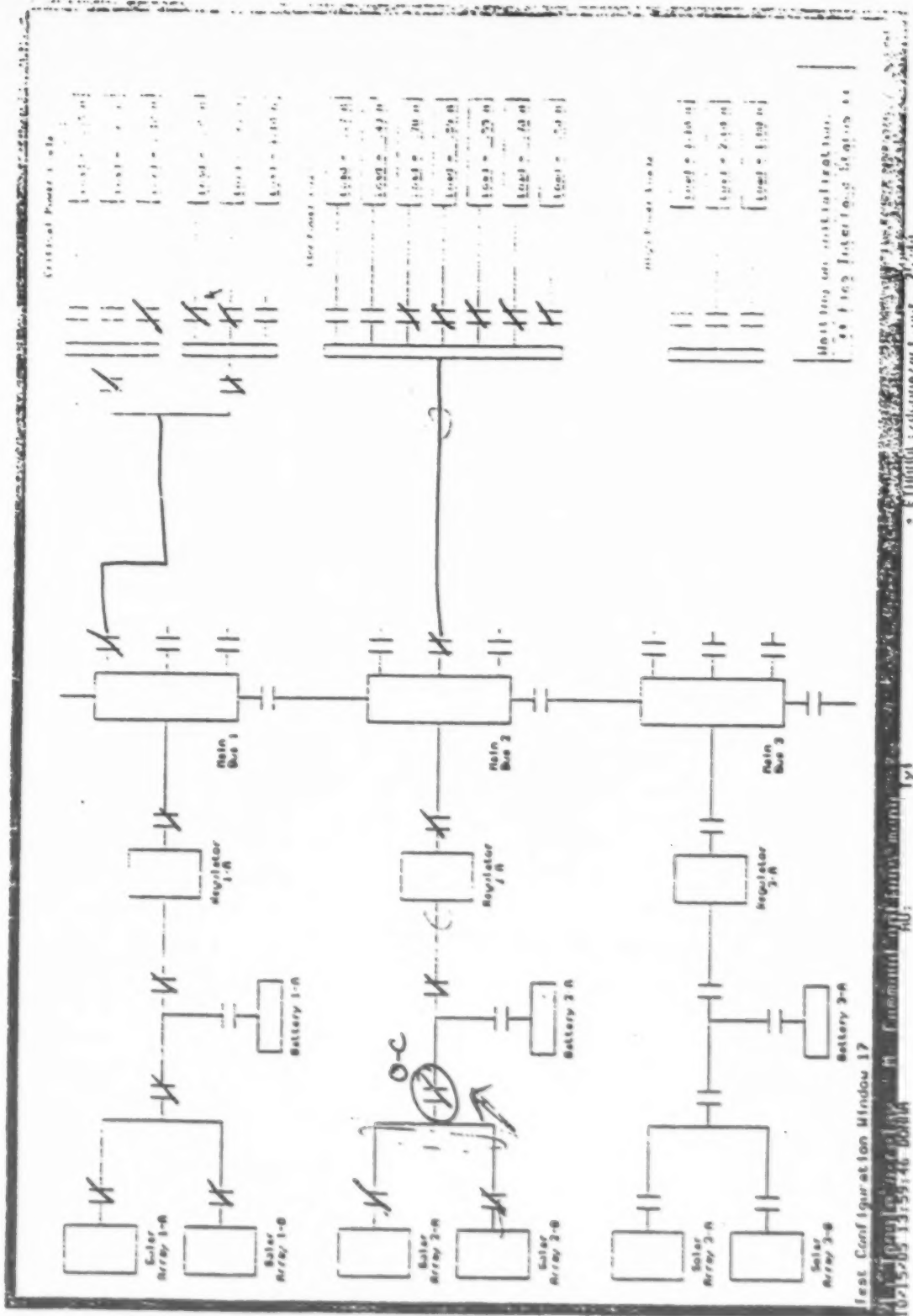


OPEN 5. DAT

Resh
O-C
SAZA P
2BP
2A P
2B P
Relay 2C
Busalt




Ex: FA

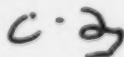

Test Configuration Window 17

• EYNARD: (donner) art. out

open5. dat

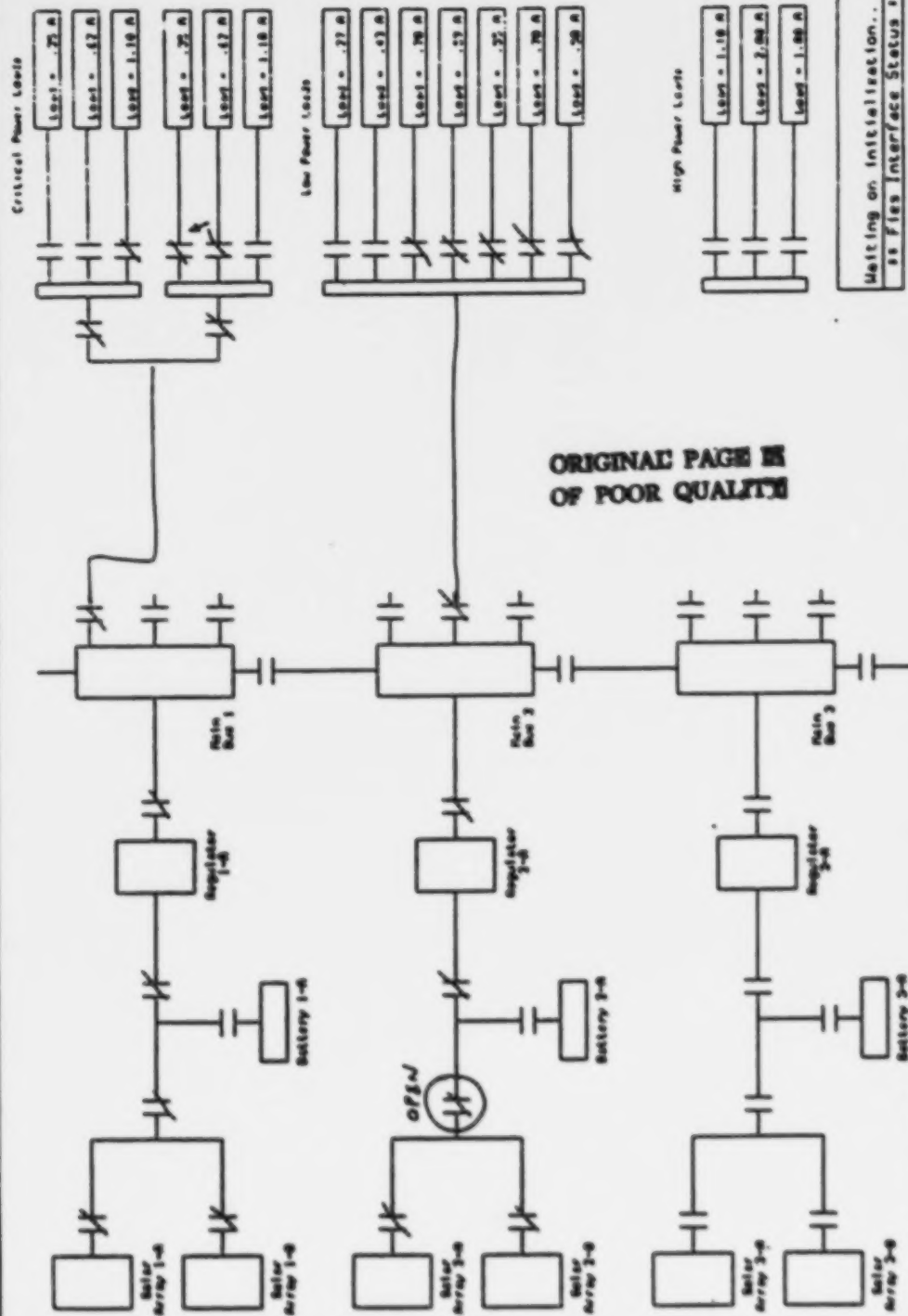

open5.dat

Fault-hyp: Open-Circuit RELAY-2C
Source Propagation from RELAY-2C to BUS-2A

Fault-hyp: OPEN-CIRCUIT RELAY-2C
Source Propagation from BUS-2A to SENSOR-2B

Fault-hyp: OPEN-CIRCUIT RELAY-2C
Predicted Current Effect: ZERO Consistent at Sensor SENSOR-2B
Source Propagation from SENSOR-2B to RELAY-2B

Fault-hyp: OPEN-CIRCUIT RELAY-2C
Source Propagation from RELAY-2B to SOLAR-ARRAY-2B

Fault-hyp: OPEN-CIRCUIT RELAY-2C
End-Source Propagation from SOLAR-ARRAY-2B

Fault-hyp: OPEN-CIRCUIT RELAY-2C
Source Propagation from BUS-2A to SENSOR-2A

Fault-hyp: OPEN-CIRCUIT RELAY-2C
Predicted Current Effect: ZERO Consistent at Sensor SENSOR-2A
Source Propagation from SENSOR-2A to RELAY-2A

Fault-hyp: OPEN-CIRCUIT RELAY-2C
Source Propagation from RELAY-2A to SOLAR-ARRAY-2A

Fault-hyp: OPEN-CIRCUIT RELAY-2C
End-Source Propagation from SOLAR-ARRAY-2A

Fault-hyp: Open-Circuit RELAY-2C
Sink Propagation from RELAY-2C to SENSOR-2C

Fault-hyp: OPEN-CIRCUIT RELAY-2C
Predicted Current Effect: ZERO Consistent at Sensor SENSOR-2C
Sink Propagation from SENSOR-2C to BUS-2B

Fault-hyp: OPEN-CIRCUIT RELAY-2C
Sink Propagation from BUS-2B to RELAY-2E

Fault-hyp: OPEN-CIRCUIT RELAY-2C
Sink Propagation from RELAY-2E to SENSOR-2E

Fault-hyp: OPEN-CIRCUIT RELAY-2C
Predicted Current Effect: ZERO Consistent at Sensor SENSOR-2E
Sink Propagation from SENSOR-2E to REGULATOR-2A

Fault-hyp: OPEN-CIRCUIT RELAY-2C
Sink Propagation from REGULATOR-2A to RELAY-2F

Fault-hyp: OPEN-CIRCUIT RELAY-2C
Sink Propagation from RELAY-2F to SENSOR-2F

Fault-hyp: OPEN-CIRCUIT RELAY-2C
Predicted Current Effect: ZERO Consistent at Sensor SENSOR-2F
Sink Propagation from SENSOR-2F to BUS-2C

Fault-hyp: OPEN-CIRCUIT RELAY-2C
Sink Propagation from BUS-2C to RELAY-2H

Fault-hyp: OPEN-CIRCUIT RELAY-2C
Sink Propagation from RELAY-2H to SENSOR-2G

Fault-hyp: OPEN-CIRCUIT RELAY-2C
Predicted Current Effect: ZERO Consistent at Sensor SENSOR-2G
Sink Propagation from SENSOR-2G to BUS-2D

Fault-hyp: OPEN-CIRCUIT RELAY-2C
Sink Propagation from BUS-2D to RELAY-2H

Fault-hyp: OPEN-CIRCUIT RELAY-2C
Sink Propagation from RELAY-2H to LOAD-2H

F1

6

Propagation from BUS-2A to SENSOR-2A

Fault Hypothesis RESISTIVE-SHORT-CIRCUIT at SOLAR-ARRAY-2B

Predicted Effect Is Inconsistent at Sensor SENSOR-2A

redicted Value: HIGH

isor Value: ZERO

ng All Initial Fault Hypotheses:

EN-CIRCUIT SOLAR-ARRAY-2A

SISTIVE-SHORT-CIRCUIT SOLAR-ARRAY-2A

EN-CIRCUIT SOLAR-ARRAY-2B

SISTIVE-SHORT-CIRCUIT SOLAR-ARRAY-2B

EN-CIRCUIT RELAY-2C

EN-CIRCUIT BUS-2A

ng Final Fault Hypotheses:

PEN-CIRCUIT RELAY-2C

PEN-CIRCUIT BUS-2A

SENSOR-32
Voltage: 33.124816
ed Voltage: 0.0
Voltage: NORMAL

1 Current: 0.0
ed Current: 0.0
Current: NORMAL

s at SENSOR-22
1 Voltage: 33.437412
ed Voltage: 0.0
Voltage: NORMAL

1 Current: 0.0
ed Current: 0.0
Current: NORMAL

s at SENSOR-12
1 Voltage: 33.437412
ed Voltage: 0.0
Voltage: NORMAL

1 Current: 0.0
ed Current: 0.0
Current: NORMAL

SENSOR-36
1 Voltage: 0.0
ed Voltage: -0.0300024
Voltage: NORMAL

1 Current: 0.0
ed Current: -0.0300024
Current: NORMAL

C-: F-9

6

Normal Voltage: 0.9374978
 Faulted Voltage: 0.0
 Qual Voltage: NORMAL

Normal Current: 0.007056
 Faulted Current: 0.0
 Qual Current: NORMAL

Readings at SENSOR-3A

Normal Voltage: 0.9374978
 Faulted Voltage: 0.0
 Qual Voltage: NORMAL

Normal Current: 0.0
 Faulted Current: 0.0
 Qual Current: NORMAL

Readings at SENSOR-2F

Normal Voltage: 30.312422
 Faulted Voltage: 0.0
 Qual Voltage: ZERO

Normal Current: 2.6387118
 Faulted Current: 0.0
 Qual Current: ZERO

Readings at SENSOR-2E

Normal Voltage: 33.740012
 Faulted Voltage: 0.007056
 Qual Voltage: ZERO

Normal Current: 2.6387118
 Faulted Current: 0.007056
 Qual Current: ZERO

Readings at SENSOR-2C

Normal Voltage: 30.31241
 Faulted Voltage: 0.0
 Qual Voltage: ZERO

Normal Current: 2.6380008
 Faulted Current: 0.0
 Qual Current: ZERO

Readings at SENSOR-2D

Normal Voltage: 33.740012
 Faulted Voltage: 0.0
 Qual Voltage: ZERO

Normal Current: 0.0
 Faulted Current: 0.0
 Qual Current: NORMAL

Readings at SENSOR-2B

Normal Voltage: 30.24001
 Faulted Voltage: 0.0
 Qual Voltage: NORMAL

11

Normal Current: 1.2885278
Faulted Current: 0.0
Qual Current: ZERO

Readings at SENSOR-2A

Normal Voltage: 36.24881
Faulted Voltage: 0.007858
Qual Voltage: NORMAL

Normal Current: 1.3671838
Faulted Current: 0.007858
Qual Current: ZERO

Readings at SENSOR-1F

Normal Voltage: 29.988824
Faulted Voltage: 2.008778
Qual Voltage: NORMAL

Normal Current: 2.008778
Faulted Current: 2.008778
Qual Current: NORMAL

Readings at SENSOR-1E

Normal Voltage: 34.062412
Faulted Voltage: 2.008778
Qual Voltage: NORMAL

Normal Current: 2.148432
Faulted Current: 2.008778
Qual Current: NORMAL

Readings at SENSOR-1C

Normal Voltage: 36.31241
Faulted Voltage: 1.06312
Qual Voltage: NORMAL

Normal Current: 1.06312
Faulted Current: 1.06312
Qual Current: NORMAL

Readings at SENSOR-1D

Normal Voltage: 34.062412
Faulted Voltage: 0.106312
Qual Voltage: NORMAL

Normal Current: 0.106312
Faulted Current: 0.106312
Qual Current: NORMAL

Readings at SENSOR-1B

Normal Voltage: 36.24881
Faulted Voltage: 0.878884
Qual Voltage: NORMAL

Normal Current: 0.878884
Faulted Current: 0.878884
Qual Current: NORMAL

APPENDIX C

FIES II Software Design Specification

APPENDIX - C

VIES II Design Specification

Table of Contents

- I. System Overview
 - A. Initialization
 - B. Fault Isolation
- II. Microprocessor System Software Modular Profile
 - A. Hierarchical decomposition
 - B. Software Module descriptions
- III. Symbolics System Software Modular Profile
 - A. Hierarchical decomposition
 - B. Software Module descriptions
- IV. Symbolics Application expert system Software Modular Profile
 - A. Hierarchical decomposition
 - B. Software Module descriptions
- V. Interface Description
 - A. Overview
 - B. Transmission senders
 - C. Transmission receivers
 - D. Data transmission formats
 - E. Command functions summary

I. System Overview

This section is a high level description of the normal operation of the FIES system in terms of data flow across the interfaces of the system. For the purposes of this description four interfaces have been identified. These interfaces are breadboard to microprocessor, microprocessor to symbolics, symbolics to microprocessor and microprocessor to breadboard.

There are two distinct processing phases in the FIES system. The first phase is initialization phase which begins with breadboard, microprocessor and symbolics power up, includes user selection and download of an initial configuration for the breadboard and concludes when the microprocessor notifies the Symbolics that the breadboard has achieved steady state configuration. The second phase begins with fault insertion into a steady state configuration and concludes with the successful isolation and correction of a fault by the expert system.

A. Initialization

1.0 Power up microprocessor and breadboard

Power is applied simultaneously to the microprocessor and the breadboard by throwing the "power on" circuit breaker on the main control panel. This results in self test by both the microprocessor and B/B. Following successful self test the breadboard is placed in a 'safe' default configuration.

2.0 Microprocessor Initial Program Load

Following successful self test, control is transferred to a command file that loads the microprocessor FIES application software. Interrupts from the breadboard are enabled and the microprocessor begins handling interrupts from the breadboard and storing data in memory tables. This data acquisition cycle repeats itself every 3 milliseconds. Interrupts from the Symbolics are also enabled.

3.0 Power Up Symbolics

Power on to the Symbolics results in self test by the Symbolics.

4.0 Symbolics system Software Initial Program Load

Following successful self test, Symbolics system software is loaded into memory. Communication between the Symbolics and the microcomputer is now established and is confirmed by a control sequence handshake.

5.0 Initial Configuration Load

Following successful Symbolics IPL, the user is prompted with a configuration load option menu. Following selection of a configuration option, the Symbolics downloads the selected configuration to the microprocessor. Interrupts from the microprocessor are enabled and the Symbolics waits for the microprocessor upload of the steady state data values.

6.0 Microprocessor Configuration Load

Configuration load from the Symbolics interrupts the microprocessor. The interrupt is handled by an Interrupt Service Request and control is passed to a program that sets the breadboard to the initial configuration and records the initial configuration and the error band data in memory tables.

7.0 Microprocessor Steady State Detect

The microprocessor then begins sampling the breadboard a 3 ms. intervals until steady state is detected. When steady state is detected the steady state values are uploaded to the Symbolics. Following this upload the microprocessor enables interrupts from the Symbolics and continues to sample data from the breadboard.

8.0 Symbolics Steady State Detect

A steady state condition upload from the microprocessor results in an interrupt at the Symbolics. An communication handler reads the data and places the data in a global area of memory. A message is sent to the expert system that the steady state condition has been received. The expert reads the steady state values, performs preliminary processing and goes to sleep. Interrupts from the microprocessor are enabled. A message is output to the terminal indicating that the initial configuration has been successfully initialized and that the system is ready for fault insertion. This concludes initialization processing.

B. Fault Isolation

1.0 Fault Insertion

The user determines which faults are applicable to the current configuration by analyzing the LED display and the system architecture map on the front panel. The user inserts a fault into the steady state configuration, using the front panel of the breadboard.

2.0 Microprocessor Fault Detection

The microprocessor is currently sampling nominal conditions on the breadboard a 3 ms. intervals. When a data point is sampled outside the error tolerance specified by the error bands, the microprocessor uploads the exception values to the Symbolics. This is defined to be an unsolicited data transfer. Following an unsolicited data transfer, the microprocessor disables interrupts from the breadboard, enables interrupts from the Symbolics. If the Symbolics does not respond within 5 ms. a watchdog timer fires, triggering a routine that places the breadboard into a "safe" condition. The error band(s) violated are then in "Emergency" condition.

3.0 Symbolics Fault Detection (Unsolicited Data Transfer)

An upload by the microprocessor to the Symbolics interrupts the Symbolics. A service routine handles the interrupt and places the data into global memory. A message is sent to the expert system that an exception has occurred. This triggers the expert to read the data and to begin fault evaluation.

4.0 Symbolics requests for data (solicited request for data)

The expert may require further data from the microprocessor concerning the status of the breadboard. In this event, the Symbolics sends an interrupt to the microprocessor. The Symbolics then waits on a response VIA RS232 XMIT from the microprocessor. The microprocessor handles the RS232 interrupt, interprets the requests, reads the data from A/D and sends an interrupt VIA RS232 XMIT to the Symbolics. On the Symbolics side an ISR handles the interrupt, places the data in a global area of memory and sends a message to the expert that the data has been received.

5.0 Symbolics requests for controls (Solicited request for control)

The expert may require controls on its behalf by the microprocessor. The sequence of events for requesting a control is the same as that described above. The control is performed by the microprocessor.

6.0 Evaluation loop until fault determination

The loop described by 3.0-5.0 continues until fault isolation/correction.

II. Microprocessor system software modular profile

A. Hierarchical decomposition

- 1.0 Self test
- 2.0 Data acquisition
 - 2.1 Combination I/O board handler
 - 2.2 A/D board handler
- 3.0 Main driver
 - 3.1 Emergency band violation handler
 - 3.2 Caution/warning band handler
 - 3.3 Command interpreter
 - 3.3.1 Request for data handler
 - 3.3.1.1 Micro computer transmission handler
 - 3.3.2 Request for control handler
 - 3.3.2.1 Microcomputer relay control handler
 - 3.3.3 Request for initial configuration handler

B. Software Module Descriptions

1.0 Module name: Self Test

a. Responsibilities

Check safe breadboard operation following power up.

b. Description

This program will be executed on power-up or when the user switches the system into self test from the front panel.

This program is interrupt driven by the CPU board timer on level 4. It is also resident in memory with the main program, but totally reconfigures the system. If the breadboard is to be re-started as a slave to the expert system, the main program must be re-entered from the top.

The program re-configures the 3 mSec clock CPU board to be 2 seconds. With every 2 second IRQ, the program closes another relay (according to a predefined configuration list) and limit checks the results (also predefined). The relays are closed in a direction from the power modules towards the loads, allowing power to be applied methodically to the system. The 2 second period allows the user time to watch the process (specifically the power output needles on the H.P. power supplies).

c. Subordinate routines

None

d. Implementation

8086 assembler

2.0 Data Acquisition

2.1 Module name: Combination I/O Board Handler

a. Responsibilities:

Service Main Control Panel

b. Description

The function of this module is to display current values to the 24 character LED and to handle faults inserted into the breadboard from the control panel. There are 4 sources of interrupts that must be handled. These sources and their lit positions to be polled are shown below.

1 ms. timer for switch debounce
(DB0)

Gas Discharge Display - RCVR Empty
(DB1)

Gas Discharge Display - XMIT Empty
(DB2)

User Repeat Function
(DB7)

This routine executes every 1 millisecond, provided no higher interrupt levels are currently being serviced. Its execution time will normally be extremely short, since the primary responsibility is to check if any of the main panel switch settings have been changed.

c. Subordinate routines

None

d. Implementation

8086 Assembler

a. Responsibilities

Service A/D Board Conversions

The sampling Timer on the CPU board is the only source of interrupts on level 4.

b. Description

Although each board (there are 4) is capable of giving an IRQ when it has completed the conversion process, we choose to use an external timer. The rationale is as follows:

- o An A/D conversion is composed of the following delay elements: channel select, analog mux delay, A/D conversion settling time, digital gain control. The last two elements are of variable delay and may not even be one on some boards. If each board supplied its own IRQ, we may become "out of sync" in our sampling.
- o If we choose to consider handling power system faults which decay with time, we will need to dynamically adjust our sampling rate. The use of a single programmable timer to do this allows us this flexibility.

The timer is therefore set to approximately 3 milliseconds. At the timer IRQ, the handler starts at the top of the list of measurements and does limit checking on the fly. There is more than enough time to complete the entire list of measurements (even if the other IRQ handlers interrupt this program) prior to the next timer IRQ.

Since the boards are not individually IRQ driven, care must be taken to insure that good measurements are read, and that the loop timing is minimized. The following sequence of events should be observed:

1. Select a channel of A/D Board 1 and command the conversion to start.
2. Do the same for Boards 2, 3, 4.
3. Poll Board #1 until conversion complete and read measurement.
4. Select a new channel on Board 1 and restart conversion.
5. Limit check old Board 1 results.
6. Perform steps 3,4,5 rotating through the sequence Board 2, 3, 4, 1, 2, 3, 4, . . . etc.

The total conversion time is only on the order of 25 microseconds, so approximately 125 steps of the 8086 10MHz clock need to be stepped off. This is approximately 15 assembly level instructions with which to do limit checking. The limit checking process will require on the order of 25 assembly level instructions. Therefore, the limit checking is somewhat buried some of checking time in the conversion time. There are 4 boards which require 16 measurements each.

$4 \times 16 \times 25 \text{ microseconds} = 1.60 \text{ milliseconds}$, so the 3 millisecond timing loop is adequate, leaving 1.4 milliseconds for the non-buried limit checking and any communications interrupts. The 3 milliseconds represents the smallest possible sampling interval.

c. Subordinate routines

None

d. Implementation

8086 assembler

3.0 Module name: Main driver

a. Responsibilities

Initialization of breadboard to steady state following power up. Error flags detection during normal operations. Should an error be detected, it is the responsibility of the main program to activate the appropriate error handlers.

b. Description

The main program will place the breadboard in a safe state following power up. This includes opening all of the relays and placing the system in a stable configuration. Main will then wait on interrupts. Interrupts will be enabled from the breadboard, in the context of a data acquisition cycle, on the RS232 port, in the context of experts systems requests from the microprocessor. Interrupts from the Symbolics have the higher priority. When such an interrupt is detected, control is passed to the command interpreter, described below. An interrupt from the breadboard triggers the error/caution/warning detection cycle, performed by the routines described in sections.

Main will run in one of two states. The first state is monitor steady state configuration mode. This occurs only following initial configuration. Here, main waits to detect a steady state. Upon steady state detection, a complete set of node information is uploaded to the Symbolics.

The second state is fault detection scan. Here main handles interrupts from the breadboard and passes control to subordinate routines for emergency/warning/caution detection processing.

c. Subordinate Programs:

3.1 Emergency band violation handler

3.2 Caution/warning band handler

3.3 Command Interpreter

d. Implementation

8086 assembler

3.1 Module name: Emergency band violation handler (acts as a software circuit breaker)

a. Responsibilities

Detect and flag voltage and current measurements out of range and set relays in order to ensure safe breadboard operation.

b. Description

This program is activated when a node has violated the EMERGENCY board limit for either current or voltage. The routine is responsible for determining that the measurement is not spurious, and that the error condition is stable. This routine commands the opening of the relay which controls the node(s) is the watchdog timer fires. Following a control initiated by this module, the module should send a message to the expert system that a relay has been forced open or closed.

c. Subordinate routines

Microcomputer transmission handler

d. Implementation

8086 assembler

3.2 Module name: Caution/warning band handler

a. Responsibilities

Detect and flag current and voltage out of range

b. Description

This program is activated when a caution or warning band has been violated and there exists no EMERGENCY band violation anywhere in the system. This routine is responsible for building the communication stream to be sent to the Symbolics, upon determination of an error condition.

c. Subordinate routines

Microcomputer transmission handler

d. Implementation

8086 assembler

3.3 Module name: Command Interpreter

a. Responsibilities

Control is passed to this routine upon interruption of Main by the Symbolics. This routine must handle the message, parse the command byte and pass control to the appropriate routine.

b. Description

This module is a command interpreter. Valid commands are detailed in the interface software description. Upon interrupt from the Symbolics the module places the message in an input buffer and parses the command byte. If the command is valid the starting address and ending address of the data in memory are passed to the appropriate routine. The command interpreter then returns to a read and wait state, awaiting further interrupts from the Symbolics.

c. Subordinate routines

Request for data handler

Request for control handler

Request for initial configuration handler

d. Implementation

8086 assembler

3.3.1 Module name: Request for data handler

a. Responsibilities

Retrieve and format data for transmission to the Symbolics

b. Description

Control passes to this module from the command interpreter. This routine must parse the request for data command, determine for which nodes it must gather data, read the data from memory, format the data for transmission and pass the starting and ending address of the stream to the transmission handler.

c. Subordinate routines

Microcomputer transmission handler

d. Implementation

8086 assembler

III. Symbolics system software modular profile

A. Hierarchical decomposition

1.0 Expert system command interpreter/receiver

- 1.1 Unsolicited data transfer handler
- 1.2 Solicited data transfer handler
- 1.3 Unsolicited relay transfer handler
- 1.4 Steady state values handler

2.0 Expert system communication sender

- 2.1 Request for data from microprocessor
- 2.2 Request for control by microprocessor
- 2.3 Request for configuration download

B. Software module descriptions

1.0 Module name: Expert system command interpreter receiver (ESCR)

a. Responsibilities

Handle transmissions from microprocessor

b. Description

The ESCR will handle interrupts from the microprocessor, validate the input stream, store the data in memory, interpret the command byte of the header record and, based on the value of the command byte, transfer control to the appropriate subordinate function.

c. Subordinate functions

Unsolicited data transfer handler

Solicited data transfer handler

Unsolicited relay transfer handler

Steady state values handler

d. Implementation

Lisp machine process

1.1 Module name: Unsolicited data transfer handler

a. Responsibilities

Interface between ESCR and expert system

b. Description

When ESCR detects and unsolicited data transfer, control is transferred to this function. The function processes the data, formats it for compatibility with the expert system, transfers the data into memory and notifies the expert system that the transfer has occurred.

c. Subordinate routines

Expert system

d. Implementation

Lisp function, called from ESCR.

1.2 Module name: Solicited data transfer handler

a. Responsibilities

Interface between ESCR and expert system

b. Description

When ESCR detects an solicited data transfer, control is transferred to this function. The function processes the data, formats it for compatibility with the expert system, transfers the data into memory and notifies the expert system that the transfer has occurred.

c. Subordinate routines

Expert system.

d. Implementation

Lisp function, called from ESCR.

1.3 Module name: Unsolicited relay transfer handler

a. Responsibilities

Interface between ESCR and expert system

b. Description

When ESCR detects an unsolicited relay transfer, control is transferred to this function. The function processes the data, formats it for compatibility with the expert system, transfers the data into memory and notifies the expert system that the transfer has occurred.

c. Subordinate routines

Expert system

d. Implementation

Lisp function, called from ESCR.

1.4 Module name: Steady state values handler

a. Responsibilities

Interface between ESCR and expert system

b. Description

When ESCR detects and steady state value transfer, control is transferred to this function. The function processes the data, formats it for compatibility with the expert system, transfers the data into memory and notifies the expert system that the transfer has occurred.

c. Subordinate routines

Expert system

d. Implementation

Lisp function, called from ESCR.

2.0 Module name: Expert system communication sender (ECS)

a. Responsibilities

Send transmissions to microprocessor

b. Description

The ECS will download data streams to the microprocessor.

c. Subordinate functions

None

d. Implementation

Lisp function, called by routines sending data to the microprocessor.

2.1 Module name: Request for data from microprocessor

a. Responsibilities

Format requests for data from expert system to microprocessor

b. Description

This function will be called by the expert system. The expert system will specify the data items for which it requests information. This routine will format the request, include the transmission header information and pass control to the ESCS for transmission of the output stream.

c. Subordinate functions

ESCS

d. Implementation

Lisp function, called from expert system.

2.2 Module name: Request for control by microprocessor

a. Responsibilities

Format requests for controls from expert system to microprocessor

b. Description

This function will be called by the expert system. The expert system will specify the relays for which it requests controls. This routine will format the request, include the transmission header information and pass control to the ESCS for transmission of the output stream.

c. Subordinate functions

ESCS

d. Implementation

Lisp function, called from expert system.

2.3 Module name: Request for configuration download

a. Responsibilities

Format requests for initial configuration by microprocessor

b. Description

This function will be called from the user interface. The function will be passed the name of the file containing the initial configuration for the breadboard. This includes relay-code mappings, current-voltage mappings and initial warning and caution error bands. This routine will format the request, include the transmission header information and pass control to the EDCS for transmission of the output stream.

c. Subordinate functions

EDCS

d. Implementation

Lisp function, called from user interface.

3.3.1.1 Module name: Microcomputer Transmission Handler

a. Responsibilities

Send formatted data streams to the Symbolics

b. Description

This module called as a subroutine to the main program, and other service routines needing to transmit data to the expert system. The message to be transmitted will be placed in an input buffer somewhere in the memory of the microcomputer. The starting and ending addresses of the stream to be transmitted will be passed to the transmission handler. The program will check for valid protocol and upload the stream to the Symbolics.

c. Subordinate routines

None

d. Implementation

8086 assembler

3.3.2 Module name: Request for control handler

a. Responsibilities

Perform controls on behalf of Symbolics

b. Description

Control passes to this module from the command interpreter. This routine must parse the request for controls(s) command, determine for which relays it must execute controls and pass the relay numbers to the microcomputer control handler.

c. Subordinate routines

Microcomputer relay control handler

d. Implementation

8086 assembler

3.3.2.1 Module name: Microcomputer Relay Control Handler

a. Responsibilities

Control Relays

b. Description

This program is non-IRQ driven and is called as a subroutine to the main program, and other service routines needing to alter the relay settings.

The board requires a 48 bit mask register to enable/disable the system relays. The board also has an override switch which disables all relays in the event of system power up or emergencies.

The board handler processes a list of relay numbers which are to be turned on. The handler constructs the 48 bit mask to the board in 16 bit quantities.

c. Subordinate routines

None

d. Implementation

8086 assembler

3.3.3 Module name: Request for initial configuration handler

a. Responsibilities

Perform initialization per instructions contained in configuration download message from Symbolics.

b. Description

Control passes to this module from the command interpreter. This routine must initialize the breadboard to the requested state and initialize data tables in microcomputer memory. These tables include error band values and node-relay mappings. This program will return control to Main and set the monitor initial steady state flag in Main.

c. Subordinate routines

Microcomputer relay control handler

d. Implementation

8086 assembler

IV. Symbolics application expert system software modular profile

A. Hierarchical decomposition

1.0 User interface

2.0 Configuration initialization

3.0 Fault-data initialization

4.0 Hypothesis Generation

5.0 Hypothesis mediation

6.0 Correction

7.0 Explanation

B. Software module descriptions

1.0 Module name: User interface

a. Responsibilities

Allow user to select an existing configuration or set up an initial configuration

b. Description

This program will be implemented in Lisp or ART. It will access a small data base of existing configurations. It will also allow for user defined configurations. Once a configuration has been defined, it will be downloaded to the microsystem. Ideally, this will be an interactive module that will incorporate the ART graphics package.

c. Subordinate functions

Request for configuration download.

d. Implementation

ART and Lisp on the Symbolics.

2.0 Module name: Configuration initialization

a. Responsibilities

Establish the system configuration description and the error band data within the ART environment.

b. Description

This program will be implemented in ART. The circuit components and nodes will be predefined. The operations to be implemented will be: (1) determination of configuration dependent source/sink relationships; and (2) insertion of configuration dependent error bands.

c. Subordinate functions

Notice of completion sent to interface/user. System ready to insert fault.

d. Implementation

ART module.

3.0 Module name: Fault-data initialization

a. Responsibilities

Enter data incurred after a fault was inserted.

b. Description

This program will be implemented in ART. The main function will be to enter faulted data into the ART representation of the system.

c. Subordinate functions

None.

d. Implementation

ART module

4.0 Module name: Hypothesis generation

a. Responsibilities

Generate hypotheses including: fault type and fault location

b. Description

This module will be implemented in ART. It will be based on: (1) qualitative reasoning; (2) source/sink relationships; (3) fault descriptions and (4) a modular representation of the power system.

c. Subordinate functions

None

d. Implementation

ART module.

5.0 Module name: Hypothesis mediation

a. Responsibilities

Prune off incorrect hypotheses.

b. Description

This module will be implemented using ART's viewpoint facility. The techniques used will be both causal and hieristic-based. In specific cases, directives to flip relays will be sent to the breadboard.

c. Subordinate functions

Directives to change the relay configuration and return the effected data.

d. Implementation

ART module.

6.0 Module name: Correction

a. Responsibilities

If possible, reconfigure the system to work around the fault. Otherwise make proper recommendations to the user.

b. Description

This module will be implemented in ART. It will make use of heuristic and causal reasoning techniques when applicable. It will send relay change directives to the breadboard when necessary. It will hypothesize a correction, analyze it, and request it.

c. Subordinate functions

Relay change directives will be sent to the breadboard.

d. Implementation

ART module.

7.0 Module name: Explanation

a. Responsibilities

Report fault and explanation to the user.

b. Description

Report the fault and a trace of the reasoning path followed to arrive at the decision. This may allow for limited user interaction, and may incorporate graphics into the explanation facility.

c. Subordinate functions

None

d. Implementation

ART module.

V. Interface description

A. Overview

In this section we define the interfaces in term of sender-receiver relationships in the system. There are 4 sender relationships and 4 receiver relationships. Sender relationships are breadboard to microprocessor, microprocessor to Symbolics, Symbolics to microprocessor and microprocessor to breadboard. Receivers are microprocessor from breadboard, Symbolics from microprocessor, microprocessor from Symbolics and breadboard from microprocessor.

Examination of these sender-receiver relationships allows a framework for defining the exact data that must be transferred across any given interface and also allow the identification of the software modules that must be constructed in the interface software.

B. Transmission senders

1.0 Breadboard to microprocessor

1.1 Requirement: Data generation

The breadboard will generate complete data sets at a 3ms. frequency. Data acquisition by the microprocessor will be interrupt driven. The microprocessor must handle interrupts, perform limit checks and store the data within the 3 ms. time frame.

2.0 Microprocessor to Symbolics

2.1 Requirement: Unsolicited data transfers

The microprocessor must detect and report exceptions relative to the initial configuration error bands. This detection must occur within the 3 ms. data acquisition cycle described above.

2.2 Requirement: Solicited data transfers

The microprocessor must send data to the Symbolics following a request for data.

2.3 Requirement: Report unsolicited forced controls

The microprocessor must send data to the Symbolics following a forced control. A forced control is initiated by the microprocessor in order to prevent board failure. This will occur only under extraordinary circumstances. In this respect the microprocessor acts as a software circuit breaker.

2.4 Requirement: Steady state data value upload

The microprocessor will send the steady state data values to the Symbolics following configuration load and steady state detect.

3.0 Symbolics to microprocessor

3.1 Requirement: Configuration load

The Symbolics must send the initial configuration to the microprocessor.

3.2 Requirement: Solicited requests for data

The Symbolics will send requests for data to the microprocessor.

3.3 Requirement: Solicited request for control

The Symbolics will send requests for controls to the microprocessor.

4.0 Microprocessor to breadboard

4.1 Requirement: Set safe configuration

The microprocessor must initialize the breadboard to a safe configuration following power on self test.

4.2 Requirement: Set initial configuration

The microprocessor must initialize the breadboard to the initial configuration requested by the user.

4.3 Requirement: Set relays on request for control

The microprocessor must respond to requests for control from the expert.

C. Transmission receivers

1.0 Microprocessor from breadboard

1.1 Requirement: Data Acquisition

The microprocessor must be capable of handling interrupt driven data acquisition at the rate of 3ms. per cycle.

2.0 Symbolics from microprocessor

2.1 Requirement: Handle unsolicited data transfers

The Symbolics must handle interrupts from the microprocessor, identify unsolicited data transfers and pass the data to the expert system.

2.2 Requirement: Handle solicited data transfers

The Symbolics must handle interrupts from the microprocessor, identify solicited data transfers and pass the data to the expert system.

2.3 Requirement: Handle unsolicited control report

The Symbolics must handle interrupts from the microprocessor, identify unsolicited control reports and pass the data to the expert system.

2.4 Requirement: Handle steady state value table upload

The Symbolics must handle interrupts from the microprocessor, identify steady state table uploads and pass the data to the expert system.

3.0 Microprocessor from Symbolics

3.1 Requirement: Handle request for configuration load

The microprocessor must handle interrupts from the Symbolics, identify request for a configuration load and transfer control to the routine that performs configuration load.

3.2 Requirement: Handle request for data (solicited)

The microprocessor must handle interrupts from the Symbolics, identify a request for data and transfer control to the routine that performs solicited request for data.

3.3 Requirement: Handle request for control (solicited)

The microprocessor must handle interrupts from the Symbolics, identify a request for control and transfer control to the routine that handles solicited request for control.

4.0 Breadboard from microprocessor

4.1 Requirement: Set relays

The breadboard must respond to configuration set commands issued by the microprocessor.

D. Data transmission formats

1.0 Protocol description

1.1 Header records

This section describes header records for data transmission formats. These header records will be used to identify the type of message that is being sent and to trigger the appropriate receiver function on the receiver side of the interface. Record formats are described by relative byte address in the record.

1.2 Header record format

Command byte	0
Checksum	1-2

1.3 Trailer records

Trailer records are used to indicate end of transmission.

1.4 Trailer record format

End of transmission	0
---------------------	---

Always '*'

2.0 Transmission formats

A transmission, including headers, trailers and the description of the transmitted data is described for each of the messages in the system.

2.1 Data generation by breadboard

2.2 Microprocessor to symbolics

2.2.1 Unsolicited data transfer

Command byte	0	always = 'u'
Checksum	1-2	16 bit integer
Node id	3-4	16 bit integer
Error type	5	
' ' = N/A		
'n' =		
'c' = caution		
'w' = warning		
'e' = error		
Error direction	6	
' ' = N/A		
'h' = above limit		
'l' = below limit		
Voltage	7-12	
Current	13-19	

Repeating groups, bytes 3-19 until trailer record is encountered (see trailer record, end of transmission).

2.2.2 Solicited data transfer

Command byte	0	always 's'
(same as 3.2.1.1)		

2.2.3 Unsolicited relay status: relay forced closed

Command byte	0	always 'r'
Relay id	1-2	
Relay status	3	
'o' = open		
'c' = closed		
'f' = forced close		

Repeating groups, bytes 1-3 until trailer record is encountered (see trailer record, end of transmission).

2.2.4 Steady state table upload

Command byte (same as 3.2.1.1)	0	always 'z'
-----------------------------------	---	------------

2.3 Symbolics to microprocessor

2.3.1 Configuration load

Command byte	0	always 'i'
Checksum	1-2	16 bit integer
Node id	3-4	16 bit integer
Voltage flag	5	
1 = measure voltage		
0 = don't		
Current flag	6	
Error band low	7-12	
Warning band low	13-18	
Caution band low	19-24	
Error band high	25-30	
Warning band high	31-36	
Caution band high	37-42	

Repeating group of bytes 3-42 until end of transmission

2.3.2 Requests for data transfer (solicited)

Command byte	0	always 'd'
Node id	1-2	

Repeating groups of bytes 1-2 until end of transmission

2.3.3 Requests for control

Command byte	0	always 'c'
Relay id	1-2	
Relay status	3	
'o' = open		
'c' = closed		
'f' = force close		

Repeating groups, bytes 1-3 until trailer record is encountered (see trailer record, end of transmission).

2.3.4 Microprocessor to breadboard

2.3.4.1 Set relays

I. Command function summary

1.0 Microprocessor to symbolics

- 'u' returning unsolicited data
- 's' returning solicited data
- 'r' returning unsolicited relay status
- 'z' returning steady state value table

2.0 Symbolics to microprocessor

- 'i' configuration load
- 'd' request for data
- 'c' request for control

APPENDIX D

FIES Expert System Rules with Translation

ERRORBANDS

```
DefRule Create-Errorbands-Zero-current-Zero-voltage
  (declare (salience 850))
  (sensor-status-num-c ?sensor ?current)
  (test (and (< ?current .15) (< ?voltage 1.3)))
  (Modify
```

```
    (Schema ?sensor
      (normal-current ?current)
      (normal-voltage ?voltage)
      (current-errorband (-1.0 # .16))
      (voltage-errorband (-1 # 1.3))))))
```

"For a given sensor, if its normal current is less than .15 and its voltage is less than 1.3 then its current errorband is -1.0 to .16 and its voltage errorband is from -1 to 1.3."

0 1

```
(DefRule Create-Errorbands-Zero-Current
  (declare (salience 850))
  (sensor-status-num-c ?sensor ?current)
  (test (and (< ?current .15) (not (< ?voltage 1.3))))
  (Modify
```

```
    (Schema ?sensor
      (normal-current ?current)
      (normal-voltage ?voltage)
      (current-errorband (-1.0 # .15))
      (voltage-errorband (-1 1.3 +(?voltage - ?voltage # .1))))))
```

1

```

(DefRule Create-Errorbands-Less-Than-AMP
  (declare (salience 850))
  (sensor-status-num-c ?sensor ?current)
  (sensor-status-num-v ?sensor ?voltage)
  (test (and (not (< ?current .04))(< ?current 1.0) (not (< ?voltage 1.3)))))

(Modify
  (Scheme ?sensor
    (normal-current ?current)
    (normal-voltage ?voltage)
    (current-errorband (-1.0 .04 +(?current - .1) =(?current + .1)))
    (voltage-errorband (-1 1.3 +(?voltage - ?voltage $ .1) =(?voltage + ?voltage $ .1)))))

(DefRule Create-Errorbands
  (declare (salience 850))
  (sensor-status-num-c ?sensor ?current)
  (sensor-status-num-v ?sensor ?voltage)
  (test (and (not (< ?current 1.0)) (not (< ?voltage 1.3)))))

(Modify
  (Scheme ?sensor
    (normal-current ?current)
    (normal-voltage ?voltage)
    (current-errorband (-1.0 .15 =(?current - ?current $ .1) =(?current + ?current $ .1)))
    (voltage-errorband (-1 1.3 =(?voltage - ?voltage $ .1) =(?voltage + ?voltage $ .1)))))

```

P-DESCRIBE-CIRCUIT-2

Rule Power-Source-to-Relay-Current-Flow
 (declare (sentence 1000))

(Schema ?power-source
 (Instance-of Power-Source)
 ?fl (Potential-Sink ?relay))

Schema ?relay
 (Instance-of Relay)
 (Status closed))

(Assert
 Schema ?power-source
 (sink ?relay))

(Assert
 (Schema ?relay
 (source ?power-source)))
 (Retract ?fl))

"If some power source has some relay as a potential sink and the relay is closed then the relay is the sink for the power source."

```

(DefRule Component-to-Component--Current--Flow
  (declare (salience 1000))
  Schema ?source-component
    (Instance-of Component)
    (Source ?)
    (Potential-Sink ?sink-component))
  ?fl (Schema ?sink-component
    (Instance-of Component:Power-Sink))
    (not
      (Schema ?sink-component
        (Instance-of Relay)))
    (Assert
      (Schema ?source-component
        (sink ?sink-component)))
    (Assert
      (Schema ?sink-component
        (source ?source-component)))
    (Retract ?fl))

```

"If some source component is a component of the network and its sink is its potential sink component is in the network then the potential sink is in fact a sink for the source."

```

(DefRule Component-to-Relay-Current-Flow
  (declare (salience 1000))
  (Schema ?source-component
    (Instance of Component)
    (Source ?)
    (Potential-Sink ?sink-component))
  ?fl (Schema ?sink-component
    (Instance of Relay)
    (Status Closed))

  (Rxinit
    (Schema ?source-component
      (Source ?)))

  (Assert
    (Schema ?source-component
      (sink ?sink-component)))

  (Assert
    (Schema ?sink-component
      (source ?source-component))
    (Retract ?fl))

```

"If a source has both a relay and a nonrelay sink, consider the nonrelay sink to be the sink."

ORIGINAL PAGE IS
OF POOR QUALITY.

```
(DefRule Power-Source-to-Component-Source-Sensor
  (declare (salience 990))
  (Schema ?power-source)
  (Instance-of Power-Source)
  (Sink ?sink-component))
```

```
(Schema ?sink-component
  (Instance-of Component))
```

```
(Assert
  (Schema ?sink-component
    (Source-Sensor none)))
```

"If the source for a sink is a power source, then the sink has no source sensor."

```
(DefRule Component-to-Component-Source-Sensor
  (declare (salience 980))
  (Schema ?source-component
    (Instance-of Component)
    (Source-Sensor ?source-sensor)
    (Sink ?sink-component))
  (Schema ?sink-component
    (Instance-of Component))
  (not
    (Schema ?sink-component
      (Instance-of Sensor:Power-Sink))))
```

```
(Assert
  (Schema ?sink-component
    (source-sensor ?source-sensor)))
```

"For a given source, if it's sink is not a sensor or a power sink then the source sensor for the sink is the source's sensor."


```

(DefRule Component-to-Sensor-to-Component-Sink-Sensor-Source-Sensor
  (declare (salience 970))
  (Scheme ?source-component
    (Instance-of Component)
    (Source-Sensor ?)
    (Sink ?sensor))
  (Scheme ?sensor
    (Instance-of Sensor)
    (Sink ?sink-component))
  (Scheme ?sink-component
    (Instance-of Component))
  (Assert
    (Scheme ?source-component
      ?sink-sensor ?sensor))
  (Assert
    (Scheme ?sink-component
      (source-sensor ?sensor))))

```

"This rule is assuring that the schemes for the sensors for sources and sinks in fact say that they are the sensors for the sources and sinks."

```

(DefRule Component-toPower-Sink-Source-Sensor-Sink-Sensor
  (declare (salience 970))
  (Schema ?source-component
    (Instance-of Component)
    (Source-Sensor ?source-sensor)
    (Sink ?power-sink))
  (Schema ?power-sink
    (Instance-of Power-Sink))
  (Assert
    (Schema ?source-component
      (Sink-Sensor none)))
  (Assert
    (Schema ?power-sink
      (source-sensor ?source-sensor))))

```

"If the sink for a given source is a power sink, then the source sensor is the sensor for the source but there is no sink sensor."

```

(DefRule Component-to-Component-Sink-Sensor
  (declare (salience 960))
  (Schema ?sink-component
    (Instance-of Component
      (Sink-Sensor ?sink-sensor)
      (Source ?source-component)))
  (not
    (Schema ?sink-component
      (Instance-of Power-Sink)))
  (Schema ?source-component
    (Instance-of Component:Power-Source))
  (not
    (Schema ?source-component
      (Instance-of Sensor))))
(Assert
  (Schema ?source-component
    (sink-sensor ?sink-sensor))))

```

"If the source for a component is not a sensor and the sink is not a power sink then the sink sensor is the sensor for the sink component."

```

(DefRule Assign-I-RQ-source
  (declare (salience 950))
  (Schema ?component
    (Instance-of Component)
    (I-Rq ( (+ $?source-1 ) ( + $?sink-1 )))
    (Source ?source))
  (not
    (Schema ?component
      (I-Rq (( + $? ?source $?) ?))))
  (Modify
    (Schema ?component
      (I-Rq (( + $?source-1 ?source) ( + $?sink-1 )))))

```

"This rule builds a list of sources for a component and stores the list in I-RQ."

```
(DefRule Assign-I-RQ-sink
```

```
  (declare (salience 940))
  (Scheme ?component
    (Instance-of Component)
    (I-Rq ( $?source-i) (+ $?sink-i)))
  (not
    (Scheme ?component
      (I-Rq (? (+ $? ?sink $?))))))
  (Modify
    (Scheme ?component
      (I-Rq ( (+ $?source-i) (+ $?sink-i ?sink)))))
```

"This rule builds a list of sinks."

```
(DefRule Assign-Multiple-Sources
  (declare (salience 930))
  (Scheme ?bus
    (Instance-of bus)
    (Multiple-Sources no)
    (Source ?i)
    (Source ?2&~?i))
```

```
(Modify
  (Scheme ?bus
    (Multiple-Sources yes))))
```

"If the scheme for a bus indicates that it does not have multiple sources, but in fact it has multiple sources; then modify the scheme to show that it does have multiple sources."

ORIGINAL PAGE IS
OF POOR QUALITY

```
(DefRule Assign-Multiple-Sink-
(Declare (Salience 910))
(Schema ?bus
  (Instance-of bus)
  (Multiple-Sinks no)
  (Sink ?1)
  (Sink ?2&~?1)))
```

```
(Modify
  (Schema ?bus
    (multiple-Sinks yes))))
```

"Same as above for sinks."

```
(DefRule Assign-Coupled
(Declare (Salience 920))
(Schema ?bus
  (Instance-of bus)
  (Multiple-Source yes)
  (Source-Sensor ?source-sensor))
(Schema ?source-sensor
  (Instance-of Sensor)
  (Coupled-Sink no)))
```

```
(Modify
  (Schema ?source-sensor
    (Coupled-Sink yes))))
```

"If a bus has multiple sources, modify the schema of the source sensor for the to show that the source has a coupled sink."


```

(DefRule Find-Potential-Relay-Sinks
  (Declare (allience 905))
  (Schema ?component
    (Source-Sensor ?source-sensor)
    (potential-Sink ?potential-sink))

  (Schema ?potential-sink
    (Instance-of Relay)
    (Status Open)
    (Potential-Sink ?load))

  (Schema ?load
    (Instance-of load))

  (Assert
    (Schema ?source-sensor
      (Potential-Relay-Sink ?potential-sink))))

```

"If the potential sink for a source is an open relay and its potential sink is a load then assert that the relay is a potential sink."

ORIGINAL PAGE IS
OF POOR QUALITY

```

(DefRule Explain Hypothesis-Gen
  (declare (salience 671))

  (printout t t " Hypothesizing Faults: " )
  (printout t t " ")
  (printout t t " "))

(DefRule Find-Open-Circuit
  (declare (salience 670))
  (Schema ?component
    (instance-of component)
    (source-sensor ?source-sensor)
    (sink-sensor ?sink-sensor))

  (Schema ?source-sensor
    (instance-of sensor)
    (Qual-Current Zero:Low)
    (Qual-Voltage Normal:High ))

  (Schema ?sink-sensor
    (instance-of sensor)
    (Qual-Current Zero)
    (Qual-Voltage Zero))

  (Viewpoint ?vp
    (nor (Fault-Hypothesis Open-Circuit ?component)))

  (Sprout (Assert (Fault-Hypothesis Open-Circuit ?component))))

```

"If the source sensor for a component is registering zero or low current and normal or high voltage and its sink sensor is registering zero current and voltage then hypothesize that there is an open circuit at the component."

```

(DefRule Finkd-Open-Circuit--nos-source
  (declare (Salience 670))
  (Schema ?component
    (instance-of power-source)
    (source-sensor none)
    (sink-sensor ?sink-sensor))

```

```

(Schema ?sink-sensor
  (instance-of sensor)
  (Coupled-Sink no)
  (Qual-Current Zero)
  (Qual-Voltage Zero))

```

```

(Viewpoint ?vp
  (not (Fault-Hypothesis Open-Circuit ?component)))
(Sprout (Assert (Fault-Hypothesis Open-Circuit ?component))))

```

" If a given component has no source, its sink is not coupled and the sink sensor volatage and current are zero then hypothesize an open circuit at the component."

```
(DefRule Find-Open-Circuit-no-sink
```

```
  (declare (salience 670))
  (Schema ?component
    (instance-of component:power-sink)
    (source-sensor ?source-sensor)
    (sink-sensor none))
```

```
  (Schema ?source-sensor
    (instance-of sensor)
    (Qual-Current Zero:Low)
    (Qual-Voltage Normal:high ))
```

```
  (Viewpoint ?vp
```

```
    (not (Fault-Hypothesis Open-Circuit ?component))))
```

```
  (Sprout (Assert (Fault-Hypothesis Open-Circuit ?component))))
```

"If a component is a power sink with no sink sensor and its source sensor shows zero or low current and normal or high voltage then hypothesis an open circuit for the component."

```

(DefRule Find-Open-Circuit--Cold-Sk
  (declare (salience 670))
  (Schema ?component
    (instance of component)
    (Source-Sensor ?source-sensor)
    (Sink-Sensor ?sink-sensor))

  (Schema ?csource-sensor
    (instance of sensor)
    (Qual-Current Zero)
    (Qual-Voltage Normal))

  (Schema ?sink-sensor
    (instance of sensor)
    (Qual-Current Zero)
    (Qual-Voltage Low;Normal)
    (Coupled-Sink yes))

  (Viewpoint ?vp
    (not (Fault-Hypothesis Open-Circuit ?component)))
    (Sprout (Assert (Fault-Hypothesis Open-Circuit ?component))))

```

If a component's source sensor registers zero current and normal voltage and its sink is a coupled sink whose sensor registers zero current and low or normal voltage then hypothesize an open circuit for the component."

```

(DefRule Find-Open-Circuit-Cold-no-source
  (declare (salience 670))
  (Schema ?component
    (instance-of power-source)
    (not (instance-of relay))
    (Source-Sensor none)
    (Sink-Sensor ?sink-sensor)

    (Schema ?sink-sensor
      (instance-of sensor)
      (Qual-Current Zero)
      (Qual-Voltage Low:Normal)
      (Coupled-Sink yes))

    (Viewpoint ?vp
      (not (Fault-Hypothesis Open-Circuit ?component))))

  (Sprout (Assert (Fault-Hypothesis Open-Circuit ?component))))

```

If a source is a power source with no sensor...but not a relay...and its sink is a coupled sink whose sensors register zero current and low or no voltage then hypothesize an open circuit for the component."

ORIGINAL PAGE IS
OF POOR QUALITY

```

(DefRule Find-Short-Circuit
  (declare (salience 670))
  (Schemas ?component
    (instance-of component)
    (not (instance-of relay))
    (source-sensor ?source-sensor)
    (sink-sensor ?sink-sensor))
  (Schema ?source-sensor
    (instance-of sensor)
    (Qual Current High:Sys-Limit)
    (Qual-Voltage Low:Zero))
  (Schema ?sink-sensor
    (instance-of sensor)
    (Qual-Current Zero)
    (Qual-Voltage Zero))
  (Viewpoint ?vp
    (not (Fault-Hypothesis Short-Circuit ?component)))
  (Sprout (Assert (Fault-Hypothesis Short-Circuit ?component))))

```

"If a component is not a relay and its source sensor registers high or system limited current and low or zero voltage and its sink sensor registers zero current and voltage then hypothesize a short circuit."

ORIGINAL PAGE IS
OF POOR QUALITY

```

(DefRule Find-Short-Circuit-cold
  (declare (salience 670))
  (Schema ?component
    (instance of component)
    (not (instance of relay))
    (source sensor ?source sensor)
    (sink sensor ?sink sensor))

  (Schema ?source sensor
    (instance of sensor)
    (Qual-Current High;Sys-Limit)
    (Qual-Voltage Low;Zero))

  (Schema ?sink sensor
    (instance of sensor)
    (Coupled Sink yes)
    (Qual-Current Zero)
    (Qual-Voltage Low;Zero;Normal))

  (Viewpoint ?vp
    (not (Fault-Hypothesis Short-Circuit ?component)))

  (Sprout (Assert (Fault-Hypothesis Short-Circuit ?component))))

```

"If a component is not a relay and its source sensor registers high or system limited current and low or zero voltage and its sink is a coupled sink whose sensor registers zero current and low, zero or normal voltage then hypothesize a short circuit."

```

(DefRule Find-Short-Circuit--no-source
  (declare (salience 670))
  (Schema ?component
    (instance-of power-source)
    (not (instance-of relay))
    (source-sensor none)
    (sink-sensor ?sink-sensor))

  (Schema ?sink-sensor
    (instance-of sensor)
    (Coupled-Sink no)
    (Qual-Current Zero)
    (Qual-Voltage Low:Zero))

  (Viewpoint ?vp
    (not (Fault-Hypothesis Short-Circuit ?component)))

  (Sprout (Assert (Fault-Hypothesis Short-Circuit ?component))))

```

"If a component is a power source whose sink is not a coupled sink and the sink sensor registers zero current and low or zero voltage then hypothesize a short circuit."

```

(DefRule Find-Short-Circuit-Cpled-no-source
  (declare (salience 670))
  (Schema ?component
    (instance-of power-source)
    (not (instance-of relay))
    (source-sensor None)
    (sink-sensor ?sink-sensor))

  (Schema ?sink-sensor
    (instance-of sensor)
    (Coupled-Sink yes)
    (Qual-Current Zero)
    (Qual-Voltage Low;Zero))

  (Viewpoint ?vp
    (not (Fault-Hypothesis Short-Circuit ?component)))

  (Sprout (Assert (Fault-Hypothesis Short-Circuit ?component))))

```

"If a power source has a coupled sink whose sensor registers zero current and low or zero voltage, then hypothesize a short circuit."

```

(DefRule Find-Short-Circuit-nosink
  (declare (salience 670))
  (Schema ?component
    (instance-of power-sink;component)
    (not (instance-of relay))
    (source-sensor ?source sensor)
    (sink-sensor none))

    (Schema ?source/sensor
      (instance-of sensor)
      (Qual-Current High;Sys-Limit)
      (Qual-Voltage low;Zero ))

  (Viewpoint ?vp
    (not (Fault-Hypothesis Short-Circuit ?component))))

  (Sprout (Assert (Fault-Hypothesis Short Circuit ?component))))

```

"If a component is a power sink and its source sensor registers high or system limited current and low or zero voltage then hypothesize a short circuit."

ORIGINAL PAGE IS
OF POOR QUALITY

```

(DefRule Find-Resistive-Short-Circuit
  (declare (salience 670))
  (Schema ?component
    (instance-of component)
    (not (instance-of relay))
    (source-sensor ?source-sensor)
    (sink-sensor ?sink-sensor))

  (Schema ?source-sensor
    (instance-of sensor)
    (Qual-Current High;Sys-Limit)
    (Qual-Voltage Low;Normal))

  (Schema ?sink-sensor
    (instance-of sensor)
    (Qual-Current Low;Normal)
    (Qual-Voltage Low;Normal))

  (Viewpoint ?vp
    (not (Fault-Hypothesis Resistive-Short-Circuit ?component))))

  (Sprout (Assert (Fault-Hypothesis Resistive-Short-Circuit ?component))))

```

"If a component is not a relay and source current is high or system limited, source voltage is low or normal and sink current and voltage is low or normal then hypothesize a short circuit."

ORIGINAL PAGE IS
OF POOR QUALITY

```
(DefRule Find-Resistive-Short-Circuit-no-source
  (Declare (allence 670))
  (Schema ?component
    (instance of power-source)
    (not (instance of relay))
    (source-sensor none)
    (sink-sensor ?sink-sensor)))
```

```
(Schema ?sink-sensor
  (instance-of sensor)
  (Coupled-Sink no)
  (Qual-Current Zero:Low)
  (Qual-Voltage Zero:Low:Normal))
```

```
(Viewpoint ?vp
  (not (Fault-Hypothesis Resistive-Short-Circuit ?component)))
(Sprout (Assert (Fault-Hypothesis Resistive-Short-Circuit ?component))))
```

"If the sink sensor for a power source registers zero or low current and zero, low or normal voltage and the sink is not coupled then hypothesize a resistive short circuit."


```

(DefRule Find-Resistive-Short-Circuit-cpld-no-source
  (declare (salience 670))
  (Schema ?component
    (instance-of power-source)
    (not (instance-of relay))
    (source-sensor none)
    (sink-sensor ?sink-sensor))

  (Schema ?sink-sensor
    (instance-of sensor)
    (Coupled-Sink yes)
    (Qual-Current Zero:Low)
    (Qual-Voltage Low:Normal))

```

```

(Viewpoint ?vp

```

```

  (not (Fault-Hypothesis Resistive-Short-Circuit ?component)))

```

```

(Sprout (Assert (Fault-Hypothesis Resistive-Short-Circuit ?component))))

```

"If the sink for a power source is coupled and the sink's sensor registers zero or low current and low or normal voltage then hypothesize a short circuit."

```

(DefRule Fink-Closed-Relay-no-sksn
  (declare (salience 670))
  (Schema ?source-sensor
    (instance-of sensor)
    (Qual-Current High)
    (Qual-Voltage Normal;Low)
    (Potential-Relay-Sink ?relay))
  (Viewpoint ?vp
    (not (Fault-Hypothesis Closed-Relay ?relay)))
  (Sprout (Assert (Fault-Hypothesis Closed-Relay ?relay))))

```

"If a source sensor has no corresponding sink sensor because the sink is a relay and the source sensor registers high current and normal or low voltage then hypothesize a closed relay."

ORIGINAL PAGE IS
OF POOR QUALITY

```
(DefRule Explain Read-In
  (declare (salience 582))

  (printout t t " Reading In Faulted Values " )
  (printout t t " "))

(DefRule Read-In-Faulted Values
  (declare (salience 750))
  (sensor-status ?sensor ?current ?voltage)

  (Modify
    (Schema ?sensor
      (faulted-current ?current)
      (faulted-voltage ?voltage))))
```

"This rule modifies the database to contain the faulted values, setting the current and voltage for each sensor."

```
(DefRule Determine-Qualitative-Values-Current
  (declare (salience 740))

  (Schema ?sensor
    (faulted-current ?current)
    (current-errorband (?neg ?zero ?low ?high)))

  (bind ?qual value (assign qual ?current ?neg ?zero ?low ?high))
  (Modify
    (Schema ?sensor
      (qual current ?qual-value))))
```

"This rule assigns the qualitative value (zero, low, high, etc.) to the qualitative current for each sensor based on the contents of the error band database."

ORIGINAL PAGE IS
OF POOR QUALITY

(DefRule Determine-Qualitative-Values-Voltage
(declare (salience 740))

(Schema ?sensor
 (faulted-voltage ?voltage)
 (voltage-errorband (?neg ?zero ?low ?high)))
(bind ?qual-value (assign qual ?voltage ?neg ?zero ?low ?high))
(Modify
 (Schema ?sensor
 (qual voltage ?qual value)))

"Same as above except for voltage."

(DefRule Create-Graphics
(declare (salience 585))

(printout t t "Creating Window")
#L (create-window 'files-2' :graphics 10 300 1000 725)
#L (label window (window stream 'files-2) "FILES")
#L (expose-window 'files-2)
#L (show icon 'icon-2 'files-2)
 (printout t t " ")

(DefRule Flash-All-Icons

(declare (salience 50))
(Schema ?x
 (Has-Icon ?icon))

(printout t t "Flashing Icon" ?icon)
#L (flash-icon ?icon 3 60 'files-2)

"These rules manipulate the FILES t command window."

ORIGINAL PAGE IS
OF POOR QUALITY

(Defrule Printout-All-Faults
 (declare (salience 355))

(printout t t "Reporting All Initial Fault Hypotheses: ")
 (printout t t " ")
 (printout t t " "))

"These rules cause output to go to the screen. This rule simply outputs the heading 'Reporting All Initial Fault Hypotheses.'"

(Defrule Summarize-All-Faults

(declare (salience 350))
 (Fault-Hypothesis ?fault ?location)

(printout t t " " ?fault " " ?location)
 (printout t t " "))

"This rule outputs the fault that is currently instantiated to the variable ?fault and the location (of the fault) which is instantiated to ?location."

(Defrule Printout-Remaining-Faults flag

(declare (salience 345))

(printout t t " ")
 (printout t t "Reporting Final Fault Hypotheses: ")
 (printout t t " ")
 (printout t t " "))

(Defrule Printout-Remaining-Faults

(declare (salience 340))
 (Fault-Hypothesis ?fault ?location)
 (not (inconsistent Hypothesis ?fault ?location))
 (not (inconsistent Hypothesis ?fault ?location)))

(printout t t " " ?fault " " ?location)
 (printout t t " "))

```

Defrule Inconsistent-Load-Short-Circuit
  (declare (salience 610))
  (Fault-Hypothesis Short-Circuit ?component)

  (Schema ?component
    (instance of component:power-sink
      (source ?source& none)
      (Source-sensor ?sensor))

    (Schema ?sensor
      (instance of sensor)
      (load-sensor yes)
      (Faulted-Voltage ?value))

  (Test (> ?value 10))

  (Assert (Inconsistent-hypothesis v Short-circuit ?component)))

```

"If a component is a power sink and its voltage is greater than 10 then discard a hypothesis that there is a short circuit for the component."


```

(Defrule Inconsistent-Load-Resistive-Short-Circuit
  (declare (salience 610))
  (Fault-Hypothesis Resistive-Short-Circuit ?component)

  (Schema ?component
    (instance-of component)
    (source ?source& none)
    (Source-sensor ?sensor))

  (Schema ?sensor
    (instance-of sensor)
    (load-sensor yes)
    ?faulted-voltage ?value))

  (Test ( < ?value 10 ))

  (Assert (Inconsistent hypothesis v Resistive Short Circuit ?component)))

  "If a component is a load (power sink) and its source sensor registers a
  voltage of less than 10 then discard any hypothesis of a short circuit
  at that component."

```

```

(Defrule INconsistent-Load-Closed Relay
  (declare (salience 610))
  (Fault-Hypothesis Closed Relay ?component)

  (Schema ?sensor
    (instance-of sensor)
    (load-sensor yes)
    (Potential-Relay-Sink ?component)
    (Faulted-Voltage ?value))

  (Test (< ?value 20))

  (Assert (Inconsistent-hypothesis-v Closed Relay ?component)))

```

"If the sink for a sensor is a relay and the voltage at the sensor is less than 20 then discard any hypothesis that there is a closed relay fault at the relay."

```

(Defrule Init-Source-Prop Open
  (declare (salience 568))
  (Fault Hypothesis Open Circuit;Open Relay ?component)

  (Schema ?component
    (instance-of component)
    (source ?source & none))

  (Assert (Propagate to ac ?component ?source (Current Zero)))

```

"Voltage is zero across properly opened relays between a component and its source."

```

(Defrule Init-Sink-Prop-Open
  (declare (salience 568))
  (Fault-Hypothesis Open-Circuit;Open-Relay ?component)
  (Schema ?component
    (instance-of component)
    (sink ?sink& none))
  (Assert (Propagate-to-sk ?component ?sink (Current Zero))))

"Same as above except for relays between a component and its sink."
(Defrule Init-Source-Prop-Open-From-PSink
  (declare (salience 558))
  (Fault-Hypothesis Open-Circuit ?component)
  (Schema ?component
    (instance-of power-sink)
    (Sink none)
    (source ?source& none))
  (Assert (Propagate-to-sc ?component ?source (Current Zero))))

"if a power sink has a source and it has been hypothesized that there is an open
circuit for the power sink then propagate that hypothesis to the source."

```

```

(Defrule Init-Sink-Prop-Open-From-PSource
  (declare (salience 548))
  (Fault-Hypothesis Open-Circuit ?component)

```

```

  (Schema ?component
    (instance-of power-source)
    (Source none)
    (sink ?sink&none))

```

```

  (Assert (propagate-to sk ?component ?sink (Current Zero))))

```

"If a power source has a sink and it has been asserted that there is an open circuit for the power source then propagate the hypothesis to the sink for the power source."

```

(Defrule Init-Source-Prop-Short
  (declare (salience 548))
  (Fault-Hypothesis Short-Circuit ?component)
  (not (Inconsistent-hypothesis v Short-circuit ?component))

```

```

  (Schema ?component
    (instance-of component)
    (source ?source&none))

```

```

  (Assert (Propagate-to-sc ?component ?source (Current High))))

```

"If a short circuit is hypothesized for a load, then propagate back the high current reading."

```

(Defrule Init-Sink-Prop-Short
  (declare (salience 548))
  (Fault-Hypothesis Short-Circuit ?component)
  (not (Inconsistent-hypothesis v Short-Circuit ?component)))

```

```

(Schema ?component
  (instance of component)
  (sink ?sink& none))

```

```

(Assert (Propagate-to sk ?component ?sink (Current Zero)))

```

"If a component has been hypothesized as having a short circuit and the component has a sink then propagate the hypothesis to the sink."

```

(Defrule Init-Sink-Prop-Short-From-PSource
  (declare (salience 548))
  (Fault-Hypothesis Short-Circuit ?component)

```

```

(Schema ?component
  (instance of power-source)
  (source none)
  (sink ?sink& none))

```

```

(Assert (Propagate to sk ?component ?sink (Current Zero)))

```

"If a short circuit has been hypothesized for a power source, then propagate forward the zero current to the sink for the power source."

```

(Defrule Init-Source-Prop-Short-From-PSink
  (declare (salience 538))
  (Fault-Hypothesis Short-Circuit ?component)
  (not (inconsistent-hypothesis v Short-Circuit ?component)))

  (Schema ?component
    (instance-of power-sink
      (sink none)
      (Source ?source&~none)))

  (Assert (propagate-to-sc ?component ?source (Current High))))

If a short circuit has been hypothesized for a power sink, then propagate
back the high current from the sink to its source."
(Defrule Init-Source-Prop-RShort
  (declare (salience 528))
  (Fault-Hypothesis Resistive Short-Circuit ?component)
  (not (inconsistent-hypothesis v Resistive-Short-Circuit ?component)))

  (Schema ?component
    (instance-of component)
    (source ?source&~none))

  (Assert (propagate-to-sc ?component ?source (Current High))))

" If a resistive short circuit has been hypothesized for a component, then
propagate back the high current to the source for the component."

```



```

(Defrule Init-Sink-Prop-RShort
  (declare (salience 528))
  (Fault-Hypothesis Resistive-Short-Circuit ?component)
  (not (Inconsistent hypothesis v Resistive-Short-Circuit ?component))
  (Schema ?component
    (instance-of component)
    (Sink ?sink& none)))

```

```

(Assert (Propagate-to-sk ?component ?sink (Current Low))))

```

"If a resistive short circuit has been hypothesized for a component, then propagate forward the low current reading to its sink."

```

(Defrule Init-Sink-Prop-RShort-From-Psource
  (declare (salience 518))
  (Fault-Hypothesis Resistive-Short-Circuit ?component)
  (Schema ?component
    (instance-of power-source0)
    (source none)
    (sink ?sink& none)))

```

```

(Assert (Propagate-to-sk ?component ?sink (Current Zero))))

```

"If a resistive short circuit has been hypothesized for a power source, then propagat forward to the sink for the source the zero current."

```

(Defrule Init-Source-Prop-RShort-From-Psink
  (declare (salience 518))
  (Fault-Hypothesis Res=istive-Short-Circuit ?component)
  (not (Inconsistent-Hypothesis-v Resistive-Short-circuit ?component)))

(Schema ?component
  (instance-of power-sink)
  (sink none)
  (source ?source& none))

(Assert (Propagate-to-sc ?component ?source (Current High))))

```

"If a resistive short circuit has been hypothesized for a power sink, then propagate back the high current reading to the source for the sink."

ORIGINAL PAGE IS
OF POOR QUALITY

```
(Defrule Continue-Propagation-Sc
  (declare (salience 600))
  (propagate-to-sc ?from ?component (Current ?effect))
  (Schema ?component
    (instance-of component)
    (Source ?source& none)
    (multiple-Sources ?)
    (Multiple Sinks no))
  (not (Schema ?component
    (instance-of sensor)))
  (Fault-Hypothesis ?fault ?location)
  (not (Inconsistent-hypothesis ?fault ?location)))
```

"See next rule."

```
(Defrule Continue-Propagation-sk
  (declare (salience 599))
  (propagate-to sk ?from ?component (Current ?effect))
  (Schema ?component
    (instance-of component)
    (Sink ?sink& none)
    (Multiple Sources no)
    (Multiple Sinks ?))
  (not (Schema ?component
    (instance-of sensor)))
  (Fault-Hypothesis ?fault ?location)
  (not (Inconsistent-hypothesis ?fault ?location)))
```

"These two rules continue the propagation process initiated by the preceding rules."

ORIGINAL PAGE IS
OF POOR QUALITY

```

(Defrule Continue-Propagation-sk-2-sources
  (declare (salience 599))
  (Propagate-to-sk ?from ?component (Current zero))
  (Schema ?component
    (instance-of component)
    (Sink ?sink&~none)
    (Multiple-Sources yes)
    (Multiple-Sinks no)
    (I-Eq ((+ S? ?other-sources&~?from $?) (+ ?sink))))))

(not (Schema ?component
      (instance-of sensor)))

(Fault-Hypothesis ?fault ?location)
(not (Inconsistent-hypothesis ?fault ?location))

(Assert (Propagate-to-sc ?component ?other-source (Current high)))
(Assert (Propagate-to-sk ?component ?sink (Current Low)))

(Defrule Continue-Propagation-source-2-sks-high
  (declare (salience 600))
  (Propagate-to-sc ?from ?component (Current high))
  (not (Path-Already-followed Propagate to sc ?component high))
  (Schema ?component
    (instance-of component)
    (Source ?source&~none)
    (Multiple Sources no)
    (Multiple Sinks yes)
    (I-Eq ((+ ?source) (+ $? ?other-sinks ?from $?))))

(not (Schema ?component
      (instance-of sensor)))

(Fault-Hypothesis ?fault ?location)
(not (Inconsistent hypothesis ?fault ?location))

```

ORIGINAL PAGE IS
 OF POOR QUALITY

```

(Defrule Continue-Propagation-source-2-sks-zero
  (declare (salience 600))
  (Propagate-to-sc ?from ?component (Current zero))
  (Schema ?component
    (instance-of component)
    (Source ?sources& none)
    (Multiple-Sources no)
    (Multiple-Sinks yes)
    (I-Eq ((+ ?source) (+ $? ?other-sinks ?from $?))))
  (not (Schema ?component
    (instance-of sensor))))
(Fault-Hypothesis ?fault ?location)
(not (Inconsistent-hypothesis ?fault ?location))

(Defrule Continue-Propagation-source-2-sks-low
  (declare (salience 600))
  (Propagate-to-sc ?from ?component (Current low))
  (not (Path-Already-Followed Propagate-to-sc ?component low))
  (Schema ?component
    (instance-of component)
    (Source ?sources& none)
    (Multiple-Sources no)
    (Multiple-Sinks yes)
    (I-Eq ((+ ?source) (+ $? ?other-sinks ?from $?))))
  (not (Schema ?component
    (instance-of sensor))))
(Fault-Hypothesis ?fault ?location)
(not (Inconsistent-hypothesis ?fault ?location))

```

ORIGINAL PAGE IS
OF POOR QUALITY

```
(Defrule Sensor-Consistency-Check-Sc-consistent
  (declare (salience 600))
  (Propagate-to-Sc ?from ?component (Current ?pred-effect))
  (Schema ?component
    (instance-of sensor)
    (Qual-Current ?qual-current
      (Source ?source&~none)
      (Multiple-Sources no)
      (Multiple-Sinks no)))
```

```
(Consistent-Effect ?pred-effect ?qual-current )
(Fault-Hypothesis ?fault ?location)
(Not (Inconsistent-hypothesis ?fault ?location))
```

```
(Defrule Sensor-Consistency-Check-Sc-fadeout
  (declare (salience 600))
  (Propagate-to-Sc ?from ?component (Current ?pred-effect))
  (Schema ?component
    (instance-of sensor)
    (Qual-Current ?qual-current)
    (Source ?source&~none)
    (Multiple-Sources no)
    (Multiple-Sinks no))
```

```
(not (Consistent-Effect ?pred-effect ?qual-current ))
(Fadeout-Effect-Sc Prop ?pred-effect ?qual-current)
```

```
(Fault-Hypothesis ?fault ?location)
(not (Inconsistent-hypothesis ?fault ?location))
```



```

(Defrule Sensor-Consistency-Check-Sc-noise
  (declare (salience 600))
  (Propagate-to-Sc ?from ?component (Current ?pred-effect))
  (Schema ?component
    (instance-of sensor)
    (Qual-Current ?qual-current)
    (Source ?source&~none)
    (Multiple-Sources no)
    (Multiple-Sinks no))
  (not (Consistent-Effect ?pred-effect ?qual-current))
  (not (Fadeout-Effect-Sc-Prop ?pred-effect ?qual-current))
    (Noise-Effect ?pred-effect ?qual-current)
  (Fault-Hypothesis ?fault ?location)
  (not (Inconsistent-hypothesis ?fault ?location))

(Defrule Sensor-Consistency-Check-sk-consistent
  (declare (salience 599))
  (Propagate-to-sk ?from ?component (Current ?pred-effect))
  (Schema ?component
    (instance-of sensor)
    (Qual-Current ?qual-current)
    (Sink ?sink&~none))
  (Consistent-Effect ?pred-effect ?qual-current)
  (Fault Hypothesis ?fault ?location)
  (not (Inconsistent-hypothesis ?fault ?location))

```

```

(Defrule Sensor-Consistency-Check-sk-fadeout
  (declare (salience 599))
  (Propagate to sk ?from ?component (Current ?pred-effect))
  (not (Path-Already-Followed Propagate-to-sk ?component ?pred-effect))
  (Schema ?component
    (instance-of sensor)
    (Qual-Current ?qual-current)
    (Sink ?sink&none))
  (Not (Consistent-Effect ?pred-effect ?qual-current))
    (Fadeout-Effect-Sk-Prop ?pred-effect ?qual-current)

  (Fault Hypothesis ?fault ?location)
  (not (Inconsistent-hypothesis ?fault ?location))

(Defrule Sensor Consistency-Check sk noise
  (declare (salience 599))
  (Propagate to sk ?from ?component (Current ?pred-effect))
  (Schema ?component
    (instance-of sensor)
    (Qual-Current ?qual-current)
    (Sink ?sink&none))
  (not (Consistent-Effect ?pred-effect ?qual-current))
  (not (Fadeout-Effect Sk Prop ?pred-effect ?qual-current))
  (Noise-Effect ?pred-effect ?qual-current)
  (Fault Hypothesis ?fault ?location)
  (not (Inconsistent-hypothesis ?fault ?location))

```

```

(Defrule Sensor-Inconsistency-Check-source
  (declare (salience 601))
  (Propagate-to-Sc ?from ?component (Current ?pred effect))
  (Schema ?component
    (instance-of sensor)
    (Qual-Current ?qual-current)
    (Sink ?sink&none))
  (Not (Consistent-Effect ?pred effect ?qual-current))
  (Not (Fadeout-Effect Sk Prop ?pred effect ?qual-current))
  (Not (Noise-Effect ?pred-effect ?qual-current))
  (Fault Hypothesis ?fault ?location)
  (not (Inconsistent-hypothesis ?fault ?location)))

(Defrule Sensor-Inconsistency-Check-sk
  (declare (salience 601))
  (Propagate-to-sk ?from ?component (Current ?pred effect))
  (Schema ?component
    (instance-of sensor)
    (Qual-Current ?qual-current)
    (Sink ?sink&none))
  (Not (Consistent-Effect ?pred effect ?qual-current))
  (Not (Fadeout-Effect Sk Prop ?pred effect ?qual-current))
  (Not (Noise Effect ?pred-effect ?qual-current))
  (Fault Hypothesis ?fault ?location)
  (not (Inconsistent-hypothesis ?fault ?location)))

```

APPENDIX E

Hardware Description and Drawings

SUBSYSTEM AUTOMATION STUDY BREADBOARD


Drawing #PL849PABB1000

<u>Item #</u>	<u>Part#</u>	<u>Description</u>	<u>MFG</u>	<u>QTY</u>
1	P-10	10.5" Panels	Optima	3
2	849PABB1500	Main Control Assembly		1
3	849PABB1600	Power System Assembly		1
4	849PABB1700	Battery System Assembly		1
5	HP6255A-010	Power Supply	Hewlett Packard	3
6	HP6264B-010	Power Supply	Hewlett Packard	1
7	849PABB1900	Microcomputer Disk Drive	Intel	1
8	849PABB1400	Microcomputer Assembly	Intel	1
9	849PABB1300	Fault Insertion Assembly		1
10	849PABB1200	Map Assembly		1
11	G-319	Ventillation Grille	Optima	5
12	849PABB1100	Voltage Regulator		1

Numbers which end in 1 are schematics. Drawings beginning in PL are parts lists for the assembly drawings which follows:

- 1000 - Top Level assembly
- 11 - First assembly beneath top level
- 12 - Second assembly beneath top level
- 1110 - First assembly beneath second level

ORIGINAL PAGE IS
 OF POOR QUALITY

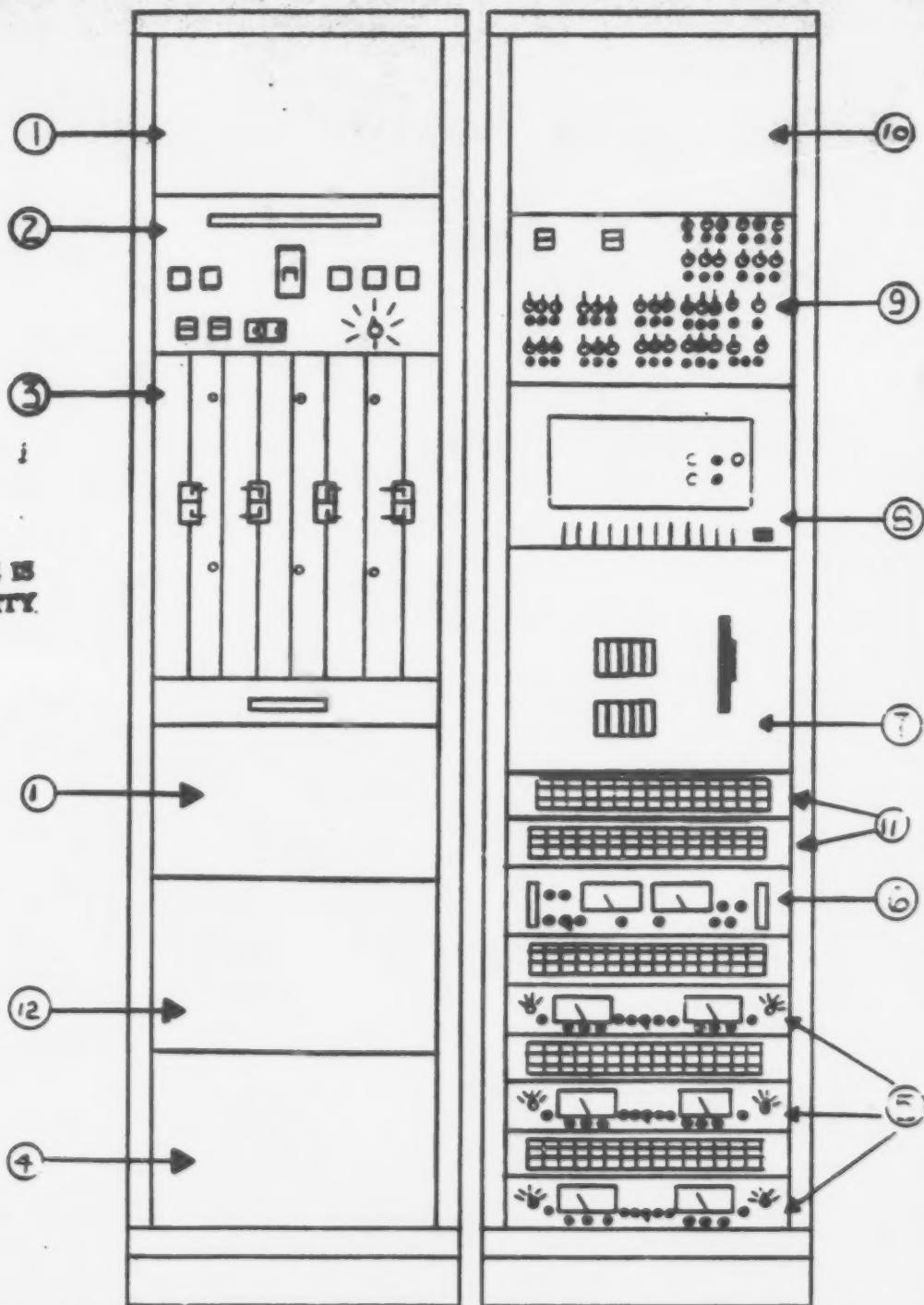


POWER SUBSYSTEM AUTOMATION STUDY
 SYSTEM ASSEMBLY DRAWING

E-2

SIZE	FSCM NO.	DWG NO.	REV
A		849 PAB81000	
SCALE	PAGE	SHEET	
1 - 1		DFI	

ORIGINAL PAGE
OF POOR QUALITY


10.1

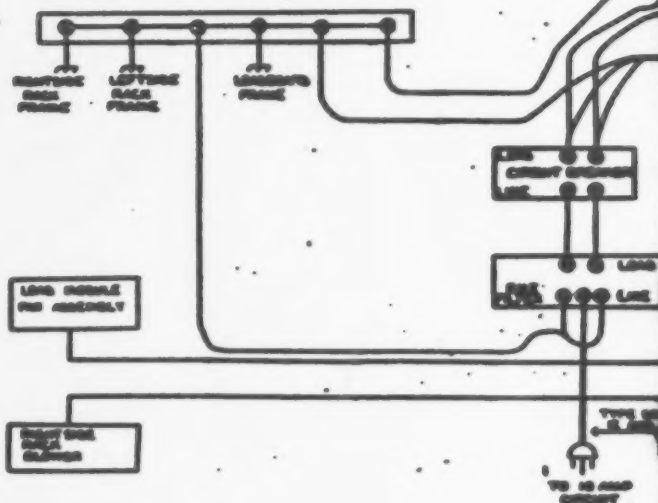

FOLDOUT FRAME

E-3

ORIGINAL PAGE IS
OF POOR QUALITY

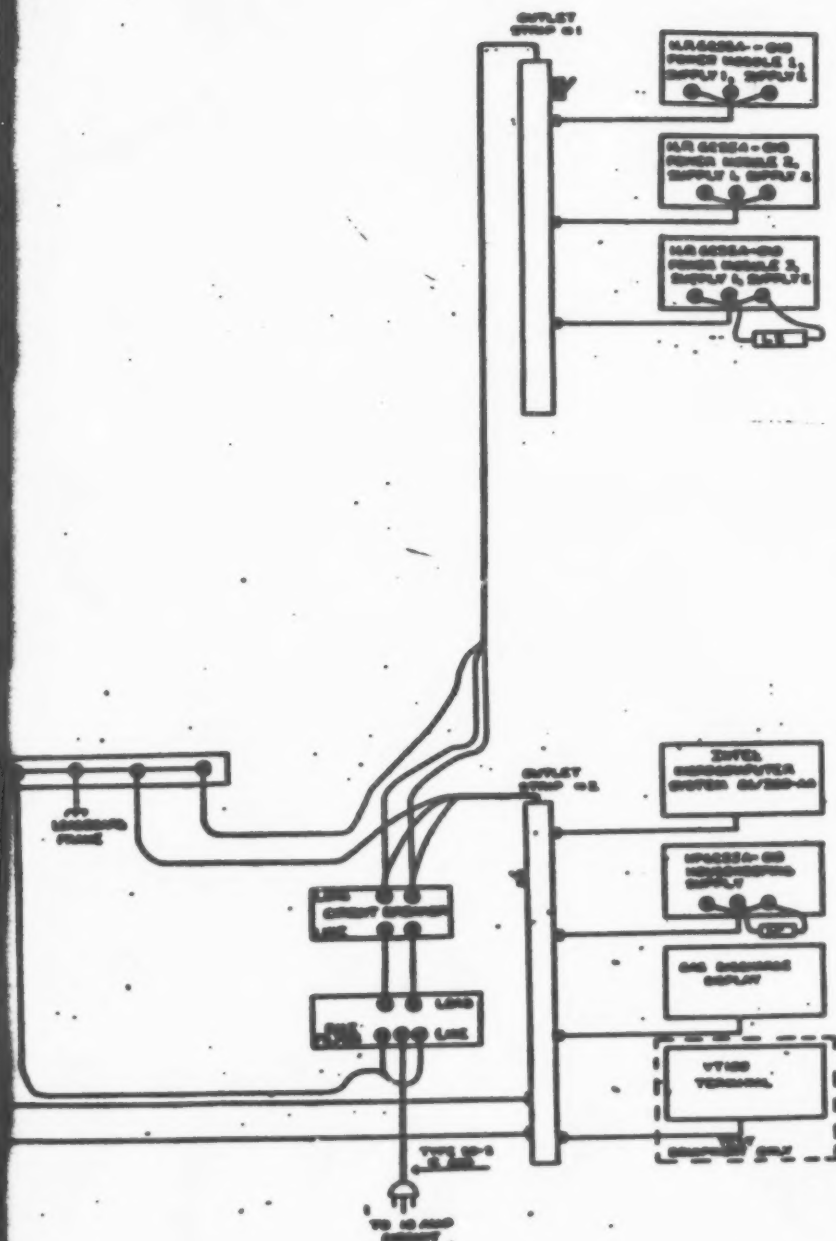

NOTE
CABLE CONNECTING STRIPPER
IN NEUTRAL (WHITE OR BLUE) WIRE
IS NOT (BLACK OR GREEN) WIRE.
C- SAFETY GROUND (GROUNDING)
AL LINE CABLES ARE TYPE 240,
3 CONDUCTOR, 10 AWG.


FOLDOUT FRAME

A.L. WIND DIAGRAM




ORIGINAL PAGE IS
OF POOR QUALITY

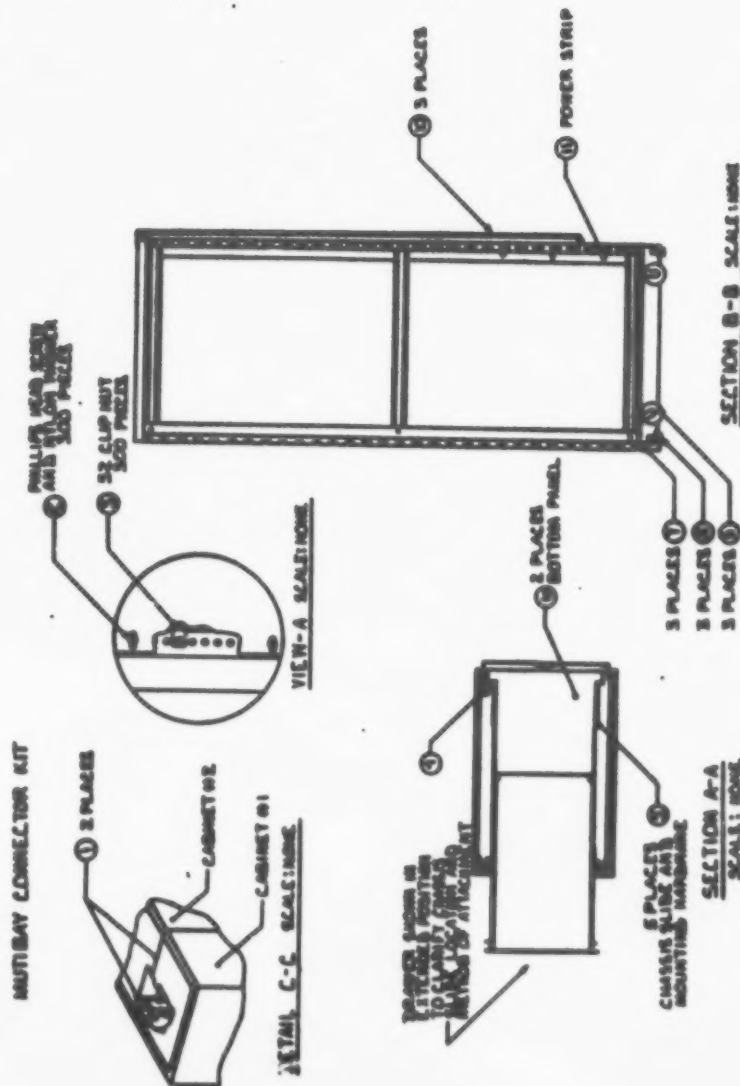POWER SUBSYSTEM AUTOMATION STUDY-
RACK ASSEMBLY



REVISIONS	DATE	BY	APP'D
1	10/14	10/14	10/14
2	10/14	10/14	10/14
3	10/14	10/14	10/14
100	10/14	10/14	10/14

RELAY AND SENSOR POSITIONS/NUMBERS

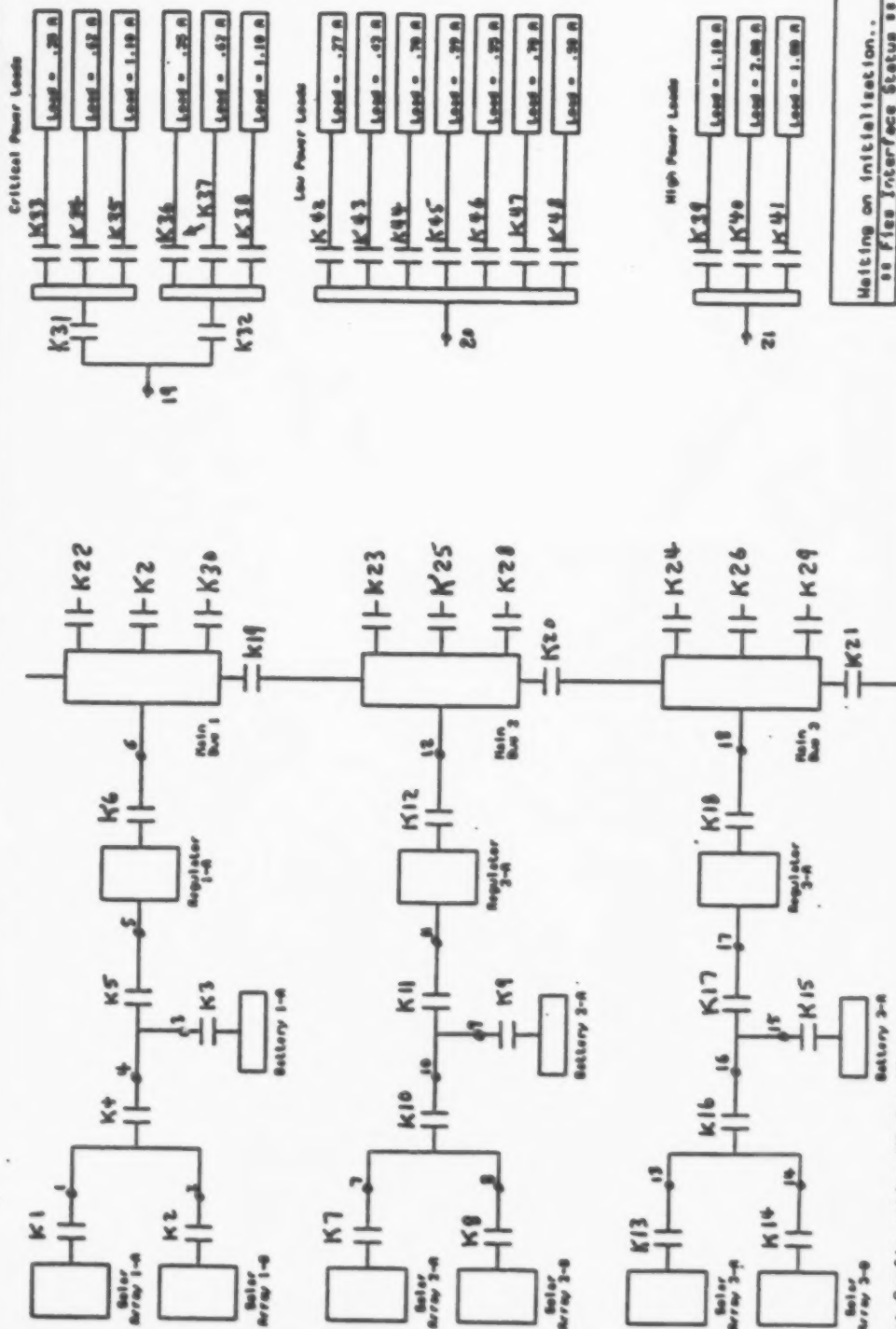

Waiting on Initialization..
to File Interface Status is

Test Configuration Window 17

14
 15
 16
 17
 535
 5


• ENHANCED: done>ert.out 75348

MAIN CONTROL ASSEMBLY

Drawing #PL849PABB1500

<u>Item #</u>	<u>Part #</u>	<u>Description</u>	<u>MFG</u>	<u>QTY</u>
1	P-10	10.5" X 19" Panel	Optima	1
2	W424-1050	Alphanumeric Display	Cherry Electric	1
3	AM2-A3-A-10-2	Circuit Breaker	Heinemann	1
4	APF2021S	Line Filter	Cornell-Dubilies	1
5	31-2111T	AC Indicator Lamps	Leecraft	2
6	31G3-2111T	DC Indicator Lamps	Leecraft	3
7	572-1321- 0804-040	Momentary Paddle Switch	Dialight	1
8	572-1121- 0804-040	2 Position Paddle Switch	Dialight	1
9	PAZ001	Rotary Switch	Centralab	1
10	3-2-11-1- 4-3-0-1	Thumbwheel Switch	C & K	1
11	RH019,150	1% Current Limiting Resistors	Dale	3
12	RC07GF201J	200,1/4 Volt Resistor 5%	Allen-Bradley	3
13	Th-112-48L	Lettering Set	Tranfertech	3

REVISIONS		DATE	BY
1	DESIGN CHANGE	10/7	EE

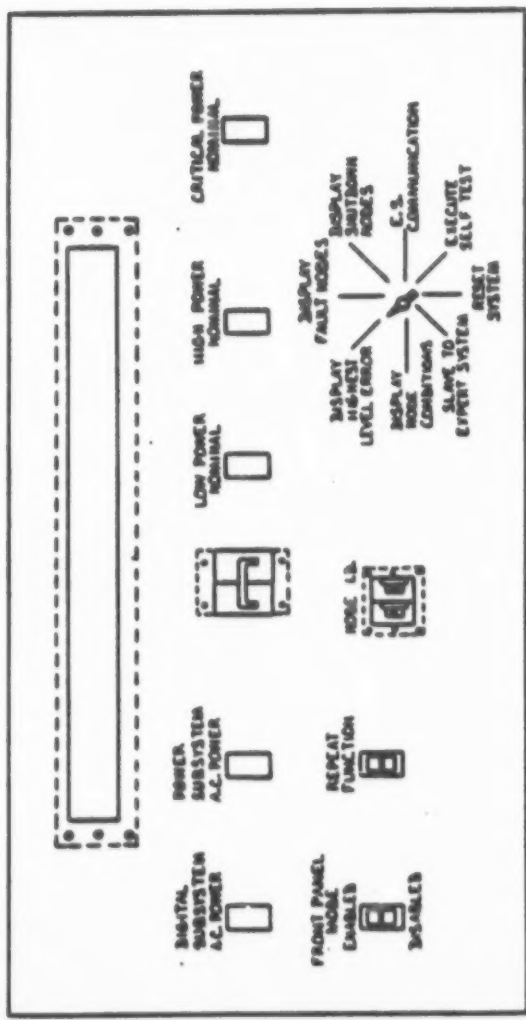

POWER SUBSYSTEM AUTOMATION STUDY
MAIN CONTROL PANEL -
ASSEMBLY DRAWING AND CRILL DETAIL

DESIGNER	DATE	REV	REV
W. J. Butler	10/7	C	04208
PROJECT NO.	849PA2B.500		
SCALE	1 OF 2		




DETAIL A, TYP 3 PL
SCALE NONE

POWER SUBSYSTEM AUTOMATION STUDY
MAIN CONTROL PANEL-
ASSEMBLY DRAWING AND DRILL DETAIL

[illegible]


FOLDOUT FRAME

ORIGINAL PAGE IS
OF POOR-QUALITY

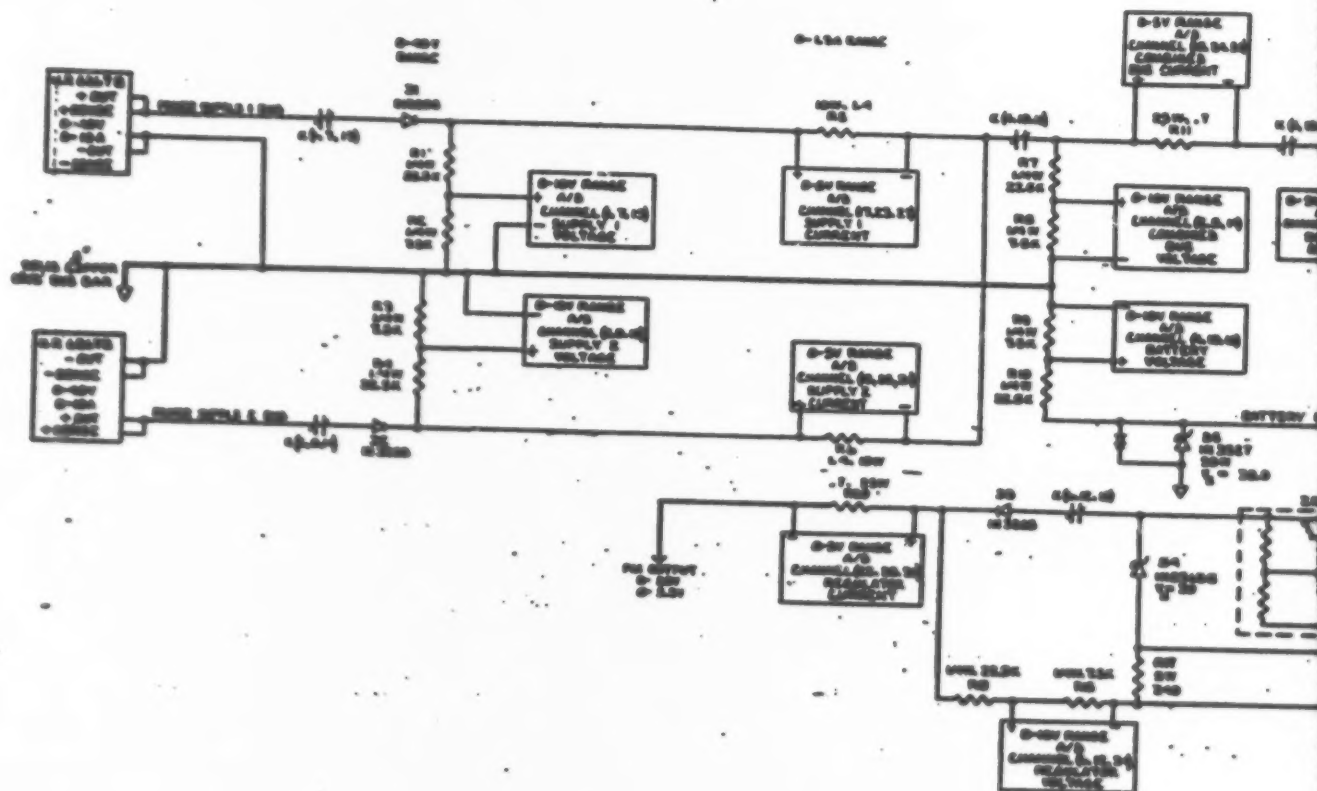

- NOTES
1. ALL RESISTORS ARE 1% TOLERANCE.
 2. ALL 10V RANGE CHANNELS 1, 2, 3, 999, 1000.

2 FOLDOUT FRAME

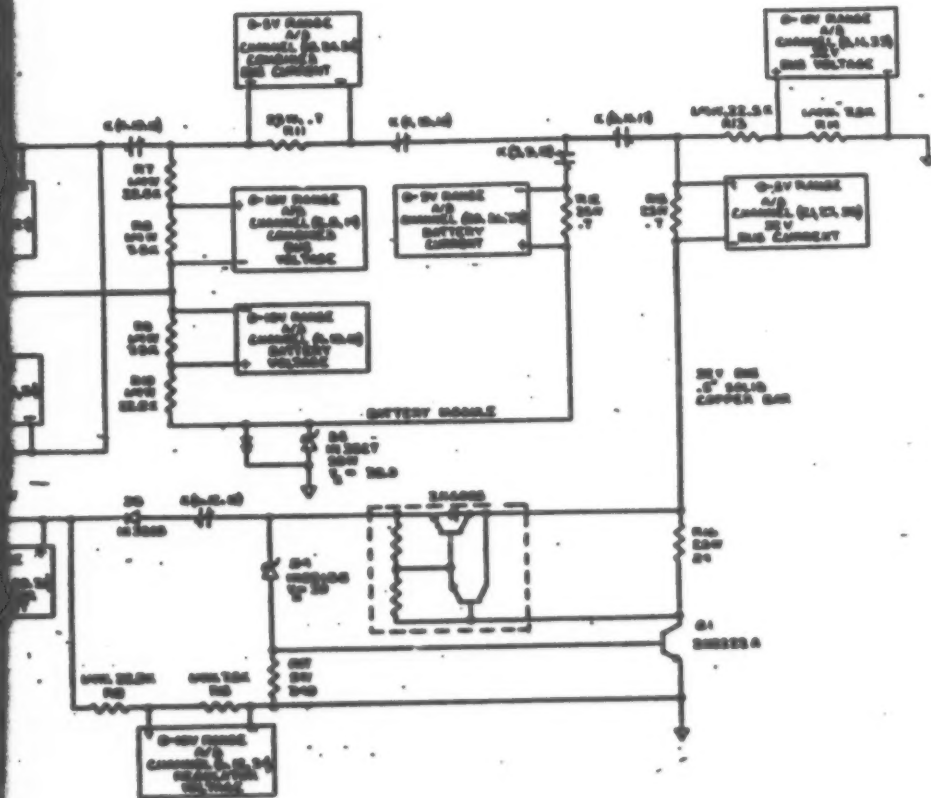

POWER MODULE 1 OF 3
BLACK BOX

Sheet 1 of 2

POWER SYSTEM - BOARD 1

Drawing #PL849PABB1610

<u>Item #</u>	<u>Part #</u>	<u>Description</u>	<u>MFG</u>	<u>QTY</u>
1		T4 Aluminum	MMC	1
2		2/56 Screw	NL Fasteners	4
3	<u>Module 39</u>			
	6321	Solid State Relay	Cryden	1
	NH-50,14 ohm	1%,50W Resistor	Dale	1
	NH-50,27 ohm	1%,50W Resistor	Dale	1
	2N6396	SCR	Motorola	1
	2N6039	Power Transistor	Motorola	1
	2N2222A	Small Signal Transistor	Motorola	1
	RS2027	1 Watt,27ohm, 1% Resistor	Dale	1
	RC07GF271J	1/4 Watt,270ohm,5% Resistor	Allen-Bradley	1
		Capton Tape		1
4	<u>Module 48</u>			
	6321	Solid State Relay	Cryden	1
	NH-50,14 ohm	1%, 50W Resistor	Dale	1
	NH-5,330 ohm	1%, 5W Resistor	Dale	3
	2N6396	SCR	Motorola	1
	2N6039	Power Transistor	Motorola	1
	2N2222A	Small Signal Transistor	Motorola	1
	RS2027	1 Watt, 27ohm, 1%	Dale	1
	RC07GF271J	1/4 Watt,270ohm, 5%	Allen-Bradley	1
		Capton Tape		1
5	<u>Module 47</u>			
	6321	Solid State Relay	Cryden	1
	NH-50,14 ohm	1%, 50W Resistor	Dale	1
	RH-50,50 ohm	1%, 5W Resistor	Dale	1
	2N6396	SCR	Motorola	1
	2N6039	Power Transistor	Motorola	1
	2N2222A	Small Signal Transistor	Motorola	1
	RS2027	1 Watt, 27 ohm, 1%	Dale	1
	RC07GF271J	1/4 Watt, 270 ohm, 5%	Allen-Bradley	1
		Capton Tape		1



POWER SYSTEM - BOARD 1
Con't

Drawing #PL849PABB1610


<u>Item #</u>	<u>Part #</u>	<u>Description</u>	<u>MFG</u>	<u>QTY</u>
6	Module 46			
	6321	Solid State Relay	Cryden	1
	NH-50,14 ohm	1%, 50W Resistor	Dale	1
	NH-50,27 ohm	1%, 50W Resistor	Dale	1
	RH-5,40 ohms	1%, 5W, Resistor	Dale	1
	2N6396	SCR	Motorola	1
	2N6039	Power Transistor	Motorola	1
	2N2222A	Small Signal Transistor	Motorola	1
	RS2027	1 Watt, 27 ohm, 1%	Dale	1
	RC07GF271J	1/4 Watt, 270 ohm, 5%	Allen-Bradley	1
		Capton Tape		1
7	Module 45			
	6321	Solid State Relay	Cryden	1
	RH-5,180ohms	1%, 5W Resistor	Dale	3
	NH-50,14ohms	1%, 50W Resistor	Dale	1
	2N6396	SCR	Motorola	1
	2N6039	Power Transistor	Motorola	1
	2N2222A	Small Signal Transistor	Motorola	1
	RS2027	1 Watt, 27 ohm, 1%	Dale	1
	RC07GF271J	1/4 Watt, 270 ohm, 5%	Allen-Bradley	1
		Capton Tape		1
8	Module 44			
	6321	Solid State Relay	Cryden	1
	NH-50,14ohms	1%, 50W Resistor	Dale	1
	RH-50,50ohms	1%, 50W Resistor	Dale	1
	2N6396	SCR	Motorola	1
	2N6039	Power Transistor	Motorola	1
	2N2222A	Small Signal Transistor	Motorola	1
	RS2027	1 Watt, 27 ohm, 1%	Dale	1
	RC07GF271J	1/4 Watt, 270 ohm, 5%	Allen-Bradley	1
		Capton Tape		1

POWER SYSTEM - BOARD 1
Con't


Drawing #PL849PASS1610

<u>Item #</u>	<u>Part #</u>	<u>Description</u>	<u>MFG</u>	<u>QTY</u>
9	<u>Module 43</u>			
	6321	Solid State Relay	Cryden	1
	NH-50,14 ohm	1%, 50W Resistor	Dale	1
	RH-5,270ohm	1%, 50W Resistor	Dale	3
	2N6396	SCR	Motorola	1
	2N6039	Power Transistor	Motorola	1
	2N2222A	Small Signal Transistor	Motorola	1
	RS2027	1 Watt, 27 ohm, 1%	Dale	1
	RC07GF271J	1/4 Watt, 270 ohm, 5%	Allen-Bradley	1
		Capton Tape		1
10	<u>Module 42</u>			
	6321	Solid State Relay		1
	NH-50,14 ohm	1%, 50W Resistor		1
	RH-10,150ohm	1%, 10W Resistor		1
	TVA-1305.5	20VF, 50V Capacitor	Sprague	1
	2N6396	SCR		1
	2N6039	Power Transistor		1
	2N2222A	Small Signal Transistor		1
	RS2027	1 Watt, 27 ohm, 1%		1
	RC07GF271J	1/4 Watt, 270 ohm, 5%		1
		Capton Tape		1
11	<u>Measurement Network</u>			
	RH-5,1ohm	1%, 5W Resistor	Dale	2
	RMC6507501F	7.5Kohm, 1% Resistor	Dale	2
	RMC65H2262F5	22.6Kohm, 1% Resistor	Dale	2
	300TE1305	20nF Capacitor	Sprague	2
12	72103	Terminal Blocks	Vernitron	2
13	DB25S	'D' Type, 25 Pin Female Connector	Ampherol	1

BOARD NO. 1 MODULE LAYOUT

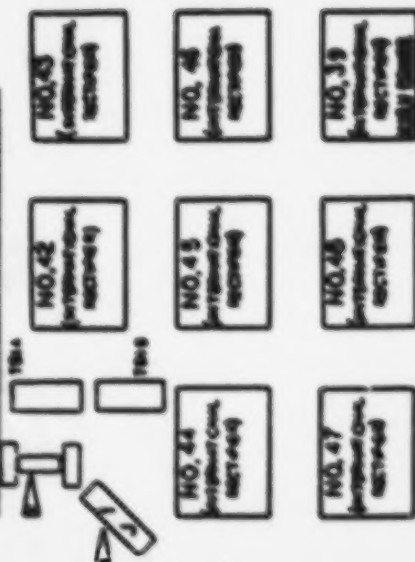

BOARD NO. 1 TERMINAL BLOCK DESCRIPTION

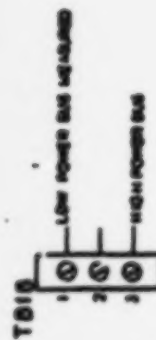

ORIGINAL PAGE IS
OF POOR QUALITY

BOARD NO. 1 J1 PIN DEFINITION


PIN NO	FOR RELAY NO	SYMBOL
1	41	EN0002
2	42	EN0003
3	43	EN0004
4	44	EN0005
5	45	EN0006
6	46	EN0007
7	47	EN0008
8	48	EN0009
9	49	EN0010
10	41	EN0011
11	42	EN0012
12	43	EN0013
13	44	EN0014
14	45	EN0015
15	46	EN0016
16	47	EN0017
17	48	EN0018
18	49	EN0019
19	41	EN0020
20	42	EN0021
21	43	EN0022
22	44	EN0023
23	45	EN0024
24	46	EN0025
25	47	EN0026
26	48	EN0027
27	49	EN0028
28	41	EN0029
29	42	EN0030
30	43	EN0031
31	44	EN0032
32	45	EN0033
33	46	EN0034
34	47	EN0035
35	48	EN0036
36	49	EN0037
37	41	EN0038
38	42	EN0039
39	43	EN0040
40	44	EN0041
41	45	EN0042
42	46	EN0043
43	47	EN0044
44	48	EN0045
45	49	EN0046
46	41	EN0047
47	42	EN0048
48	43	EN0049
49	44	EN0050
50	45	EN0051
51	46	EN0052
52	47	EN0053
53	48	EN0054
54	49	EN0055
55	41	EN0056
56	42	EN0057
57	43	EN0058
58	44	EN0059
59	45	EN0060
60	46	EN0061
61	47	EN0062
62	48	EN0063
63	49	EN0064
64	41	EN0065
65	42	EN0066
66	43	EN0067
67	44	EN0068
68	45	EN0069
69	46	EN0070
70	47	EN0071
71	48	EN0072
72	49	EN0073
73	41	EN0074
74	42	EN0075
75	43	EN0076
76	44	EN0077
77	45	EN0078
78	46	EN0079
79	47	EN0080
80	48	EN0081
81	49	EN0082
82	41	EN0083
83	42	EN0084
84	43	EN0085
85	44	EN0086
86	45	EN0087
87	46	EN0088
88	47	EN0089
89	48	EN0090
90	49	EN0091
91	41	EN0092
92	42	EN0093
93	43	EN0094
94	44	EN0095
95	45	EN0096
96	46	EN0097
97	47	EN0098
98	48	EN0099
99	49	EN0100

NOTES:


- CONNECTION J1 IS A 30-POLE TYPE BOARD CONNECTION
- REQUIREMENT: 100VDC

BOARD NO. 1 LAYOUT AND SCHEMATIC, EIES PROGRAM	
DATE: 20 MAR 65	BY: 1845PABE161C
1	2
3	4
5	6
7	8
9	10
11	12
13	14
15	16
17	18
19	20
21	22
23	24
25	26
27	28
29	30
31	32
33	34
35	36
37	38
39	40
41	42
43	44
45	46
47	48
49	50
51	52
53	54
55	56
57	58
59	60
61	62
63	64
65	66
67	68
69	70
71	72
73	74
75	76
77	78
79	80
81	82
83	84
85	86
87	88
89	90
91	92
93	94
95	96
97	98
99	100

(BOARD-1) MODULE-44

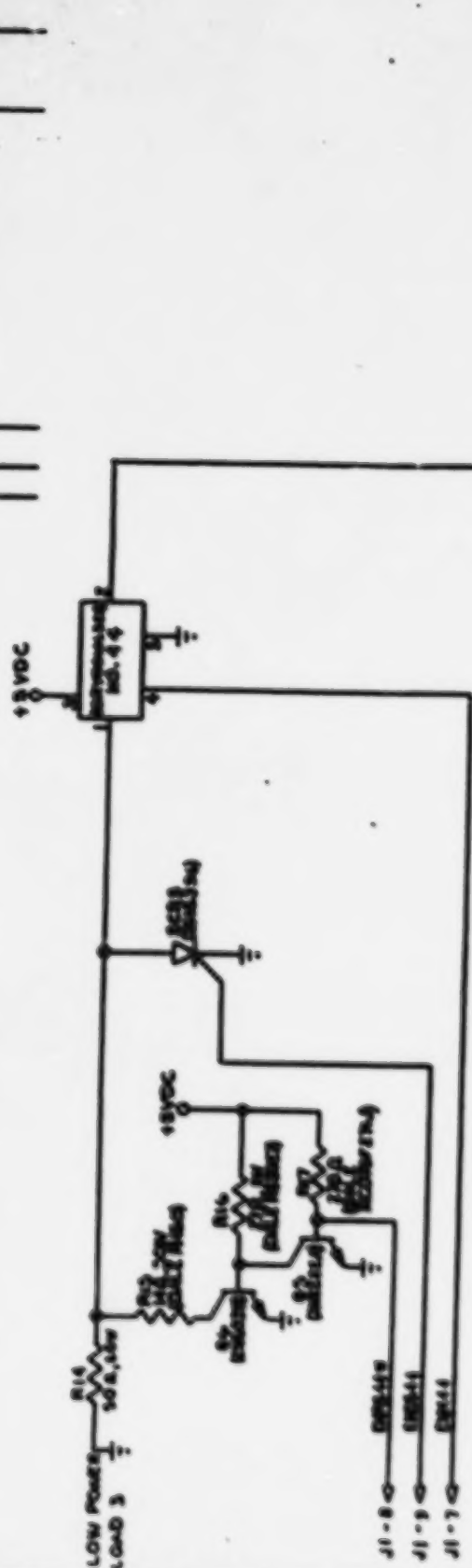


(BOARD-1) MODULE-45

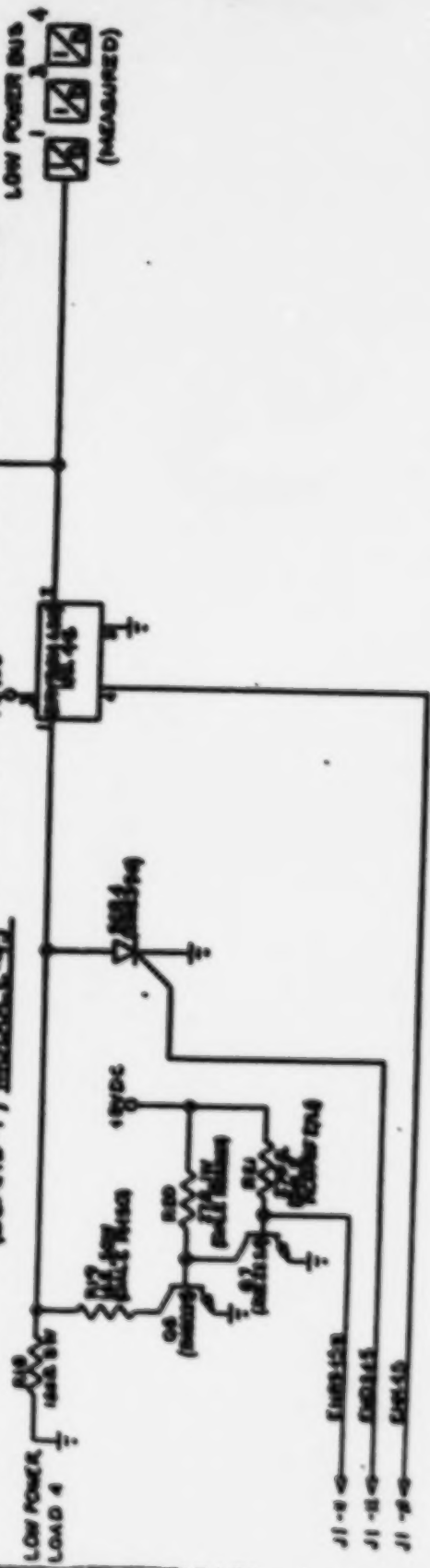

LOW POWER BUS
(MEASURED)

C 04234 849PADBI611

(BOARD-1) MODULE-42

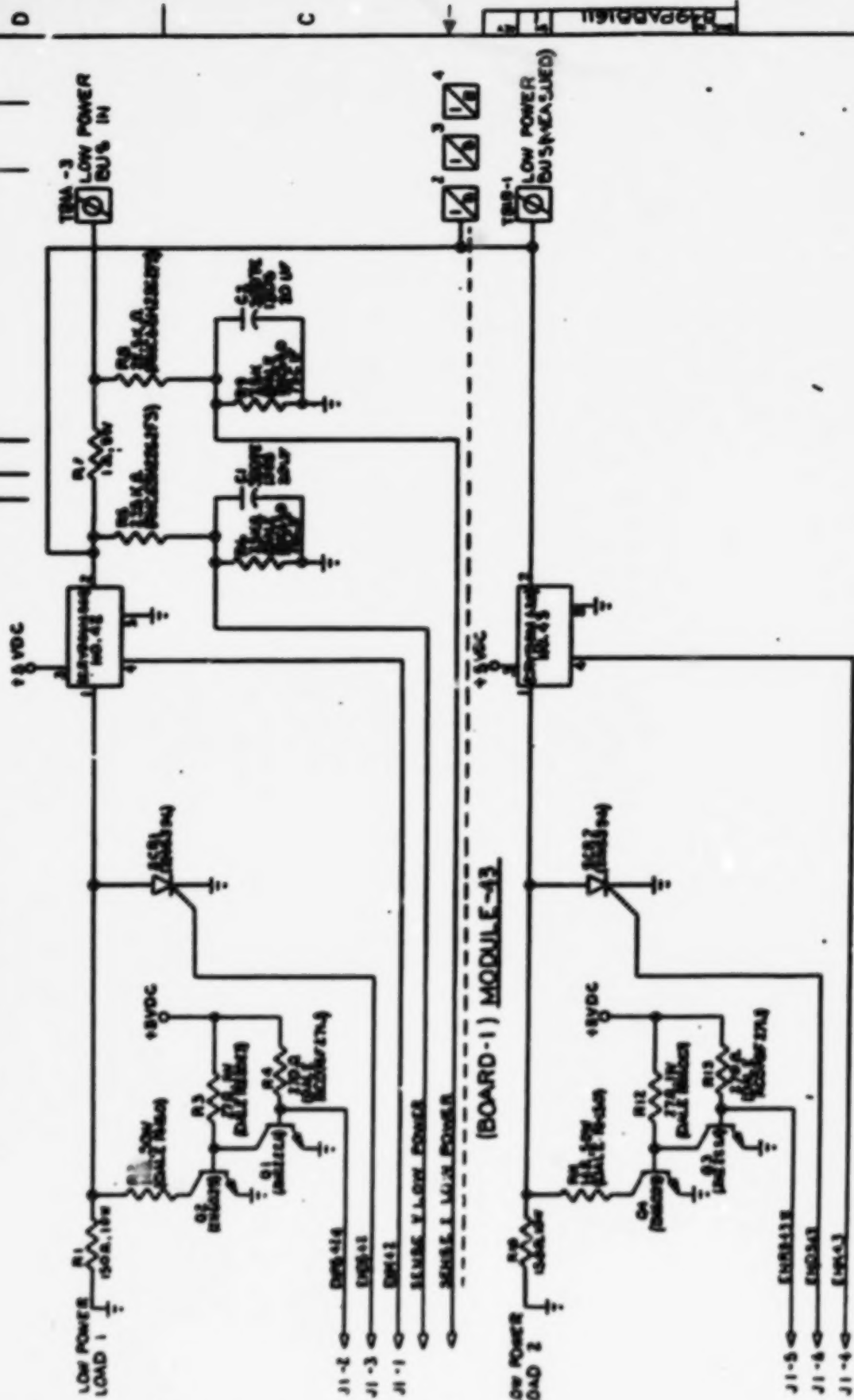

REV	04236	849PABBI611	1 OF 4
DATE	04/23/61	BY	

POWER SYSTEM - BOARD 2

Drawing #PL849PASS1620

<u>Item #</u>	<u>Part #</u>	<u>Description</u>	<u>MFG</u>	<u>QTY</u>
1		T4 Aluminum	MHC	1
2		2/56 Screw	NL Fasteners	4
3	<u>Module 38</u>			
	6321	Solid State Relay	Cryden	1
	ME-50,14 ohm	1%, 50W Resistor	Dale	1
	ME-5,270ohm	1%, 50W Resistor	Dale	1
	2N6396	SCR	Motorola	1
	2N6039	Power Transistor	Motorola	1
	2N2222A	Small Signal Transistor	Motorola	1
	RS2027	1 Watt, 27 ohm, 1%	Dale	1
	RC07GF271J	1/4 Watt, 270 ohm, 5%	Allen-Bradley	1
		Capton Tape		1
4	<u>Module 37</u>			
	6321	Solid State Relay	Cryden	1
	ME-50,14 ohm	1%, 50W Resistor	Dale	1
	H-5,50 ohm	1%, 50W Resistor	Dale	1
	2N6396	SCR	Motorola	1
	2N6039	Power Transistor	Motorola	1
	2N2222A	Small Signal Transistor	Motorola	1
	RS2027	1 Watt, 27 ohm, 1%	Dale	1
	RC07GF271J	1/4 Watt, 270 ohm, 5%	Allen-Bradley	1
		Capton Tape		1
5	<u>Module 36</u>			
	6321	Solid State Relay	Cryden	1
	ME-50,14 ohm	1%, 50W Resistor	Dale	1
	ME-5,200ohm	1%, 5W Resistor	Dale	2
	2N6396	SCR	Motorola	1
	2N6039	Power Transistor	Motorola	1
	2N2222A	Small Signal Transistor	Motorola	1
	RS2027	1 Watt, 27 ohm, 1%	Dale	1
	RC07GF271J	1/4 Watt, 270 ohm, 5%	Allen-Bradley	1
		Capton Tape		1

POWER SYSTEM - BOARD 2
Con't

Drawing #PL849PAB21620

<u>Item #</u>	<u>Part #</u>	<u>Description</u>	<u>MFG</u>	<u>QTY</u>
6	Module 35			
	6321	Solid State Relay	Cryden	1
	NH-50,14 ohm	1%, 50W Resistor	Dale	1
	NH-50,27ohm	1%, 50W Resistor	Dale	1
	2N6396	SCR	Motorola	1
	2N6039	Power Transistor	Motorola	1
	2N2222A	Small Signal Transistor	Motorola	1
	RS2027	1 Watt, 27 ohm, 1%	Dale	1
	RC07GF271J	1/4 Watt, 270 ohm, 5%	Allen-Bradley	1
		Capton Tape		1
7	Module 34			
	6321	Solid State Relay	Cryden	1
	RH-50,50 ohm	1%, 50W Resistor	Dale	1
	NH-50,14 ohm	1%, 50W Resistor	Dale	1
	2N6396	SCR	Motorola	1
	2N6039	Power Transistor	Motorola	1
	2N2222A	Small Signal Transistor	Motorola	1
	RS2027	1 Watt, 27 ohm, 1%	Dale	1
	RC07GF271J	1/4 Watt, 270 ohm, 5%	Allen-Bradley	1
		Capton Tape		1
8	Module 33			
	6321	Solid State Relay	Cryden	1
	NH-50,14 ohm	1%, 50W Resistor	Dale	1
	RH-10,100ohm	1%, 10W Resistor	Dale	1
	2N6396	SCR	Motorola	1
	2N6039	Power Transistor	Motorola	1
	2N2222A	Small Signal Transistor	Motorola	1
	RS2027	1 Watt, 27 ohm, 1%	Dale	1
	RC07GF271J	1/4 Watt, 270 ohm, 5%	Allen-Bradley	1
		Capton Tape		1


POWER SYSTEM - BOARD 2

Con't

Drawing #PL849PAB1620

<u>Item #</u>	<u>Part #</u>	<u>Description</u>	<u>MFG</u>	<u>QTY</u>
9	<u>Module 41</u>			
	6321	Solid State Relay	Cryden	1
	RE-50,14 ohm	1%, 50W Resistor	Dale	1
	RE-25,16 ohm	1%, 25W Resistor	Dale	1
	2N6396	SCR	Motorola	1
	2N6039	Power Transistor	Motorola	1
	2N2222A	Small Signal Transistor	Motorola	1
	RS2027	1 Watt, 27 ohm, 1%	Dale	1
	RC07GF271J	1/4 Watt, 270 ohm, 5%	Allen-Bradley	1
		Capton Tape		1
10	<u>Module 40</u>			
	6321	Solid State Relay		1
	RE-50,14 ohm	1%, 50W Resistor		2
	TVA-1305.5	20vF, 50V Capacitor	Sprague	1
	2N6396	SCR	Motorola	1
	2N6039	Power Transistor		1
	2N2222A	Small Signal Transistor		1
	RS2027	1 Watt, 27 ohm, 1%		1
	RC07GF271J	1/4 Watt, 270 ohm, 5%		1
		Capton Tape		1
11	<u>Measurement Network</u>			
	RE-5, 1ohm	1%, 5W Resistor	Dale	2
	RNC6507501F	7.5K ohm, 1% Resistor	Dale	2
	RNC65H2262F3	22.6K ohm, 1% Resistor	Dale	2
	300TE1305	20vF Capacitor	Sprague	2
12	72103	Terminal Blocks	Vernitron	2
13	DE253	'D' Type, 25 Pin Female Connector	Ampherol	1

BOARD NO.2 MODULE LAYOUT

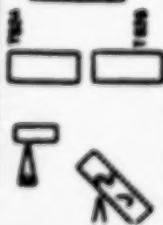

NO.40
INTERMEDIATE
SECTION
2.5-100

NO.35
INTERMEDIATE
SECTION
2.5-100

NO.34
INTERMEDIATE
SECTION
2.5-100

NO.36
INTERMEDIATE
SECTION
2.5-100

NO.36
INTERMEDIATE
SECTION
2.5-100

NO.37
INTERMEDIATE
SECTION
2.5-100

NO.38
INTERMEDIATE
SECTION
2.5-100



NOTES:

- ▷ Containing 2.5-100, 3-1000 component
- ▷ Assembly diagram attached

▷ BOARD NO.2 J2 PIN DEFINITION


PIN NO.	FOR RELAY NO.	SIGNAL
1	40	ENR40
2	40	ENR40*
3	40	ENR40*
4	41	ENR41
5	41	ENR41*
6	41	ENR41*
7	42	ENR42
8	42	ENR42*
9	42	ENR42*
10	43	ENR43
11	43	ENR43*
12	43	ENR43*
13	44	ENR44
14	44	ENR44*
15	44	ENR44*
16	45	ENR45
17	45	ENR45*
18	45	ENR45*
19	46	ENR46
20	46	ENR46*
21	46	ENR46*
22	47	ENR47
23	47	ENR47*
24	47	ENR47*
25	48	ENR48
26	48	ENR48*
27	48	ENR48*
28	49	ENR49
29	49	ENR49*
30	49	ENR49*

BOARD NO.2 TERMINAL BLOCK DESCRIPTION

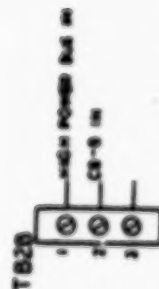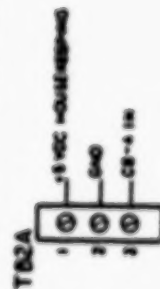


MARTIN MARETTA CORPORATION 1000 MARSHALL RD. SUITE 100 FARMINGDALE, N.Y. 11735	
BOARD NO.2 LAYOUT AND SCHEMATIC FILES PROGRAM	
DATE	1849PABR1620
REV	203605
V	

(BOARD-2) MODULE-16

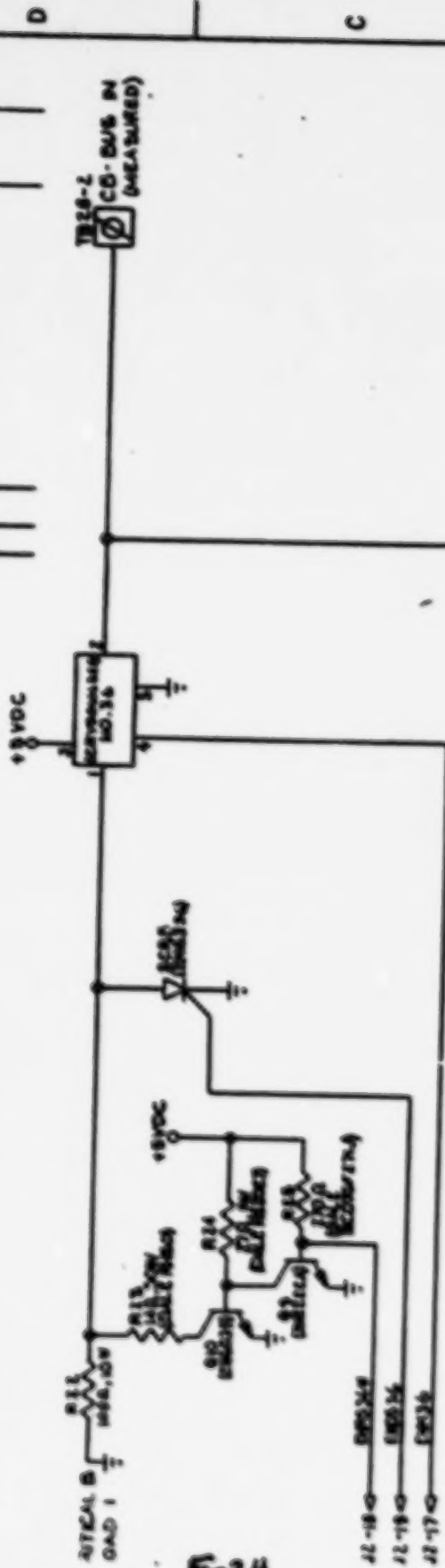



(BOARD-2) MODULE-37

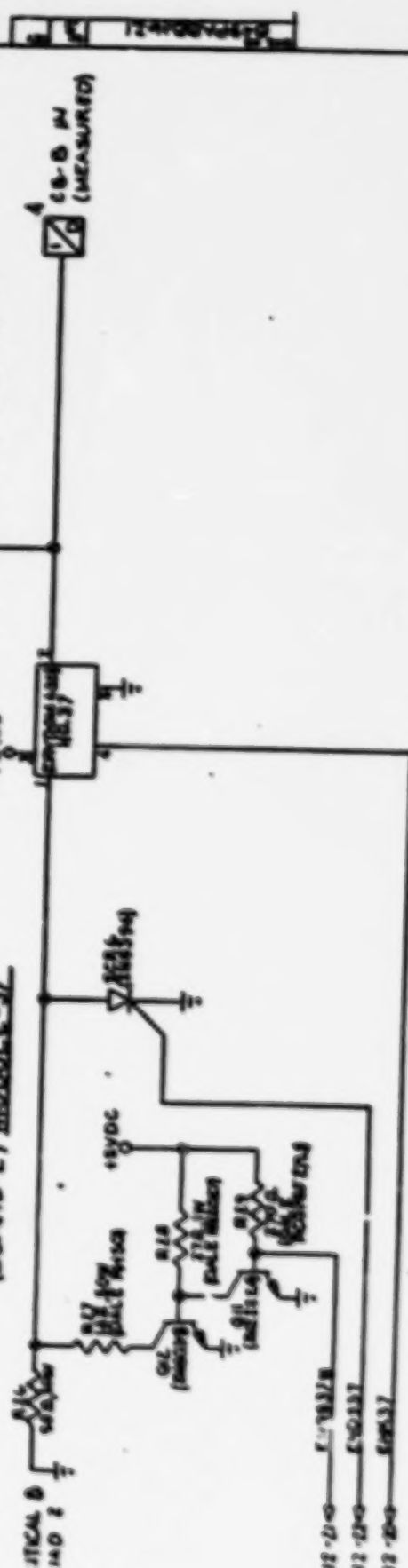

Rev	04236	849PABBI621	Rev
C	04236	849PABBI621	Rev
1	1	1	1

F-24

(BOARD-2) MODULE-33

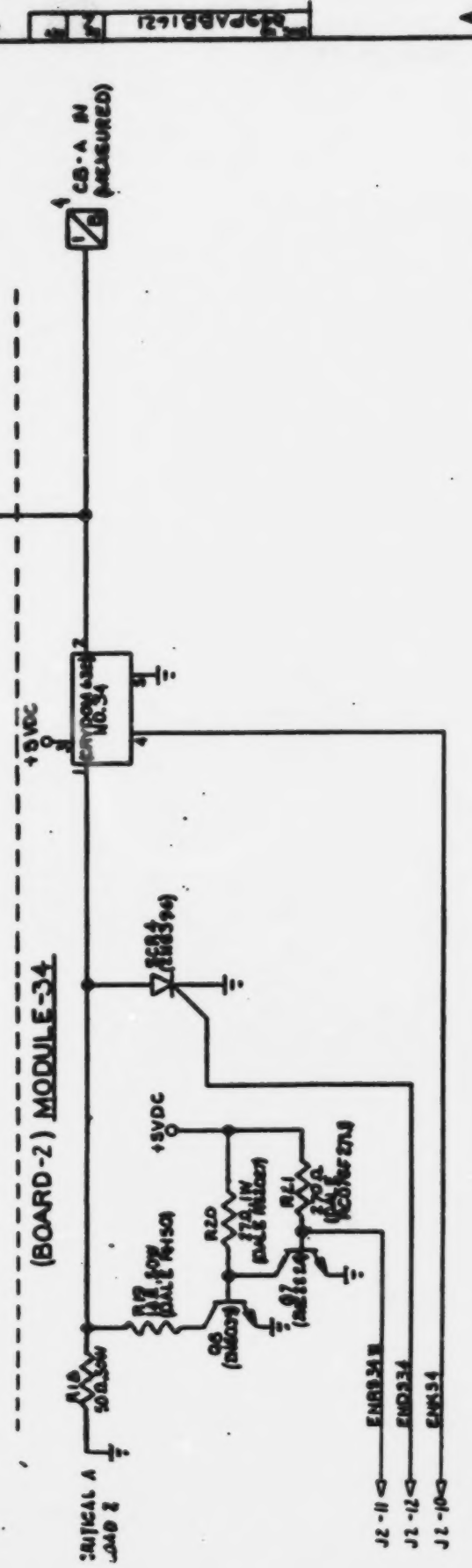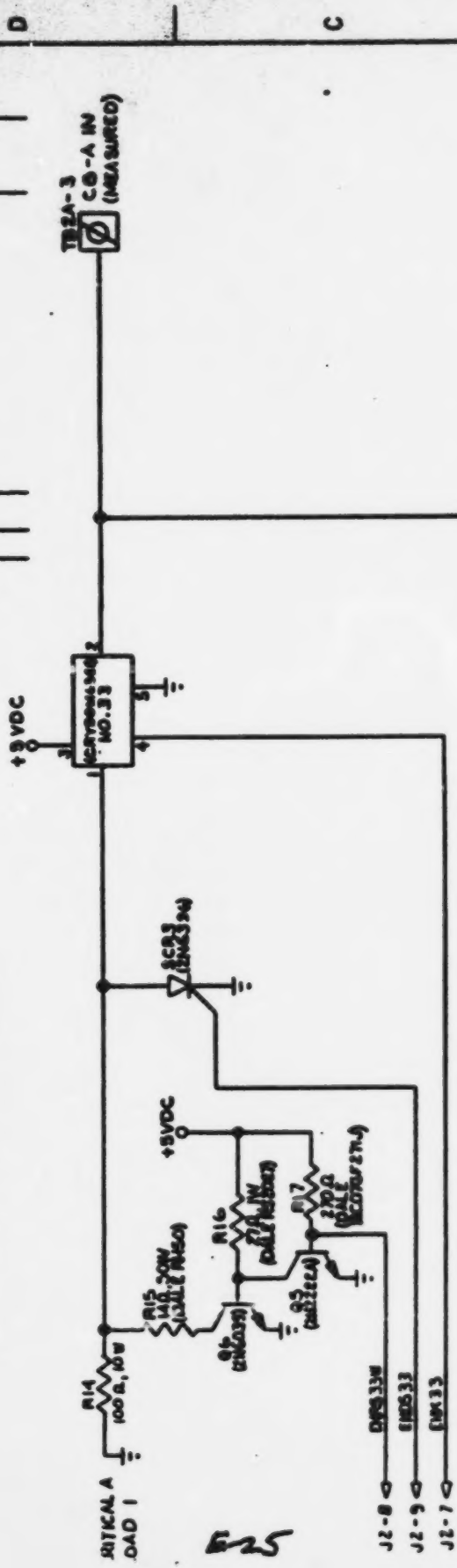

REV	04236	849PAB81621	REV
DATE	04/23/84	DATE	04/23/84

POWER SYSTEM - BOARD 3

Drawing #PL849PAB81630

<u>Item #</u>	<u>Part #</u>	<u>Description</u>	<u>MFG</u>	<u>QTY</u>
1		T4 Aluminum	MHC	1
2		2/56 Screw	NL Fasteners	4
3	<u>Module 29</u>			
	R10-E6-X2-			
	V185	DPDT Relay	Potter-Brumfield	1
	ME-50, 14 ohm	1%, 50W Resistor	Dale	1
	RC07GF201J,			
	200ohm	1/4W, 5% Resistor	Allen-Bradley	1
	2N6396	SCR	Motorola	1
	2N6039	Power Transistor	Motorola	1
	2N2222A	Small Signal Transistor	Motorola	2
	RS2027	1W, 27 ohm, 1%	Dale	1
	RC07GF271J	270 ohm, 5%, 1/4W	Allen-Bradley	2
	RE-5, .1 ohm	1%, 5W Resistor	Dale	1
	572-4820-			
	01-05-16	Terminal Post	Midland-Ross	1
		Capton Tape		1
4	<u>Module 28</u>			
	R10-E6-X2-			
	V185	DPDT Relay	Potter-Brumfield	1
	ME-50, 14 ohm	1%, 50W Resistor	Dale	1
	RC07GF201J,			
	200ohm	1/4W, 5% Resistor	Allen-Bradley	1
	2N6396	SCR	Motorola	1
	2N6039	Power Transistor	Motorola	1
	2N2222A	Small Signal Transistor	Motorola	2
	RS2027	1W, 27 ohm, 1%	Dale	1
	RC07GF271J	270 ohm, 5%, 1/4W	Allen-Bradley	2
	RE-5, .1 ohm	1%, 5W Resistor	Dale	1
	572-4820-			
	01-05-16	Terminal Post	Midland-Ross	1
		Capton Tape		1

POWER SYSTEM - BOARD 3
Circuit

Drawing 0FL04-0FARS1630


Item #	Part #	Description	MTV	QTY
5	Module 27			
	R10-S6-X2-			
	V185	DPDT Relay	Potter-Brumfield	1
	RE-50,14 ohm	1%, 50W Resistor	Dale	1
	RC07GF201J	1/4W, 5% Resistor	Allen-Bradley	1
	2N6396	SCR	Motorola	1
	2N6039	Power Transistor	Motorola	1
	2N2222A	Small Signal Transistor	Motorola	2
	RE2027	1W, 27 ohm, Resistor	Dale	1
	RC07GF271J	270 ohm, 5%, 1/4W	Allen-Bradley	2
	572-4820-			
	01-05-16	Terminal Post	Midland-Ross	1
		Capton Tape		1
6	Module 26			
	R10-S6-X2-			
	V185	DPDT Relay	Potter-Brumfield	1
	RE-50,14 ohm	1%, 50W Resistor	Dale	1
	RC07GF201J	1/4W, 5% Resistor	Allen-Bradley	1
	2N6396	SCR	Motorola	1
	2N6039	Power Transistor	Motorola	1
	2N2222A	Small Signal Transistor	Motorola	2
	RE2027	1W, 27 ohm, Resistor	Dale	1
	RC07GF271J	270 ohm, 5%, 1/4W	Allen-Bradley	2
	572-4820-			
	01-05-16	Terminal Post	Midland-Ross	1
		Capton Tape		1
7	Module 25			
	R10-S6-X2-			
	V185	DPDT Relay	Potter-Brumfield	1
	RE-50,14 ohm	1%, 50W Resistor	Dale	1
	RC07GF201J	1/4W, 5% Resistor	Allen-Bradley	1
	2N6396	SCR	Motorola	1
	2N6039	Power Transistor	Motorola	1
	2N2222A	Small Signal Transistor	Motorola	2
	RE2027	1W, 27 ohm, Resistor	Dale	1
	RC07GF271J	270 ohm, 5%, 1/4W	Allen-Bradley	2
	572-4820-			
	01-05-16	Terminal Post	Midland-Ross	1
		Capton Tape		1

POWER SYSTEM - BOARD 3
Can't

Drawing #FL849PABD1630

<u>Item #</u>	<u>Part #</u>	<u>Description</u>	<u>MFG</u>	<u>QTY</u>
8	<u>Module 21</u>			
	R10-S6-X2-			
	V185	DPDT Relay	Potter-Brumfield	1
	HM-50,14 ohm	1%, 50W Resistor	Dale	1
	RC07GF201J	1/4W, 5% Resistor	Allen-Bradley	1
	2N6396	SCR	Motorola	1
	2N6039	Power Transistor	Motorola	1
	2N2222A	Small Signal Transistor	Motorola	2
	RS2027	1W, 27 ohm, Resistor	Dale	1
	RC07GF271J	270 ohm, 5%, 1/4W	Allen-Bradley	2
		Capton Tape		1
9	<u>Module 19</u>			
	R10-S6-X2-			
	V185	DPDT Relay	Potter-Brumfield	1
	HM-50,14 ohm	1%, 50W Resistor	Dale	1
	RC07GF201J	1/4W, 5% Resistor	Allen-Bradley	1
	2N6396	SCR	Motorola	1
	2N6039	Power Transistor	Motorola	1
	2N2222A	Small Signal Transistor	Motorola	2
	RS2027	1W, 27 ohm, Resistor	Dale	1
	RC07GF271J	270 ohm, 5%, 1/4W	Allen-Bradley	2
		Capton Tape		1
10	<u>Module 20</u>			
	R10-S6-X2-			
	V185	DPDT Relay	Potter-Brumfield	1
	HM-50,14 ohm	1%, 50W Resistor	Dale	1
	RC07GF201J	1/4W, 5% Resistor	Allen-Bradley	1
	2N6396	SCR	Motorola	1
	2N6039	Power Transistor	Motorola	1
	2N2222A	Small Signal Transistor	Motorola	2
	RS2027	1W, 27 ohm, Resistor	Dale	1
	RC07GF271J	270 ohm, 5%, 1/4W	Allen-Bradley	2
		Capton Tape		1
11	72103	Terminal Blocks	Vernitron	3
12	BR258	'D' Type, 25 Pin Connector, Female	Amphenol	1

BOARD NO.3 MODULE LAYOUT

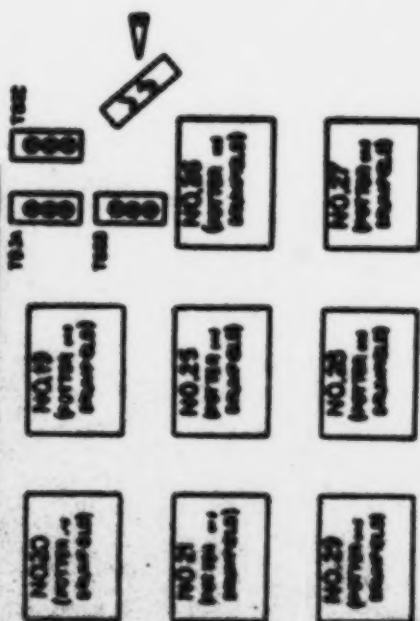


BOARD NO.3 TERMINAL BLOCK DESCRIPTION



BOARD NO.3 J2 PIN DEFINITION

PIN NO. FOR RELAY NO.

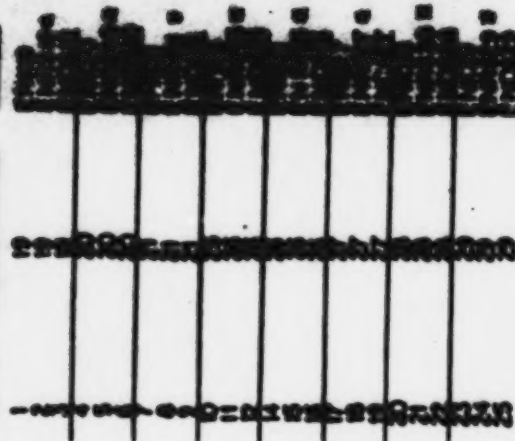



ORIGINAL FROM IN
OF FOUR QUALITIES

NOTES:



- 1. THE BOARD NO. 3 IS A POWER SUPPLY BOARD. IT IS NOT A RELAY BOARD.
- 2. THE BOARD NO. 3 IS A POWER SUPPLY BOARD. IT IS NOT A RELAY BOARD.
- 3. THE BOARD NO. 3 IS A POWER SUPPLY BOARD. IT IS NOT A RELAY BOARD.

BOARD NO.3 LAYOUT AND SCHEMATIC, EES 8000000	DATE: 10/10/60	BY: J. J. J.
REVISION: 1	DATE: 10/10/60	BY: J. J. J.
REVISION: 2	DATE: 10/10/60	BY: J. J. J.
REVISION: 3	DATE: 10/10/60	BY: J. J. J.
REVISION: 4	DATE: 10/10/60	BY: J. J. J.
REVISION: 5	DATE: 10/10/60	BY: J. J. J.
REVISION: 6	DATE: 10/10/60	BY: J. J. J.
REVISION: 7	DATE: 10/10/60	BY: J. J. J.
REVISION: 8	DATE: 10/10/60	BY: J. J. J.
REVISION: 9	DATE: 10/10/60	BY: J. J. J.
REVISION: 10	DATE: 10/10/60	BY: J. J. J.

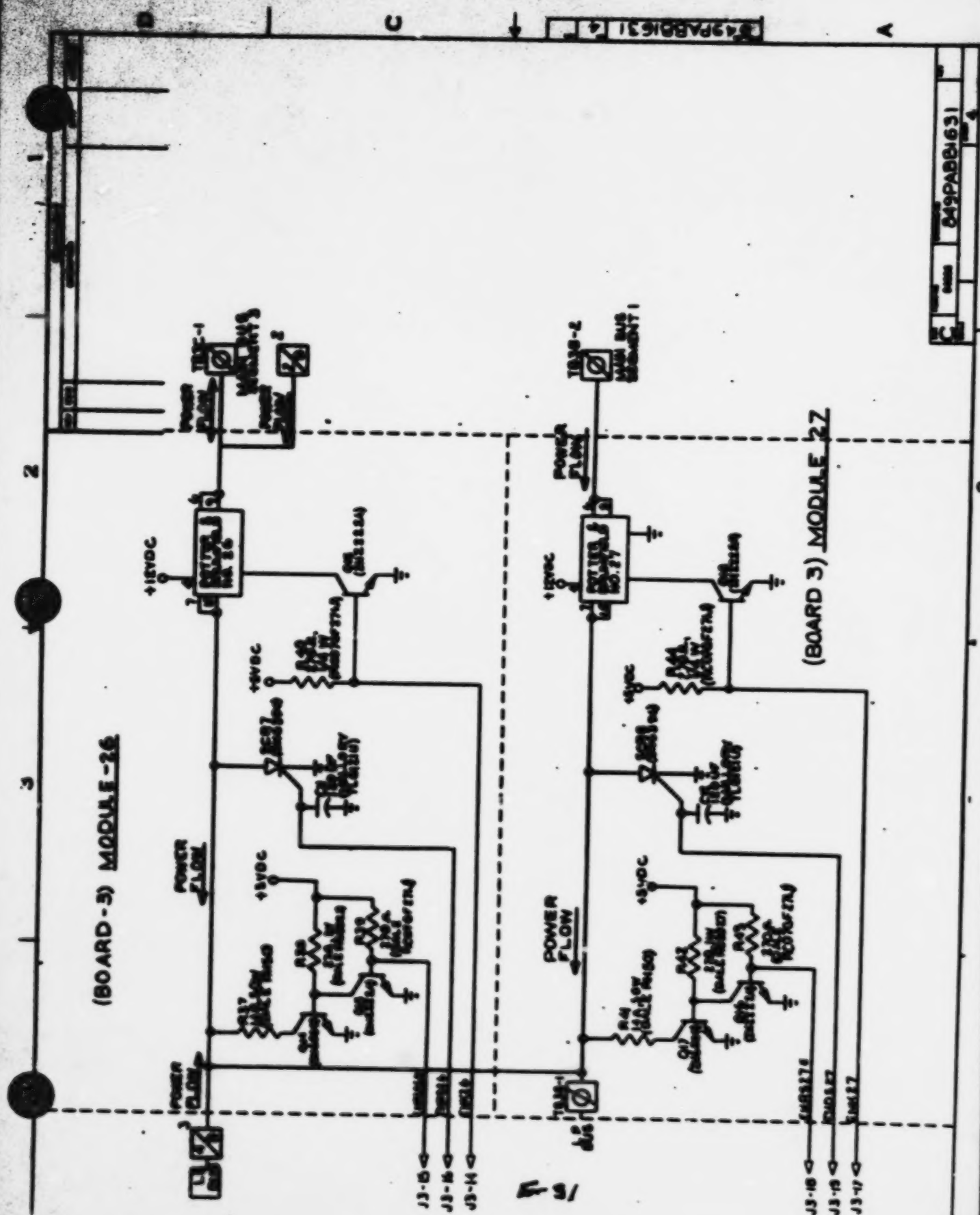

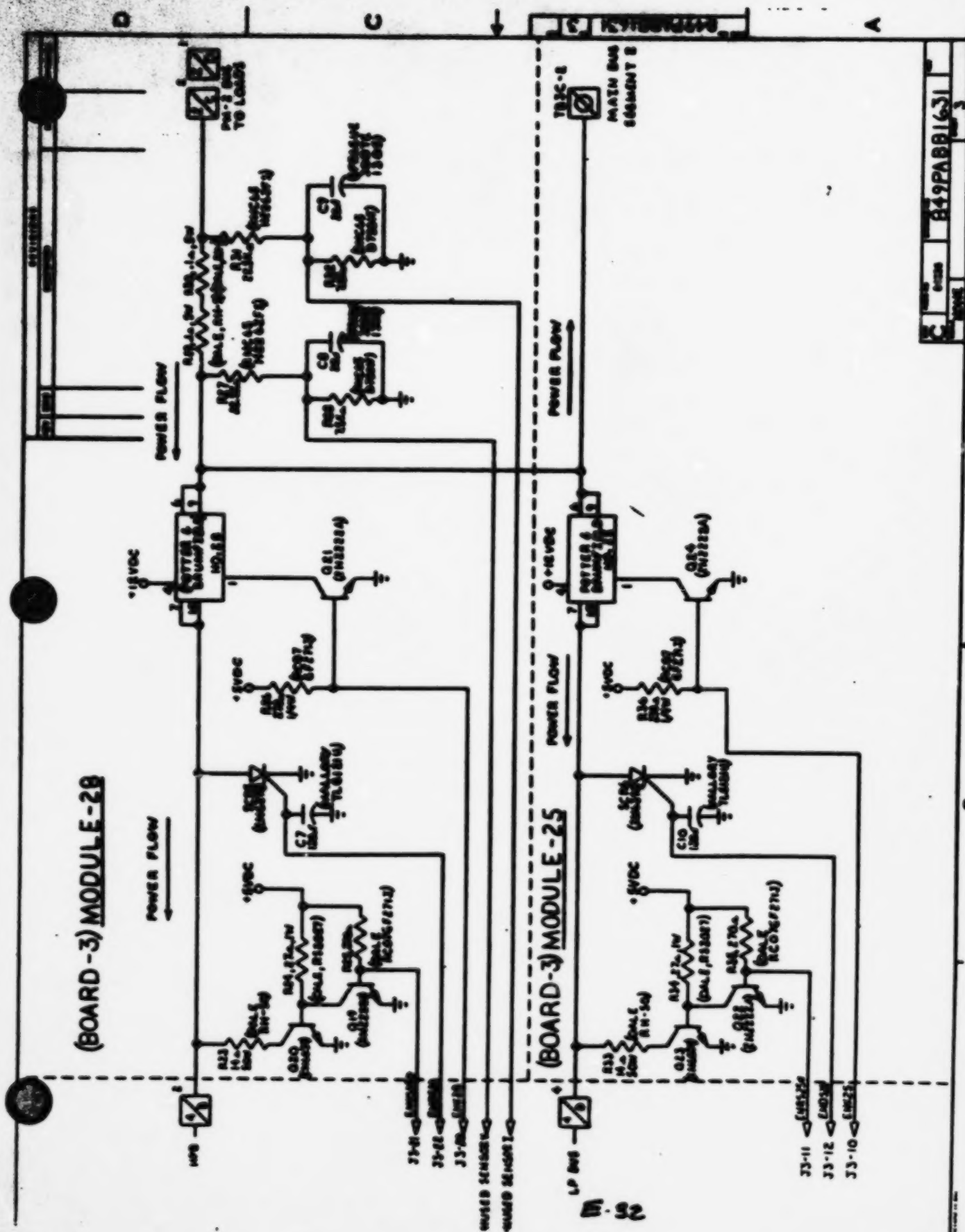

(BOARD 3) MODULE 20

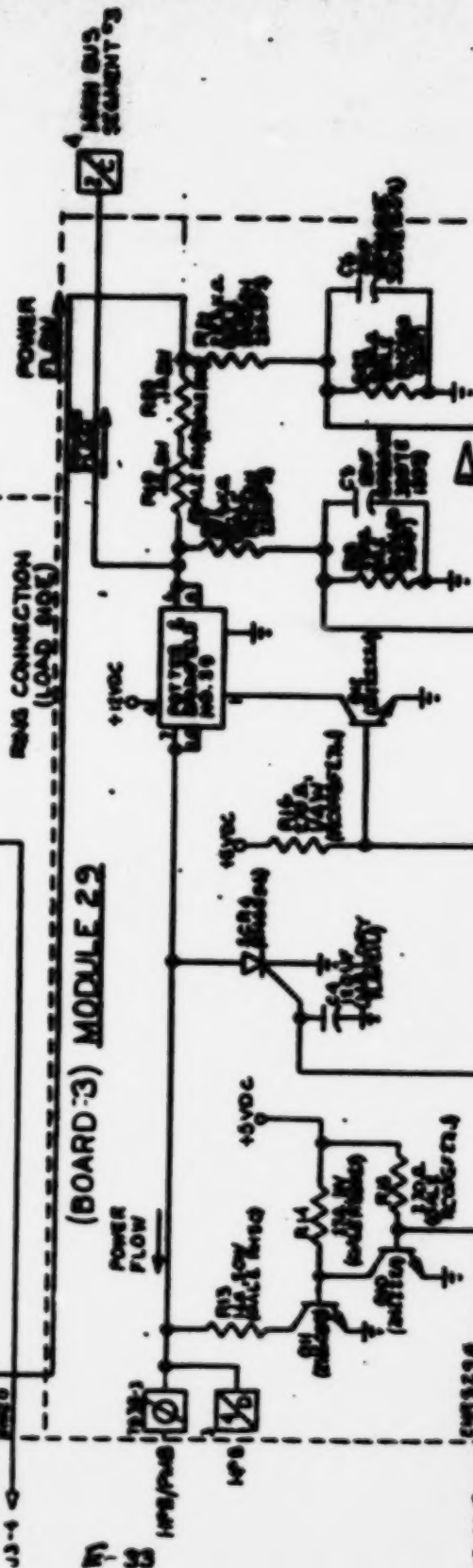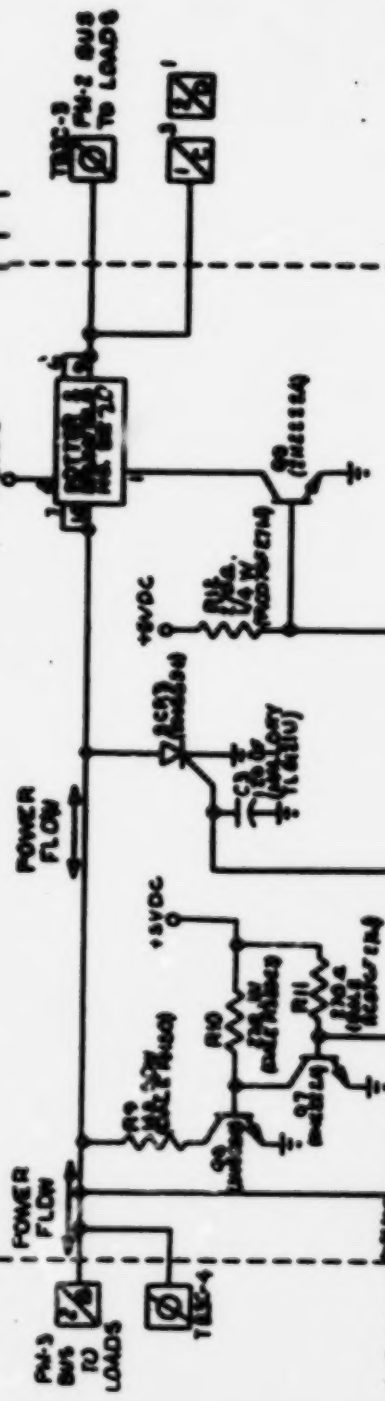

THE UNUSED SENSOR LOCATION WAS TO MEASURE POWER FLOWING TO ANY LOAD BUSLOW HIGH CRITICAL WARD IS CONSUMING POWER FROM THE MAIN BUS RING, SEGMENT 23

1



E-34



E-34

E-34

POWER SYSTEM - BOARD 4

Drawing #PL849PAB1640

<u>Item #</u>	<u>Part #</u>	<u>Description</u>	<u>MFG</u>	<u>QTY</u>
1		T4 Aluminum	MHC	1
2		2/56 Screw	NL Fasteners	4
3	<u>Module 15</u>			
	6321	Solid State Relay	Cryden	1
	RE-50, 14 ohm	1%, 50W Resistor	Dale	1
	TVA-1305.5	20vF Capacitor	Sprague	1
	RE-5, .1ohm	1%, 5W Resistor	Dale	2
	RC07GF271J	1/4W, 5% Resistor	Allen-Bradley	1
	RS2027	1W, 27 ohm, 1%	Dale	1
	2N2222A	Small Signal Transistor	Motorola	1
	2N6396	SCR	Motorola	1
	2N6039	Power Transistor	Motorola	1
	TL4121U	120vF Capacitor	Mallory	1
	RNC65H2262FS	22.6K ohm, 1% Resistor	Dale	2
	RNC65D7501F	7.5K ohm, 1% Resistor	Dale	2
	30DTE1305	20vF Capacitor	Sprague	2
4	<u>Module 17</u>			
	R10-E4-X2-			
	V185	DPDT Relay	Potter-Brumfield	1
	RE-50, 14 ohm	1%, 50W Resistor	Dale	1
	RE-5, .1 ohm	1% 5W Resistor	Dale	2
	RC07GF271J	1/4W, 5% Resistor	Allen-Bradley	1
	RS2027	1W, 27 ohm, 1%	Dale	1
	2N2222A	Small Signal Transistor	Motorola	2
	2N6396	SCR	Motorola	1
	2N6039	Power Transistor	Motorola	1
	TL412U	120vF Capacitor	Mallory	1
	RNC65H2262FS	22.6K ohm, 1%	Dale	2
	RNC65D7501F	7.5K ohm, 1%	Dale	2
	30DTE1305	20vF Capacitor	Sprague	2

POWER SYSTEM - BOARD 4
Con't

Drawing #PLS49PABE1640

<u>Item #</u>	<u>Part #</u>	<u>Description</u>	<u>MFG</u>	<u>QTY</u>
5	Module 32			
	R10-E6-X2-			
	V185	DPDT Relay	Potter-Brumfield	1
	RH-50,14 ohm	1%, 50W Resistor	Dale	1
	RH-5, .1 ohm	1% 5W Resisotr	Dale	2
	RC07GF271J	1/4W, 5% Resistor	Allen-Bradley	1
	RS2027	1W, 27 ohm, 1%	Dale	1
	2N2222A	Small Signal Transistor	Motorola	2
	2N6396	SCR	Motorola	1
	2N6039	Power Transistor	Motorola	1
	TL612U	120vF Capacitor	Mallory	1
	RNC65H2262FS	22.6K ohm, 1%	Dale	2
	RNC65D7501F	7.5K ohm, 1%	Dale	2
	300TE1305	20vF Capacitor	Sprague	2
6	Module 31			
	R10-E6-X2-			
	V185	DPDT Relay	Potter-Brumfield	1
	RH-50,14 ohm	1%, 50W Resistor	Dale	1
	RH-5, .1 ohm	1% 5W Resisotr	Dale	2
	RC07GF271J	1/4W, 5% Resistor	Allen-Bradley	1
	RS2027	1W, 27 ohm, 1%	Dale	1
	2N2222A	Small Signal Transistor	Motorola	2
	2N6396	SCR	Motorola	1
	2N6039	Power Transistor	Motorola	1
	TL612U	120vF Capacitor	Mallory	1
	RNC65H2262FS	22.6K ohm, 1%	Dale	2
	RNC65D7501F	7.5K ohm, 1%	Dale	2
	300TE1305	20vF Capacitor	Sprague	2

POWER SYSTEM - BOARD 4
Cm't

Drawing #PL849FAB1640


<u>Item #</u>	<u>Part #</u>	<u>Description</u>	<u>MFG</u>	<u>QTY</u>
7	<u>Module 30</u>			
	R10-E6-X2-			
	V185	DPDT Relay	Potter-Brumfield	1
	RH-50, 14 ohm	1%, 50W Resistor	Dale	1
	RH-5, .1 ohm	1% 5W Resistor	Dale	2
	RC07GF271J	1/4W, 5% Resistor	Allen-Bradley	1
	RS2027	1W, 27 ohm, 1%	Dale	1
	2N2222A	Small Signal Transistor	Motorola	2
	2N6396	SCR	Motorola	1
	2N6039	Power Transistor	Motorola	1
	TL412U	120vF Capacitor	Mallory	1
	RNC65H2262FS	22.6K ohm, 1%	Dale	2
	RNC65D7501F	7.5K ohm, 1%	Dale	2
	30DTE1305	20vF Capacitor	Sprague	2
8	<u>Module 24</u>			
	R10-E6-X2-			
	V185	DPDT Relay	Potter-Brumfield	1
	RH-50, 14 ohm	1%, 50W Resistor	Dale	1
	RH-5, .1 ohm	1% 5W Resistor	Dale	2
	RC07GF271J	1/4W, 5% Resistor	Allen-Bradley	1
	RS2027	1W, 27 ohm, 1%	Dale	1
	2N2222A	Small Signal Transistor	Motorola	2
	2N6396	SCR	Motorola	1
	2N6039	Power Transistor	Motorola	1
	TL412U	120vF Capacitor	Mallory	1
	RNC65H2262FS	22.6K ohm, 1%	Dale	2
	RNC65D7501F	7.5K ohm, 1%	Dale	2
	30DTE1305	20vF Capacitor	Sprague	2

POWER SYSTEM - BOARD 4
Con't

Drawing #PL849PABB1640


<u>Item #</u>	<u>Part #</u>	<u>Description</u>	<u>MFG</u>	<u>QTY</u>
9	Module 23			
	R10-E6-X2-			
	V185	DPDT Relay	Potter-Brumfield	1
	RH-50,14 ohm	1%, 50W Resistor	Dale	1
	RH-5, .1 ohm	1% 5W Resistor	Dale	2
	RC07GF271J	1/4W, 5% Resistor	Allen-Bradley	1
	RS2027	1W, 27 ohm, 1%	Dale	1
	2N2222A	Small Signal Transistor	Motorola	2
	2N6396	SCR	Motorola	1
	2N6039	Power Transistor	Motorola	1
	TL612U	120vF Capacitor	Mallory	1
	RNC65H2262FS	22.6K ohm, 1%	Dale	2
	RNC65D7501F	7.5K ohm, 1%	Dale	2
	300TE1305	20vF Capacitor	Sprague	2
10	Module 22			
	R10-E6-X2-			
	V185	DPDT Relay	Potter-Brumfield	1
	RH-50,14 ohm	1%, 50W Resistor	Dale	1
	RH-5, .1 ohm	1% 5W Resistor	Dale	2
	RC07GF271J	1/4W, 5% Resistor	Allen-Bradley	1
	RS2027	1W, 27 ohm, 1%	Dale	1
	2N2222A	Small Signal Transistor	Motorola	2
	2N6396	SCR	Motorola	1
	2N6039	Power Transistor	Motorola	1
	TL612U	120vF Capacitor	Mallory	1
	RNC65H2262FS	22.6K ohm, 1%	Dale	2
	RNC65D7501F	7.5K ohm, 1%	Dale	2
	300TE1305	20vF Capacitor	Sprague	2

(BOARD-4) MODULE-17

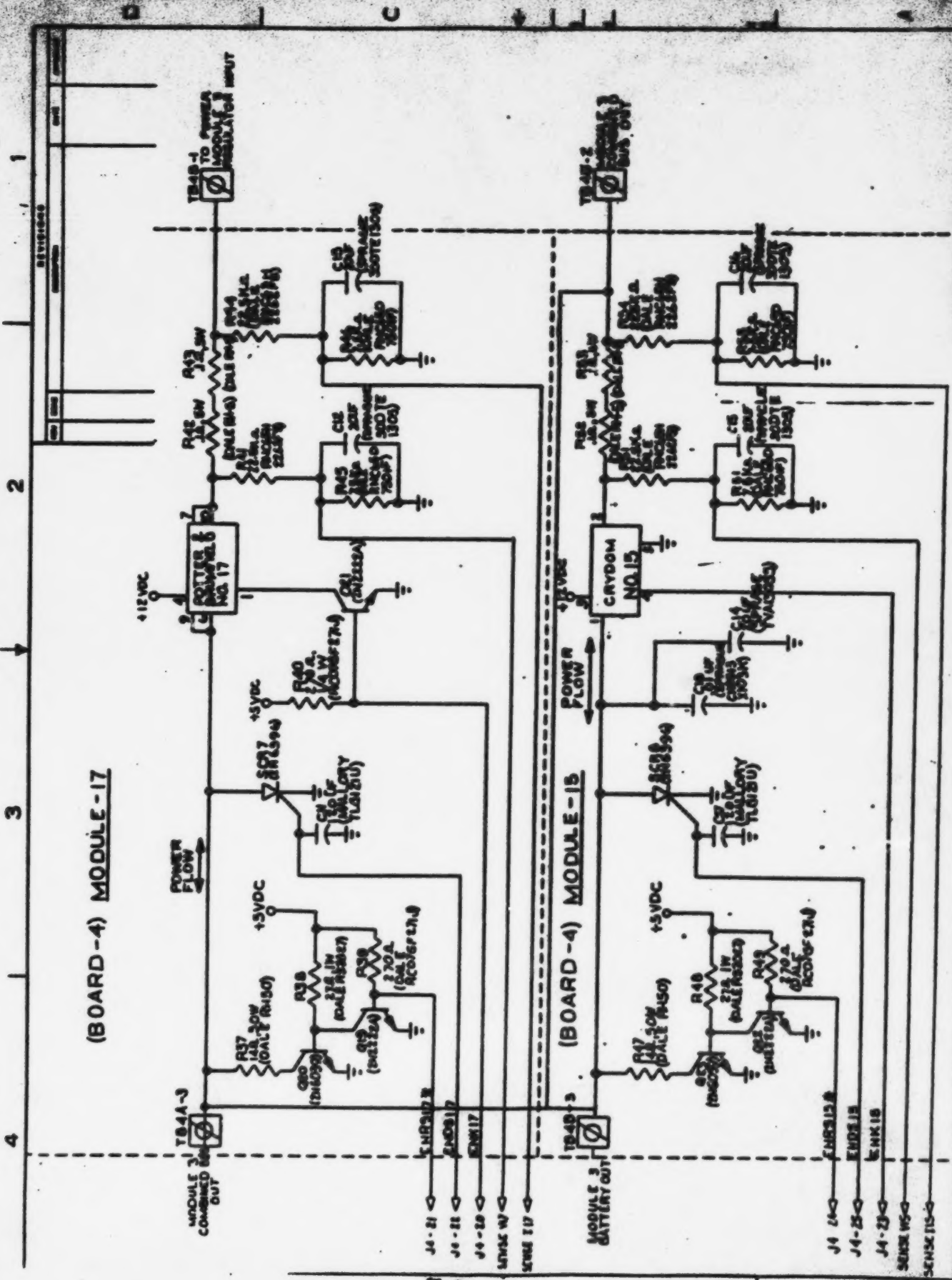

ORIGINAL PAGE IS
OF POOR QUALITY



(BOARD-4) MODULE-3I

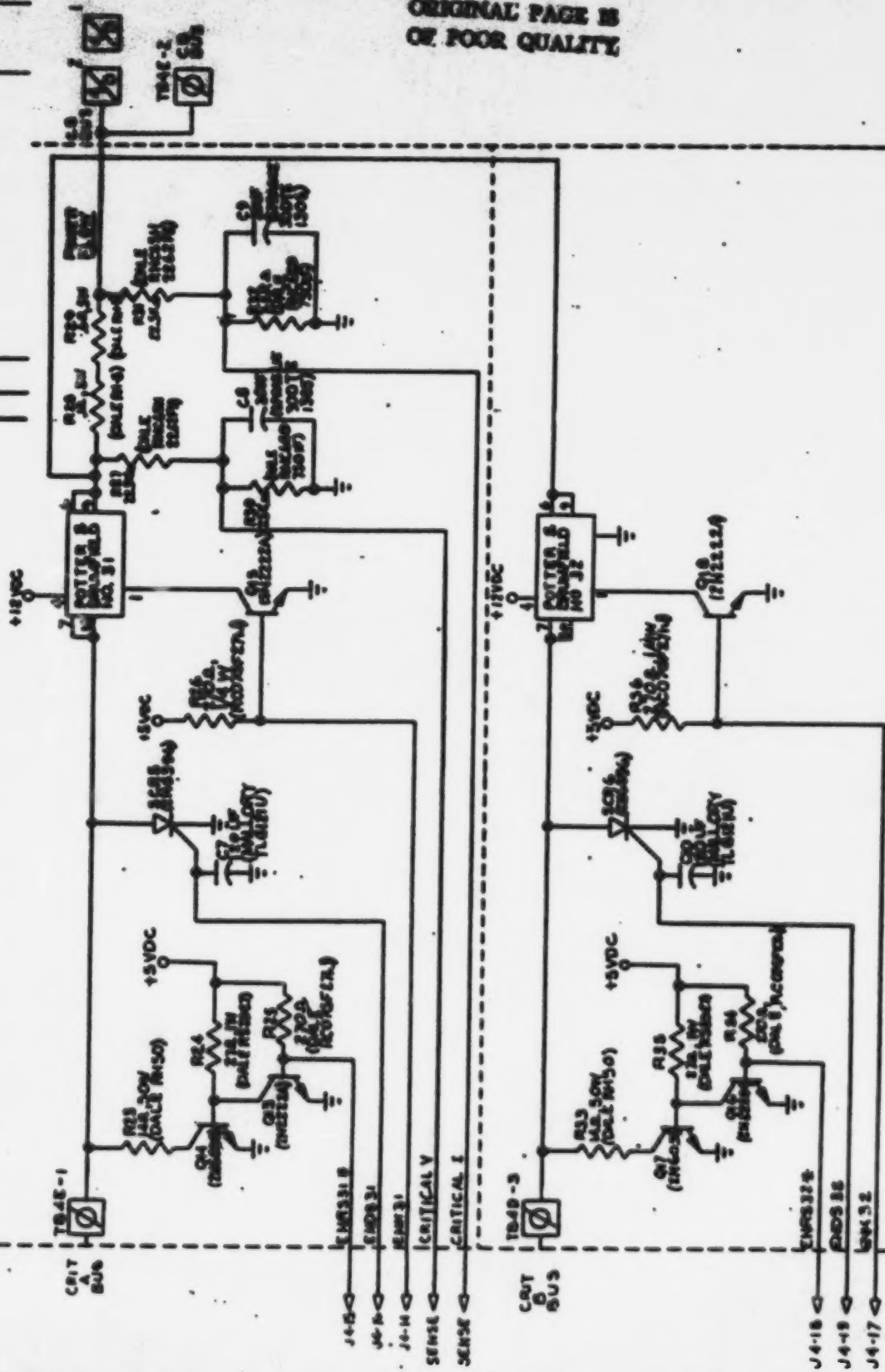


(BOARD-4) MODULE-32

849PAB01641

DATE	09/08/01
------	----------

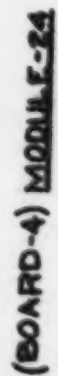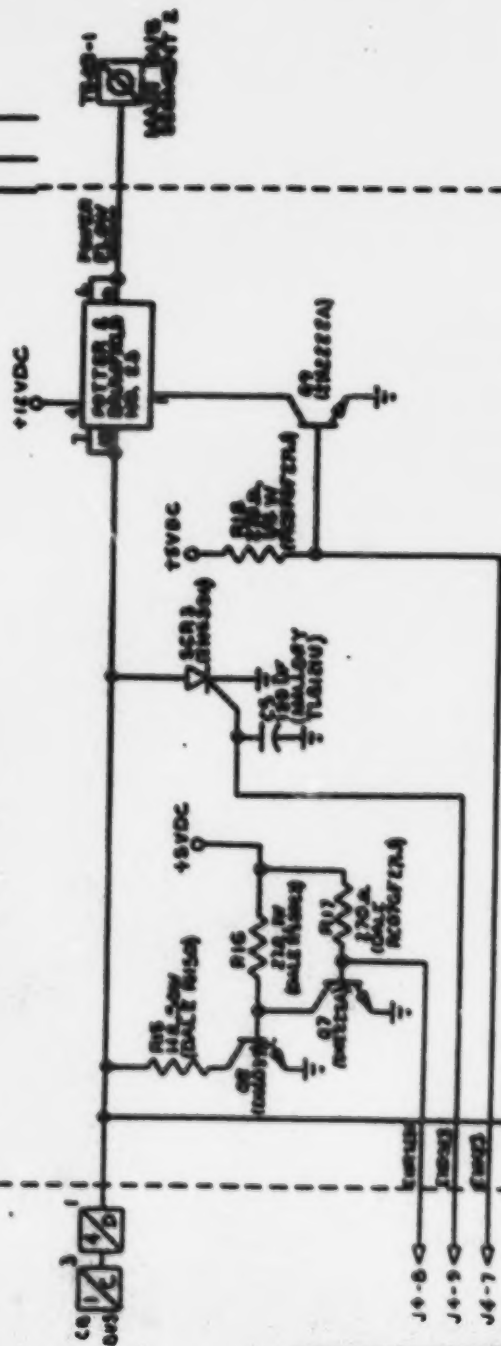

(BOARD-4) MODULE-22

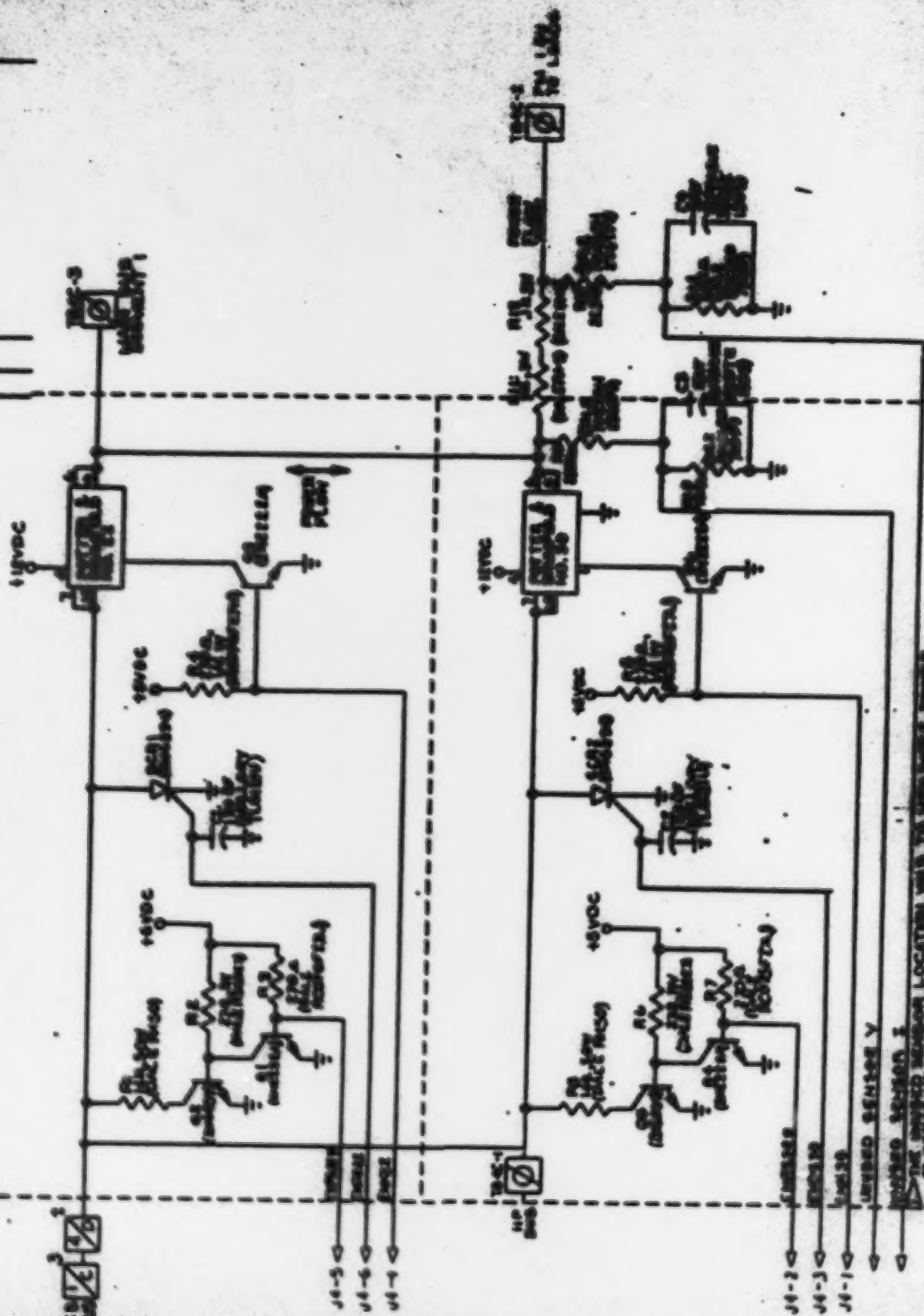

THE ABOVE SENSOR LOCATION WAS TO BE USED FOR
 PLACED TO ANY LOGS IN THE AREA OF THE
 CONTAINING POWER FROM THE POINT OF VIEW, RESISTANCE

BOARD NO. 4 MODULE LAYOUT

TB40
 TB41
 TB42
 TB43

NO. 23
(PORTER AND
SQUARED)

NO. 22
(PORTER AND
SQUARED)

NO. 24
(PORTER AND
SQUARED)

NO. 30
(PORTER AND
SQUARED)

NO. 31
(PORTER AND
SQUARED)

NO. 32
(PORTER AND
SQUARED)


NO. 17
(PORTER AND
SQUARED)

NO. 15
(PORTER AND
SQUARED)



E-43

BOARD NO. 4 TERMINAL BLOCK DESCRIPTION

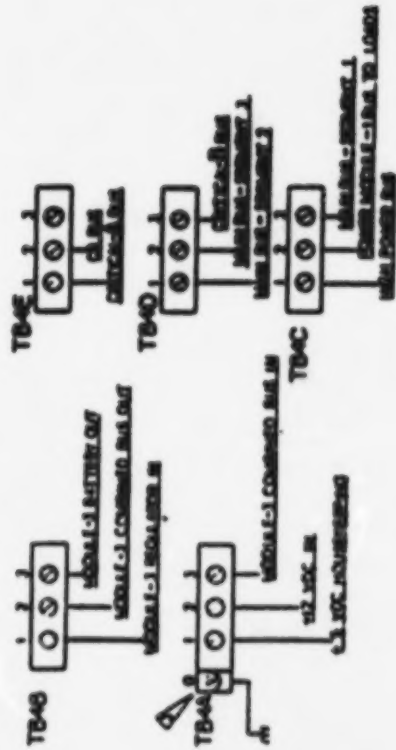

ORIGINAL PAGE IS
OF POOR QUALITY

BOARD NO. 4 J4 PIN DEFINITION

PIN NO.	DESCRIPTION	NO.
1	POWER	1
2	POWER	2
3	POWER	3
100	POWER	100

NOTES

1. NOT SHOWN TO SCALE
2. J4 IS A 25-PIN, 8-TYPE BNC CONNECTOR
3. T44, PIN 1 VIA TERMINAL BLOCK USED AS A GROUND RETURN

BOARD NO. 4 SCHEMATIC AND LAYOUT - EES PROGRAM	
DATE	8455A B1640
REVISION	203605
APPROVED	
DESIGNED BY	
CHECKED BY	
TESTED BY	
INSPECTED BY	
APPROVED BY	
DATE	

POWER SYSTEM - BOARD 5

Drawing #PLB40PAB1650

<u>Item #</u>	<u>Part #</u>	<u>Description</u>	<u>MFG</u>	<u>QTY</u>
1		T4 Aluminum	MCC	1
2		2/56 Screw	NL Fasteners	4
3	<u>Module 16</u>			
	6321	Solid State Relay	Cryden	1
	RH-50, 14 ohm	1%, 50W Resistor	Dale	1
	TVA-1305.5	20vF Capacitor	Sprague	1
	RH-5, .1ohm	1%, 5W Resistor	Dale	2
	RC07GF271J	1/4W, 5% Resistor	Allen-Bradley	1
	RS2027	1W, 27 ohm, 1%	Dale	1
	2N2222A	Small Signal Transistor	Motorola	1
	2N6396	SCR	Motorola	1
	2N6039	Power Transistor	Motorola	1
	TL6121U	120vF Capacitor	Mallory	1
	RNC65H2262FS	22.6K ohm, 1% Resistor	Dale	2
	RNC65D7501F	7.5K ohm, 1% Resistor	Dale	2
	300TE1305	20vF Capacitor	Sprague	2
4	<u>Module 18</u>			
	R10-84-32-			
	V185	DPDT Relay	Potter-Brumfield	1
	RH-50, 14 ohm	1%, 50W Resistor	Dale	1
	RH-5, .1 ohm	1% 5W Resistor	Dale	2
	RC07GF271J	1/4W, 5% Resistor	Allen-Bradley	1
	RS2027	1W, 27 ohm, 1%	Dale	1
	2N2222A	Small Signal Transistor	Motorola	2
	2N6396	SCR	Motorola	1
	2N6039	Power Transistor	Motorola	1
	TL612U	120vF Capacitor	Mallory	1
	RNC65H2262FS	22.6K ohm, 1%	Dale	2
	RNC65D7501F	7.5K ohm, 1%	Dale	2
	300TE1305	20vF Capacitor	Sprague	2

POWER SYSTEM - BOARD 5

Con't

Drawing #PLS49PABB1650

<u>Item #</u>	<u>Part #</u>	<u>Description</u>	<u>MFG</u>	<u>QTY</u>
5	Module 12			
	R10-E6-X2-			
	V185	DPDT Relay	Potter-Brumfield	1
	RH-50,14 ohm	1%, 50W Resistor	Dale	1
	RH-5, .1 ohm	1% 5W Resisotr	Dale	2
	RC07GF271J	1/4W, 5% Resistor	Allen-Bradley	1
	RS2027	1W, 27 ohm, 1%	Dale	1
	2N2222A	Small Signal Transistor	Motorola	2
	2N6396	SCR	Motorola	1
	2N6039	Power Transistor	Motorola	1
	TL612U	120vF Capacitor	Mallory	1
	RMC65R2262FS	22.6K ohm, 1%	Dale	2
	RMC65D7501F	7.5K ohm, 1%	Dale	2
	300TE1305	20vF Capacitor	Sprague	2
6	Module 14			
	6321	Solid State Relay	Cryden	1
	RH-50,14 ohm	1%, 50W Resistor	Dale	1
	TVA-1305.5	20vF Capacitor	Sprague	1
	RH-5, .1ohm	1%, 5W Resistor	Dale	2
	RC07GF271J	1/4W, 5% Resistor	Allen-Bradley	1
	RS2027	1W, 27 ohm, 1%	Dale	1
	2N2222A	Small Signal Transistor	Motorola	2
	2N6396	SCR	Motorola	1
	2N6039	Power Transistor	Motorola	1
	TL612U	120vF Capacitor	Mallory	1
	RMC65R2262FS	22.6K ohm, 1%	Dale	2
	RMC65D7501F	7.5K ohm, 1%	Dale	2
	300TE1305	20vF Capacitor	Sprague	2

POWER SYSTEM - BOARD 5
Con't



Drawing #PLB49PAEB1650


<u>Item #</u>	<u>Part #</u>	<u>Description</u>	<u>MFG</u>	<u>QTY</u>
7	<u>Module 13</u>			
	R10-R6-X2-			
	V185	DPDT Relay	Potter-Brumfield	1
	RH-50,14 ohm	1%, 50W Resistor	Dale	1
	RH-5, .1 ohm	1% 5W Resistor	Dale	2
	RC07GF271J	1/4W, 5% Resistor	Allen-Bradley	1
	RS2027	1W, 27 ohm, 1%	Dale	1
	2N2222A	Small Signal Transistor	Motorola	2
	2N6396	SCR	Motorola	1
	2N6039	Power Transistor	Motorola	1
	TL612U	120vF Capacitor	Mallory	1
	RNC65H2262FS	22.6K ohm, 1%	Dale	2
	RNC65D7501F	7.5K ohm, 1%	Dale	2
	300TE1305	20vF Capacitor	Sprague	2
8	<u>Module 8</u>			
	6321	Solid State Relay	Cryden	1
	RH-50,14 ohm	1%, 50W Resistor	Dale	1
	TVA-1305.5	20vF Capacitor	Sprague	1
	RH-5, .1 ohm	1% 5W Resistor	Dale	2
	RC07GF271J	1/4W, 5% Resistor	Allen-Bradley	1
	RS2027	1W, 27 ohm, 1%	Dale	1
	2N2222A	Small Signal Transistor	Motorola	2
	2N6396	SCR	Motorola	1
	2N6039	Power Transistor	Motorola	1
	TL612U	120vF Capacitor	Mallory	1
	RNC65H2262FS	22.6K ohm, 1%	Dale	2
	RNC65D7501F	7.5K ohm, 1%	Dale	2
	300TE1305	20vF Capacitor	Sprague	2

POWER SYSTEM - BOARD 5
Con't

Drawing #P1849PAB1650


<u>Item #</u>	<u>Part #</u>	<u>Description</u>	<u>MFG</u>	<u>QTY</u>
9	<u>Module 7</u>			
	6321	Solid State Relay	Cryden	1
	RH-50,14 ohm	1%, 50W Resistor	Dale	1
	TVA-1305.5	20vF Capacitor	Sprague	1
	RH-5, .1 ohm	1% 5W Resistor	Dale	2
	RC07GF271J	1/4W, 5% Resistor	Allen-Bradley	1
	RS2027	1W, 27 ohm, 1%	Dale	1
	2N2222A	Small Signal Transistor	Motorola	2
	2N6396	SCR	Motorola	1
	2N6039	Power Transistor	Motorola	1
	TL612U	120vF Capacitor	Mallory	1
	RNC65H2262F3	22.6K ohm, 1%	Dale	2
	RNC65D7501F	7.5K ohm, 1%	Dale	2
	300TE1305	20vF Capacitor	Sprague	2
10	<u>Module 10</u>			
	6321	Solid State Relay	Cryden	1
	RH-50,14 ohm	1%, 50W Resistor	Dale	1
	TVA-1305.5	20vF Capacitor	Sprague	1
	RH-5, .1 ohm	1% 5W Resistor	Dale	2
	RC07GF271J	1/4W, 5% Resistor	Allen-Bradley	1
	RS2027	1W, 27 ohm, 1%	Dale	1
	2N2222A	Small Signal Transistor	Motorola	2
	2N6396	SCR	Motorola	1
	2N6039	Power Transistor	Motorola	1
	TL612U	120vF Capacitor	Mallory	1
	RNC65H2262F3	22.6K ohm, 1%	Dale	2
	RNC65D7501F	7.5K ohm, 1%	Dale	2
	300TE1305	20vF Capacitor	Sprague	2

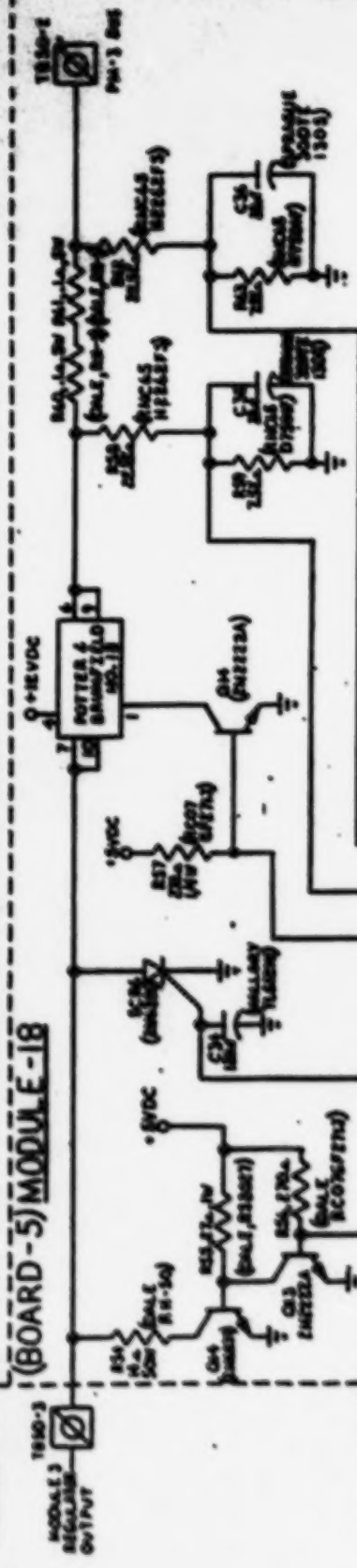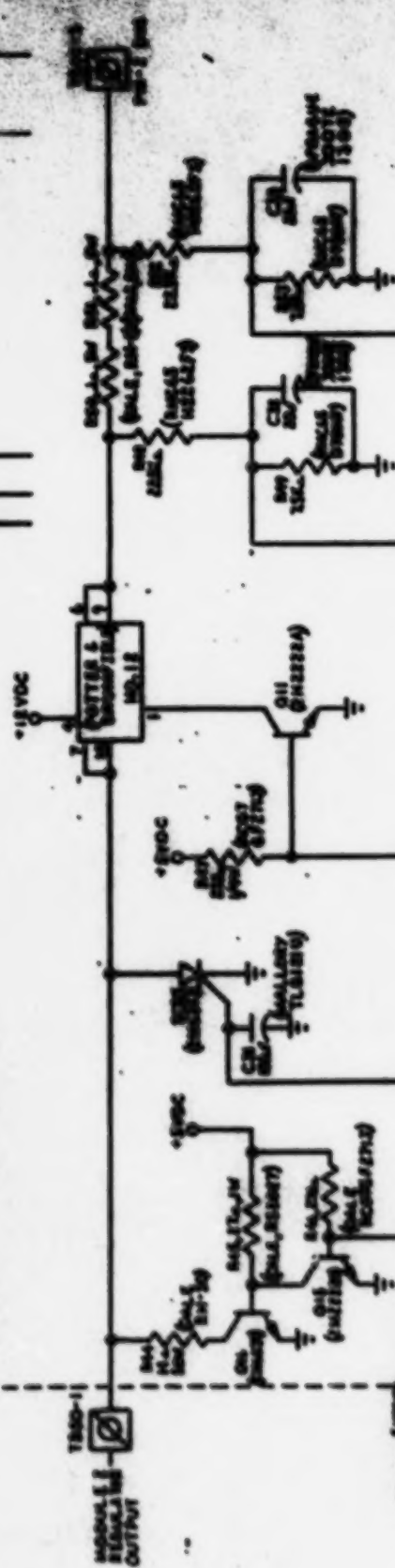

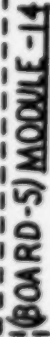

E-49

 (BOARD-5) MODULE-10

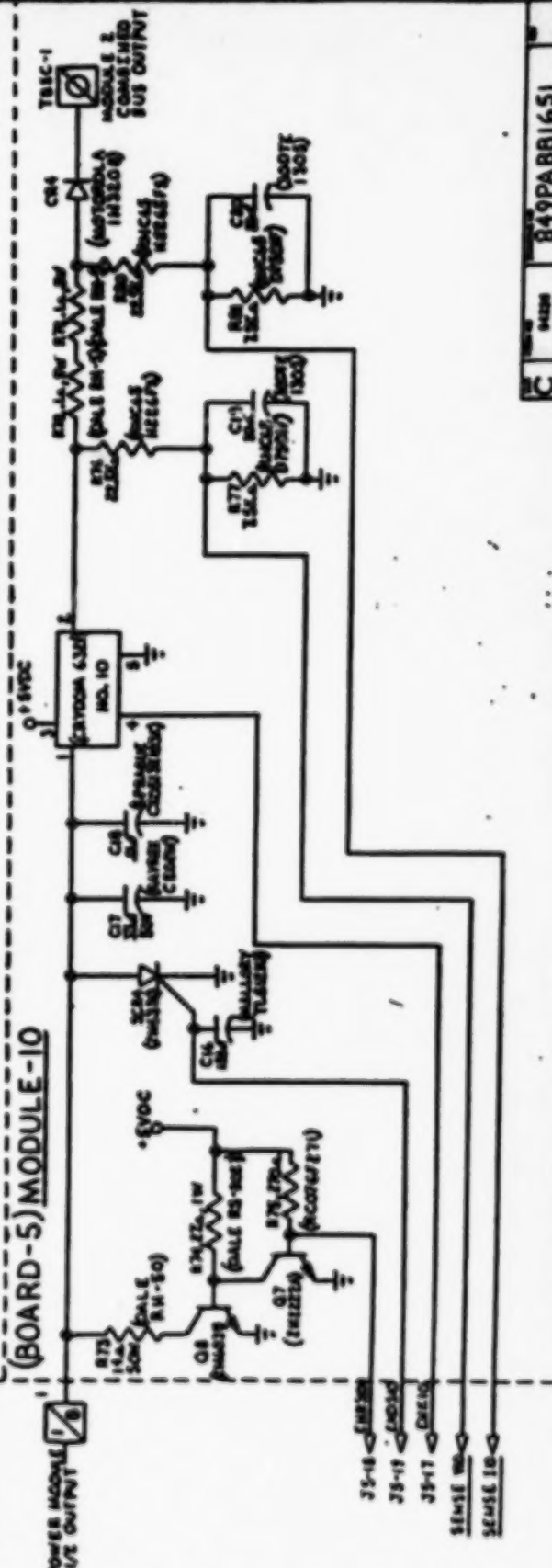


E-50




ORIGINAL PAGE IS
POOR QUALITY

BOARD NQ 5 MODULE LAYOUT

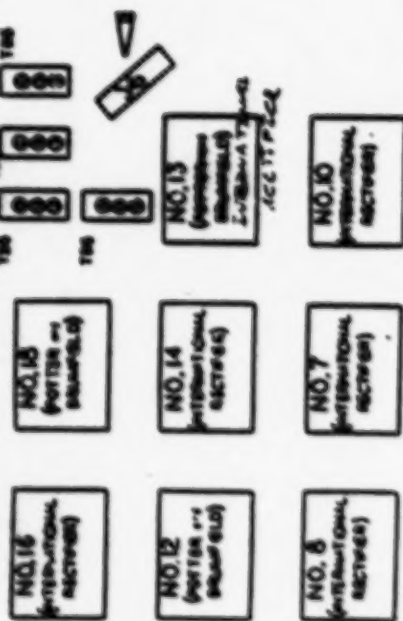

BOARD NO. 5 TERMINAL BLOCK DESCRIPTION

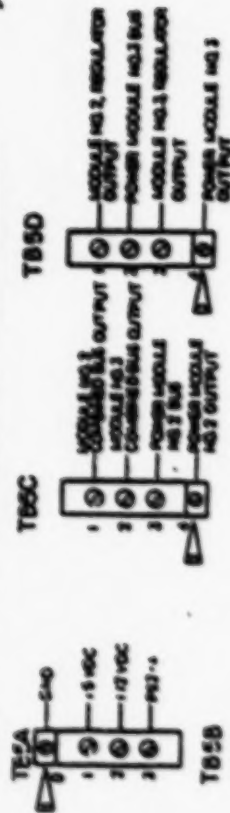

ORIGINAL PAGE IS OF POOR QUALITY

NOTES:

1. THIS MODULE WAS OBSERVED DURING A 14 GROUND CHECKOUT.
2. THE MODULE WAS OBSERVED DURING A 14 GROUND CHECKOUT.
3. THE MODULE WAS OBSERVED DURING A 14 GROUND CHECKOUT.

BOARD NO. 5, J5 PIN DEFINITION

PIN NO.	FOR RELAY NO.	SIGNAL
1	15	ENR15
2	16	ENR16
3	17	ENR17
86	100	ENR100

MARTIN MARIETTA CORPORATION	
BOARD NQ 5 LAYOUT AND SCHEMATIC, FIES PROGRAM	
DATE	10/20/60
BY	PA RACKEN

POWER SYSTEM - BOARD 6

Drawing #PL849PAB81660

<u>Item #</u>	<u>Part #</u>	<u>Description</u>	<u>MFG</u>	<u>QTY</u>
1		T4 Aluminum	MHC	1
2		2/56 Screw	NL Fasteners	4
3	<u>Module 9</u>			
	6321	Solid State Relay	Cryden	1
	RH-50,14 ohm	1%, 50W Resistor	Dale	1
	TVA-1305.5	20vF Capacitor	Sprague	1
	RH-5, .1ohm	1%, 5W Resistor	Dale	2
	RC07GF271J	1/4W, 5% Resistor	Allen-Bradley	1
	RS2027	1W, 27 ohm, 1%	Dale	1
	2N2222A	Small Signal Transistor	Motorola	1
	2N6396	SCR	Motorola	1
	2N6039	Power Transistor	Motorola	1
	TL6121U	120vF Capacitor	Mallory	1
	RNC65H2262FS	22.6K ohm, 1% Resistor	Dale	2
	RNC65D7501F	7.5K ohm, 1% Resistor	Dale	2
	30DTE1305	20vF Capacitor	Sprague	2
	LK0513K103K	.01 VF Capacitor	Sprague	1
4	<u>Module 11</u>			
	R10-E6-X2-			
	V185	DPDT Relay	Potter-Brumfield	1
	RH-50,14 ohm	1%, 50W Resistor	Dale	1
	RH-5, .1 ohm	1% 5W Resisotr	Dale	2
	RC07GF271J	1/4W, 5% Resistor	Allen-Bradley	1
	RS2027	1W, 27 ohm, 1%	Dale	1
	2N2222A	Small Signal Transistor	Motorola	2
	2N6396	SCR	Motorola	1
	2N6039	Power Transistor	Motorola	1
	TL612U	120vF Capacitor	Mallory	1
	RNC65H2262FS	22.6K ohm, 1%	Dale	2
	RNC65D7501F	7.5K ohm, 1%	Dale	2
	30DTE1305	20vF Capacitor	Sprague	2

POWER SYSTEM - BOARD 6
Con't

Drawing #PLD49PAB51660

<u>Item #</u>	<u>Part #</u>	<u>Description</u>	<u>MFG</u>	<u>QTY</u>
5	<u>Module 6</u>			
	R10-E6-X2-			
	V185	DPDT Relay	Potter-Brumfield	1
	RH-50, 14 ohm	1%, 30W Resistor	Dale	1
	RH-5, .1 ohm	1% 5W Resistor	Dale	2
	RC07GF271J	1/4W, 5% Resistor	Allen-Bradley	1
	RS2027	1W, 27 ohm, 1%	Dale	1
	2N2222A	Small Signal Transistor	Motorola	2
	2N6396	SCR	Motorola	1
	2N6039	Power Transistor	Motorola	1
	TL612U	120vF Capacitor	Mallory	1
	RNC65H2262F8	22.6K ohm, 1%	Dale	2
	RNC65D7501F	7.5K ohm, 1%	Dale	2
	300TE1305	20vF Capacitor	Sprague	2
6	<u>Module 3</u>			
	6321	Solid State Relay	Cryden	1
	RH-50, 14 ohm	1%, 50W Resistor	Dale	1
	RH-5, .1ohm	1%, 5W Resistor	Dale	2
	RC07GF271J	1/4W, 5% Resistor	Allen-Bradley	1
	RS2027	1W, 27 ohm, 1%	Dale	1
	2N2222A	Small Signal Transistor	Motorola	2
	2N6396	SCR	Motorola	1
	2N6039	Power Transistor	Motorola	1
	TL612U	120vF Capacitor	Mallory	1
	RNC65H2262F8	22.6K ohm, 1%	Dale	2
	RNC65D7501F	7.5K ohm, 1%	Dale	2
	300TE1305	20vF Capacitor	Sprague	2

POWER SYSTEMS - BOARD 6
Cm't

Drawing #PLS49PAB1660

<u>Item #</u>	<u>Part #</u>	<u>Description</u>	<u>MFG</u>	<u>QTY</u>
7	Module 5			
	K10-84-12-			
	V185	DPDT Relay	Potter-Brumfield	1
	RE-50, 14 ohm	1%, 50W Resistor	Dale	1
	RE-5, .1 ohm	1% 5W Resistor	Dale	2
	RC07GF271J	1/4W, 5% Resistor	Allen-Bradley	1
	RS2027	1W, 27 ohm, 1%	Dale	1
	2N2222A	Small Signal Transistor	Motorola	2
	2N6396	SCR	Motorola	1
	2N6039	Power Transistor	Motorola	1
	TL612U	120vF Capacitor	Mallory	1
	RNC65H2262FS	22.6K ohm, 1%	Dale	2
	RNC65D7501F	7.5K ohm, 1%	Dale	2
	300TE1305	20vF Capacitor	Sprague	2
8	Module 2			
	6321	Solid State Relay	Cryden	1
	RE-50, 14 ohm	1%, 50W Resistor	Dale	1
	RE-5, .1 ohm	1% 5W Resistor	Dale	2
	RC07GF271J	1/4W, 5% Resistor	Allen-Bradley	1
	RS2027	1W, 27 ohm, 1%	Dale	1
	2N2222A	Small Signal Transistor	Motorola	2
	2N6396	SCR	Motorola	1
	2N6039	Power Transistor	Motorola	1
	TL612U	120vF Capacitor	Mallory	1
	RNC65H2262FS	22.6K ohm, 1%	Dale	2
	RNC65D7501F	7.5K ohm, 1%	Dale	2
	300TE1305	20vF Capacitor	Sprague	2
	RC07GF471J	470, 1/4W Resistor	Allen-Bradley	2
	TL6121U	120vF Capacitor	Mallory	1
	1N3208	Diode	Motorola	1
	LE0513K103K	.01Vf Capacitor	Sprague	1


FORM 3-64 - BOARD 1

Chit


Drawing 0714-070001400

<u>Item #</u>	<u>Part #</u>	<u>Description</u>	<u>MFG</u>	<u>QTY</u>
9	Module 1			
	6321	Solid State Relay	Cryden	1
	RE-50, 14 ohm	1%, 50W Resistor	Dale	1
	RE-5, .1 ohm	1% 5W Resistor	Dale	2
	RC07GF271J	1/4W, 5% Resistor	Allen-Bradley	1
	RS2027	1W, 27 ohm, 1%	Dale	1
	2N2222A	Small Signal Transistor	Motorola	2
	2N6396	SCR	Motorola	1
	2N6039	Power Transistor	Motorola	1
	CM20M	33vF Capacitor	RAYTEK	1
	RC65H2262FS	22.6K ohm, 1%	Dale	2
	RC65D7501F	7.5K ohm, 1%	Dale	2
	30VTE1305	20vF Capacitor	Sprague	2
	RC07GF471J	470, 1/4W Resistor	Allen-Bradley	2
	TL612U	120vF Capacitor	Mallory	1
	1N3208	Diode	Motorola	1
	LK0513X103K	.01vF Capacitor	Sprague	1
10	Module 4			
	6321	Solid State Relay	Cryden	1
	RE-50, 14 ohm	1%, 50W Resistor	Dale	1
	RE-5, .1 ohm	1% 5W Resistor	Dale	2
	RC07GF271J	1/4W, 5% Resistor	Allen-Bradley	1
	RS2027	1W, 27 ohm, 1%	Dale	1
	2N2222A	Small Signal Transistor	Motorola	2
	2N6396	SCR	Motorola	1
	2N6039	Power Transistor	Motorola	1
	TL612U	120vF Capacitor	Mallory	1
	RC65H2262FS	22.6K ohm, 1%	Dale	2
	RC65D7501F	7.5K ohm, 1%	Dale	2
	30VTE1305	20vF Capacitor	Sprague	2
	RC07GF471J	470, 1/4W Resistor	Allen-Bradley	2
	TL612U	120vF Capacitor	Mallory	1
	1N3208	Diode	Motorola	1
	LK0513X103K	.01vF Capacitor	Sprague	1

BOARD NO. 6 MODULE LAYOUT

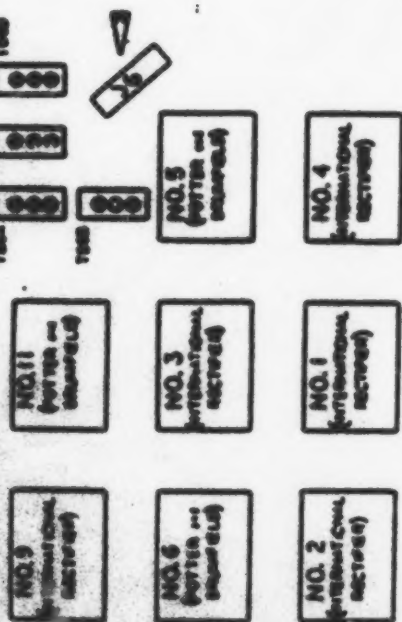

BOARD NO. 6 TERMINAL BLOCK DESCRIPTION

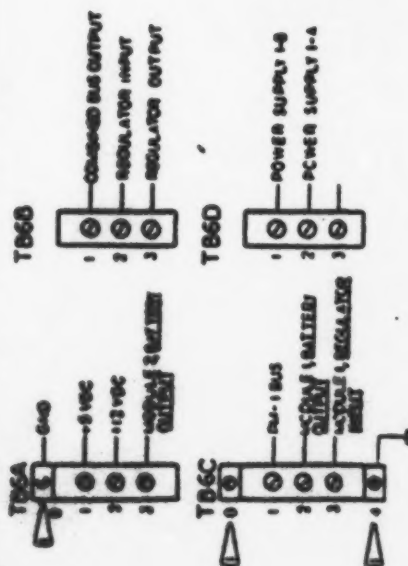

ORIGINAL PAGE IS
OF POOR QUALITY





BOARD NO. 6 J6 PIN DEFINITION

PIN NO.	FOR RELAY NO.	RELAY
1	1	RELAY 1
2	2	RELAY 2
3	3	RELAY 3
100	100	RELAY 100



NOTE:

- 1. RELAY 1, RELAY 2, RELAY 3, RELAY 99, RELAY 100.


BOARD NO. 6 LAYOUT AND SCHEMATIC, EIES PROGRAM	
DATE	203605
DESIGNED BY	83PA881660
CHECKED BY	
APPROVED BY	
REVISIONS	
1	
2	
3	
100	

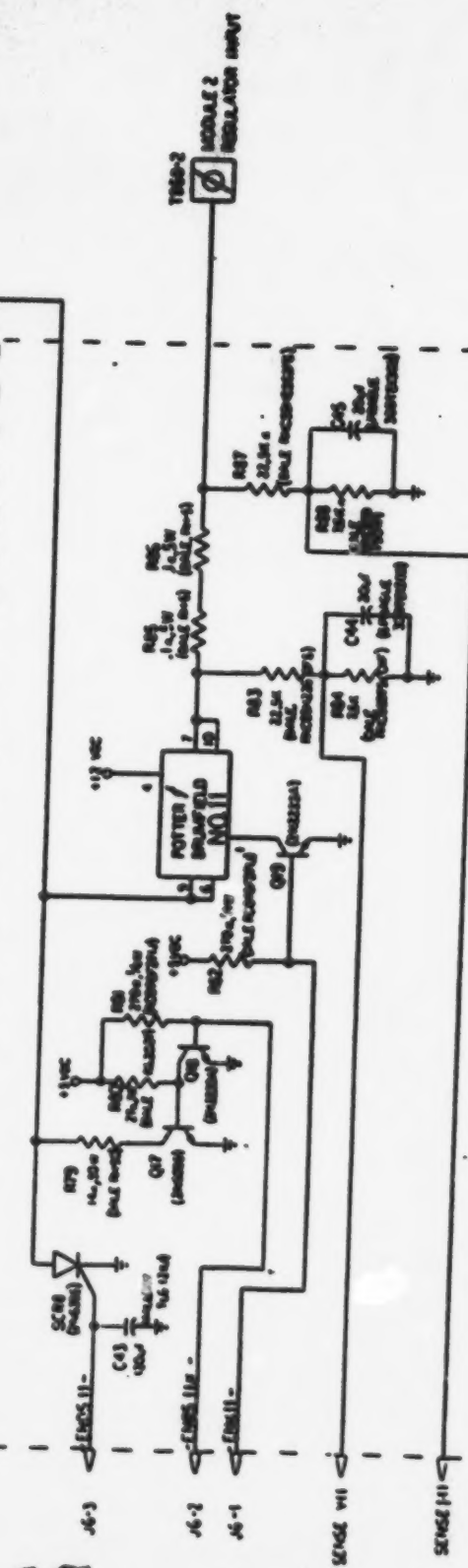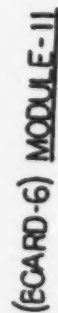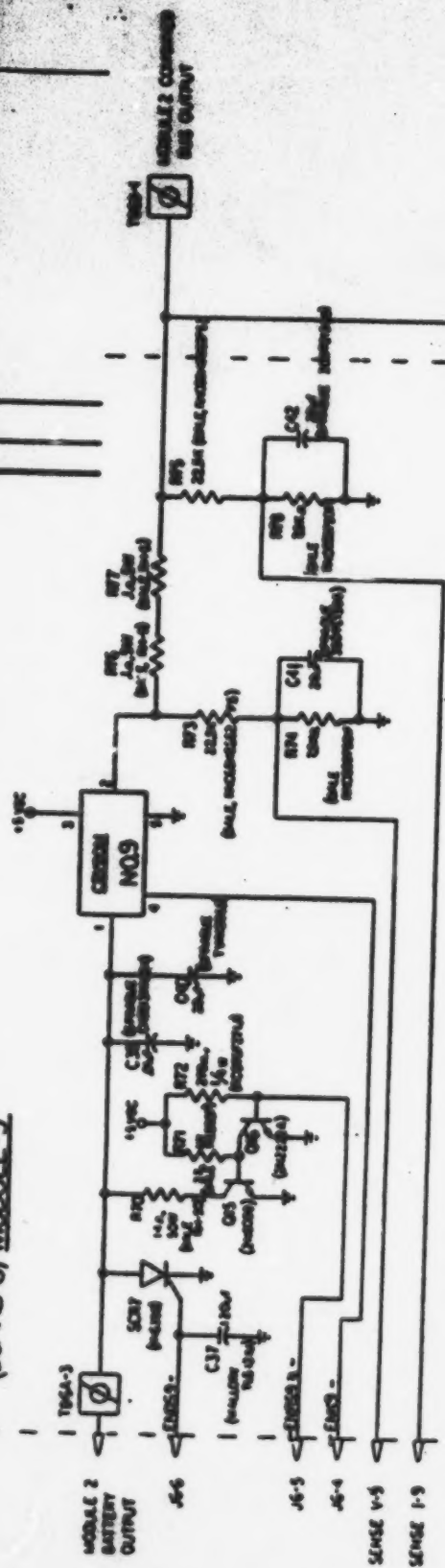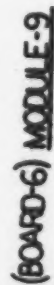

(BOARD-6) MODULE-5

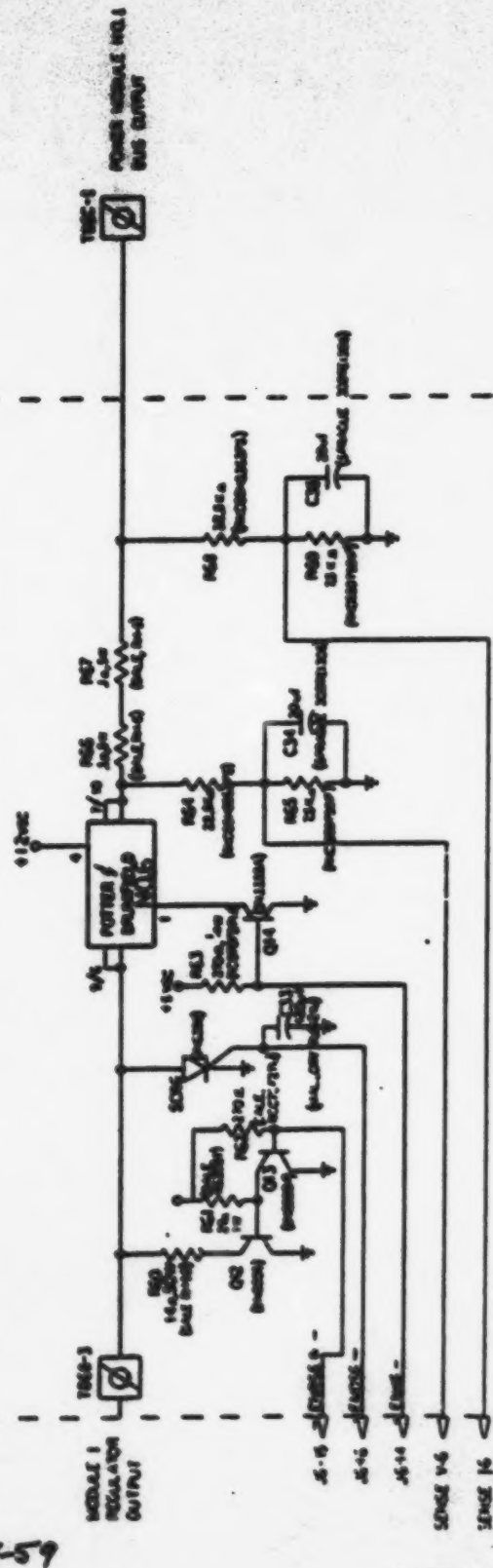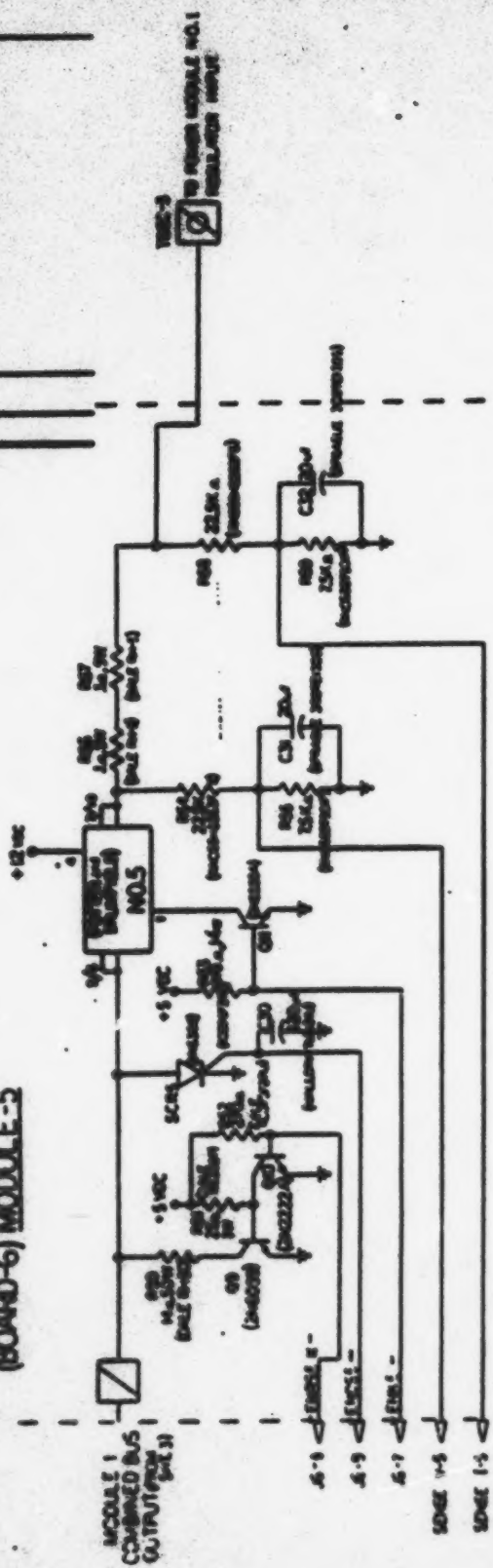


(BOARD-6) MODULE-1

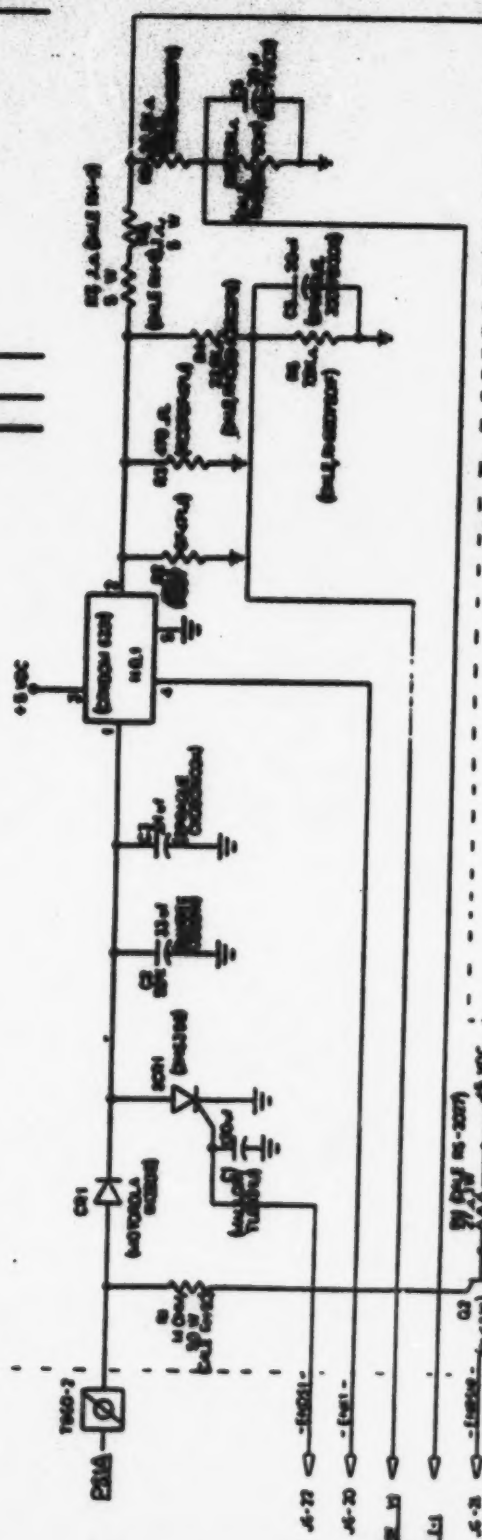

ORIGINAL PAGE IS
OF POOR QUALITY

(BOARD-6) MODULE-2

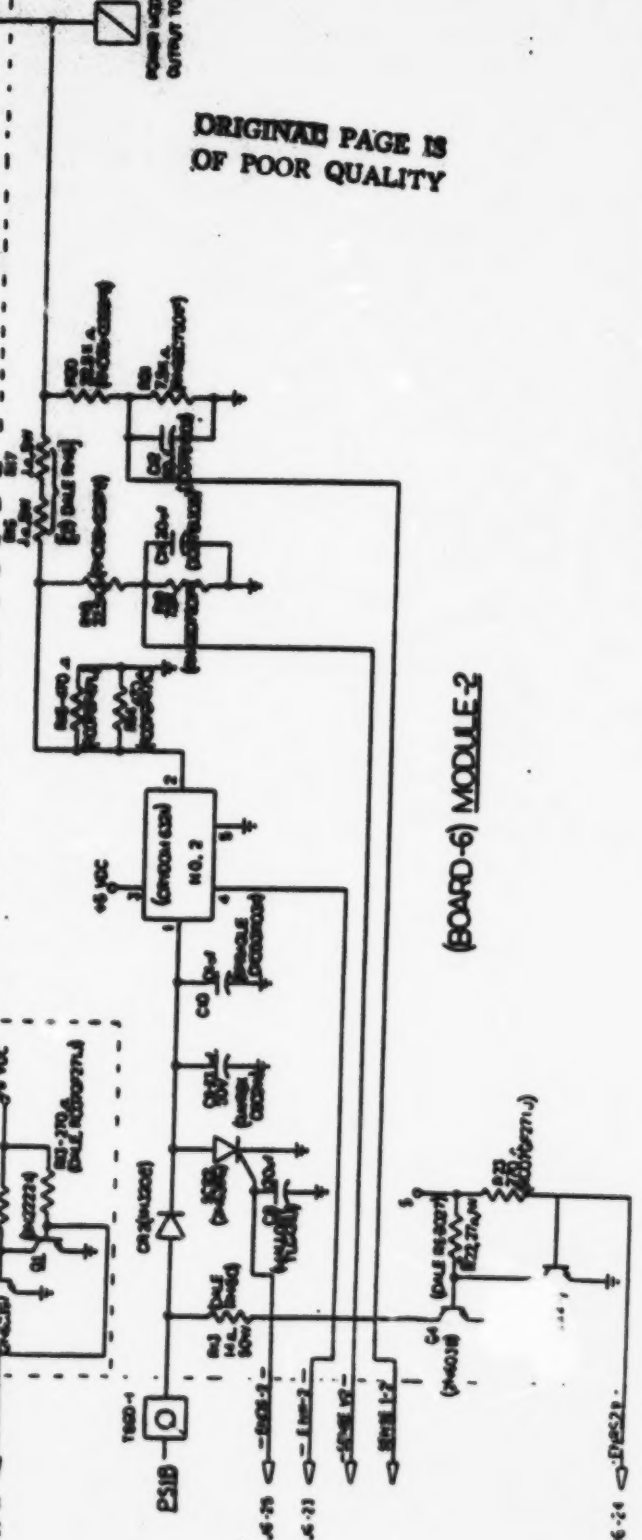

849PABEC60

C 00000

2

3

4

5

6

7

8

9

10

11

12

13

14

15

16

17

18

19

20

21

22

23

24

25


26

27

BATTERY SYSTEM ASSEMBLY

Drawing #PLS49PARB1700

<u>Item #</u>	<u>Part #</u>	<u>Description</u>	<u>MFG</u>	<u>QTY</u>
1	P-10	10.5" X 19" Panel	Optima	1
2	D22-30	Drawer Slides	Optima	1
3		T4 Aluminum-3/16"	MHC Stock	1
4	H-10	Set of Panel Handles	Optima	1
5	25CELL1414-0	Battery Modules	Eagle-Pitcher	3
6	KPSE04B-10-68	Connector Blackshells	Amphenol	3
7	8502-002	20 Gauge wire-red	Belden	1
8	8502-010	20 Gauge wire-black	Belden	1
9	86-12-312	12 Volt Power Supply	Sola-Electric	1
10		Lugs		5
11		T4 Aluminum - 1/4"	MHC Stock	1
12		#8/32 Bolts	NL Fasteners	26
13		#8/32 Nuts	NL Fasteners	26
14		#8 Lockwashers	NL Fasteners	26
15		#8 Flatwashers	NL Fasteners	26
16	17614C	Power Cord	Belden	1

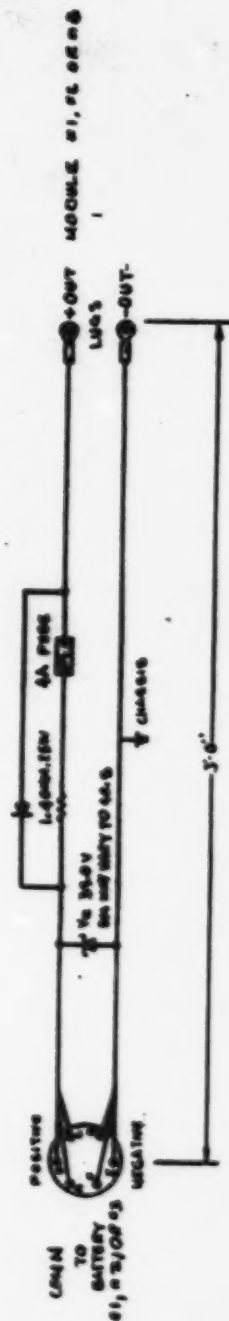


BATTERY MODULE CABLES

- 1) CONSTANT VOLTAGE POWER SUPPLY (IN A CONSTANT LIMIT MODE, WILL SUPPLY ACROSS THE LIMITING RESISTOR A CONSTANT CURRENT OF 1.0/3.0 OHMS (POWER CONSUME BASED) AS LONG AS THE BATTERY VOLTAGE REMAINS AT OR BELOW 32.0/2.0 VOLTS. ABOVE THESE BATTERY VOLTAGES, A CONSTANT VOLTAGE OF 32.0 VOLTS WILL BE APPLIED TO THE BATTERY.
- 2) THE 10 AMP-HOUR BATTERY WILL CONSUME IN APPROXIMATELY 07.0/2.0 HOURS.
- 3) BATTERIES WILL BE DISCONNECTED FROM THE CHARGE SOURCE WHEN THE CHARGING CURRENT FALLS BELOW .1A (ONCE MINIMUM RESISTANCE OF THE CHARGE RESISTOR).

- 1) NOMINAL BATTERY VOLTAGE = 25 CELLS X 1.35 VOLTS/CELL = 33.75V
- 2) NOMINAL BATTERY VOLTAGE - VOLTAGE AT APPROXIMATE VALUE OF LIMIT RESISTOR = 33.75 - 32.25 = 1.5V
- 3) NOMINAL BATTERY VOLTAGE - SHORT CIRCUIT = 33.75 - 25.0 A
- 4) BATTERY CAPACITY = 10 AH
- 5) IN LIMIT RESISTOR = (1.5V)² / 1.0 = 22.5 WATTS

DATE	FIGURE NO.	REVISION NO.	REV.
	C	04236	
SCALE		SHEET	
		1	

WI	SOLINERD	E-H
52	WIRE-WRAP	1-4
87	WIRE-WRAP	87-86
21	WIRE-WRAP	27-28
103	WIRE-WRAP	103-103
50	WIRE-WRAP	50-29
40	WIRE-WRAP	40-41
42	WIRE-WRAP	42-43
44	WIRE-WRAP	44-45
46	WIRE-WRAP	46-47
48	WIRE-WRAP	48-49
50	WIRE-WRAP	50-51
53	WIRE-WRAP	53-54
51	WIRE-WRAP	1-1
84	WIRE-WRAP	84-85
86	WIRE-WRAP	73-81
73	WIRE-WRAP	18-16
18	WIRE-WRAP	21-15

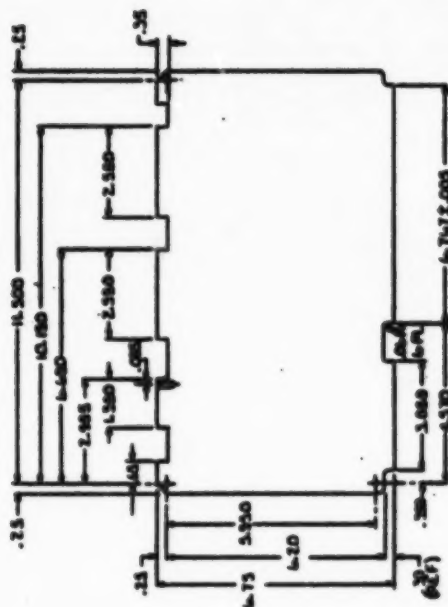

SBC 317 SIO PC BOARD ASSEMBLY

349 PAB 1470

10


2

2

3

4


E-64

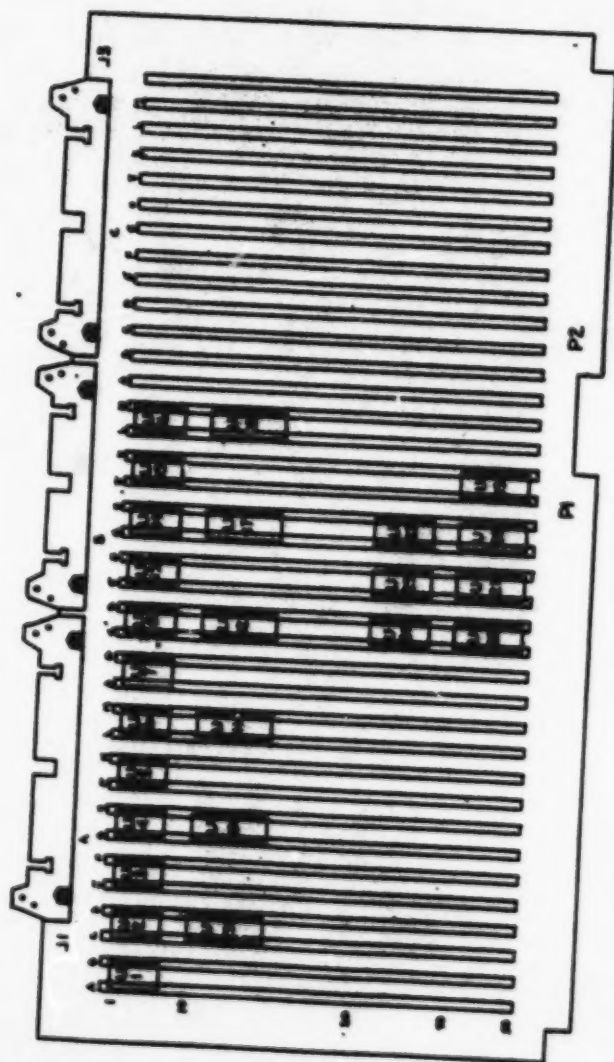

E-65

C		1	
C		2	
C		3	
C		4	


ORIGINAL PAGE IN
OF POOR QUALITY

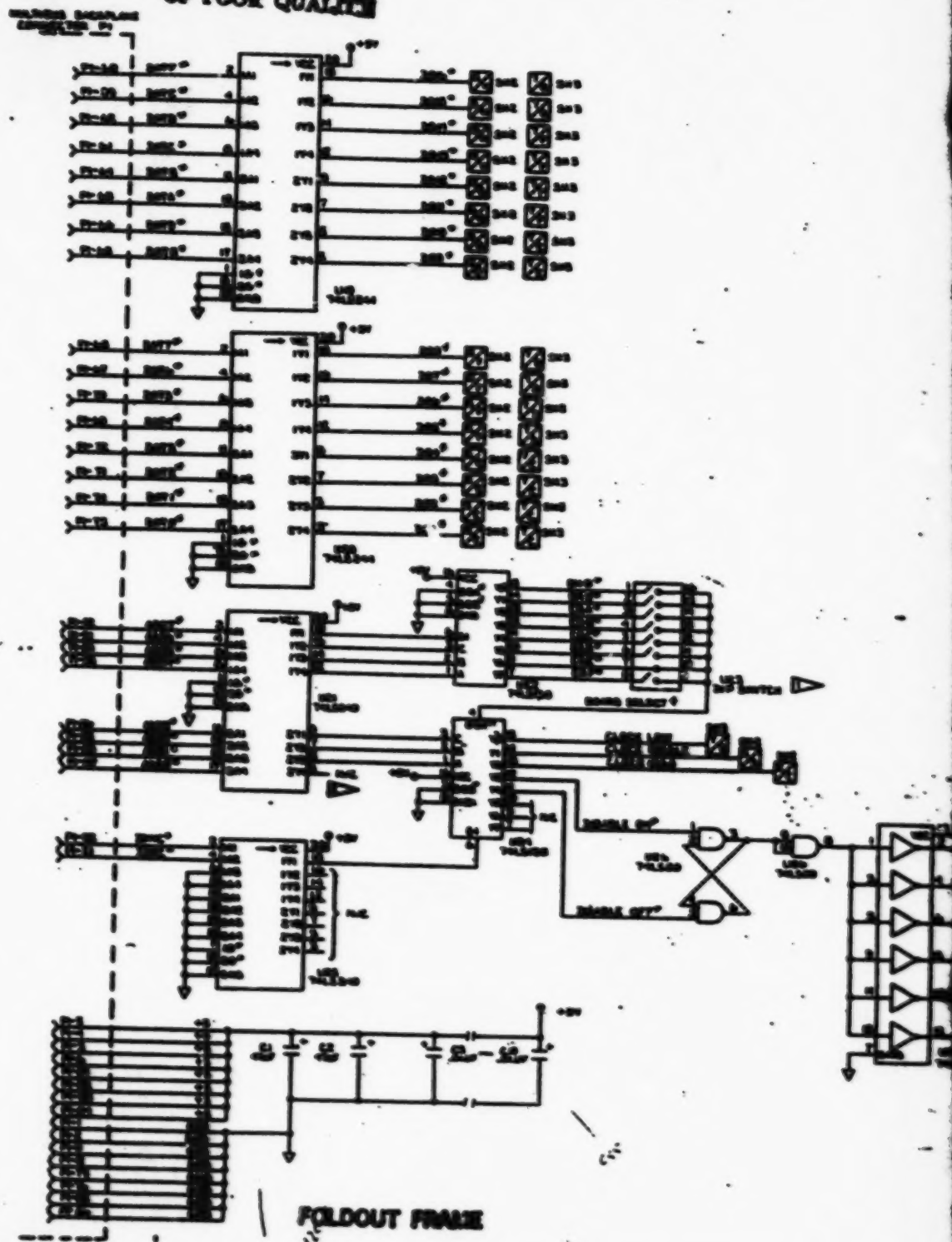

E-66


[illegible]

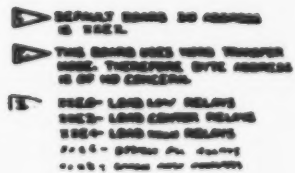A vertical scale bar with markings from A to H. A horizontal line is drawn at the level of 'D'. The text "1000000" is written vertically along the bar.




7-11-68 10:00 AM 0-07025410

ORIGINAL PAGE IS
OF POOR QUALITY

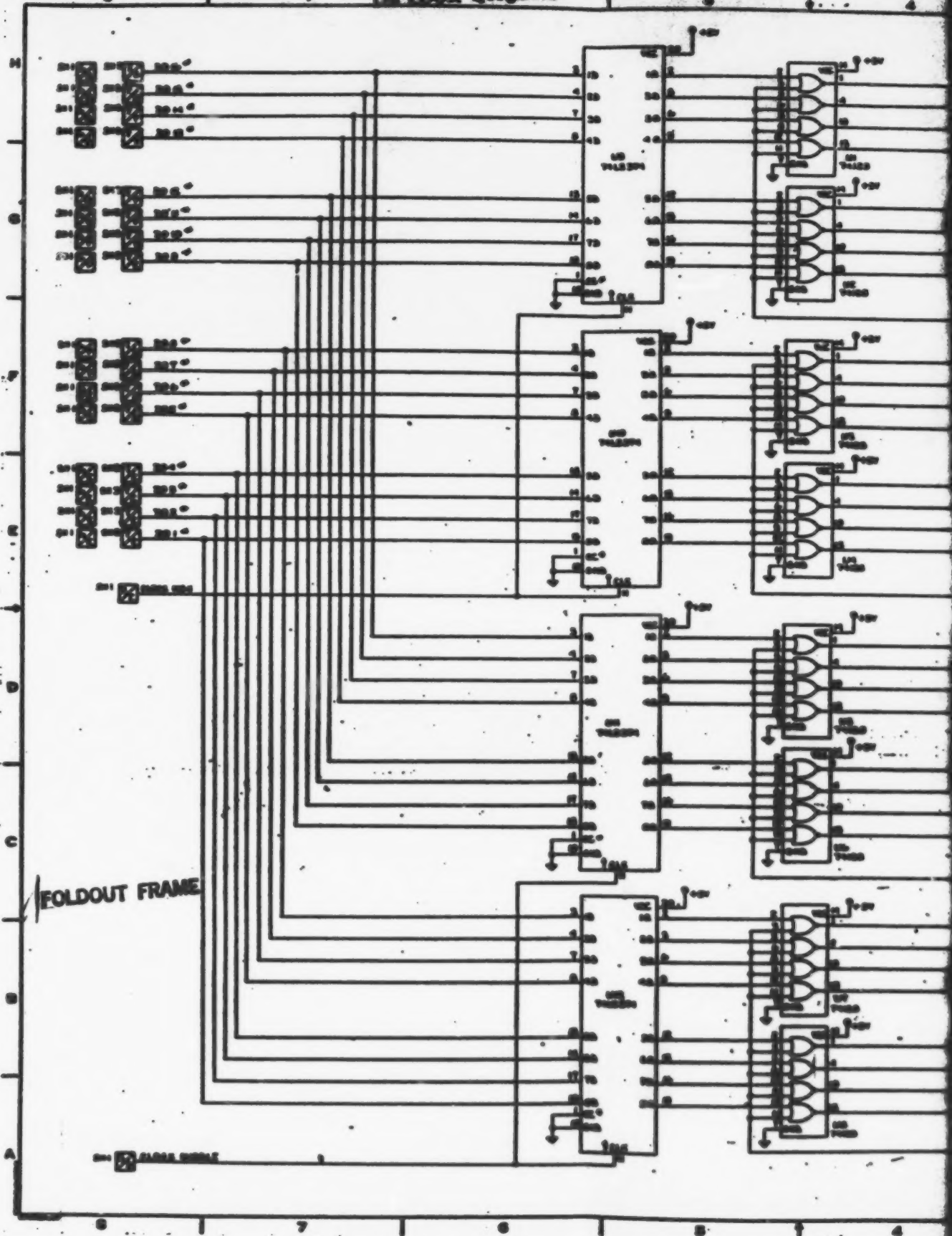

E-67

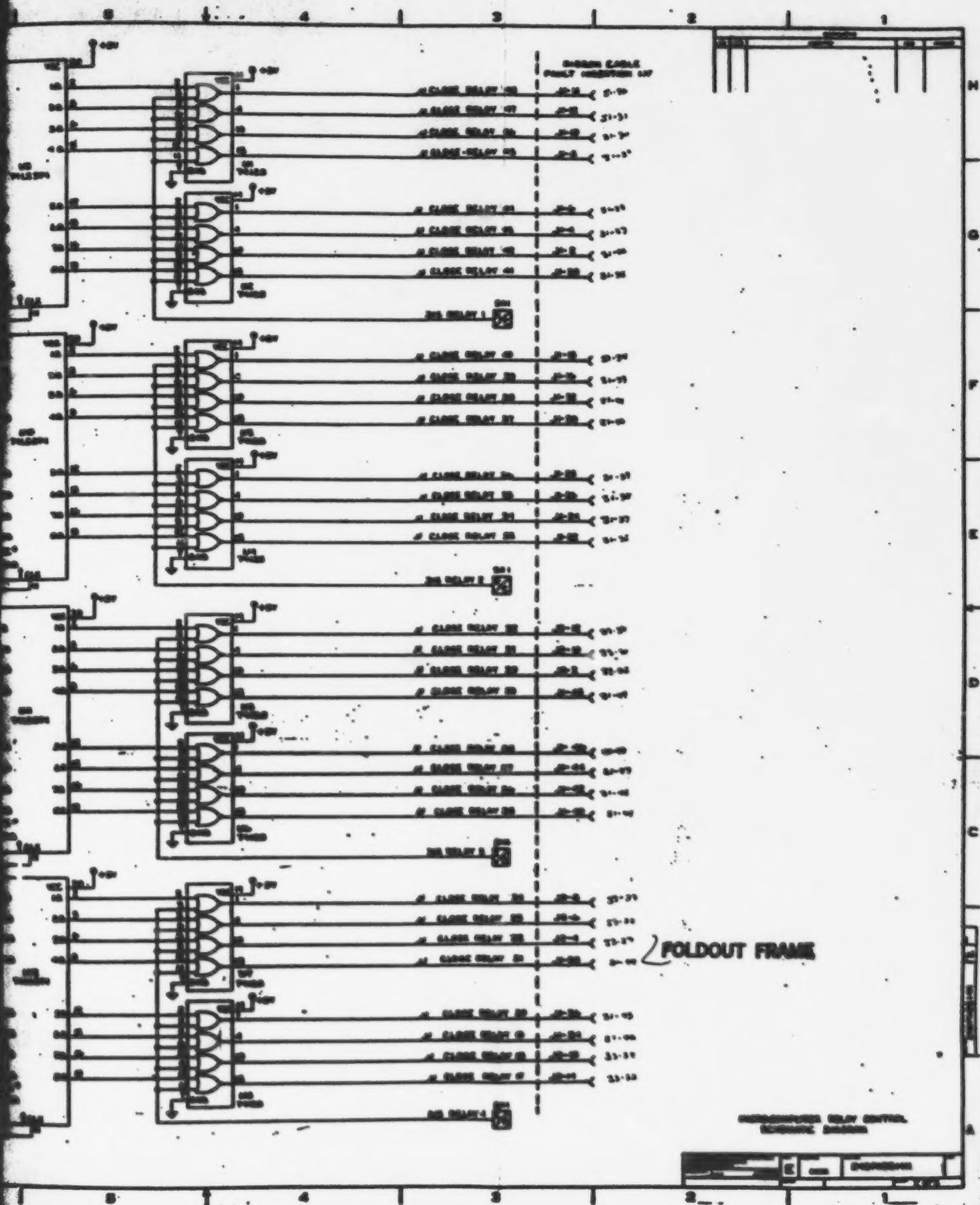


FOLDOUT FRAME

INTERMEDIATE RELAY CONTROL
SCHEMATIC DIAGRAM

DATE	BY	REVISION

ORIGINAL PAGE IS
OF POOR QUALITY

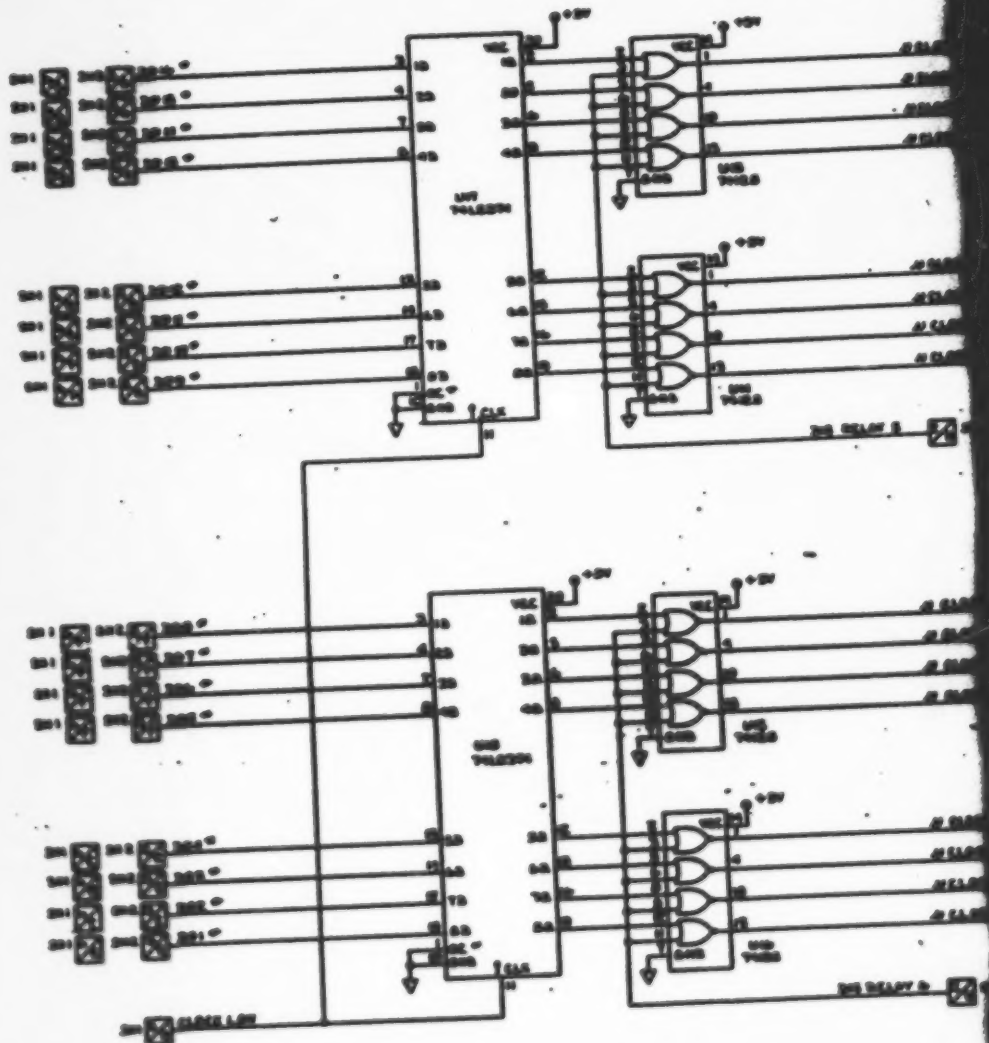

FOLDOUT FRAME

E-68

FAULT INDICATION ASSEMBLY

Drawing #P1049PAMB1300

<u>Item #</u>	<u>Part #</u>	<u>Description</u>	<u>MFG</u>	<u>QTY</u>
1	P-10	10.5"x19" Panel	Optima	1
2	DRE-30	Drawer Slides	Optima	1
3		T4 Aluminum 3/16"	MHC stock	1
4	H-10	Set of Panel Handles	Optima	1
5	HMP-0200	Integrated Lamps	Hewlett Packard	48
6	MST-105E	3 Position toggle switches	Leecraft	48
7	572-1121- 0804-040	2 Position paddle switches	Dialight	2
8	39TB3	Terminal Barrier strip	Control Design	1
9	9L28050	Wiring Harness	3M/Newark	1
10		Perforated Base	MHC stock	1
11	849PAMB1310	Wire Wrap Assemblies	MHC	2
12	13P12BC	12 Gauge wire - red	Carol	1
13		Terminal Lugs		8
14	TH-112-48L	Lettering set	Transfertech	3
15		#8/32 Bolts	NL Fasteners	20
16		#8/32 Nuts	NL Fasteners	20
17		#8 Lockwashers	NL Fasteners	20
18		#8 Flatwashers	NL Fasteners	20
19	13R12BC	12 Gauge Wire - black	Carol	1
20	TOS121V	120 VF, 25V Capacitor	Mallory	1




0-SP4881300	C	0000	0-SP4881300
-------------	---	------	-------------

ORIGINAL PAGE IS
OF POOR QUALITY

NOTES

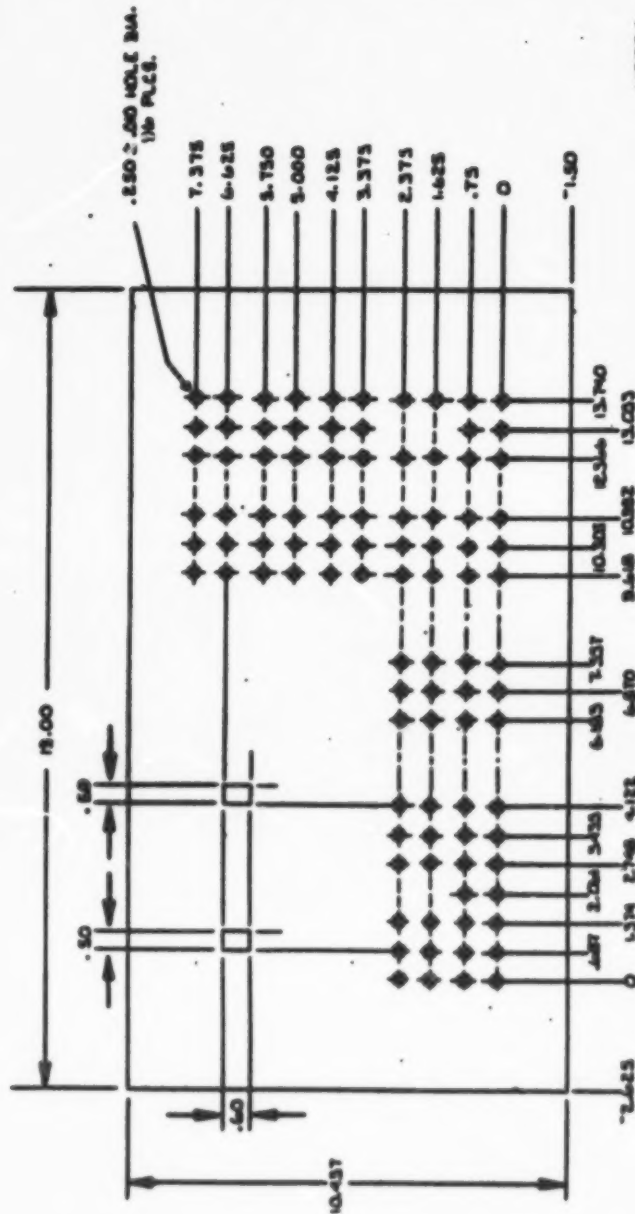1. PANEL MATERIAL IS .125 ALUMINUM T-6 AFTER DRILL PANEL IS PAINTED GRAY #45 AND KRYLON COATED.




POWER SUBSYSTEM AUTOMATION STUDY
FAULT INSERTION PANEL -
ASSEMBLY DRAWING AND DRILL DETAIL

DATE	20 FEB 85
DESIGNER	C
CHECKED	
APPROVED	
PROJECT NO.	845MD81500
SHEET NO.	2 OF 3

REVISION HISTORY

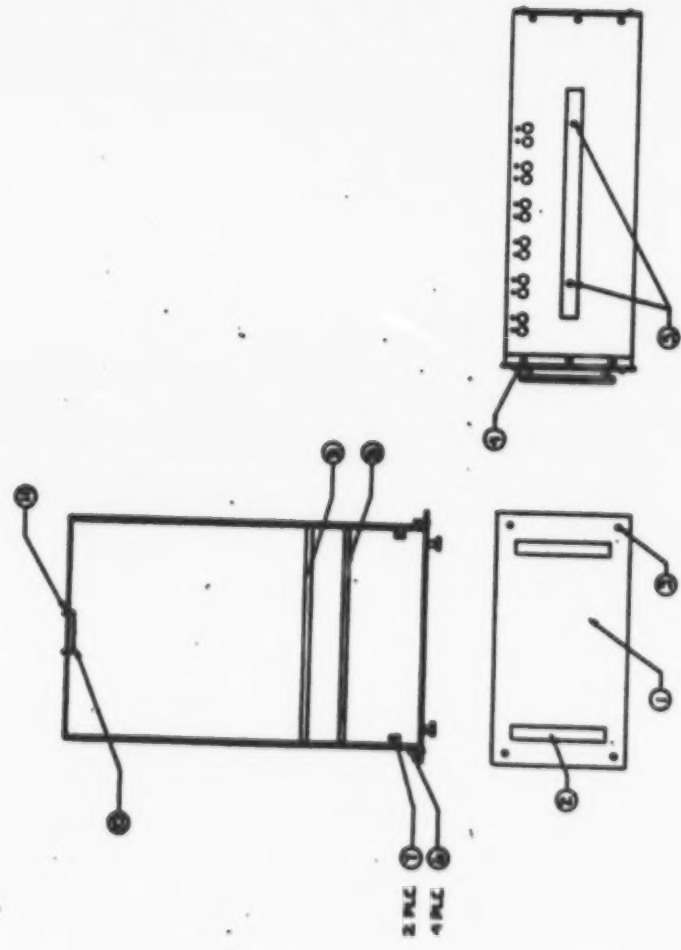POWER SUBSYSTEM AUTOMATION STUDY -
FAULT INSERTION MODULE ASSEMBLY




E-72

1
2
3
4

ORIGINAL PAGE IS
OF POOR QUALITY

FAULT INSERTION PANEL INTERFACE

PART NO. 1113		REV. 1 OF 1	
DATE 11/1/68		BY 1113	
C		B-48P480130	
20-1113		20-1113	

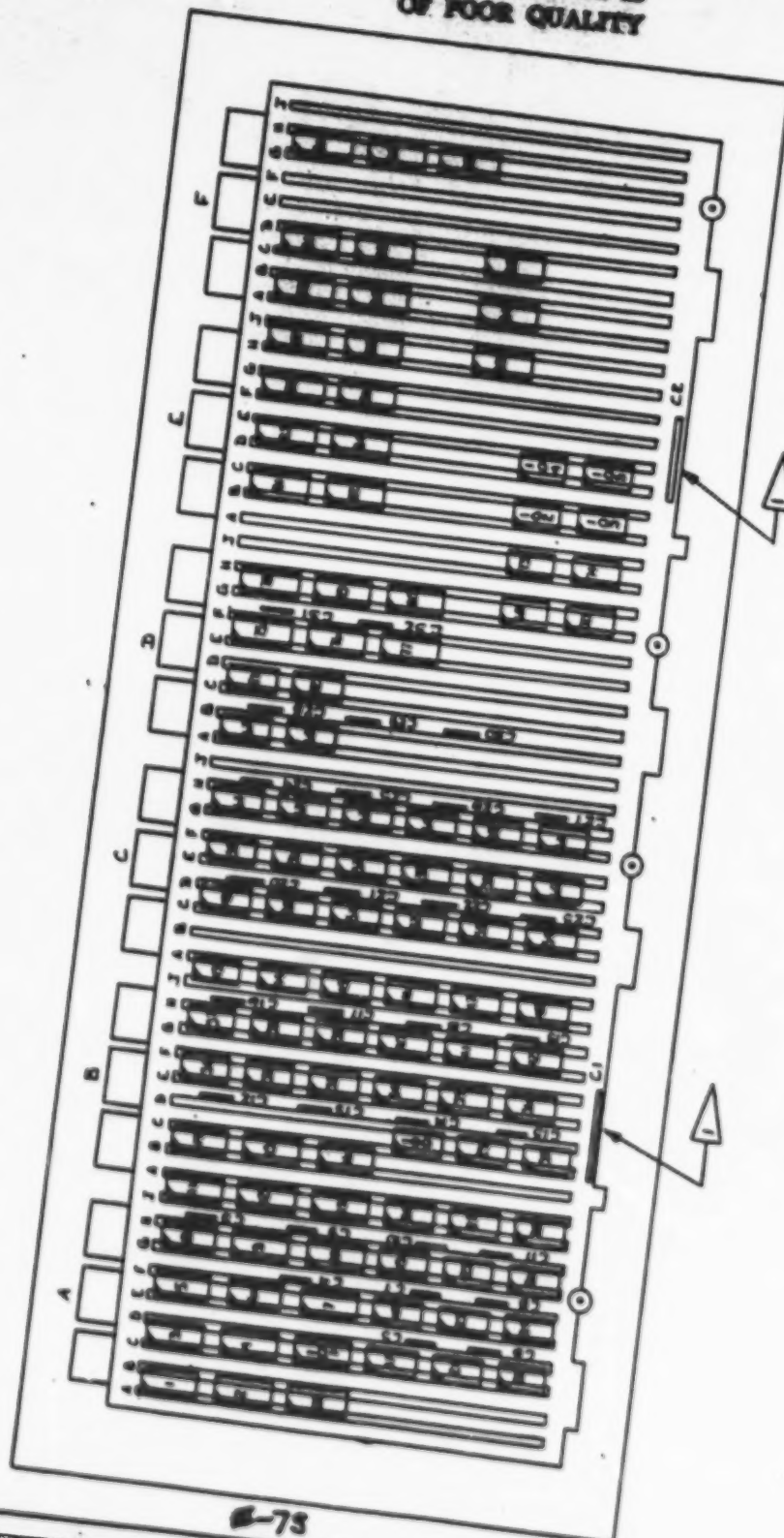

2

3

4


6-73

NOTES:




C1 AND C2 ARE MOUNTED ON THE
REAR (INTERIOR) SIDE OF THE BOARD.

PAGE 13
QUALITY

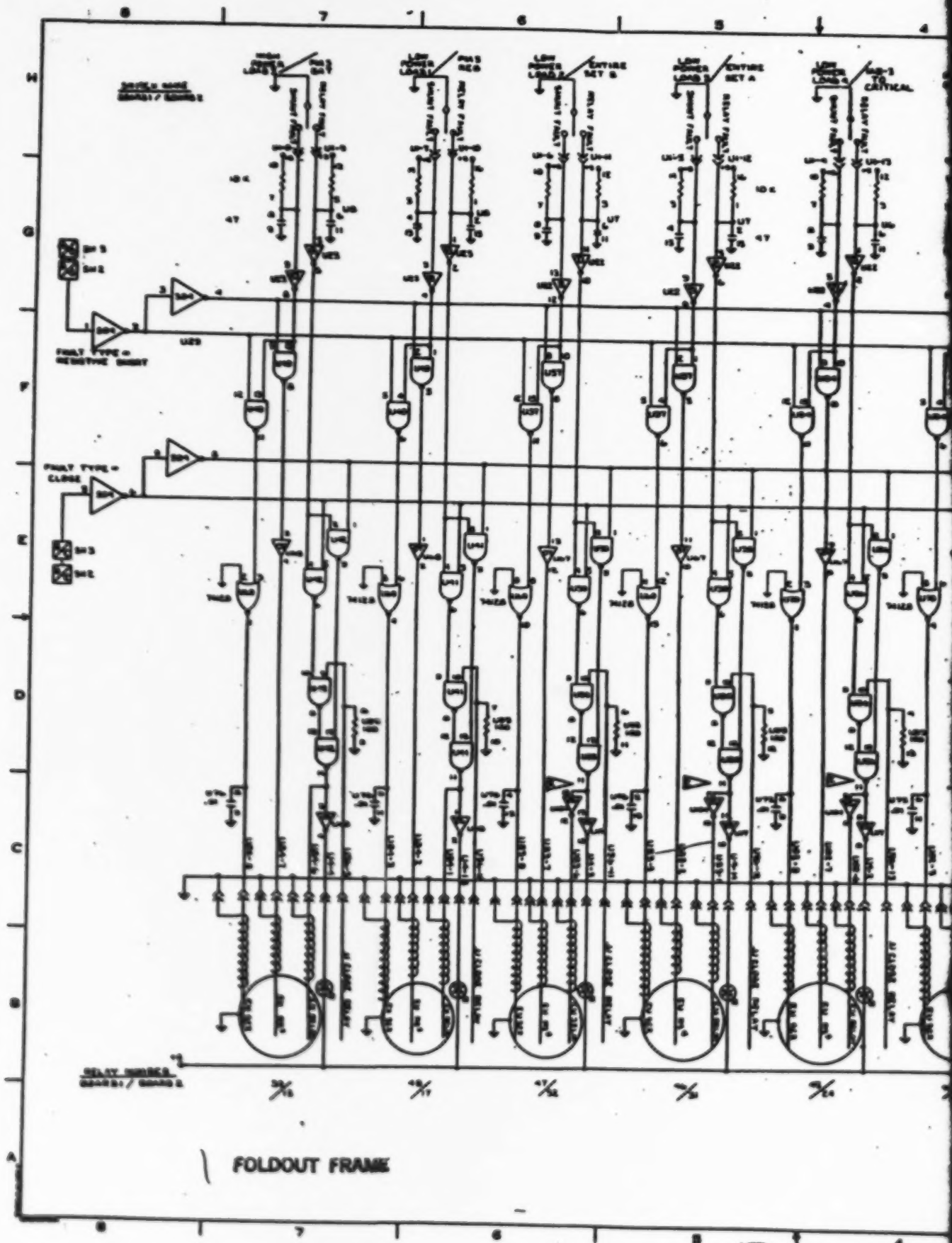

E-74

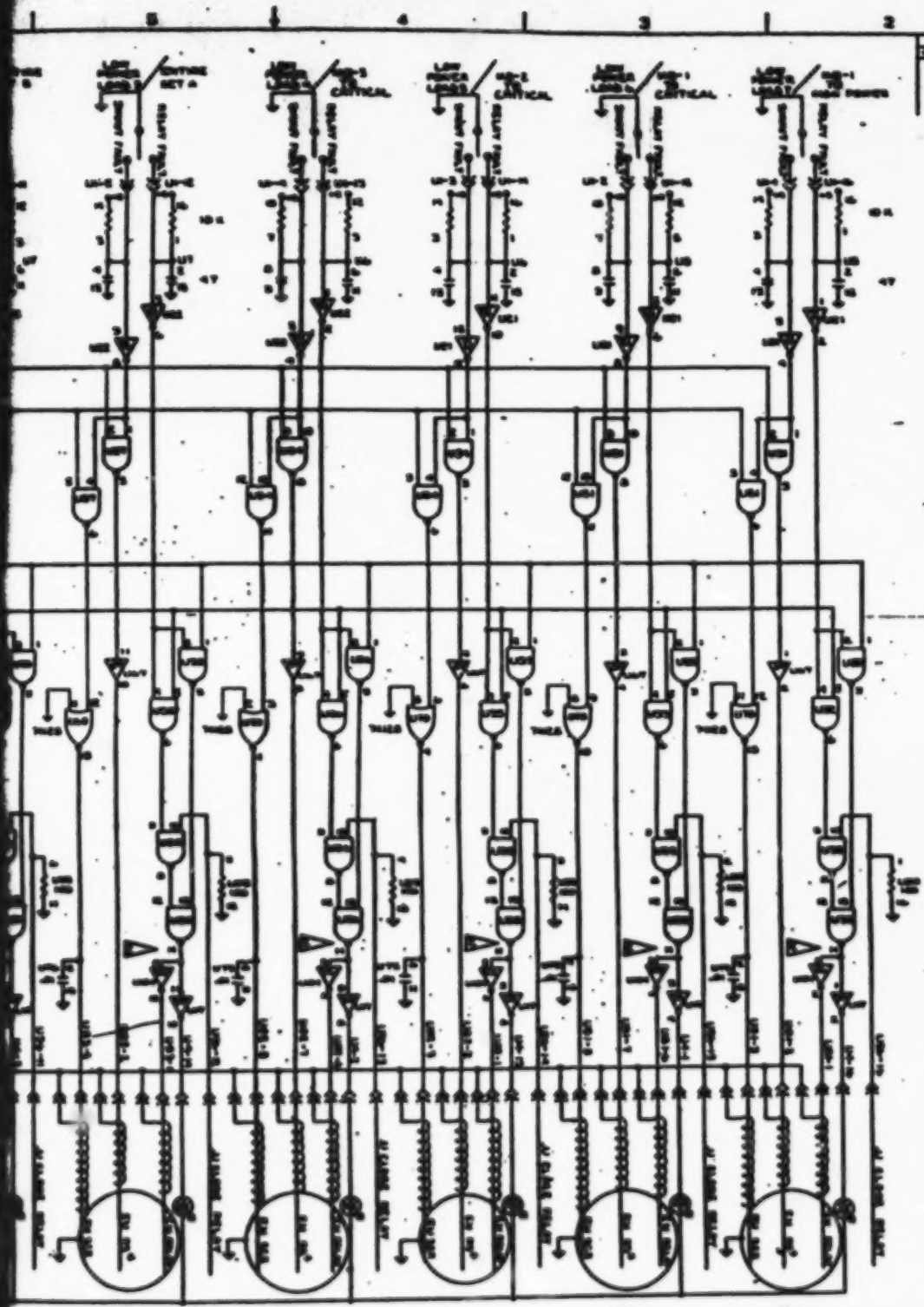

1	2	3	4	5
1	2	3	4	5
1	2	3	4	5
1	2	3	4	5


THIS IS A
 COPY OF THE
 ORIGINAL
 DRAWING
 AND IS NOT
 TO BE USED
 FOR REPRODUCTION
 OF THE ORIGINAL
 DRAWING

2 FOLDOUT FRAME

ONLY INSERTION 2/7
 REVERSE DESIGN

1	2	3	4	5
1	2	3	4	5
1	2	3	4	5
1	2	3	4	5


FOLDOUT FRAME

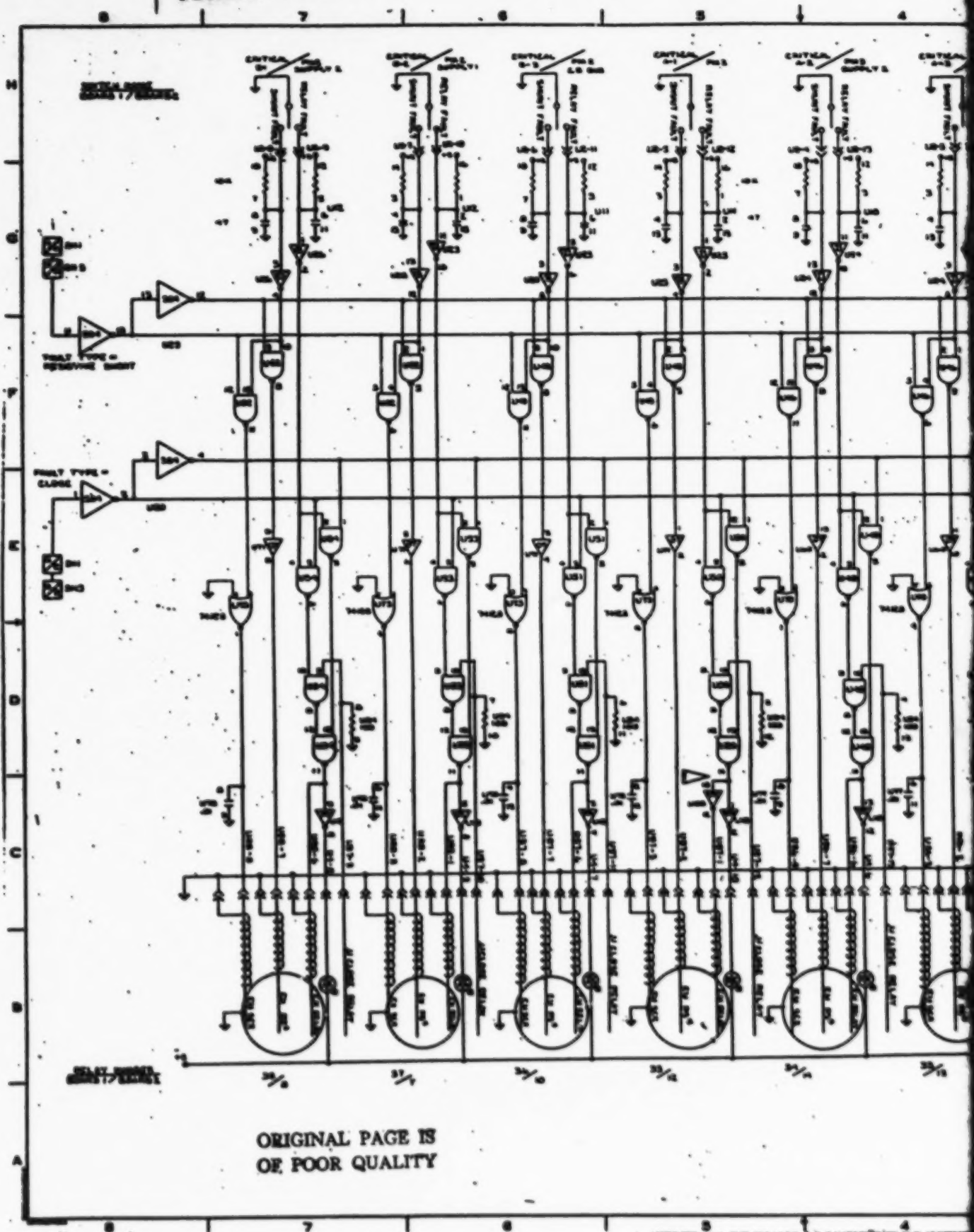



ORIGINAL PAGE IS
OF POOR QUALITY


E-75

FOLDOUT FRAME

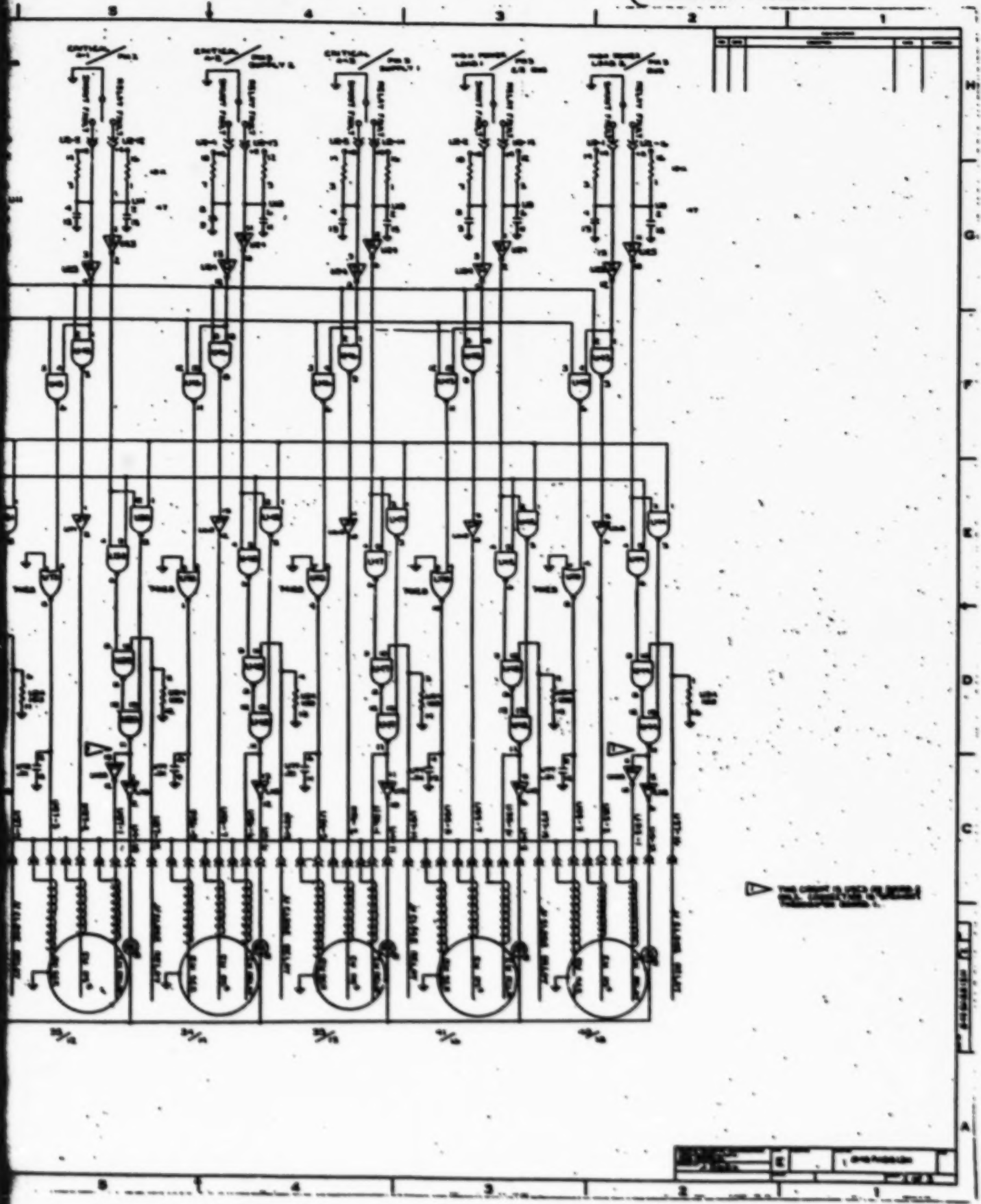

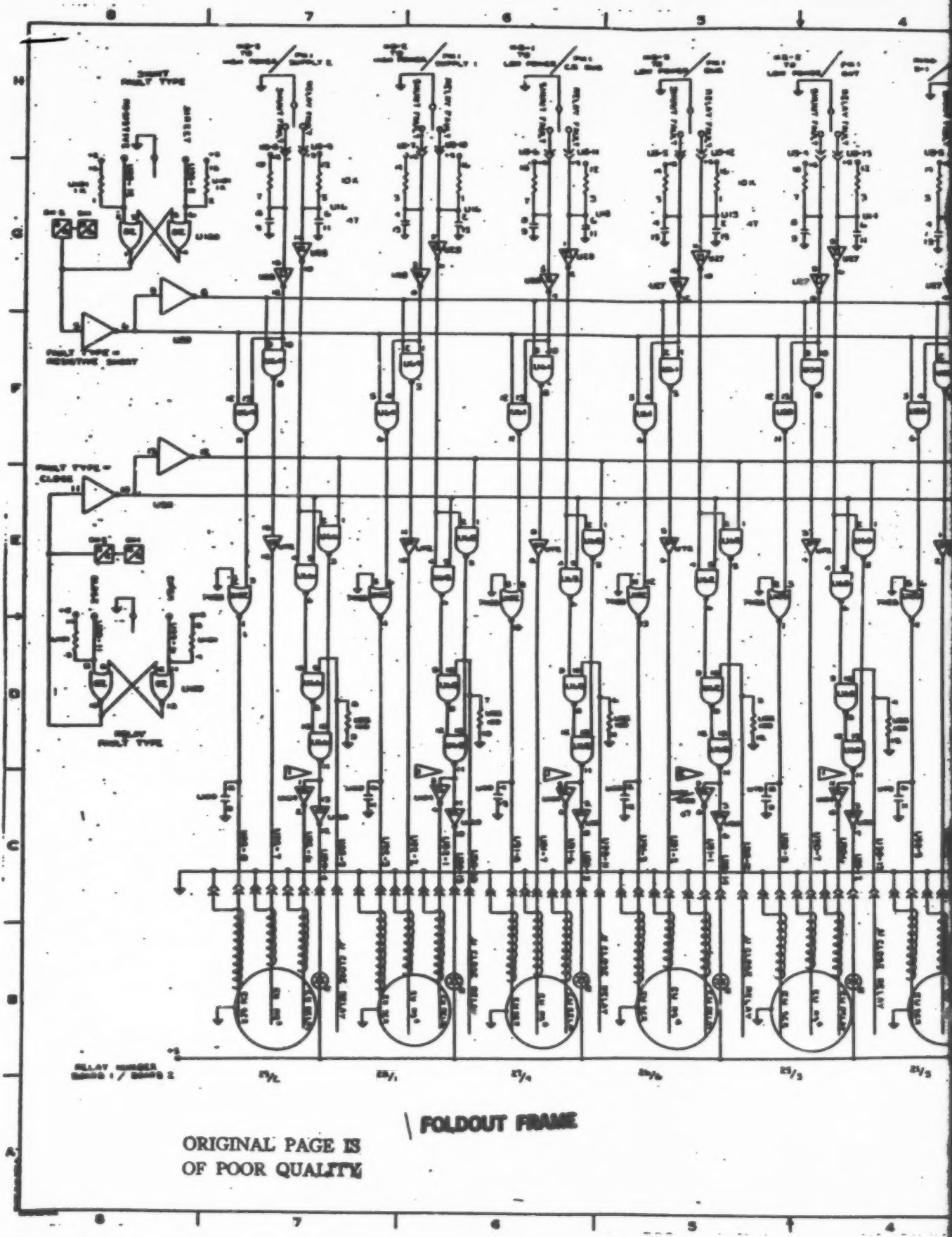

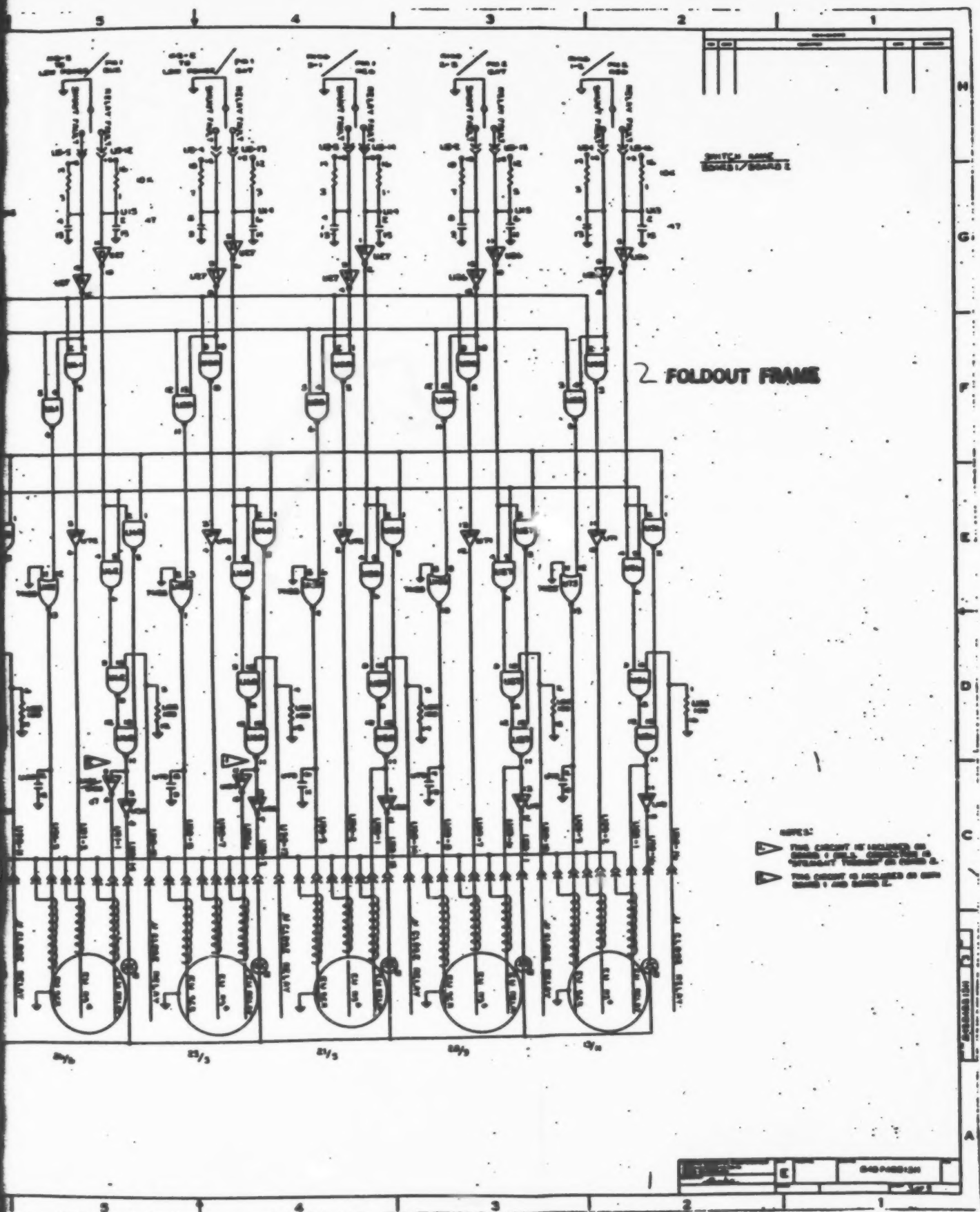

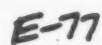[illegible]


ORIGINAL PAGE IS
OF POOR QUALITY

TABLE J1
SIGNAL DESCRIPTION


J1-1	N/C	J1-26	CLOSE RELAY 25
J1-2	CLOSE RELAY 46	J1-27	N/C
J1-3	N/C	J1-28	CLOSE RELAY 26
J1-4	CLOSE RELAY 45	J1-29	N/C
J1-5	N/C	J1-30	CLOSE RELAY 27
J1-6	CLOSE RELAY 44	J1-31	N/C
J1-7	N/C	J1-32	CLOSE RELAY 28
J1-8	CLOSE RELAY 43	J1-33	N/C
J1-9	N/C	J1-34	CLOSE RELAY 29
J1-10	CLOSE RELAY 42	J1-35	N/C
J1-11	N/C	J1-36	CLOSE RELAY 30
J1-12	CLOSE RELAY 41	J1-37	N/C
J1-13	N/C	J1-38	CLOSE RELAY 31
J1-14	CLOSE RELAY 40	J1-39	N/C
J1-15	N/C	J1-40	CLOSE RELAY 32
J1-16	CLOSE RELAY 39	J1-41	N/C
J1-17	N/C	J1-42	CLOSE RELAY 33
J1-18	CLOSE RELAY 38	J1-43	N/C
J1-19	N/C	J1-44	CLOSE RELAY 34
J1-20	CLOSE RELAY 37	J1-45	N/C
J1-21	N/C	J1-46	CLOSE RELAY 35
J1-22	CLOSE RELAY 36	J1-47	N/C
J1-23	N/C	J1-48	CLOSE RELAY 36
J1-24	CLOSE RELAY 35	J1-49	N/C
J1-25	N/C	J1-50	N/C

TABLE J2
SIGNAL DESCRIPTION

J2-1	N/C	J2-25	CLOSE RELAY 6
J2-2	CLOSE RELAY 36	J2-27	N/C
J2-3	N/C	J2-28	CLOSE RELAY 40
J2-4	CLOSE RELAY 32	J2-29	N/C
J2-5	N/C	J2-30	CLOSE RELAY 7
J2-6	CLOSE RELAY 33	J2-31	N/C
J2-7	N/C	J2-32	CLOSE RELAY 8
J2-8	CLOSE RELAY 34	J2-33	N/C
J2-9	N/C	J2-34	CLOSE RELAY 9
J2-10	CLOSE RELAY 35	J2-35	N/C
J2-11	N/C	J2-36	CLOSE RELAY 10
J2-12	CLOSE RELAY 36	J2-37	N/C
J2-13	N/C	J2-38	CLOSE RELAY 11
J2-14	CLOSE RELAY 37	J2-39	N/C
J2-15	N/C	J2-40	CLOSE RELAY 12
J2-16	CLOSE RELAY 38	J2-41	N/C
J2-17	N/C	J2-42	CLOSE RELAY 13
J2-18	CLOSE RELAY 39	J2-43	N/C
J2-19	N/C	J2-44	CLOSE RELAY 14
J2-20	CLOSE RELAY 40	J2-45	N/C
J2-21	N/C	J2-46	CLOSE RELAY 15
J2-22	CLOSE RELAY 41	J2-47	N/C
J2-23	N/C	J2-48	CLOSE RELAY 16
J2-24	CLOSE RELAY 42	J2-49	N/C
J2-25	N/C	J2-50	N/C

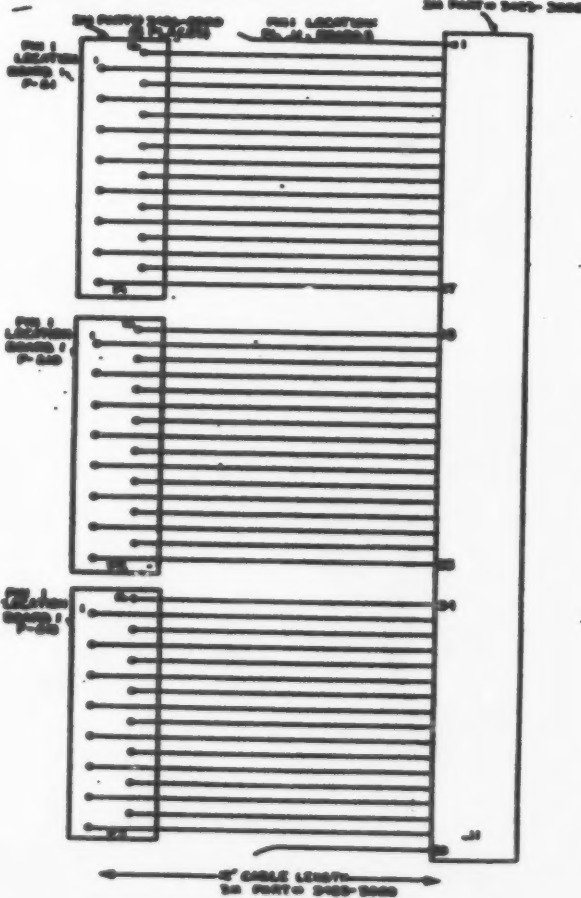

FOLDOUT FRAME



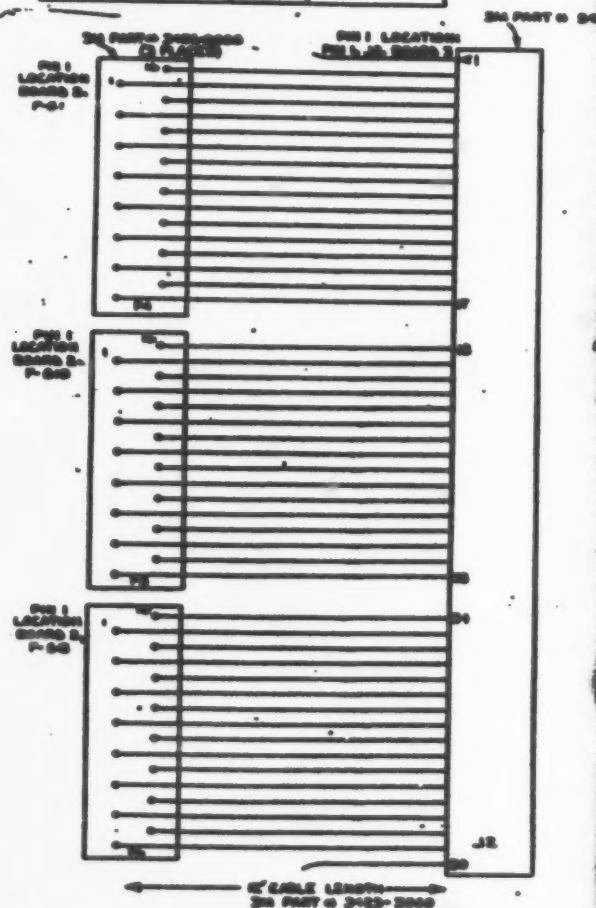


MAP ASSEMBLY

Drawing #PL849PAB1200

<u>Item #</u>	<u>Part #</u>	<u>Description</u>	<u>MFG</u>	<u>QTY</u>
1	P10-White	10.5" X 19" Panel	Optima	1

RELAY AND SENSOR POSITIONS/NUMBERS

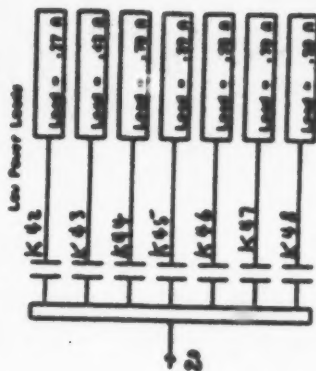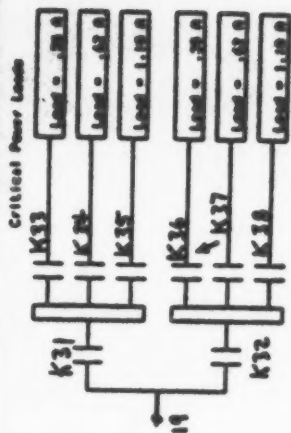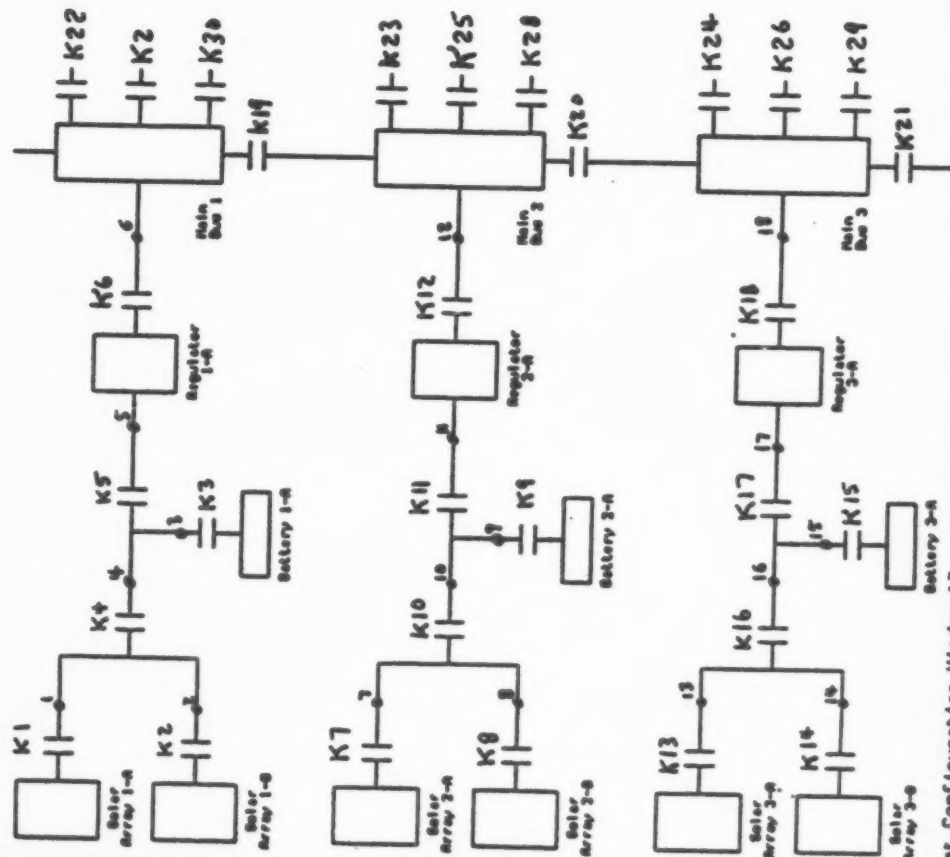

Waiting on initialization...
as per interface status

VENTILLATION GRILLE

<u>Item #</u>	<u>Part #</u>	<u>Description</u>	<u>MFG</u>	<u>QTY</u>
1	G-319	10.5" X 19" Panel	Optima	5

VOLTAGE REGULATOR ASSEMBLY**Drawing # PL849PABB1100**

<u>Item #</u>	<u>Part #</u>	<u>Description</u>	<u>MFG</u>	<u>QTY</u>
1	KD1-3.0	3AMP Circuit Breaker	Heinemann	3
2	SU2A1	FAN, 120 VAC	Sprite	1
3	17614C	Power Cord	Belden	1
4	849PABB1110	Voltage Regulator	MMC	1
5	849PABB1120	Battery Protection	MMC	1
6	849PABB1130	Supply Disconnection	MMC	1
7	P-10	10.5" X 19" Panel	Optima	1
8		#8/32 Bolts		20
9		#8/32 Nuts		20
10		#8 Lockwashers		20
11		#8 Flatwashers		20

BOARD - G - VOLTAGE

PIN	SINGLE-ENDED	DIFFERENTIAL	PIN	SINGLE-ENDED	DIFFERENTIAL	MEASURED AT DELAY 0
1	Not Used	Not Used	2	Not Used	Not Used	SENSOR
3	Analog Return	Analog Return	4	CH 0	CH 0 HI	54
5			6	CH 8	CH 0 LO	'GND'
7			8	CH 1	CH 1 HI	51
9			10	CH 9	CH 1 LO	'GND'
11			12	CH 2	CH 2 HI	52
13			14	CH 10	CH 2 LO	'GND'
15			16	CH 3	CH 3 HI	55
17			18	CH 11	CH 3 LO	'GND'
19			20	CH 4	CH 4 HI	53
21			22	CH 12	CH 4 LO	'GND'
23			24	CH 5	CH 5 HI	56
25			26	CH 13	CH 5 LO	'GND'
27			28	CH 6	CH 6 HI	57
29			30	CH 14	CH 6 LO	'GND'
31			32	CH 7	CH 7 HI	59
33			34	CH 15	CH 7 LO	'GND'
35	Analog Return	Analog Return	36	Not Used	Not Used	
37	Not Used	Not Used	38	Not Used	Not Used	
39	Digital Common	Digital Common	40	Clock Out	Clock Out	
41			42	Ext. Trigger In	Ext. Trigger In	
43			44	BOS Status Out	BOS Status Out	
45	Digital Common	Digital Common	46	BOS Status Out	BOS Status Out	
47	Analog Return	Analog Return	48	Analog Return	Analog Return	
49	-15V	-15V	50	+15V	+15V	

NOTE:

All odd-numbered pins (1, 3, . . . 49) are on component side of the board. Pin 1 is the right-most pin when viewed from the component side with the board extractors at the top.

GND IS THE LOCAL GND AT THE SENSOR

Table 2.14 Analog Input Connector J2 Pin Assignments

BOARD - G - VOLTAGE

PIN	SINGLE-ENDED	DIFFERENTIAL	PIN	SINGLE-ENDED	DIFFERENTIAL	MEASURED AT DELAY 0
1	Not Used	Not Used	2	Not Used	Not Used	SENSOR
3	Analog Return	Analog Return	4	CH 16	CH 8 HI	510
5			6	CH 24	CH 8 LO	'GND'
7			8	CH 17	CH 9 HI	57
9			10	CH 25	CH 9 LO	'GND'
11			12	CH 18	CH 10 HI	58
13			14	CH 26	CH 10 LO	'GND'
15			16	CH 19	CH 11 HI	513
17			18	CH 27	CH 11 LO	'GND'
19			20	CH 30	CH 12 HI	514
21			22	CH 28	CH 12 LO	'GND'
23			24	CH 21	CH 13 HI	512
25			26	CH 29	CH 13 LO	'GND'
27			28	CH 22	CH 14 HI	510
29			30	CH 30	CH 14 LO	'GND'
31			32	CH 23	CH 15 HI	516
33			34	CH 31	CH 15 LO	'GND'
35	Analog Return	Analog Return	36	Not Used	Not Used	
37	Not Used	Not Used	38			
39			40			
41			42			
43			44			
45	Not Used	Not Used	46	Not Used	Not Used	
47	Analog Return	Analog Return	48	Analog Return	Analog Return	
49	-15V	-15V	50	+15V	+15V	

NOTE:

All odd-numbered pins (1, 3, . . . 49) are on component side of the board. Pin 1 is the right-most pin when viewed from the component side with the board extractors at the top.

E-03

Table 2.15 Analog Input Connector J3 Pin Assignments

~~DOUBLE FRAME~~

BOARD -1 - VOLTAGE

PIN	SINGLE ENDED	DIFFERENTIAL	PIN	SINGLE ENDED	DIFFERENTIAL	MEMBERED AT RELAY #
1	Not Used	Not Used	2	Not Used	Not Used	K39
3	Analog Return	Analog Return	4	CH 0	CH 0 HI	
5			6	CH 8	CH 0 LO	
7			8	CH 1	CH 1 HI	BATTERY 1
9			10	CH 9	CH 1 LO	
11			12	CH 2	CH 2 HI	BATTERY 2
13			14	CH 10	CH 2 LO	
15			16	CH 3	CH 3 HI	BATTERY 3
17			18	CH 11	CH 3 LO	
19			20	CH 4	CH 4 HI	K31
21			22	CH 12	CH 4 LO	
23			24	CH 5	CH 5 HI	K15
25			26	CH 13	CH 5 LO	
27			28	CH 6	CH 6 HI	K17
29			30	CH 14	CH 6 LO	
31			32	CH 7	CH 7 HI	BOARD 1
33			34	CH 15	CH 7 LO	
35	Analog Return	Analog Return	36	Not Used	Not Used	
37	Not Used	Not Used	38	Not Used	Not Used	
39	Digital Common	Digital Common	40	Clock Out	Clock Out	
41			42	Ext. Trigger In	Ext. Trigger In	
43			44	EOC Status Out	EOC Status Out	
45	Digital Common	Digital Common	46	EOS Status Out	EOS Status Out	
47	Analog Return	Analog Return	48	Analog Return	Analog Return	
49	-15V	-15V	50	+15V	+15V	

NOTE:

'GND' IS THE LOCAL GND AT THE SENSOR
All odd-numbered pins (1, 3, . . . 49) are on component side of the board. Pin 1 is the right-most pin when viewed from the component side with the board extractors at the top.

NC = NO CONNECTION

Table 2.14 Analog Input Connector J2 Pin Assignments

PIN	SINGLE ENDED	DIFFERENTIAL	PIN	SINGLE ENDED	DIFFERENTIAL	MEMBERED AT RELAY #
1	Not Used	Not Used	2	Not Used	Not Used	B1
3	Analog Return	Analog Return	4	CH 16	CH 8 HI	
5			6	CH 24	CH 8 LO	
7			8	CH 17	CH 9 HI	B1
9			10	CH 25	CH 9 LO	
11			12	CH 18	CH 10 HI	
13			14	CH 26	CH 10 LO	
15			16	CH 19	CH 11 HI	
17			18	CH 27	CH 11 LO	
19			20	CH 20	CH 12 HI	
21			22	CH 28	CH 12 LO	
23			24	CH 21	CH 13 HI	
25			26	CH 29	CH 13 LO	
27			28	CH 22	CH 14 HI	
29			30	CH 30	CH 14 LO	
31			32	CH 23	CH 15 HI	
33			34	CH 31	CH 15 LO	
35	Analog Return	Analog Return	36	Not Used	Not Used	
37	Not Used	Not Used	38			
39			40			
41			42			
43			44			
45	Not Used	Not Used	46	Not Used	Not Used	
47	Analog Return	Analog Return	48	Analog Return	Not Used	
49	-15V	-15V	50	+15V	+15V	

NOTE:

All odd-numbered pins (1, 3, . . . 49) are on component side of the board. Pin 1 is the right-most pin when viewed from the component side with the board extractors at the top.

E-84

Table 2.15 Analog Input Connector J3 Pin Assignments

BOARD - 2 - CURRENT

PIN	SINGLE-ENDED	DIFFERENTIAL	PIN	SINGLE-ENDED	DIFFERENTIAL	MEASURED AT RELAY #
1	Not Used	Not Used	2	Not Used	Not Used	
3	Analog Return	Analog Return	4	CH 0	CH 0 HI 54 +	K 4
5			6	CH 8	CH 0 LO 54 -	
7			8	CH 1	CH 1 HI 51 -	K 1
9			10	CH 9	CH 1 LO 51 -	
11			12	CH 2	CH 2 HI 52 +	K 2
13			14	CH 10	CH 2 LO 52 -	
15			16	CH 3	CH 3 HI 55 +	K 5
17			18	CH 11	CH 3 LO 55 -	
19			20	CH 4	CH 4 HI 53 +	K 3
21			22	CH 12	CH 4 LO 53 -	
23			24	CH 5	CH 5 HI 56 +	K 6
25			26	CH 13	CH 5 LO 56 -	
27			28	CH 6	CH 6 HI 511 +	K 11
29			30	CH 14	CH 6 LO 511 -	
31			32	CH 7	CH 7 HI 59 +	K 9
33			34	CH 15	CH 7 LO 59 -	
35	Analog Return	Analog Return	36	Not Used	Not Used	
37	Not Used	Not Used	38	Not Used	Not Used	
39	Digital Common	Digital Common	40	Clock Out	Clock Out	
41			42	Ext. Trigger In	Ext. Trigger In	
43			44	BOC Status Out	BOC Status Out	
45	Digital Common	Digital Common	46	BOS Status Out	BOS Status Out	
47	Analog Return	Analog Return	48	Analog Return	Analog Return	
49	-15V	-15V	50	+15V	+15V	

NOTE:

All odd-numbered pins (1, 3, . . . 49) are on component side of the board. Pin 1 is the right-most pin when viewed from the component side with the board extractors at the top.

+ IS THE SENSE POINT
CLOSEST TO
THE POWER SOURCE

BOARD - 2 - CURRENT

Table 2.14 Analog Input Connector J2 Pin Assignments

PIN	SINGLE-ENDED	DIFFERENTIAL	PIN	SINGLE-ENDED	DIFFERENTIAL	MEASURED AT RELAY #
1	Not Used	Not Used	2	Not Used	Not Used	
3	Analog Return	Analog Return	4	CH 10	CH 8 HI 510 +	K 10
5			6	CH 24	CH 8 LO 510 -	
7			8	CH 17	CH 9 HI 57 +	K 7
9			10	CH 25	CH 9 LO 57 -	
11			12	CH 18	CH 10 HI 58 +	K 8
13			14	CH 26	CH 10 LO 58 -	
15			16	CH 19	CH 11 HI 513 +	K 13
17			18	CH 27	CH 11 LO 513 -	
19			20	CH 20	CH 12 HI 514 +	K 14
21			22	CH 28	CH 12 LO 514 -	
23			24	CH 21	CH 13 HI 512 +	K 12
25			26	CH 29	CH 13 LO 512 -	
27			28	CH 22	CH 14 HI 518 +	K 18
29			30	CH 30	CH 14 LO 518 -	
31			32	CH 23	CH 15 HI 516 +	K 16
33			34	CH 31	CH 15 LO 516 -	
35	Analog Return	Analog Return	36	Not Used	Not Used	
37	Not Used	Not Used	38			
39			40			
41			42			
43			44			
45	Not Used	Not Used	46	Not Used	Not Used	
47	Analog Return	Analog Return	48	Analog Return	Not Used	
49	-15V	-15V	50	+15V	+15V	

NOTE:

All odd-numbered pins (1, 3, . . . 49) are on component side of the board. Pin 1 is the right-most pin when viewed from the component side with the board extractors at the top.

E-15

Table 2.15 Analog Input Connector J3 Pin Assignments

B2

BOARD 3 - CURRENT

PIN	SINGLE-ENDED	DIFFERENTIAL	PIN	SINGLE-ENDED	DIFFERENTIAL	MEASURED AT RELAY 31
1	Not Used	Not Used	2	Not Used	Not Used	SCABER
3	Analog Return	Analog Return	4	CH 0	CH 0 HI	521 +
5			6	CH 8	CH 0 LO	521 -
7			8	CH 1	CH 1 HI	522 +
9			10	CH 9	CH 1 LO	522 -
11			12	CH 2	CH 2 HI	523 +
13			14	CH 10	CH 2 LO	523 -
15			16	CH 3	CH 3 HI	524 +
17			18	CH 11	CH 3 LO	524 -
19			20	CH 4	CH 4 HI	519 +
21			22	CH 12	CH 4 LO	519 -
23			24	CH 5	CH 5 HI	515 +
25			26	CH 13	CH 5 LO	515 -
27			28	CH 6	CH 6 HI	517 +
29			30	CH 14	CH 6 LO	517 -
31			32	CH 7	CH 7 HI	520 +
33			34	CH 15	CH 7 LO	520 -
35	Analog Return	Analog Return	36	Not Used	Not Used	BOARD 1
37	Not Used	Not Used	38	Not Used	Not Used	
39	Digital Common	Digital Common	40	Clock Out	Clock Out	
41			42	Ext. Trigger In	Ext. Trigger In	
43			44	BOS Status Out	BOS Status Out	
45	Digital Common	Digital Common	46	BOS Status Out	BOS Status Out	
47	Analog Return	Analog Return	48	Analog Return	Analog Return	
49	-15V	-15V	50	+15V	+15V	

NOTE:

All odd-numbered pins (1, 3, . . . 49) are on component side of the board. Pin 1 is the right-most pin when viewed from the component side with the board extractors at the top.

+ 15.711C. SEVERAL POSITION CLOSEST TO THE POWER SOURCE

BOARD 3 - CURRENT

Table 2.14 Analog Input Connector J2 Pin Assignments

NC = NOT CONNECTED

PIN	SINGLE-ENDED	DIFFERENTIAL	PIN	SINGLE-ENDED	DIFFERENTIAL
1	Not Used	Not Used	2	Not Used	Not Used
3	Analog Return	Analog Return	4	CH 16	CH 8 HI
5			6	CH 24	CH 8 LO
7			8	CH 17	CH 9 HI
9			10	CH 25	CH 9 LO
11			12	CH 18	CH 10 HI
13			14	CH 26	CH 10 LO
15			16	CH 19	CH 11 HI
17			18	CH 27	CH 11 LO
19			20	CH 20	CH 12 HI
21			22	CH 28	CH 12 LO
23			24	CH 21	CH 13 HI
25			26	CH 29	CH 13 LO
27			28	CH 22	CH 14 HI
29			30	CH 30	CH 14 LO
31			32	CH 23	CH 15 HI
33			34	CH 31	CH 15 LO
35	Analog Return	Analog Return	36	Not Used	Not Used
37	Not Used	Not Used	38		
39			40		
41			42		
43			44		
45	Not Used	Not Used	46	Not Used	Not Used
47	Analog Return	Analog Return	48	Analog Return	Not Used
49	-15V	-15V	50	+15V	+15V

NOTE:

All odd-numbered pins (1, 3, . . . 49) are on component side of the board. Pin 1 is the right-most pin when viewed from the component side with the board extractors at the top.

F-86

Table 2.15 Analog Input Connector J3 Pin Assignments

ORIGINAL PAGE IS
OF POOR QUALITY

ADD-0

(bytes)	Jumper
2K (16 bits)	none (no connection on 90, 91, 92, 93)
1M (20 bits)	90-91
16M (24 bits)	90, 91 and 92-93

Range Jumper

ADR4 must be connected to GND

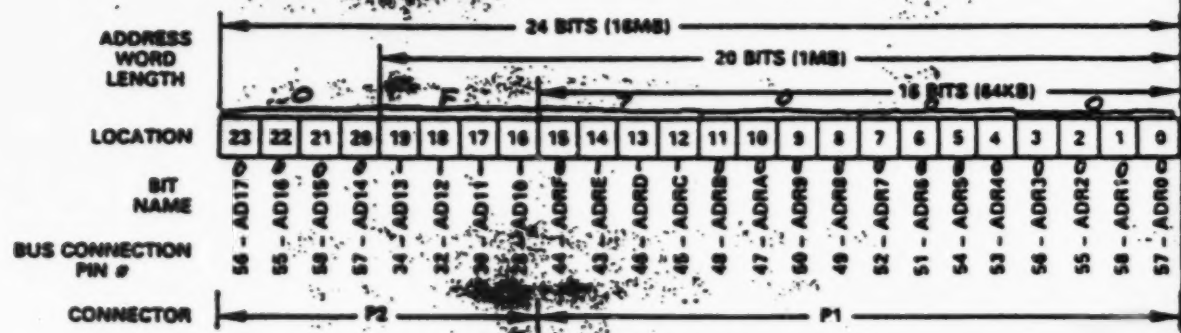


Figure 2.1 Memory Address Assignment

ADDRESS JUMPERS

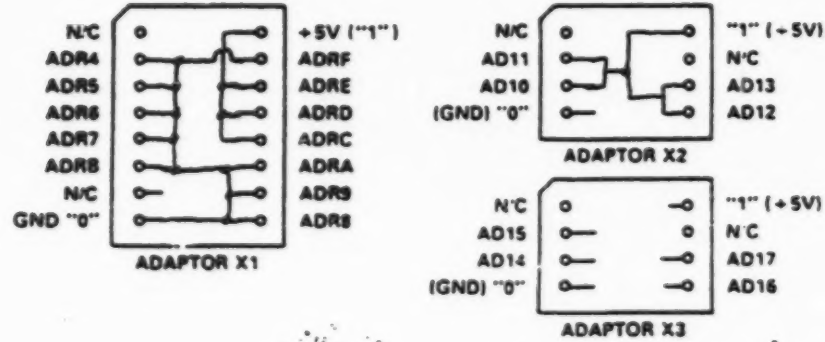


Figure 2.2 RTI-711-732 Jumper Blocks

2.0 MULTIPLEXER CONFIGURATION

The multiplexer can accommodate 16 single-ended or 8 differential input channels, and can be expanded to accommodate an additional 16 single-ended or 8 differential input channels as described in paragraph 2.17. The RTI-711-732 boards are shipped with jumpers configured for single-ended channel operation as shown in Figure 2.3a. If differential channel operation is required, reconfigure the jumpers as illustrated in Figure 2.3b. The jumpers shown in Figure 2.3a are intended to be used in practice keep the jumpers as short as possible.

Addressable Memory Range (bytes)	Jumper
64K (16 bits)	None (no connection on 90, 91, 92, 93)
1M (20 bits)	90-91
16M (24 bits)	90-91 and 92-93

Example:

Figure 2.1 shows

Note that each of the address bits (ADR) must be jumpered with either GND (0) or +5V (1).

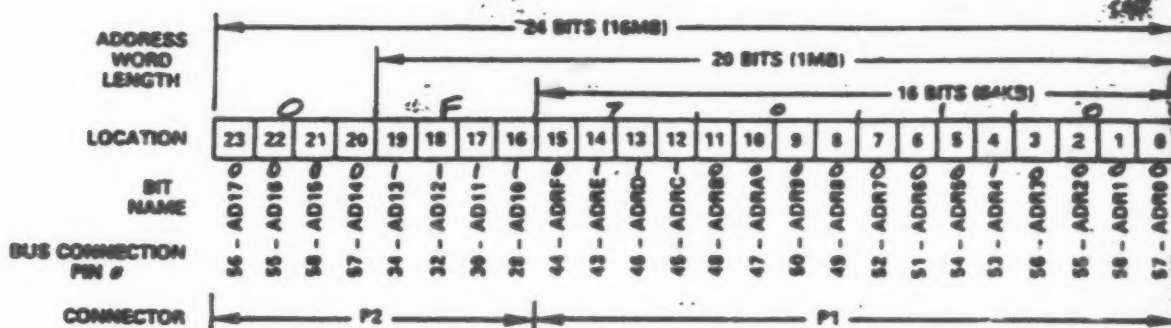


Figure 2.1 Memory Address Assignment

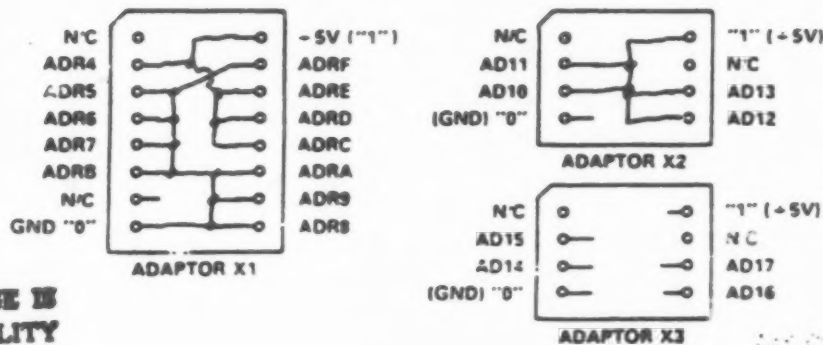


Figure 2.2 RTI-711 732 Jumper Blocks

2.4 MULTIPLEXER CONFIGURATION

The multiplexer can accommodate 16 single-ended or 8 differential input channels and can be expanded to accommodate an additional 16 single-ended or 8 differential input channels as described in paragraph 2.17. The RTI-711 732 boards are shipped with jumpers configured for single-ended channel operation as shown in Figure 2.3a. If differential channel operation is required, reconfigure the jumpers as illustrated in Figure 2.3b. The jumpers shown in Figure 2.3 are illustrative; for clarity, in practice keep the jumpers as short as possible.

ORIGINAL PAGE IS OF POOR QUALITY

Addressable Memory Range
(bytes)

Jumper

64K (16 bits)

none (no connection on 90-91, 92-93)

1M (20 bits)

90-91

16M (24 bits)

90-91 and 92-93

Table 2.1 Memory Range Jumpers

Example:

Figure 2.2 shows how to configure jumpers for a memory address of 35F700

Note that each of the address bits AD17-ADR4 must be jumpered either to GND (0) or -5V (1).

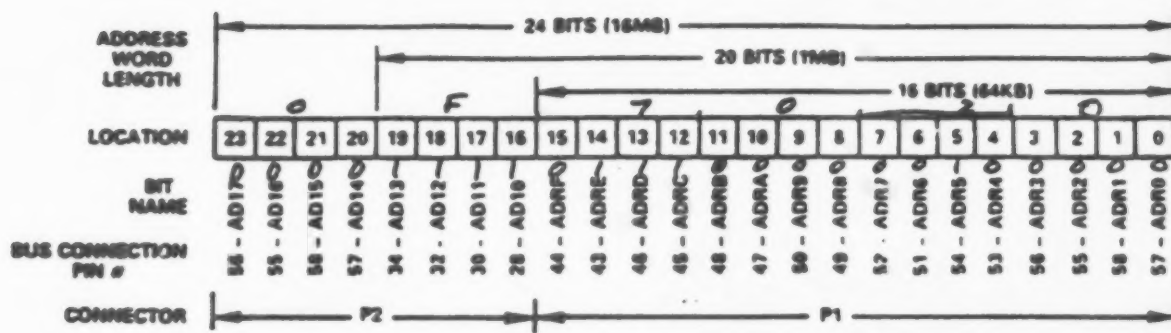


Figure 2.1 Memory Address Assignment

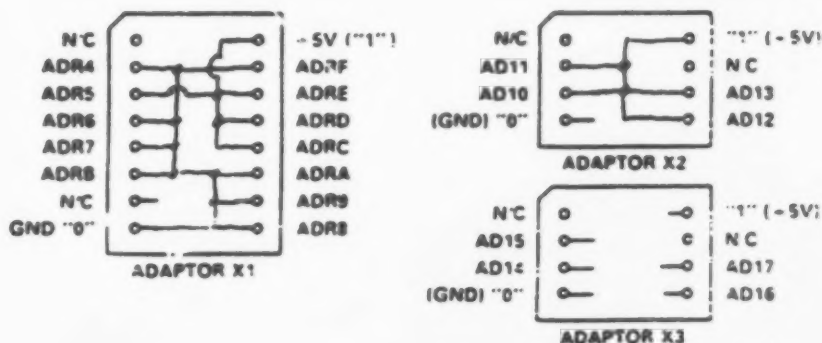


Figure 2.2 RTI-711 732 Jumper Blocks

2.4 MULTIPLEXER CONFIGURATION

The multiplexer can accommodate 16 single-ended or 8 differential input channels, and can be expanded to accommodate an additional 16 single-ended or 8 differential input channels as described in paragraph 2.17. The RTI-711 732 boards are shipped with jumpers configured for single-ended channel operation, as shown in Figure 2.3a. If differential operation is required, the jumpers must be reconfigured as shown in Figure 2.3b. The RTI-711 732 boards are shipped with jumpers configured for single-ended channel operation, as shown in Figure 2.3a. If differential operation is required, the jumpers must be reconfigured as shown in Figure 2.3b. The RTI-711 732 boards are shipped with jumpers configured for single-ended channel operation, as shown in Figure 2.3a. If differential operation is required, the jumpers must be reconfigured as shown in Figure 2.3b.

A/D-3

ORIGINAL PAGE 11
OF POOR QUALITY

Addressable Memory Range (bytes)	Jumper
256K (16 bits)	none (no connection on 90-92-93)
1M (20 bits)	90-91
16M (24 bits)	90-91 and 92-93

Table 2.3 Memory Range Jumpers

Example:

Figure 2.2 shows how to configure the jumpers for a memory address of 35F700. Note that each of the address bits AD17-ADR4 must be jumpered either to GND (0) or +5V (1).

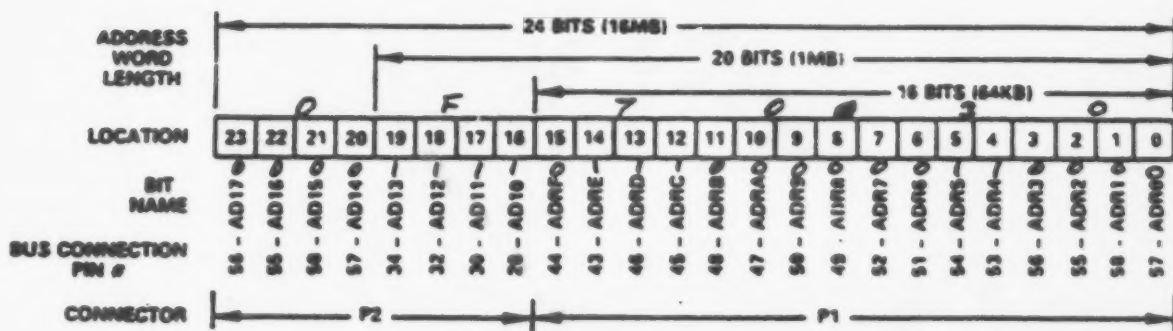


Figure 2.1 Memory Address Assignment

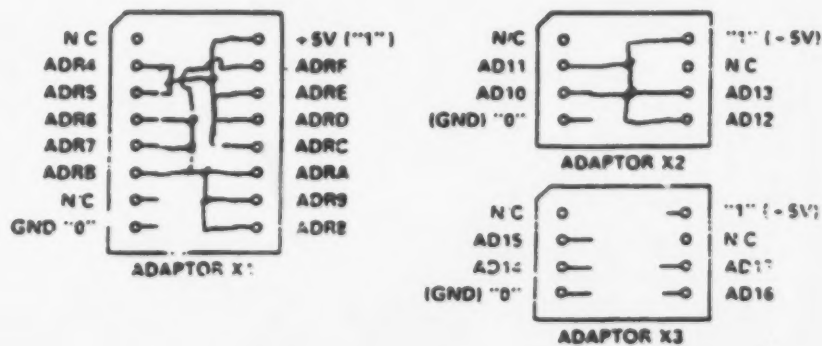


Figure 2.2 RTI-711 732 Jumper Blocks

2.9 MULTIPLEXER CONFIGURATION

The multiplexer can accommodate 16 single-ended or 8 differential input channels, and can be expanded to accommodate an additional 16 single-ended or 8 differential input channels as described in paragraph 2.17. The RTI-711 732 boards are shipped with jumpers configured for single-ended channel operation, as shown in Figure 2.3. The jumpers are located on the back of the board, and are labeled as follows: J1, J2, J3, J1865, J1866,

